

Module 2

Unit 2

TRANSISTOR (BJT)

Review Questions

- 1 Define current gains α and β . How are they related?
- 2 In transistor design, the base has most critical features as compared to emitter and collector. Discuss.
- 3 Why do we bias a transistor? What are the considerations in choosing an appropriate biasing scheme?
- 4 Draw $I - V$ characteristics (Collector characteristics) for a transistor and discuss the salient features.
- 5 Explain 'base width modulation' and its influence on transistor characteristics.
- 6 What is collector feedback bias? How does this biasing provide stability to the circuit?
- 7 Give reasons for the wide use of 'voltage divider bias' in BJT amplifiers.
- 8 Discuss the flow of three currents I_E , I_B and I_C in a forward biased emitter junction and reverse biased collector junction.

Problems

2.1 A transistor has current gain of 0.99 when used in common base (CB) configuration. How much will be the current gain of this transistor in common emitter (CE) configuration ?

Solution :- The current gain in common base circuit is written as α , and it has been given equal to 0.99.

α and current gain in common emitter configuration β are related as

$$\beta = \frac{\alpha}{1 - \alpha}$$

Therefore,

$$\beta = \frac{0.99}{1 - 0.99} = 99$$


or $\beta = 99$

2.2 Determine the minimum value of current gain β required to put the transistor in saturation when

$$V_{in} = +5V.$$

$$\text{Assume, } V_{BE(sat)} = 0.8 \text{ V,}$$

$$V_{CE(sat)} = 0.12 \text{ V}$$

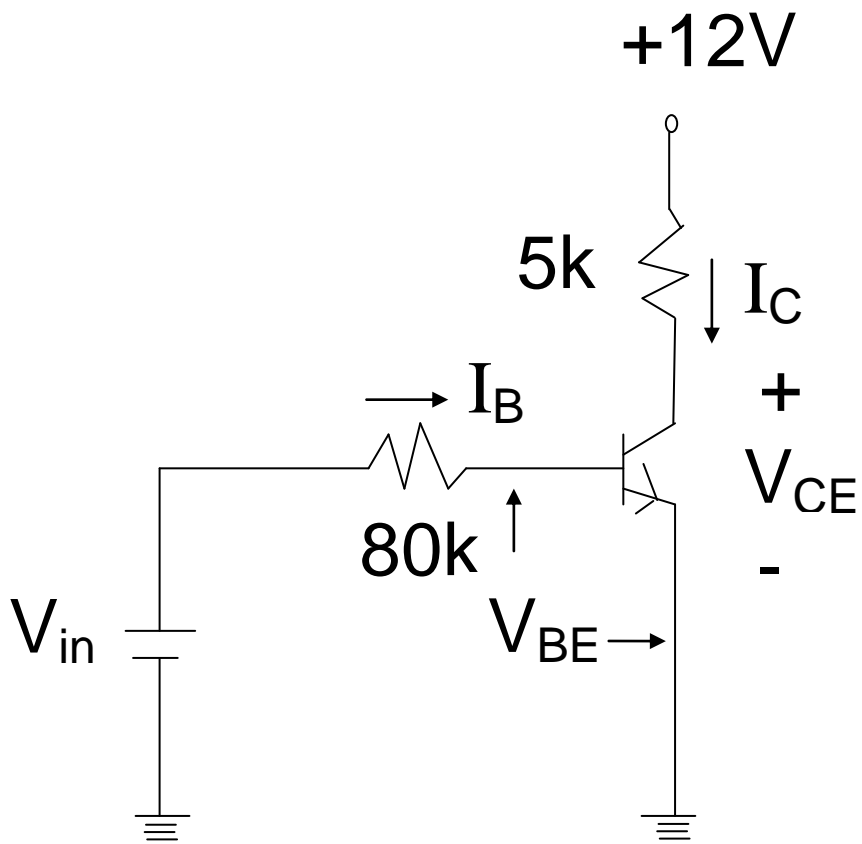

Solution:- Let I_B and I_C be base current and collector current respectively (see fig. above).

Taking +5V as input voltage V_{in} , the summation of voltages (Kirchhoff's voltage law, KVL) in the base-emitter loop gives

$$8 \times 10^3 \times I_B + V_{BE} - 5V = 0$$

We assume that the transistor is in saturation, so that

$$V_{BE} = V_{BE(Sat)} = 0.8 \text{ V}$$

Therefore ,

$$80 \times 10^3 \times I_B + 0.8 \text{ V} - 5V = 0$$

$$\text{or , } I_B = \frac{4.2V}{80 \times 10^3} = 0.0525mA$$

Summation of voltages in the collector loop gives,

$$5 \times 10^3 \times I_C + V_{CE} = 12 \text{ V}$$

$$\text{or } I_C = \frac{12 - 0.2}{5 \times 10^3} = 2.36mA$$

And the condition for the transistor in saturation is that the minimum value of gain β ,

$$\beta_{\min} = I_C / I_B = \frac{2.36mA}{0.525mA} \approx 45,$$


or $\beta_{\min} = 45$.

2.3 The fixed bias circuit shown in figure uses a silicon transistor with $V_{BE} = 0.7V$.

(a) Find the collector current, I_C , and voltage V_{CE} , if β of transistor is 60.

(b) Find I_C and V_{CE} if β changes to 80.

What conclusions may be drawn?

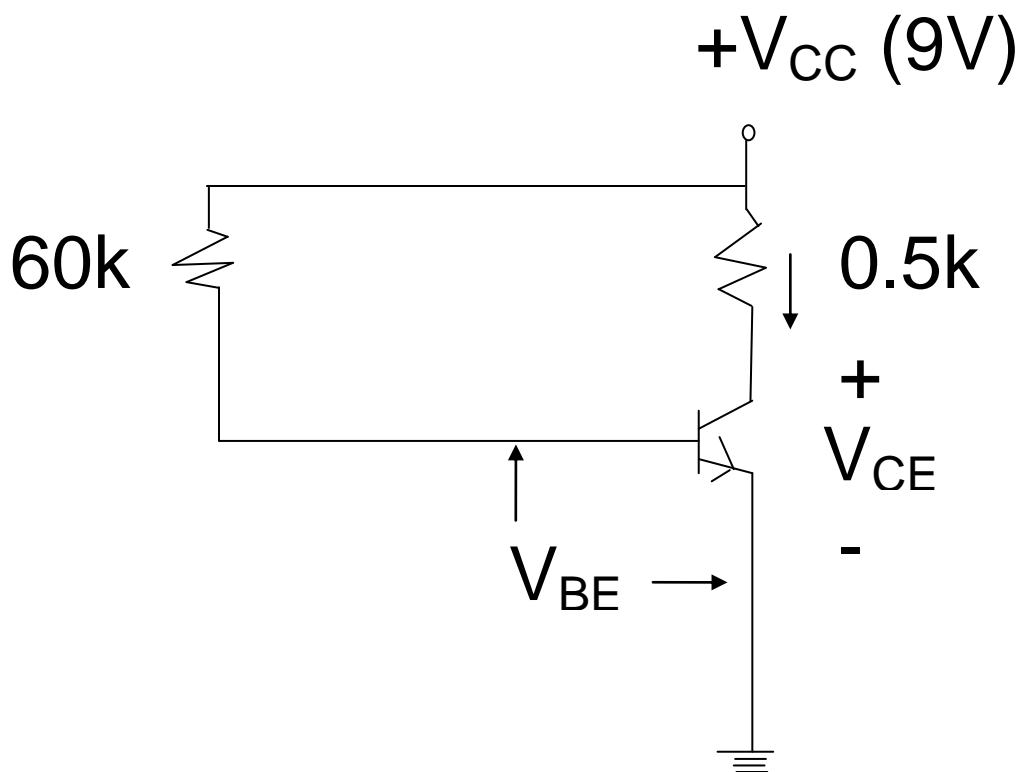

Solution:-

(a) Summation of voltages in base-emitter loop results in

$$V_{CC} = R_B I_B + V_{BE}$$

$$\text{or } I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{9 - 0.7}{60 \times 10^3} = 0.138 \text{ mA}$$

and,

$$\begin{aligned} I_C &= \beta I_B \\ &= 60 \times 0.138 \text{ mA} \end{aligned}$$

$$I_C = 8.28 \text{ mA}$$

Summation of voltages in the collector circuit gives,

$$R_C I_C + V_{CE} = V_{CC}$$

$$\begin{aligned} \text{Or } V_{CE} &= V_{CC} - I_C R_C \\ &= 9 - 8.28 \times 10^{-3} \times 0.5 \times 10^3 \\ &= 9 - 4.14 \end{aligned}$$

$$\text{Or } V_{CE} = 4.86 \text{ V}$$

Thus the operating point values are

$$I_C = 8.28 \text{ mA}, \text{ and}$$

$$V_{CE} = 4.86 \text{ V}$$

(b) Proceeding in the same way, and if the current gain β equals 80, then

Since $I_B = 0.138 \text{ mA}$, therefore

$$I_C = \beta I_B = 80 \times 0.138 \text{ mA}$$

$$\text{or } I_C = 12.42 \text{ mA}$$

$$\begin{aligned}\text{And } V_{CE} &= V_{CC} - I_C R_C \\ &= 9 - 12.42 \times 10^{-3} \times 0.5 \times 10^3 \\ &= 9 - 6.21\end{aligned}$$

$$V_{CE} = 2.79 \text{ V}$$

With $\beta = 80$, the operating point values are :

$$I_C = 12.42 \text{ mA, and}$$

$$V_{CE} = 2.79 \text{ V}$$

CONCLUSIONS:-


Changes in collector current I_C when β changes from 60 to 80 are from 8.28 mA to 12.42 mA.

And V_{CE} changes from 4.86V to 2.79V.

These changes are drastic and operation may shift to regions to give distorted output.

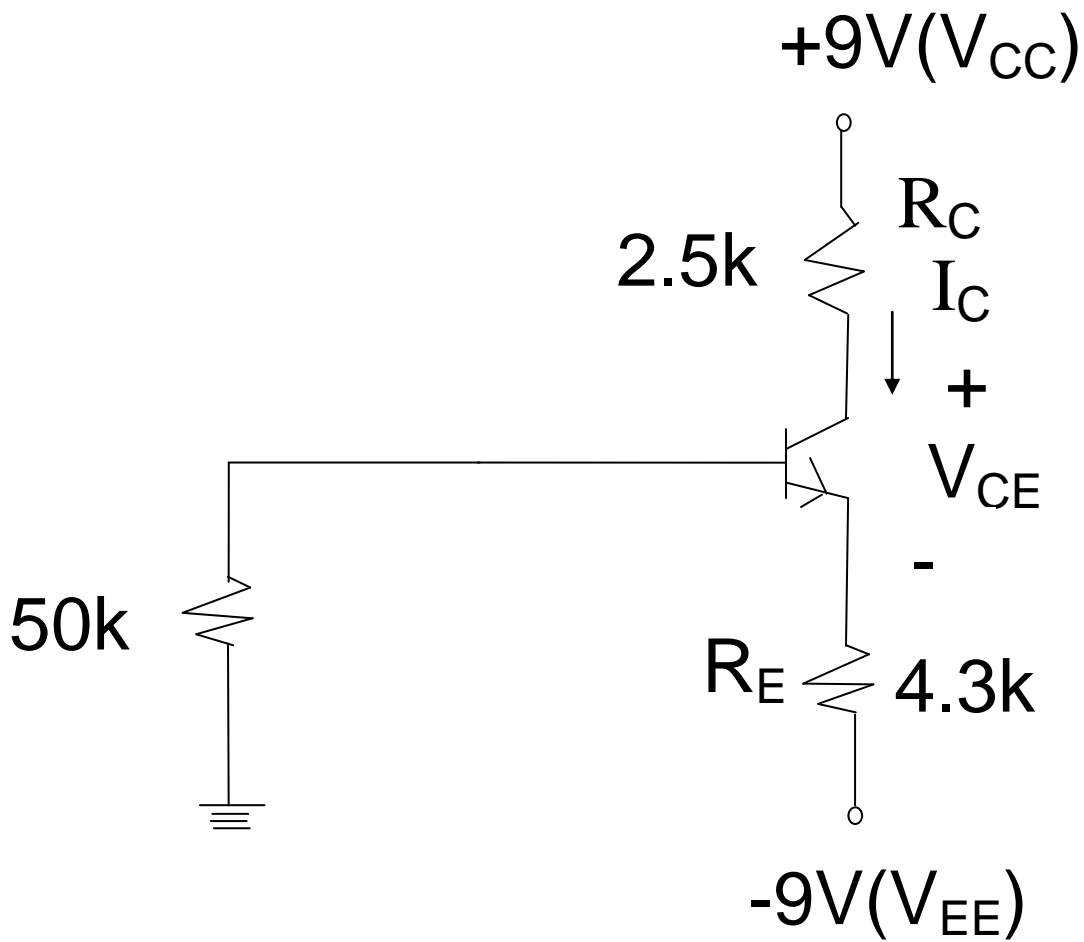2.4 Find out the operating point current I_{CQ} , and voltage V_{CEQ} in the circuit shown.

($V_{BE} = 0.7\text{ V}$, β of transistor is 200).



Solution:-

Considering the potential difference across the resistor R_E , the emitter current I_E ($\approx I_C$) may be written as,

$$I_E \approx I_C = \frac{V_{EE} - V_{BE}}{R_E} = \frac{9 - 0.7}{4.3 \times 10^3}$$

$$\text{or } I_C = I_{CQ} = 1.93 \text{ mA}$$

Voltage summation in the collector circuit leads to,

$$V_{CC} = R_C I_C + V_{CE}$$

$$\text{or } V_{CE} = V_{CC} - R_C I_C$$


$$= 9 - 2.5 \times 10^3 \times 1.93 \times 10^{-3}$$

$$= 9 - 4.83$$

$$\text{or } V_{CE} = V_{CEQ} = 4.17 \text{ V}$$

2.5 Calculate the approximate value for the base resistor R_B which will forward bias the emitter junction of silicon transistor ($\beta = 100$) in the circuit. Collector – emitter voltage V_{CE} of 2.5 V reverse biases the collector.

($V_{BE} = 0.7V$)

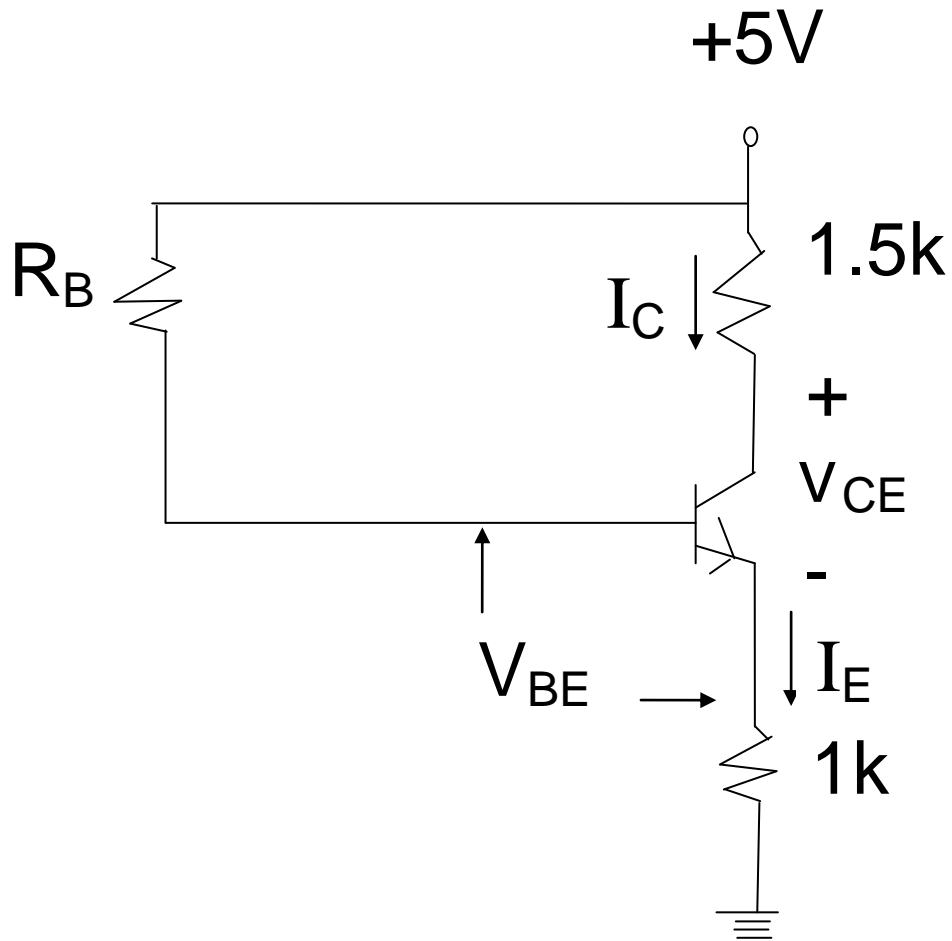

Solution:-

We assume that the emitter junction is in forward bias and $V_{BE} = 0.7V$.

Summation of voltages in the base-emitter circuit results in,

$$R_B I_B + V_{BE} + R_E I_E = V_{CC}$$

Since $I_C = I_E$,

$$\text{and } \beta I_B \text{ or } I_B = \frac{I_C}{\beta} = \frac{I_E}{\beta}$$

Then above equation yields,

$$R_B \cdot \frac{I_E}{\beta} + V_{BE} + R_E I_E = V_{CC}$$

$$\text{or } I_E \left(\frac{R_B}{\beta} + R_E \right) = V_{CC} - V_{BE} = 5.0 - 0.7$$

$$\text{or } I_E \left(\frac{R_B}{\beta} + R_E \right) = 4.3 \quad \text{------(A)}$$

Now, summation of voltages in the collector – emitter circuit gives,

$$R_C I_C + V_{CE} + R_E I_E = V_{CC}$$

Because $I_C = I_E$

And substituting for other parameters

$$I_E (R_C + R_E) = V_{CC} - V_{CE} = 5.0 - 2.5 = 2.5$$

$$\text{or } I_E = \frac{2.5}{(R_C + R_E)} = \frac{2.5}{(1.5 + 1) \times 10^3} = 1 \text{mA}$$


Substituting $I_E = 1 \text{mA}$ in eqⁿ (A)

$$1 \times 10^{-3} \left(\frac{R_B}{100} + 1 \times 10^3 \right) = 4.3$$

$$R_B = 330 \times 10^3 \Omega$$

$$\text{or } R_B = 330 \text{ k}\Omega$$

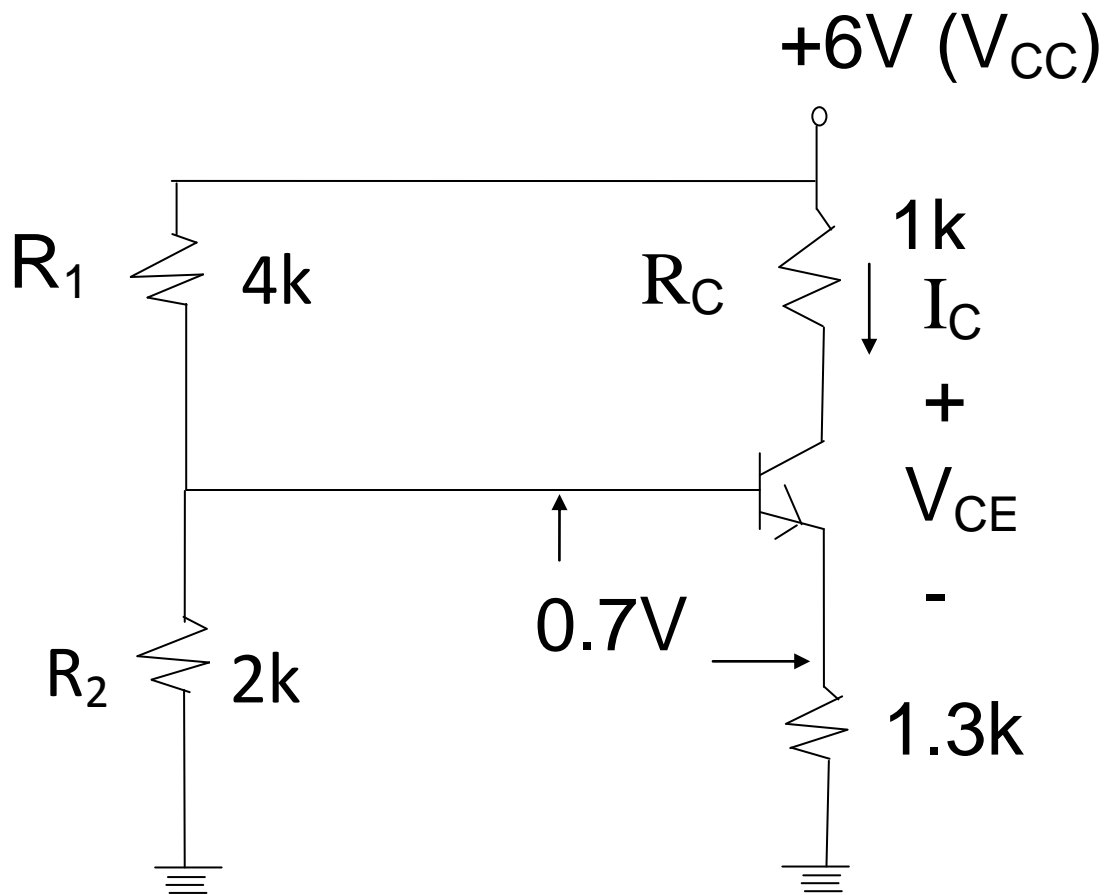2.6 The operating point values of current $I_C (= I_{CQ})$ and voltage $V_{CE} (= V_{CEQ})$ in the circuit have magnitudes of 0.9 mA and 3.72 V respectively when the current gain β for the transistor is 100. The transistor in the circuit is replaced by another one with $\beta = 200$. Calculate the new values of I_{CQ} and V_{CEQ} . What do you infer?



Solution:-

Thevenized voltage V_{th} across R_2 is

$$\begin{aligned}V_{TH} &= \frac{2 \times 10^3}{2 \times 10^3 + 4 \times 10^3} \times V_{CC} \\ &= \frac{2}{6} \times 6 \\ &= 2V\end{aligned}$$

That is $V_{TH} = 2V$

And, as we have derived the relation earlier,

$$I_E = I_{CQ} = \frac{V_{TH} - V_{BE}}{R_E + R_{TH}/\beta}$$

Where Thevenized resistance R_{TH} is

$$R_{TH} = R_1 \parallel R_2 = 4k \parallel 2k = 1.33 \text{ k}\Omega,$$

Then with $\beta = 200$,

$$\begin{aligned}I_E = I_C = I_{CQ} &= \frac{2 - 0.7}{1.3 \times 10^3 + 0.006 \times 10^3} \\ \text{or } I_{CQ} &= 0.995 \text{ mA}\end{aligned}$$

Further, summation of voltage in the collector circuit under the condition

$I_C = I_E$ leads to,

$$V_{CC} = I_C (R_C + R_E) + V_{CE}$$

$$\begin{aligned}\text{Or, } V_{CE} = V_{CEQ} &= V_{CC} - I_C (R_C + R_E) \\ &= 6V - 0.995 \text{ mA} (1k + 1.3k)\end{aligned}$$


$$\text{Or } V_{CEQ} = 3.71V$$

Inference:

The circuit is highly stable as the change in collector current is $0.995 - 0.99 = 0.005$ mA only (change is $\approx 0.5\%$) which is negligible. Similarly V_{CE} changes only 0.3% which is also negligible when β changes by 100% i.e from 100 to 200.

(2.7) Calculate the value of resistor R_B in the circuit shown to put V_{CE} at 3.0V

($V_{BE} = 0.7V$ and $\beta = 80$)

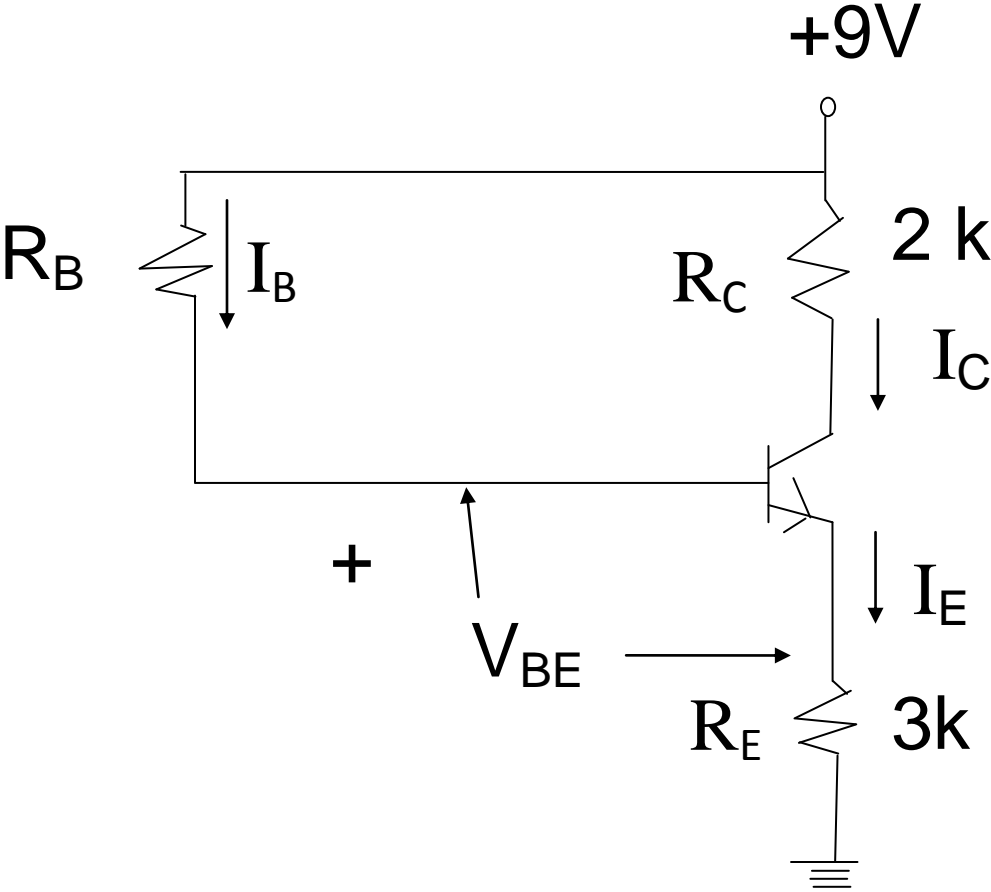

Solution:-

Summation of voltages in the base-emitter circuit gives,

$$R_B I_B + V_{BE} + R_E I_E = V_{CC}$$

Now, $V_{BE} = 0.7 \text{ V}$, and $I_C = I_E$.

$$\text{Also, } I_B = \frac{I_C}{\beta} = \frac{I_C}{80}$$

Substituting these in above equation, and taking resistances in $k\Omega$,

$$\begin{aligned} R_B \cdot \frac{I_C}{80} + 3k \times I_C &= V_{CC} - V_{BE} \\ &= 9 - 0.7 = 8.3 \end{aligned}$$

$$\text{or } R_B \cdot \frac{I_C}{80} + 3k \cdot I_C = 8.3 \text{ -----(A)}$$

Summation of voltages in the collector circuit results in,

$$I_C R_C + V_{CE} + I_E \times 3k = 9V$$

$$\text{or } I_C \times 2k + 3.0V + I_C \times 3k = 9V$$

$$\text{or } I_C (2k + 3k) = 9 - 3 = 6V$$

$$\text{or } I_C = \frac{6V}{5k} = 1.2mA$$

Substituting the value of I_C in eqn (A)

$$R_B \cdot \frac{1.2}{80} + 3k \times 1.2mA = 8.3V$$

$$\text{or } R_B = \frac{4.7}{0.015mA} = 313.3k$$

$$R_B \approx 313k$$