

Unit – V

Field Effect Transistors and MOSFETS


5.1 In a JFET drain current is maximum when V_{GS} is

- (a) Zero
- (b) Positive
- (c) Negative
- (d) Equal to pinch-off voltage

5.2 An n-channel JFET has pinch-off voltage $V_p = -4$ volts. Given $V_{GS} = -1V$, the minimum V_{DS} for the device to operate in the pinch-off region will be


- (a) + 1V
- (b) + 3V
- (c) + 4V
- (d) + 5V

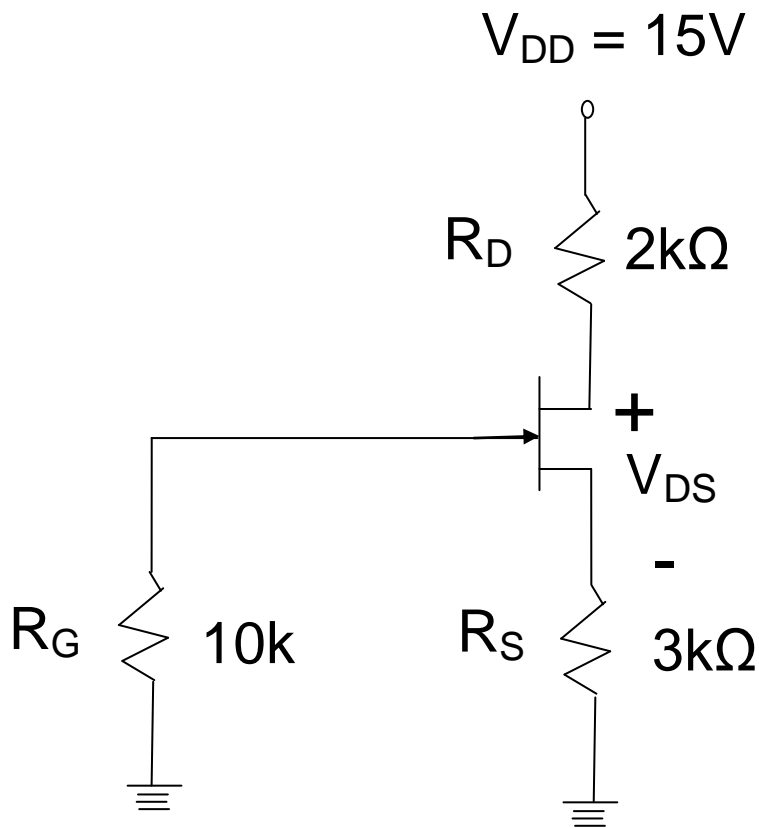5.3 In the self bias circuit for n-JFET shown in figure, V_{GS} is




- (a) + 5V
- (b) - 5V
- (c) +6V
- (d) -6V

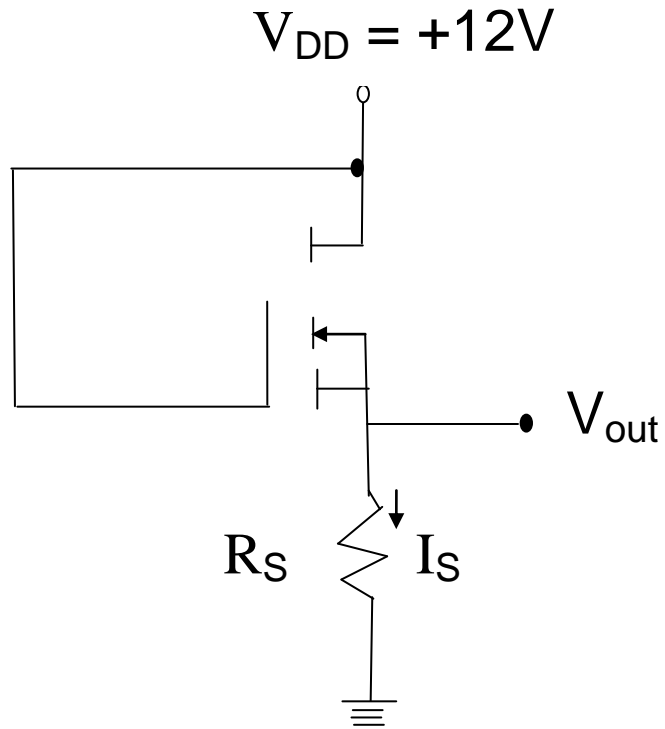5.4 Pick up the correct value of R_S that will give $V_{out} = 5V$. The parameters of MOSFET in the circuit shown are : $V_T = 2V$ and device constant $k = 500\mu A/V^2$




- (a) 400 Ω
- (b) 600 Ω
- (c) 800 Ω
- (d) 1200 Ω

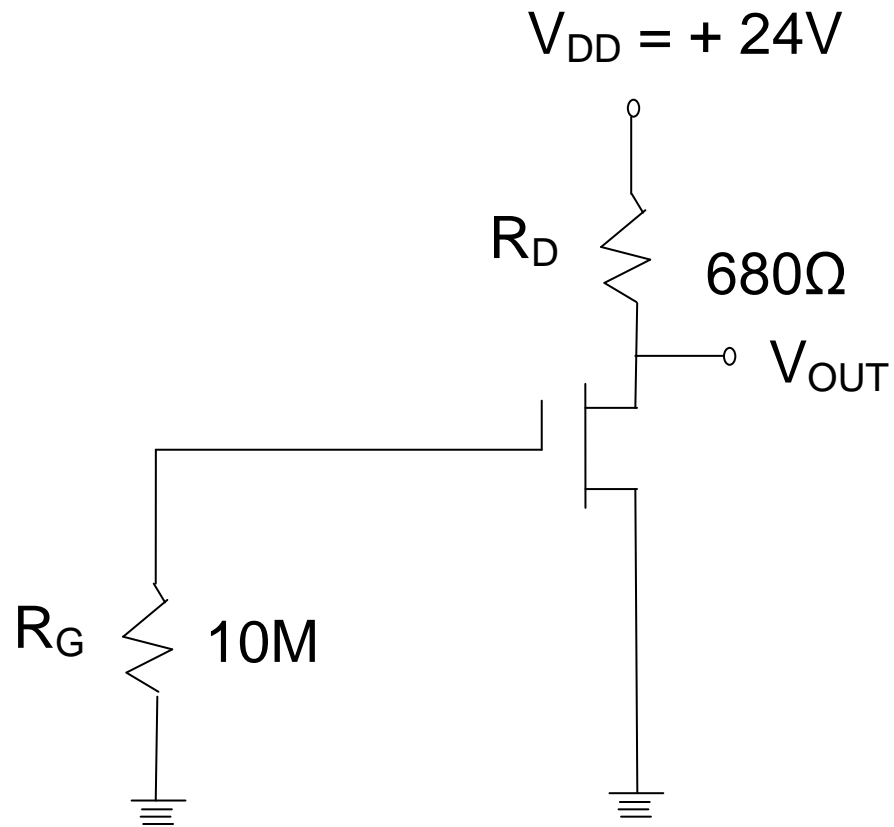5.5 The DMOSFET in the circuit shown has $V_{GS(OFF)} = -6V$ and $I_{DSS} = 10mA$. V_{OUT} is,



- (a) 21.6 V
- (b) 17.2 V
- (c) 19.6 V
- (d) 15.2 V

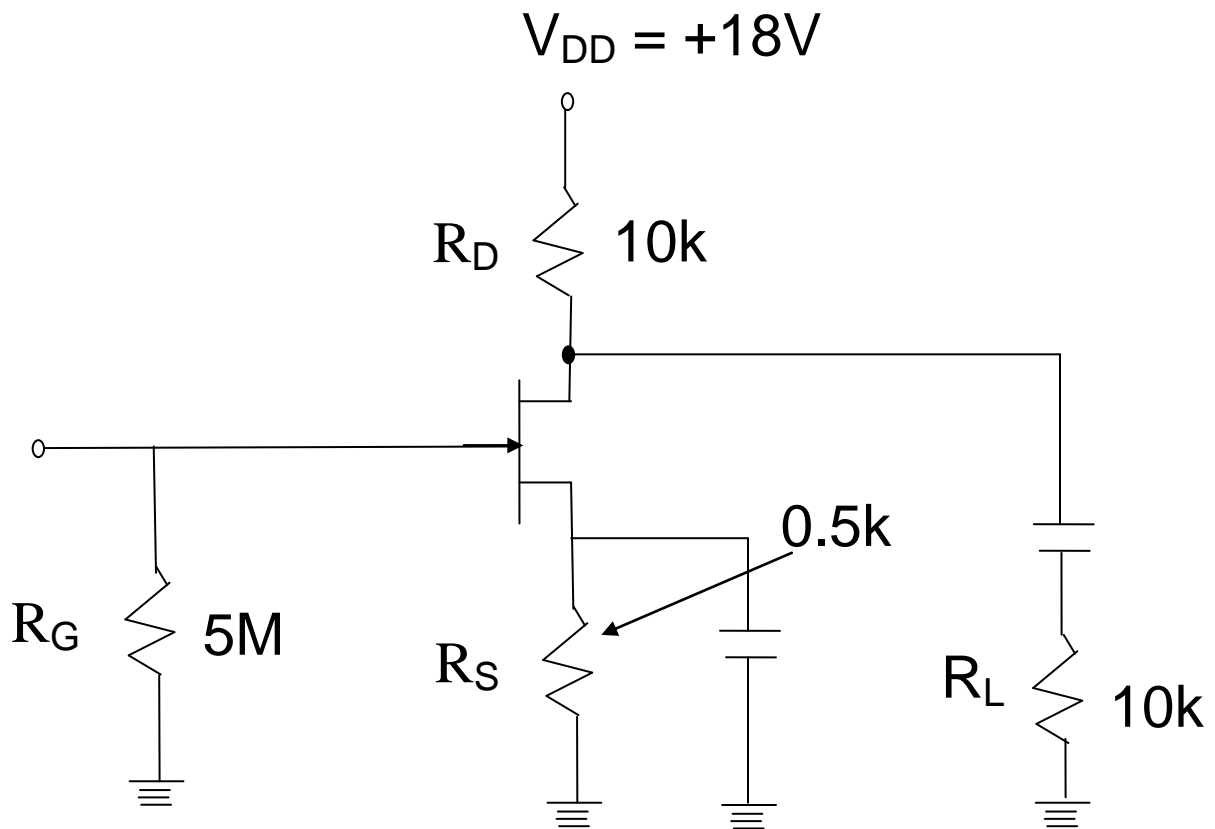5.6 For the common-source amplifier circuit shown, how much is the voltage gain?
 The transconductance of the transistor is $4000\mu\text{S}$. Capacitors may be taken as short as signal frequency.



- (a) 40
- (b) 20
- (c) 10
- (d) 6.6

5.7 The power consumption is least in CMOS circuits as compared to NMOS and PMOS circuits. This is because, in CMOS

- (a) Both the transistors remain in off-state most of the time.
- (b) Small voltages are required.
- (c) High value resistors are used
- (d) Both the transistors go to on-state simultaneously only for a very short time during change of states.

5.8 Which of the following statements is not true for common source (CS) amplifier.

- (a) It is most widely used as compared to common-drain or common-gate amplifiers
- (b) It has high voltage gain
- (c) There is no phase inversion
- (d) It has high input impedance.

Answers:

- 5.1 (a) 5.2 (b) 5.3 (d) 5.4 (a) 5.5 (b) 5.6 (b)
5.7 (d) 5.8 (c)