



Lecture #3 :

Note Title

2/23/2010

- Sense the difference between desired and actual
- Integrate the error (difference)
- Drive the output such that the error reduces

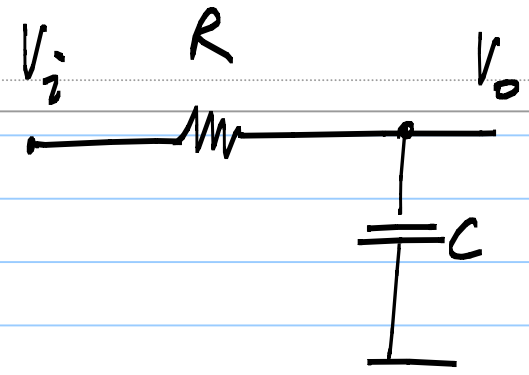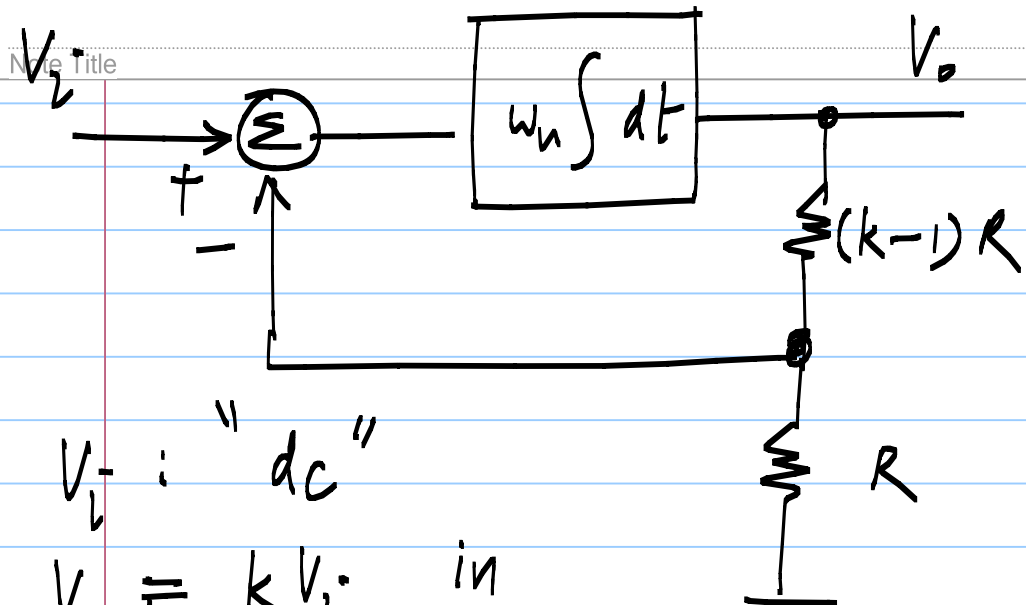Any error in sensing translates to an error in the output



12/23/2010

V_i : "dc"
 $V_o = kV_i$ in steady state

$$RC \cdot \frac{dV_o}{dt} = V_i - V_o$$

$$\frac{1}{\omega_n} \cdot \frac{dV_o}{dt} = \underline{\underline{V_i - \frac{V_o}{k}}}$$


$$V_o(t) = V_o(0) \exp\left(-\frac{\omega_n}{k} \cdot t\right) + V_i \left[1 - \exp\left(-\frac{\omega_n}{k} t\right) \right]$$


Response of the negative feedback amplifier to a

Note Title

12/23/2010

Step input.

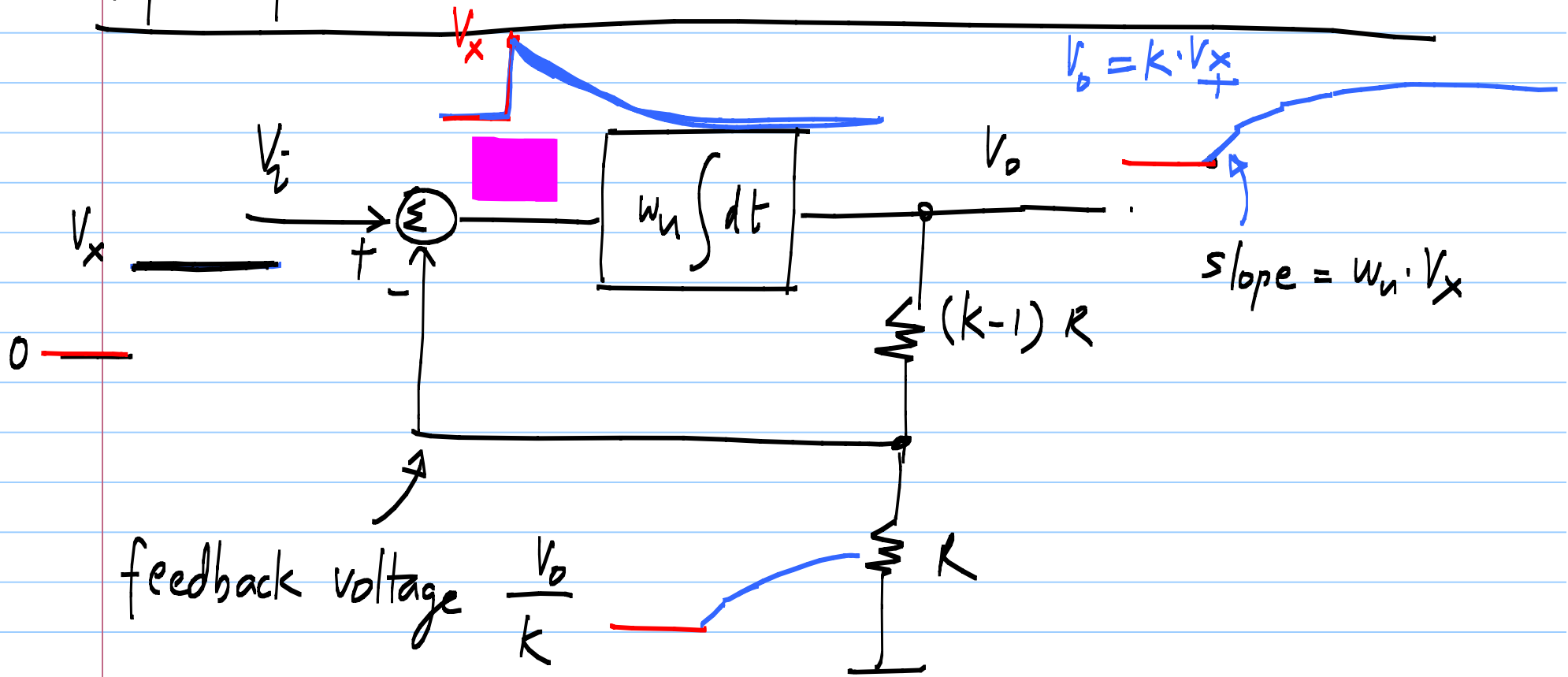

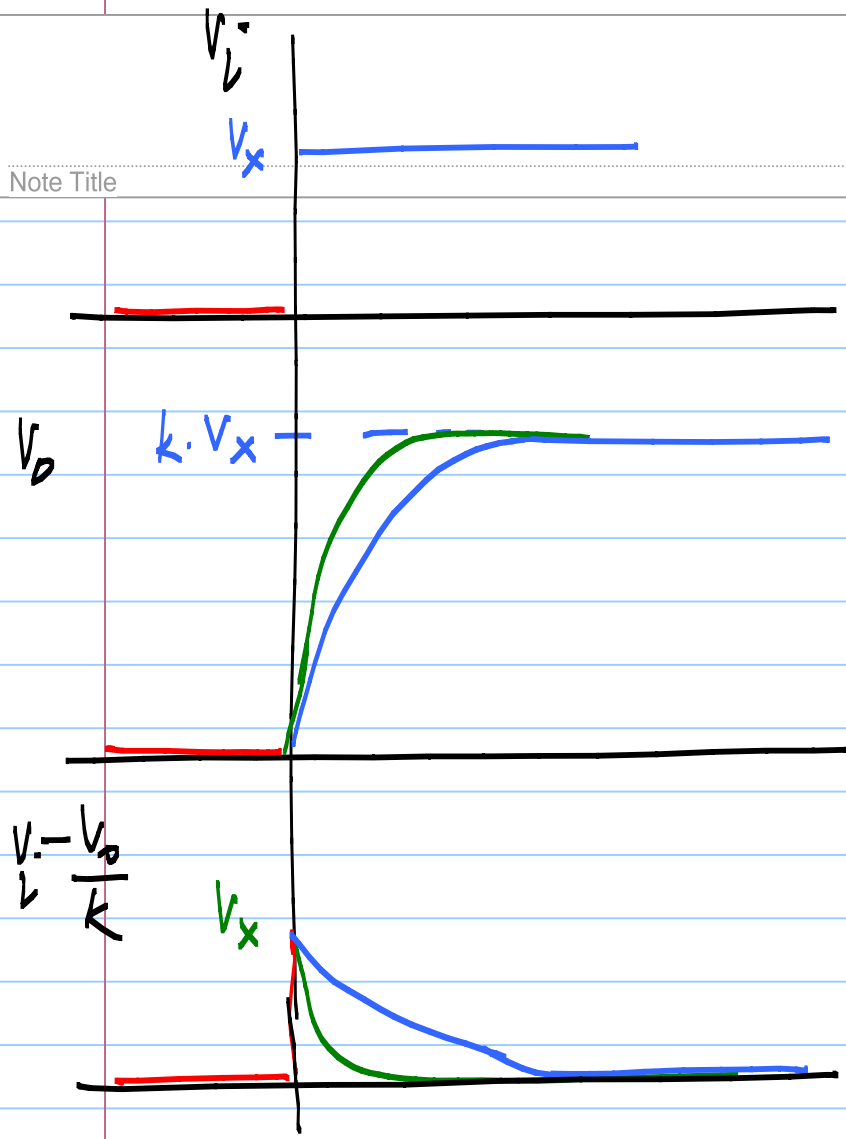

$4 - 6 \left(\frac{k}{\omega_n} \right)$ to reach 99%
of steady state



Higher ω_n :

- faster approach to steady state
- smaller energy ("area") of the error $\frac{v_i - v_o}{k}$

$$V_o(t) = V_o(0) \exp\left(-\frac{\omega_n t}{k}\right) + kV_i \cdot \left[1 - \exp\left(-\frac{\omega_n t}{k}\right)\right]$$

(for constant V_i)


time constant = $\frac{k}{\omega_n}$

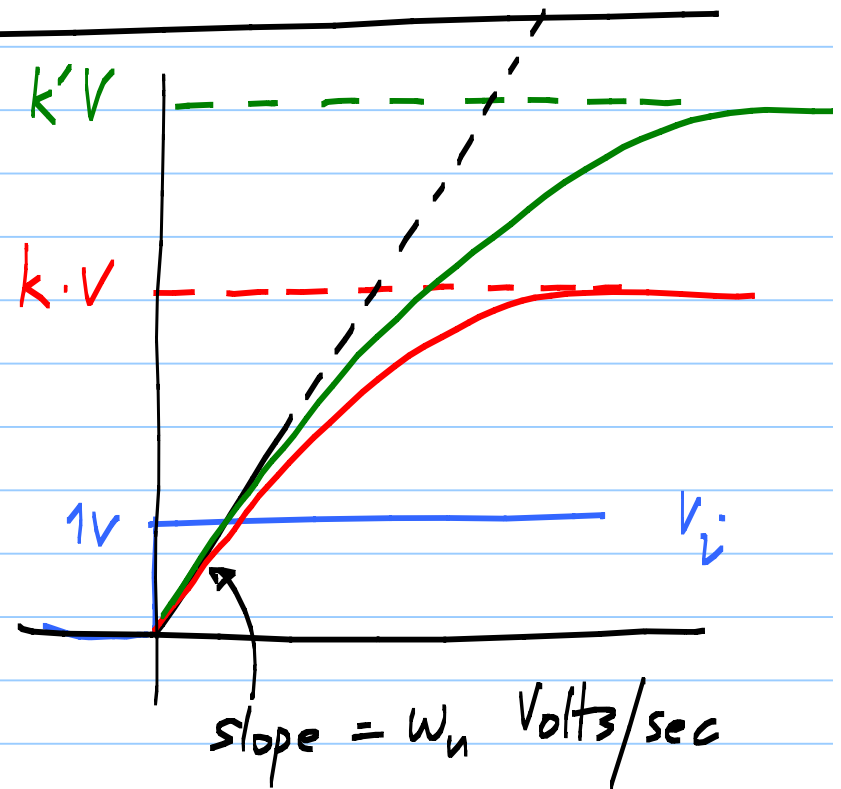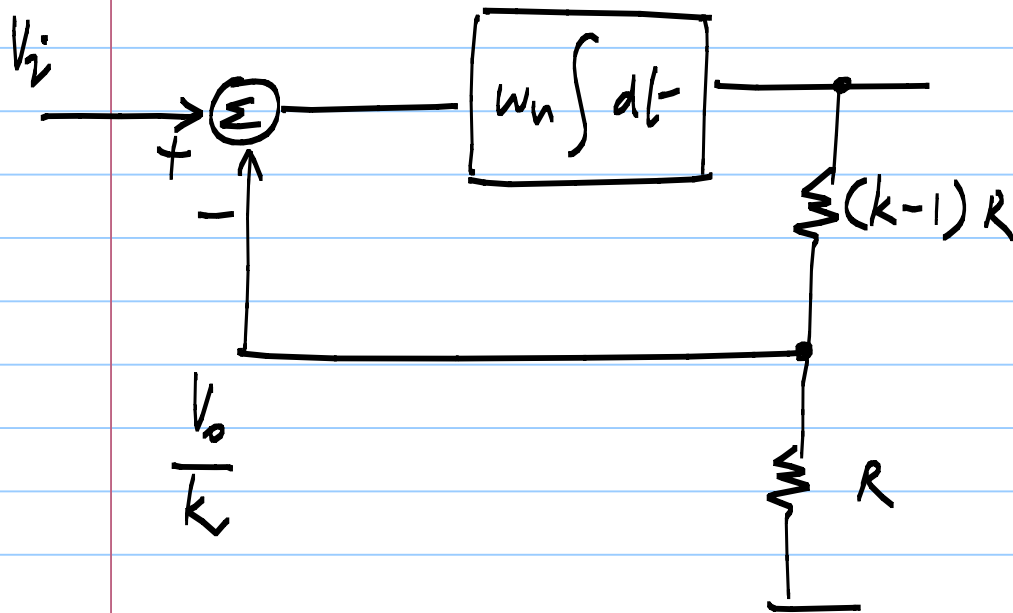

Response of the amplifier to sinusoidal inputs

Note Title

12/23/2010

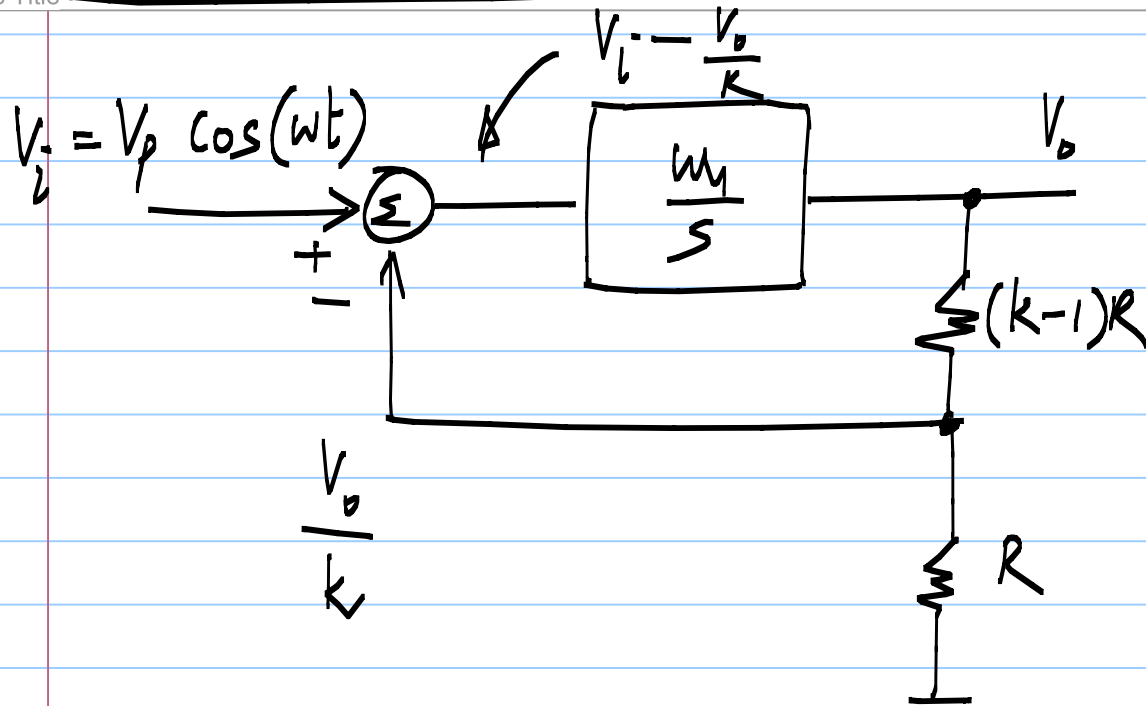

$$\left(V_i - \frac{V_o}{k} \right) \cdot \frac{\omega_n}{s} = V_o$$

$$V_i \frac{\omega_n}{s} = V_o \left(\frac{\omega_n}{k \cdot s} + 1 \right)$$

$$\frac{V_o}{V_i} = \left[\frac{\omega_n/s}{\frac{\omega_n}{k \cdot s} + 1} \right]$$

$$H(s) = \frac{V_o}{V_i} = \frac{k}{1 + k \frac{s}{\omega_n}}$$


$$H(0) = k$$

$$\times \frac{k \cdot s}{\omega_n}$$

Integrator:

Note Title

12/23/2010

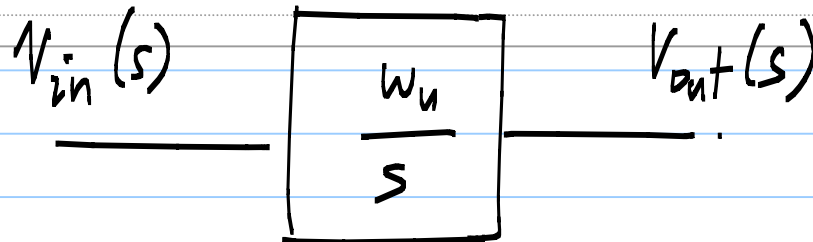

$$\underline{V_{out}(s) = \frac{\omega_n}{s} \cdot V_{in}(s)}$$

$$\underline{V_{out}(t) = \omega_n \int V_{in}(t) dt}$$


$$s = j\omega \quad V_{out}(j\omega) = \frac{\omega_n}{j\omega} V_{in}(j\omega)$$

$$\frac{V_{out}}{V_{in}} = \frac{\omega_n}{j\omega}$$

Transfer function of the integrator : $H(j\omega) = \frac{\omega_n}{j\omega}$

Note Title


12/23/2010

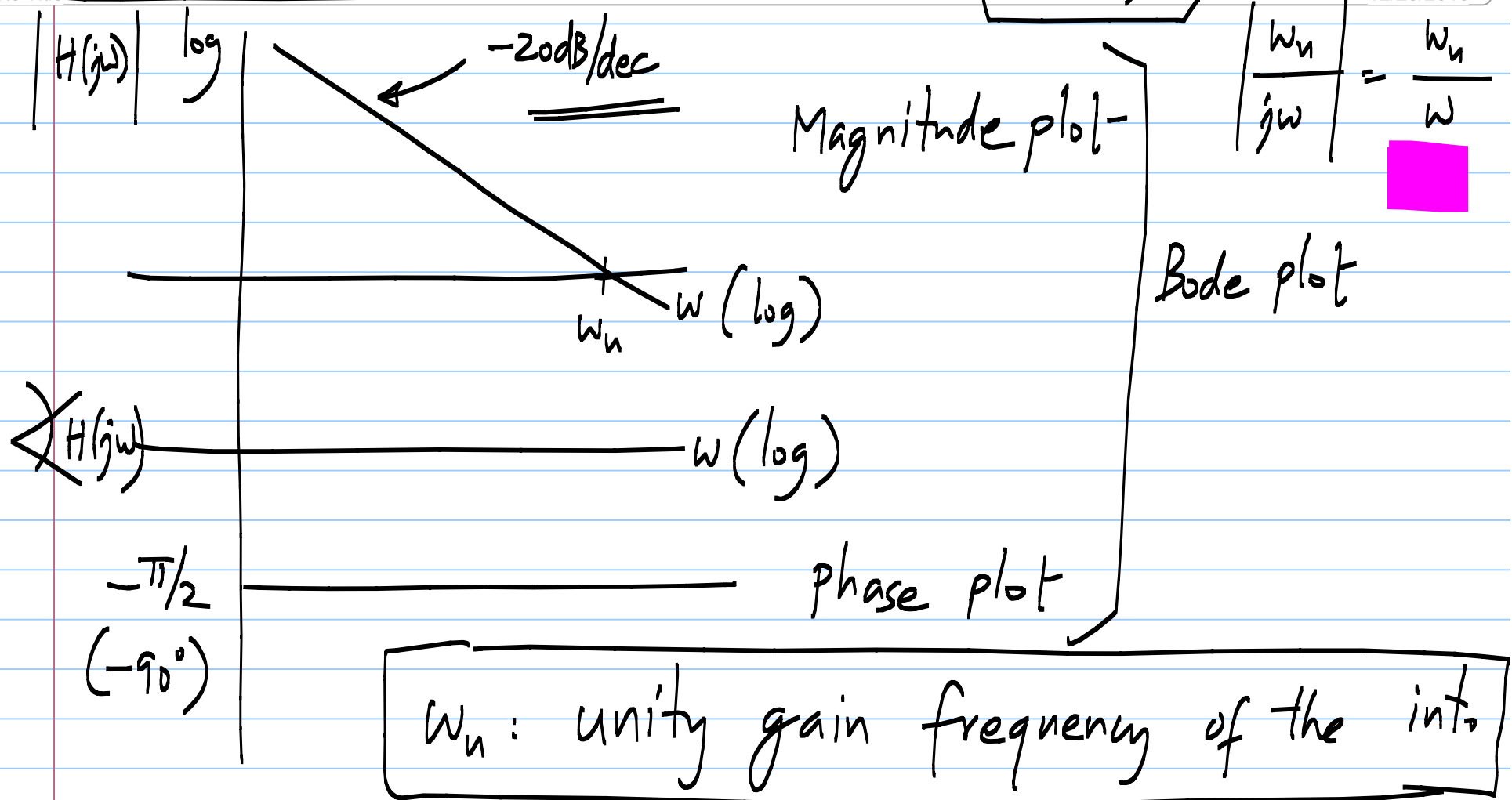

$$H(s) = \frac{V_o}{V_i} = \frac{k}{1 + s \cdot \frac{k}{\omega_n}}$$

12/23/2010

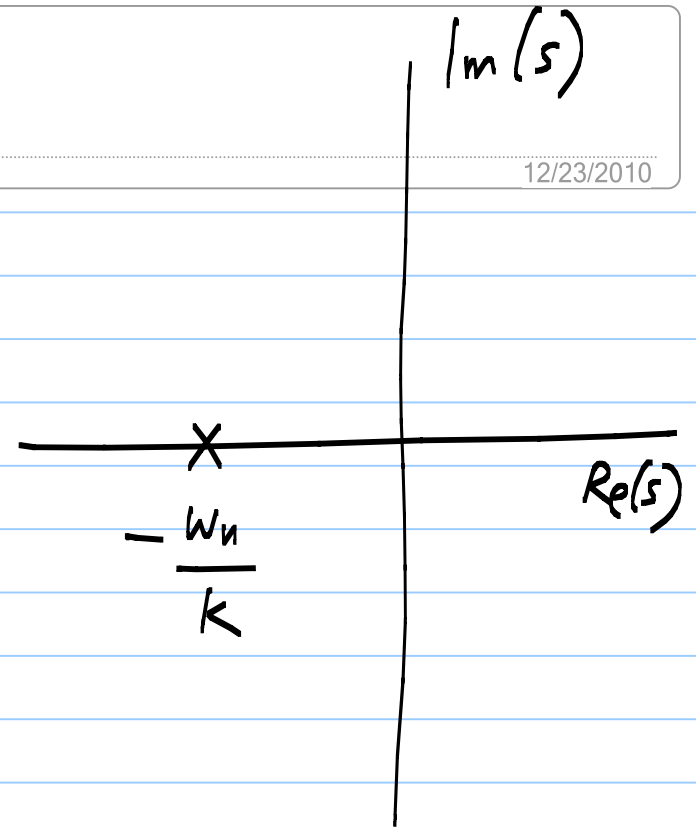- DC gain $(H(0)) = k$
- pole at $-\frac{\omega_n}{k}$



Negative feedback amplifier transfer function :

Note Title

12/23/2010

$$H(s) = \frac{k}{1 + s \cdot \frac{k}{\omega_n}}$$

$$H(j\omega) = \frac{k}{1 + j\omega \cdot \frac{k}{\omega_n}}$$

$$|H(j\omega)| = \frac{k}{\sqrt{1 + \frac{k^2 \omega^2}{\omega_n^2}}}$$

$$\angle H(j\omega) = -\tan^{-1}\left(\frac{\omega \cdot k}{\omega_n}\right)$$

