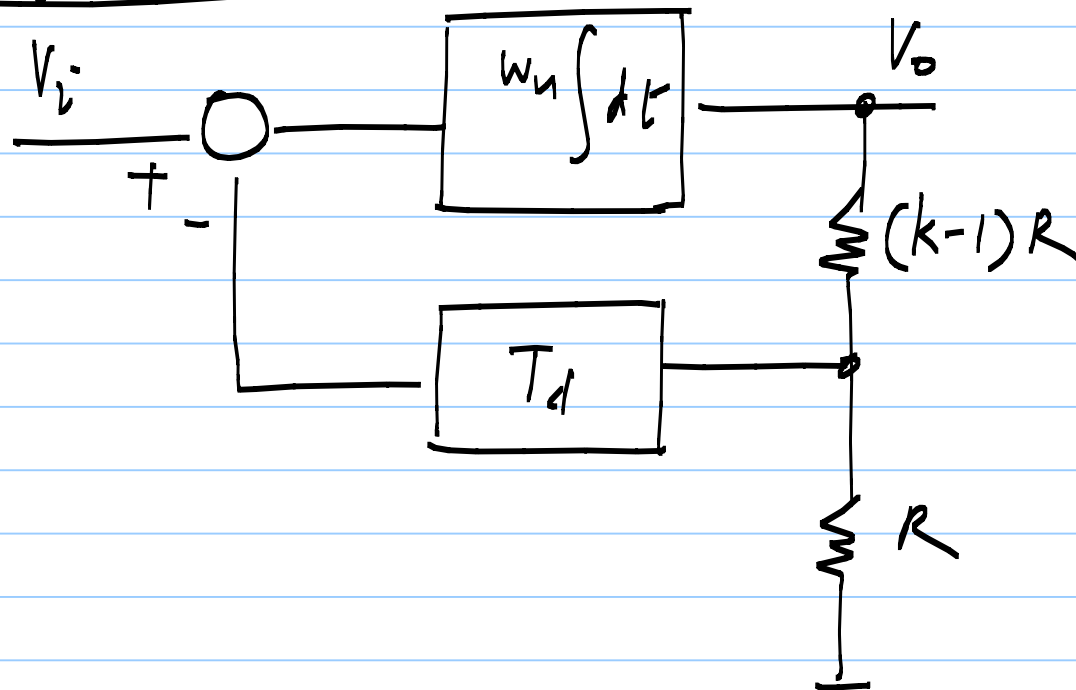


Negative feedback amplifier with delay



$$\frac{dV_o(t)}{dt} = -\frac{w_u}{k} V_o(t - T_d)$$

$$V_o(t) = V_p \exp(\sigma t)$$

$$\sigma' + \exp(-\sigma' T) = 0$$

* Has two solutions for $T < 1/e$

T	σ_1'	σ_2'
0	-1	$-\infty$
0.1	-1.1	-35.8
$1/e$	$-e$	$-e$

$$\sigma' = \frac{\sigma}{\omega_n/k}$$

$$T = \frac{T_d}{k/\omega_n}$$

$$\sigma = e \cdot \frac{\omega_n}{k}$$

$$2.718 \frac{\omega_n}{k}$$


With delay faster, no overshoot

nkeef539 neg1bwdelay schematic : Jan 12 23:34:08 2011

Transient Response

Note Title

11

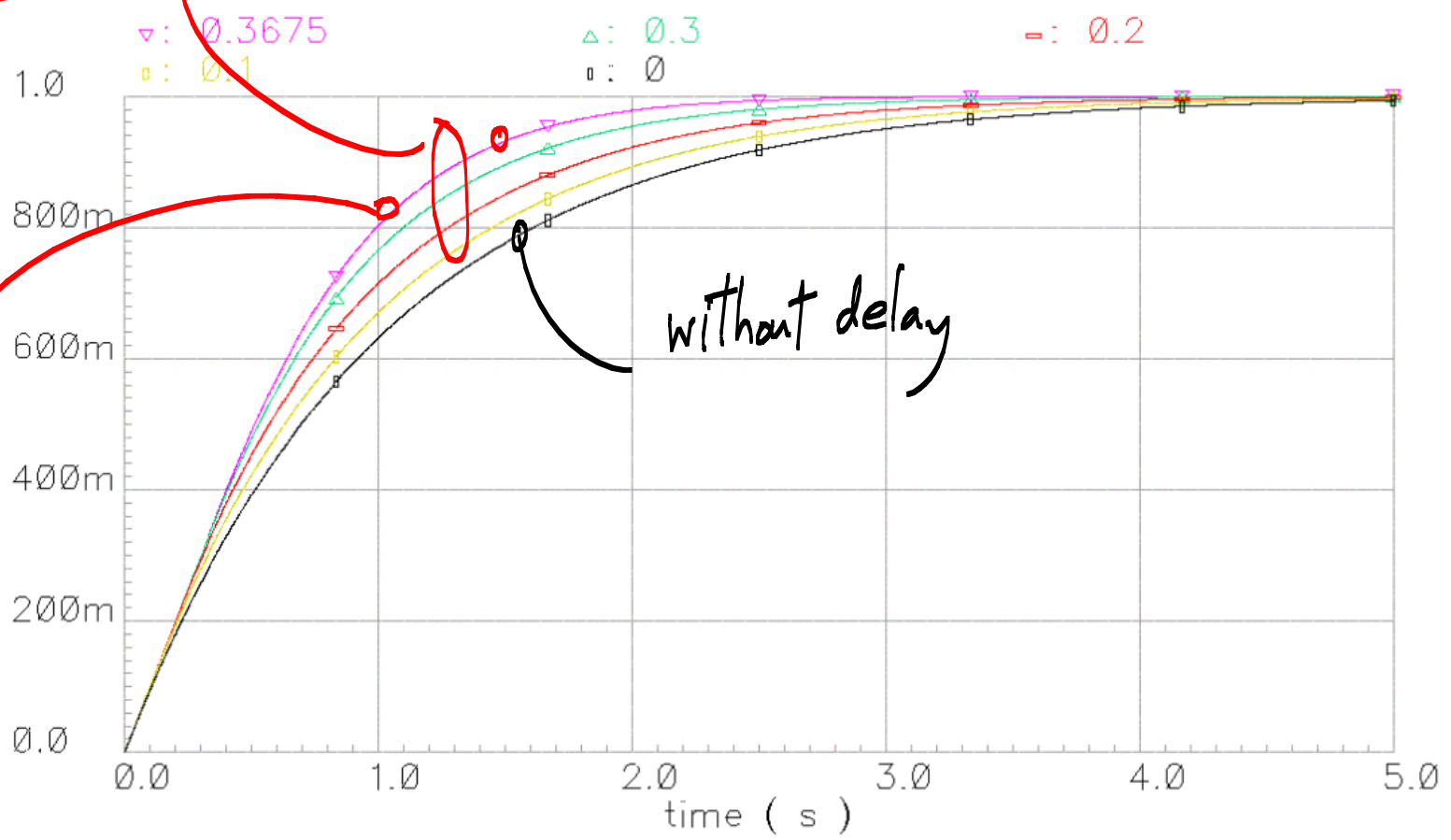

$$\underline{T > \frac{1}{\omega}}$$

$$\underline{\frac{dV_o}{dt} = -\frac{\omega_n}{K} \cdot V_o(t - T_d)}$$

$$V_o(t) = \exp(\sigma t) \quad \underline{\sigma: \text{real}}$$

$$\underline{V_o(t) = \exp((\sigma + j\omega)t)}$$

$$(\sigma + j\omega) \cdot \cancel{\exp((\sigma + j\omega)t)} = -\frac{\omega_n}{K} \cancel{\exp((\sigma + j\omega)t)} \cdot \exp(-(\sigma + j\omega)T_d)$$

$$\sigma + j\omega = -\frac{\omega_n}{k} \cdot \exp(-(\sigma + j\omega) \cdot T_d)$$

$$= -\frac{\omega_n}{k} \cdot \exp(-\sigma T_d) \cdot \exp(-j\omega T_d)$$

$$= -\frac{\omega_n}{k} \exp(-\sigma T_d) \left[\begin{array}{l} \cos(\omega T_d) \\ -j \sin(\omega T_d) \end{array} \right]$$

$$\left. \begin{array}{l} \sigma = -\frac{\omega_n}{k} \exp(-\sigma T_d) \cos(\omega T_d) \\ \omega = \frac{\omega_n}{k} \exp(-\sigma T_d) \sin(\omega T_d) \end{array} \right\} \text{Solve for } \sigma, \omega$$

$$\sigma = -\frac{\omega_n}{k} \exp(-\sigma T_d) \cos(\omega T_d)$$

$$\omega = \frac{\omega_n}{k} \exp(-\sigma T_d) \sin(\omega T_d)$$

$$\left[\begin{array}{l} \sigma' = -\exp(-\sigma' T) \cos(\omega' T) \\ \omega' = \exp(-\sigma' T) \cdot \sin(\omega' T) \end{array} \right]$$

$$\sigma' = \frac{\sigma}{\omega_n/k}$$

$$\omega' = \frac{\omega}{\omega_n/k}$$

$$T = \frac{T_d}{k/\omega_n}$$

$$\sigma' = -\exp(-\sigma' \tau) \cos(\omega' \tau) \quad (1)$$

$$\omega' = \exp(-\sigma' \tau) \cdot \sin(\omega' \tau) \quad (2)$$

$$(1)^2 + (2)^2 : \quad \sigma'^2 + \omega'^2 = \exp(-2\sigma' \tau) \quad (3)$$

$$\frac{(1)}{(2)} = -\frac{\cos(\omega' \tau)}{\sin(\omega' \tau)} \quad (4)$$


$$\sigma'^2 + \omega'^2 = \exp(-2\sigma'\tau)$$

Note Title

1/19/2011

$$\sigma'^2 + \omega'^2 = 1$$

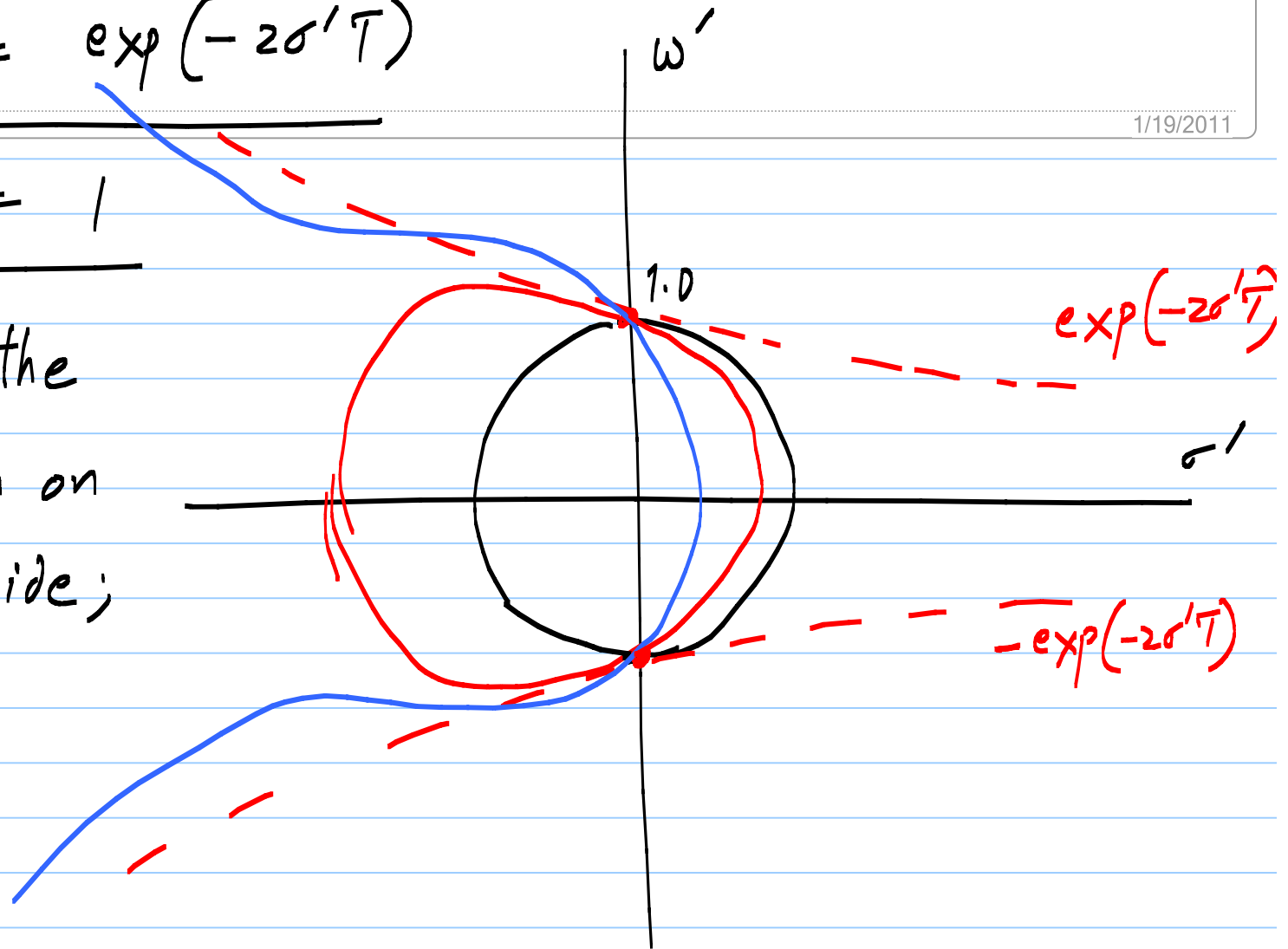For $\tau > 1/e$, the curve is open on the left side; passes through $(0, 1)$ & $(0, -1)$




$$\frac{\sigma}{\omega'} = \frac{\cos(\omega' T)}{\sin(\omega' T)}$$

$$\sigma' = \omega' \frac{\cos(\omega' T)}{\sin(\omega' T)}$$

$$= \frac{\omega' T}{T} \cdot \frac{\cos(\omega' T)}{\sin(\omega' T)}$$

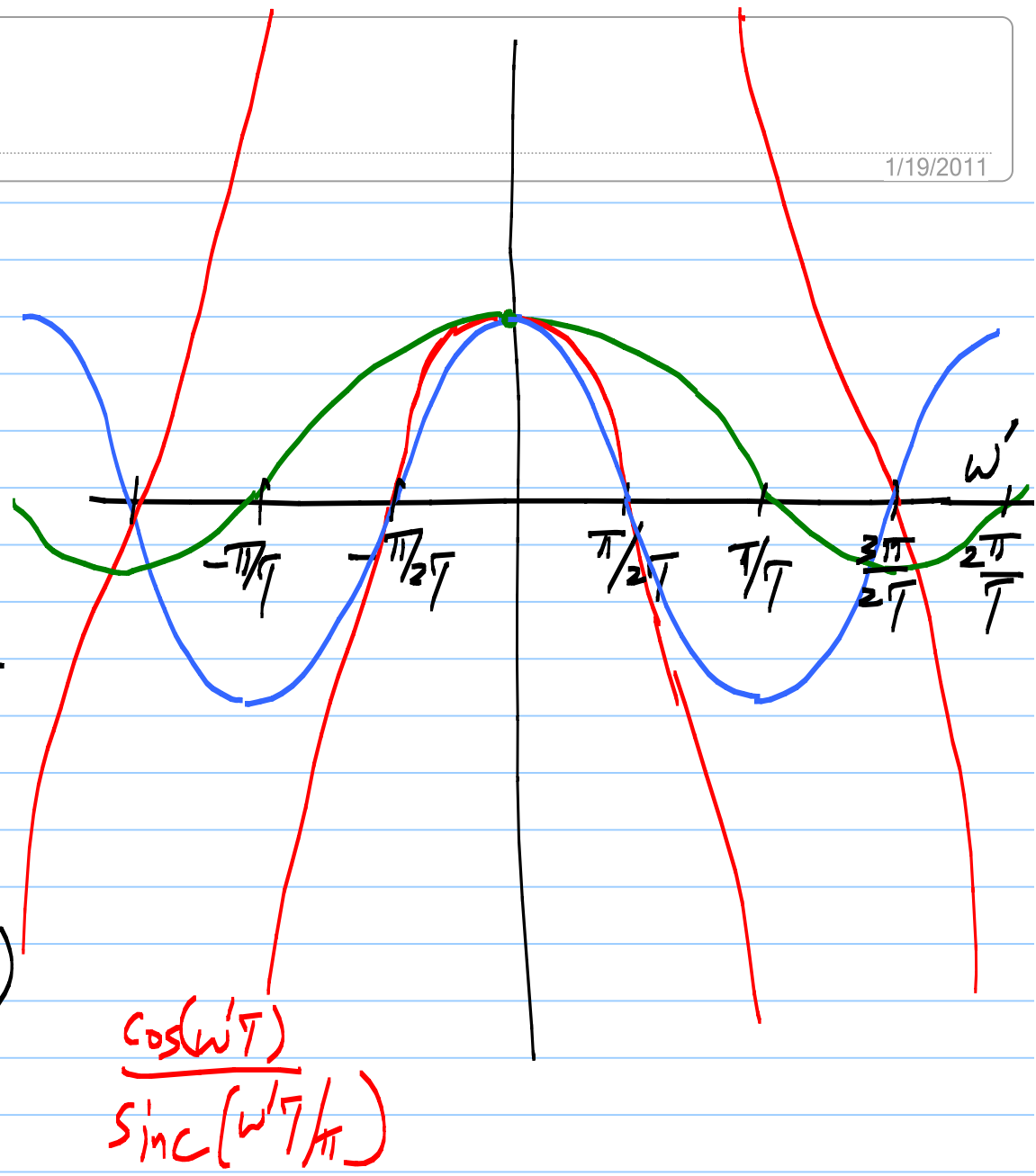
$$= \frac{1}{T} \cdot \frac{\cos(\omega' T)}{\text{sinc}\left(\frac{\omega' T}{\pi}\right)}$$



$$\sigma' = -\frac{1}{T} \cdot \frac{\cos(\omega'T)}{\text{sinc}\left(\frac{\omega'T}{\pi}\right)}$$

Note Title

1/19/2011

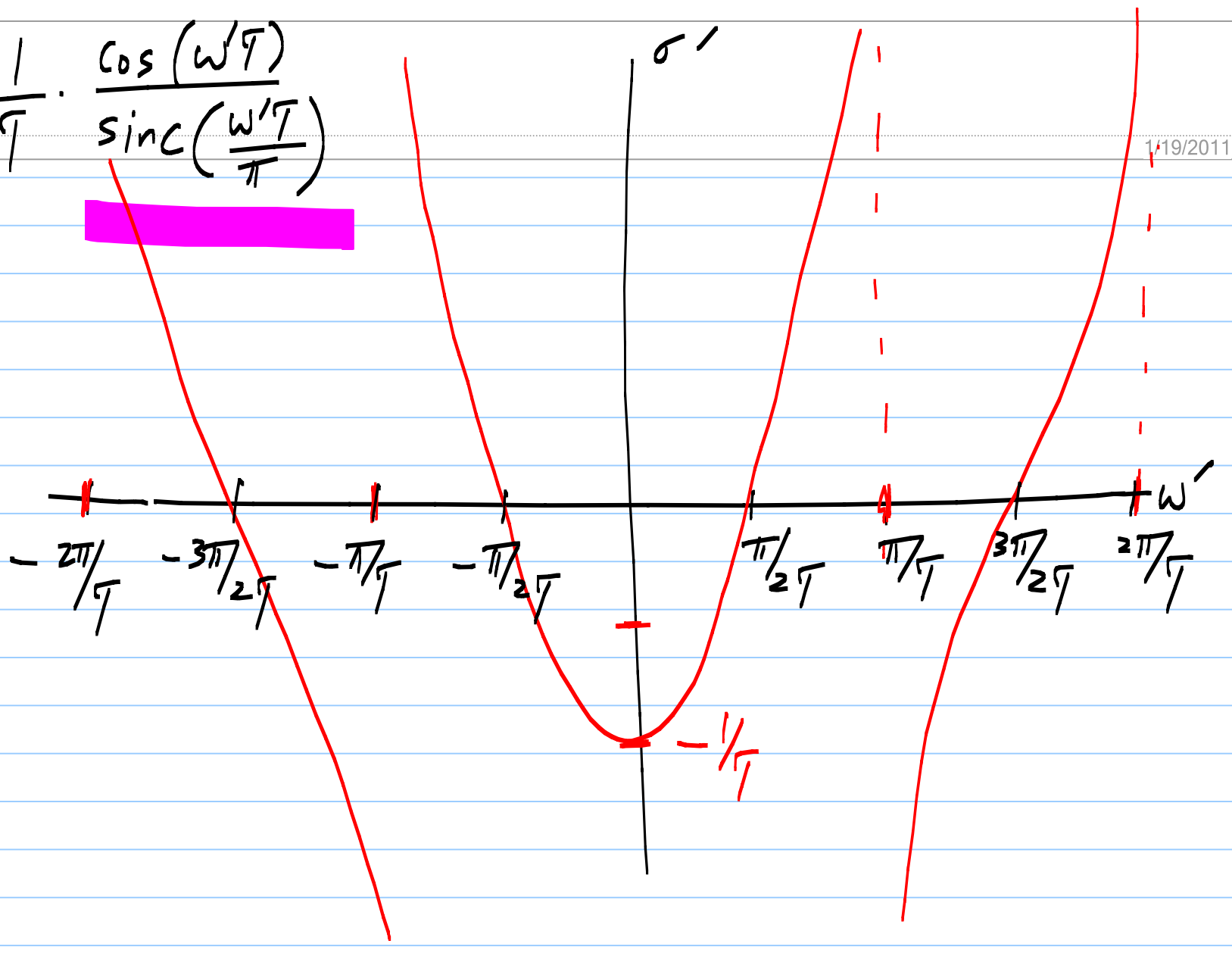

$$\sigma'^2 + \omega'^2 = \exp(-2\sigma'\tau)$$

Note Title


1/19/2011

$$\sigma' = -\frac{1}{\tau} \frac{\cos \omega'\tau}{\text{sinc}(\omega'\tau/\pi)}$$

Instability ($\sigma' > 0$)

for $\pi/2\tau < 1$

$$\tau > \pi/2$$

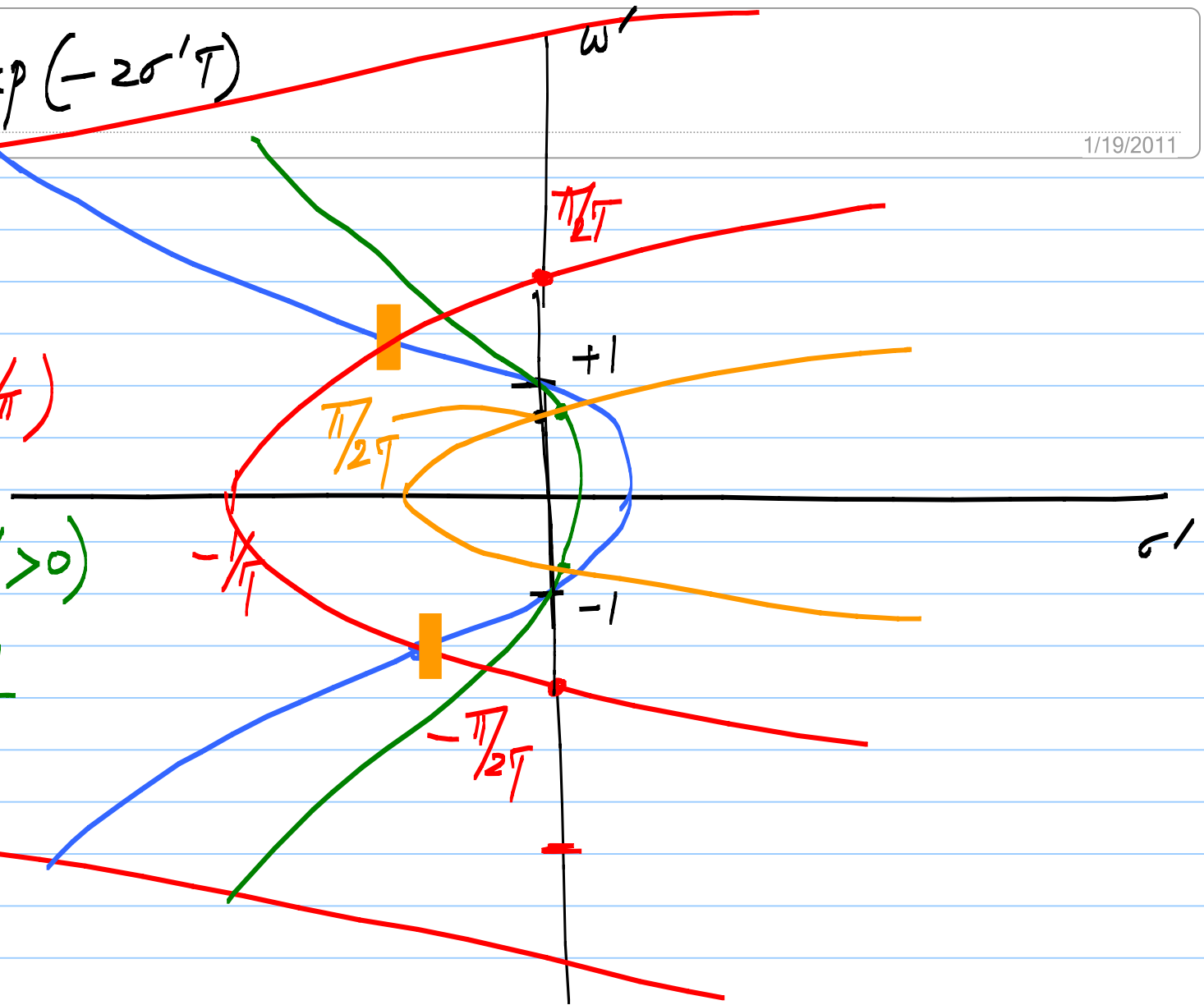

For $T > 1/e$:

Note Title

1/19/2011

* Infinite number of solutions

$$\sigma'_1, \sigma'_2, \dots$$

$$\omega'_1, \omega'_2, \dots$$

$$\sum_{k=1}^{\infty} A_k \exp((\sigma_k + j\omega_k)t)$$

$$\approx A_1 \exp((\sigma_1 + j\omega_1)t)$$

σ_1, ω_1 :

lowest frequency
solutions

(closest to
the origin)

* $\sigma' > 0$ for $T > \pi/2$


$$T_d > \frac{\pi}{2} \cdot \left(\frac{k}{\omega_n} \right)$$

$$\approx \underline{\underline{1.5 \left(\frac{k}{\omega_n} \right)}}$$

$$\underline{A_1 \exp((\sigma_1 + j\omega_1)t) + A_2 \exp((\sigma_1 - j\omega_1)t)}$$

$$\exp(\sigma_1 t) \cdot 2 \cos(\omega_1 t)$$
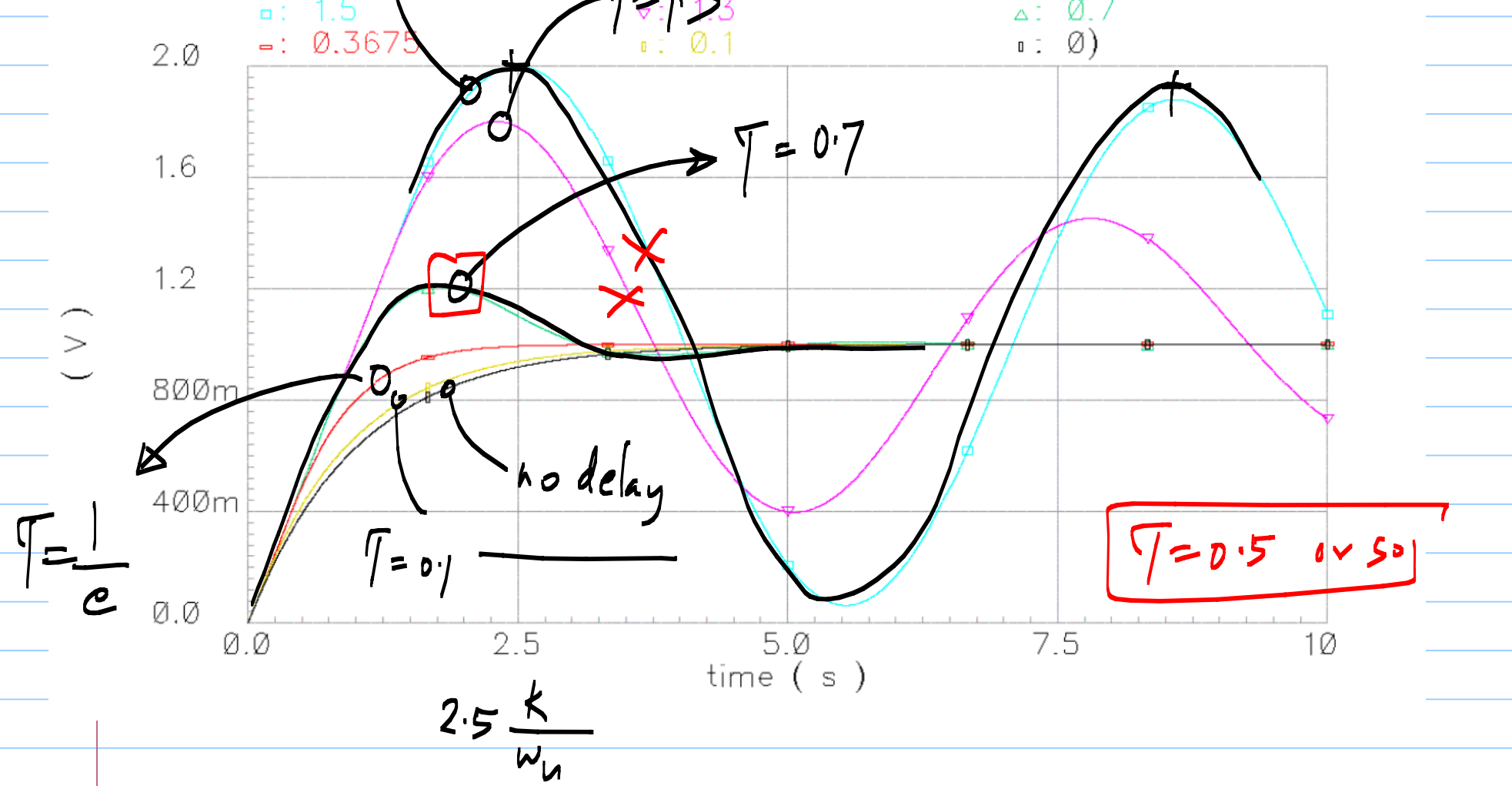
$$\underline{a_1 \exp(\sigma_1 t) \cos(\omega_1 t) + a_2 \exp(\sigma_1 t) \sin(\omega_1 t)}$$



$V_o(t)$

Not

nkee539 negfbwdelay schematic : Jan 12 23:42:53 2011


Transient Response

$\zeta = \pi/2$

$\zeta = 1.5$

$\zeta = 1/6$

1/19/2011

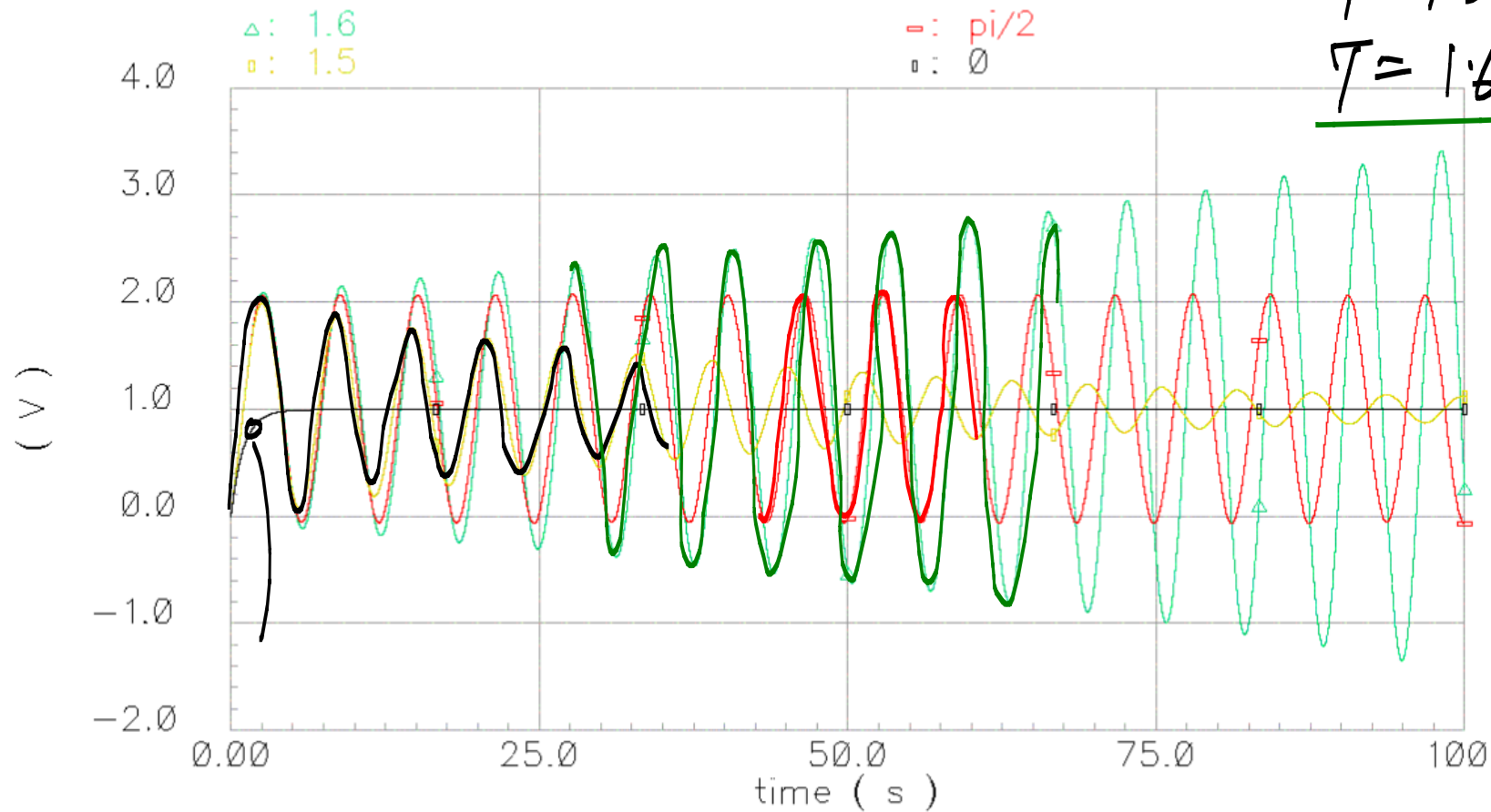

$\zeta = \pi/2 : \sigma' = 0, \omega' = \pm 1$

Negative feedback amplifier with delay

Note Title

1/19/2011

* Small delays speed up the response

* $\zeta = 1/e$: $(T_d = \frac{1}{2.718} \frac{k}{\omega_n})$, fastest response without overshoot

* $\frac{1}{e} < \zeta < \frac{\pi}{2}$: stable response, with ringing

* $\zeta > \frac{\pi}{2}$: Unstable

* In practice $\zeta < 0.5$