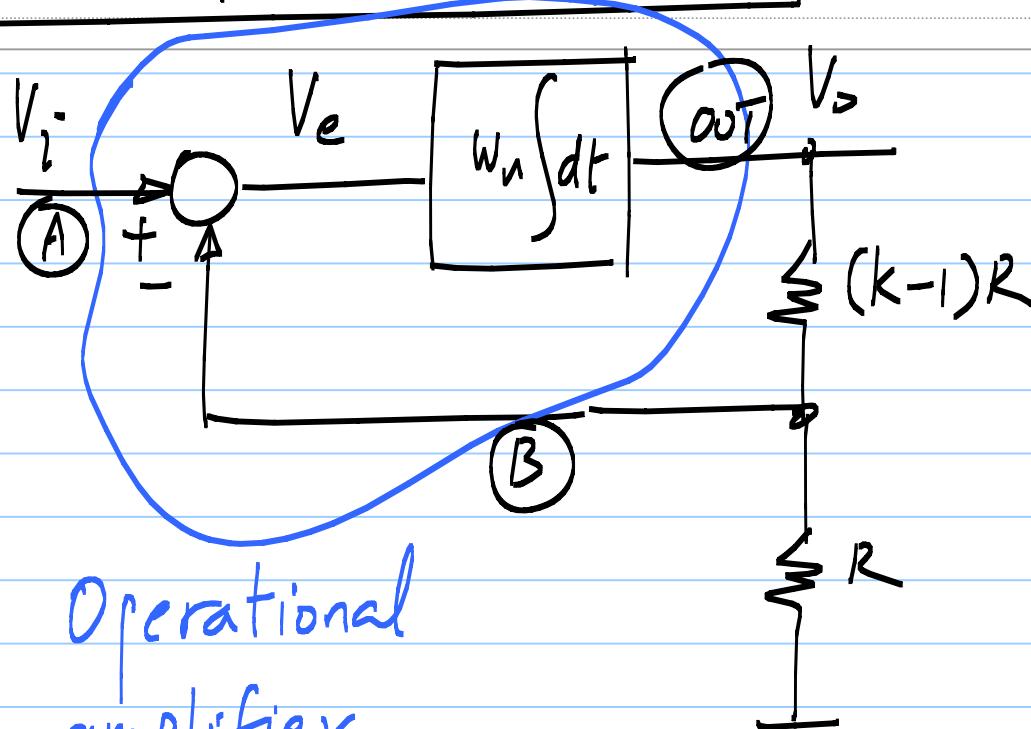



Negative feedback amplifier:

Note Title


OUT
1/20/2011




= Operational
amplifier
(OPAMP)

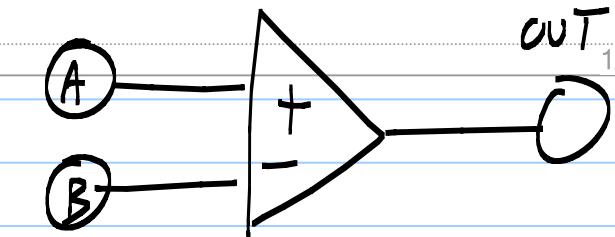


Non-inverting
amplifier

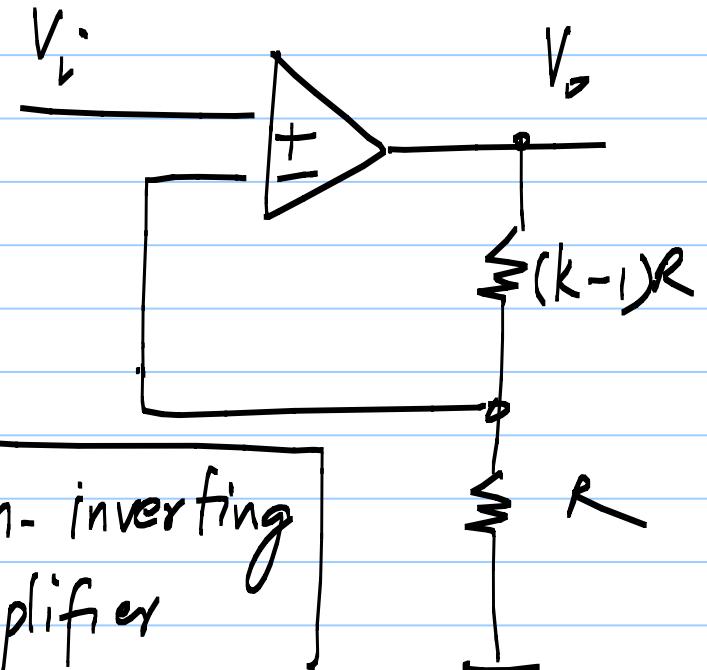

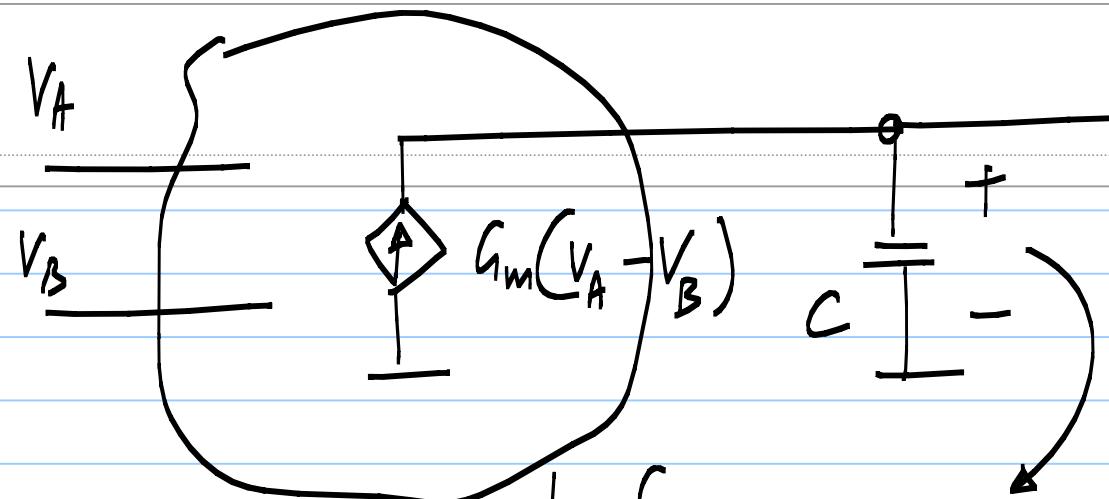

$$\frac{1}{C} \int G_m(V_A - V_B) \cdot dt$$


$$i_C = C \cdot \frac{dV_C}{dt}$$

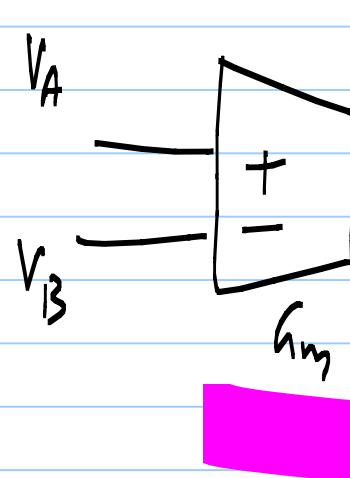


VCCS OR

Transconductor

$$V_C = \frac{1}{C} \cdot \int i_C dt$$

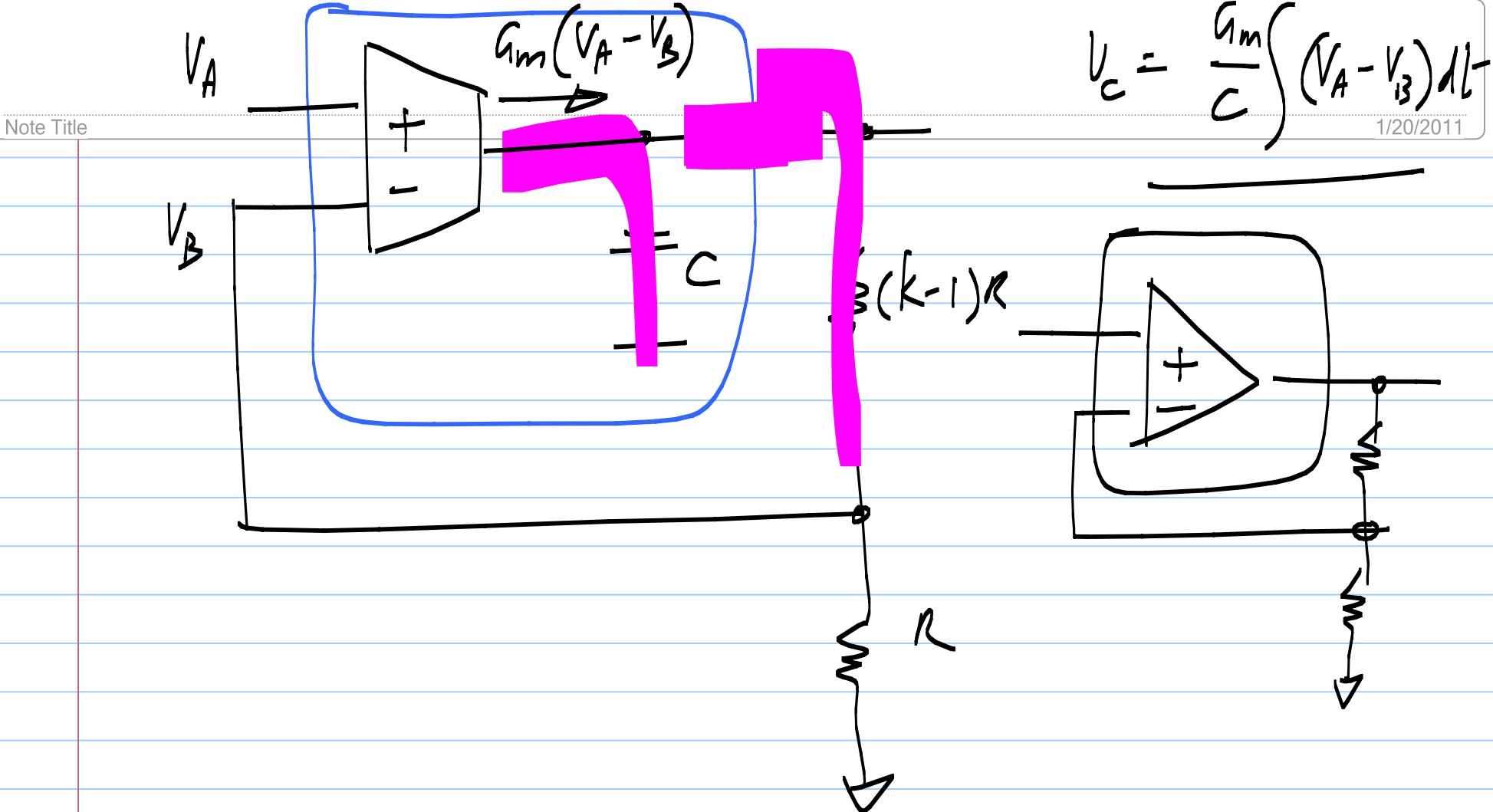


Note Title

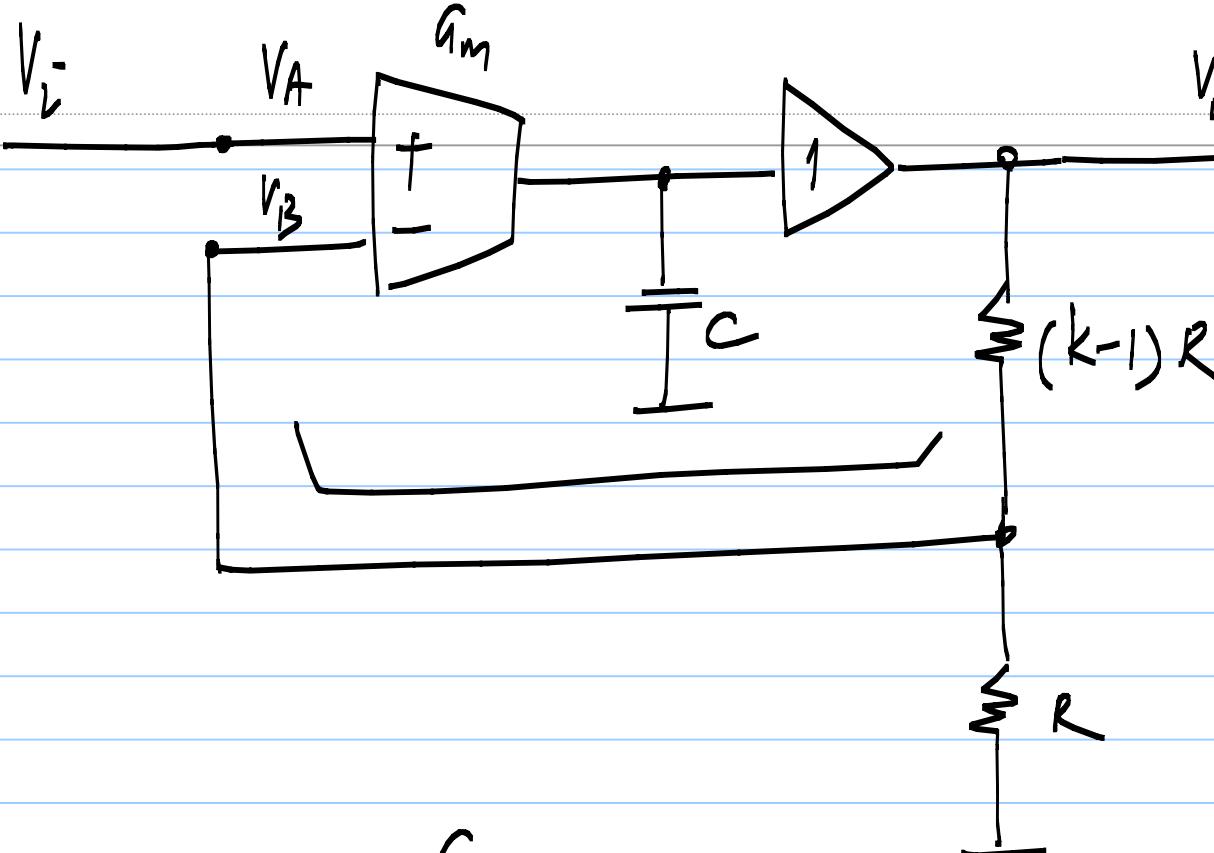

$$\omega_n = \frac{g_m}{C}$$

$$V_o = \frac{g_m}{C} \int (V_A - V_B) \cdot dt$$

$$\omega_n \int (V_A - V_B) \cdot dt$$

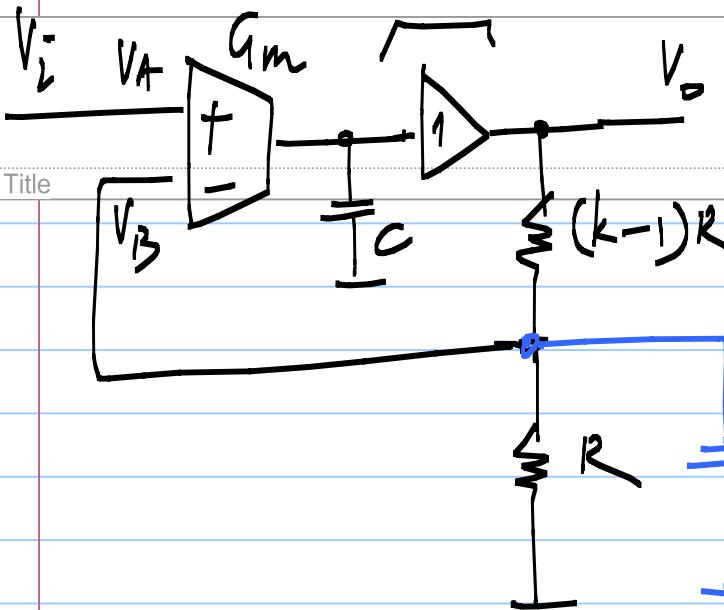

* Voltage buffer

1/20/2011

Transfer function = 1
(ideal)

$$\text{In reality} = 1 \cdot \frac{(1 + s/z_1) \dots}{(1 + s/p_1) \dots}$$

* Voltage divider
pole due to
parasitic capacitance C_p


* Transconductor

$$\frac{I_{\text{out}}}{V_A - V_B} = G_m \cdot \frac{(1 + s/z_1) \dots}{(1 + s/p_1) \dots}$$

Voltage divider:

Note Title

1/20/2011

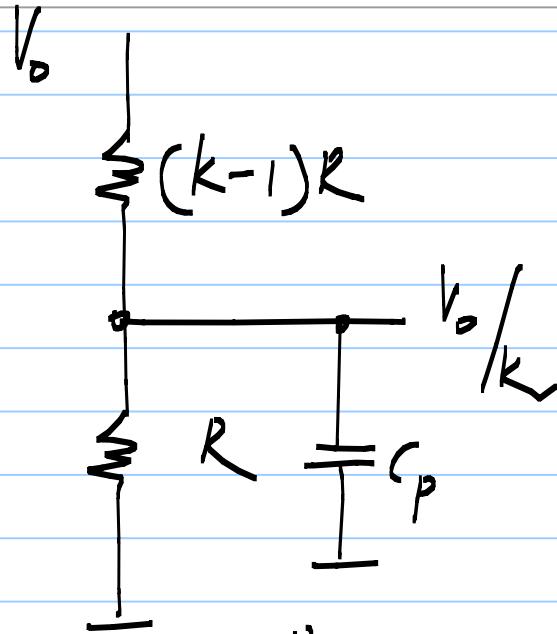


$$= \frac{1}{k} \cdot \frac{1}{\left(1 + \frac{\Sigma}{P_2}\right)}$$

$$P_2 = \frac{k}{k-1} \cdot \frac{1}{C_p R}$$

$$= \frac{1}{k} \cdot \frac{1}{1 + \frac{k-1}{k} \cdot SGR}$$

$$V_o \cdot \frac{R}{1 + SGR} = \frac{1}{k + (k-1)SGR}$$

$$\frac{R}{1 + SGR} + (k-1)R$$

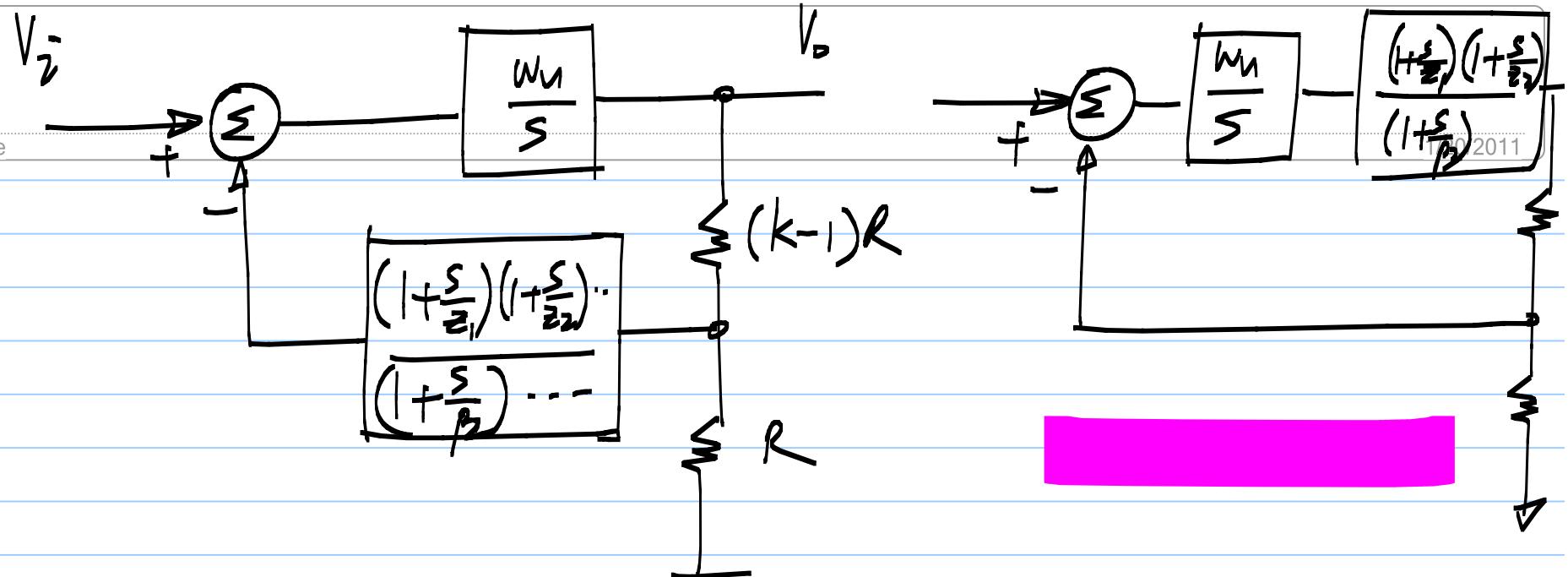


- * Extra poles & zeros in the system
- * Poles & zeros
 - Transconductor*
 - Buffer*
 - Voltage divider*
- * Modeled by poles/zeros in the fb. path / fwd path

Model all the extra poles & zeros in the forward

Note Title

1/20/2011

path

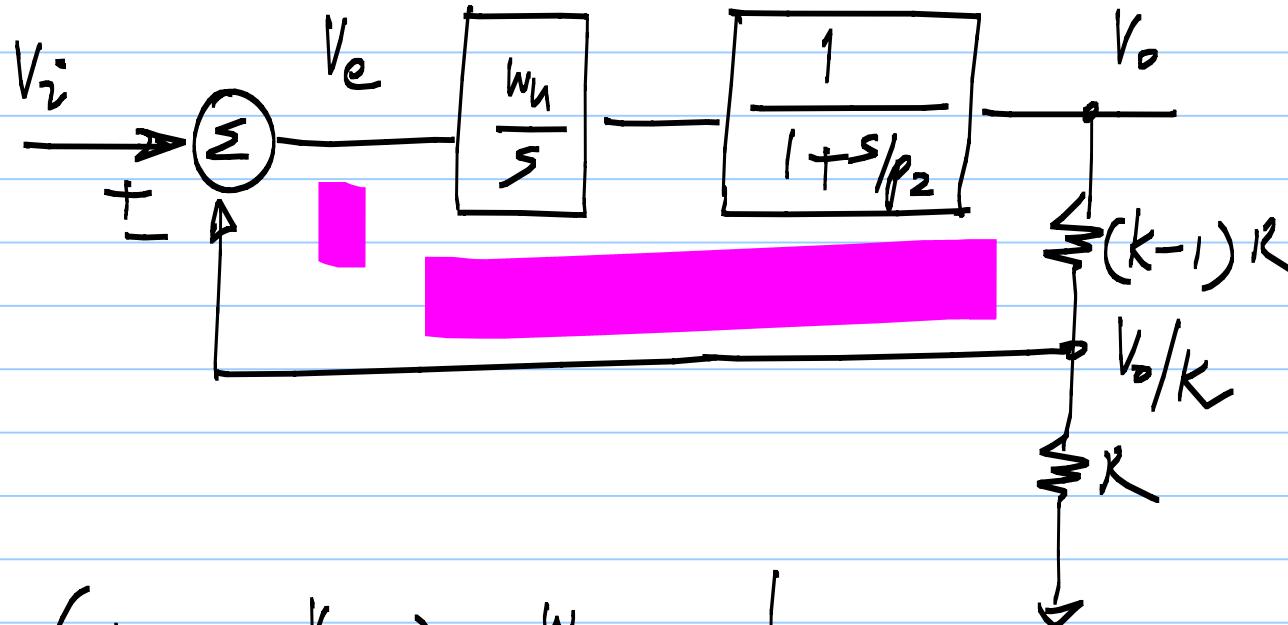

$$\left(V_o - \frac{V_o}{k} \right) \cdot \frac{\omega_n}{s} \cdot \frac{1}{1+s/p_2} = V_o$$

Note Title

1/20/2011

$$\left(V_i - \frac{V_o}{k} \right) \frac{\omega_n}{s} \frac{1}{1 + \frac{s}{\rho_2}} = V_o$$

$$V_i = V_o \cdot \frac{s}{\omega_n} \cdot \left(1 + \frac{s}{\rho_2} \right) + \frac{V_o}{k}$$

$$\frac{V_o}{V_i} = \frac{1}{\frac{1}{k} + \frac{s}{\omega_n} + \frac{s^2}{\omega_n \rho_2}}$$

$$= k \frac{1}{1 + \frac{s \cdot k}{\omega_n} + \frac{s^2 \cdot k}{\omega_n \rho_2}}$$

$$\frac{V_o}{V_i} = k \cdot \left| + s \cdot \frac{k}{\omega_n} + s^2 \cdot \frac{k}{\omega_n \cdot p_2} \right|$$

$$= k \cdot \left[\frac{\omega_n \cdot p_2 / k}{s^2 + s \cdot p_2 + \frac{\omega_n \cdot p_2}{k}} \right] \quad \frac{p_2}{2 \sqrt{\frac{\omega_n \cdot p_2}{k}}}$$


natural frequency $= \omega_n = \sqrt{\frac{\omega_n \cdot p_2}{k}}$

damping factor $= \zeta = \frac{1}{2} \frac{\sqrt{p_2}}{\sqrt{\omega_n / k}}$

Negative feedback amplifier with an extra pole in the fwd path

1/20/2011

* Second order transfer fn.

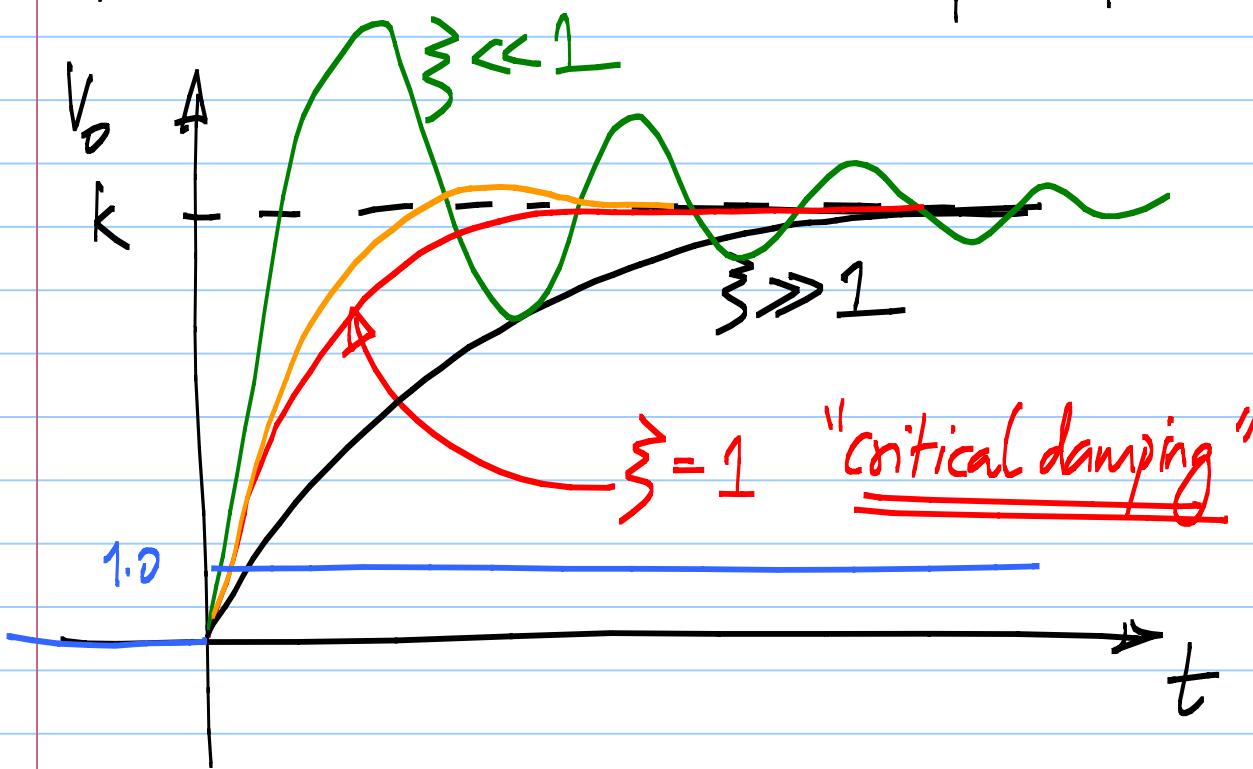

$$\text{dc gain} = k$$
$$\omega_n = \sqrt{P_2 \cdot \frac{m}{K}}$$

$$\zeta = \frac{1}{2} \frac{\sqrt{P_2}}{\sqrt{m/K}}$$

Desired response
: critically damped
slightly ~~underdamped~~

$$\zeta = 1.0$$

$$\zeta = \frac{1}{2} \sqrt{\frac{P_2}{w_n/k}} = 1.0$$

1/20/2011

Note Title

Underdamped response

if $\zeta < 1$

$$P_2 = 4 \cdot \left(\frac{w_n}{k} \right)$$

$$\zeta = 1$$

\equiv


$$T_d = \frac{1}{c} \left(\frac{k}{w_n} \right)$$

$$P_2 = 4 \cdot \frac{w_n}{k}$$

$$P_2 \ll 4 \cdot \frac{w_n}{k}$$

Critical damping

Note Title

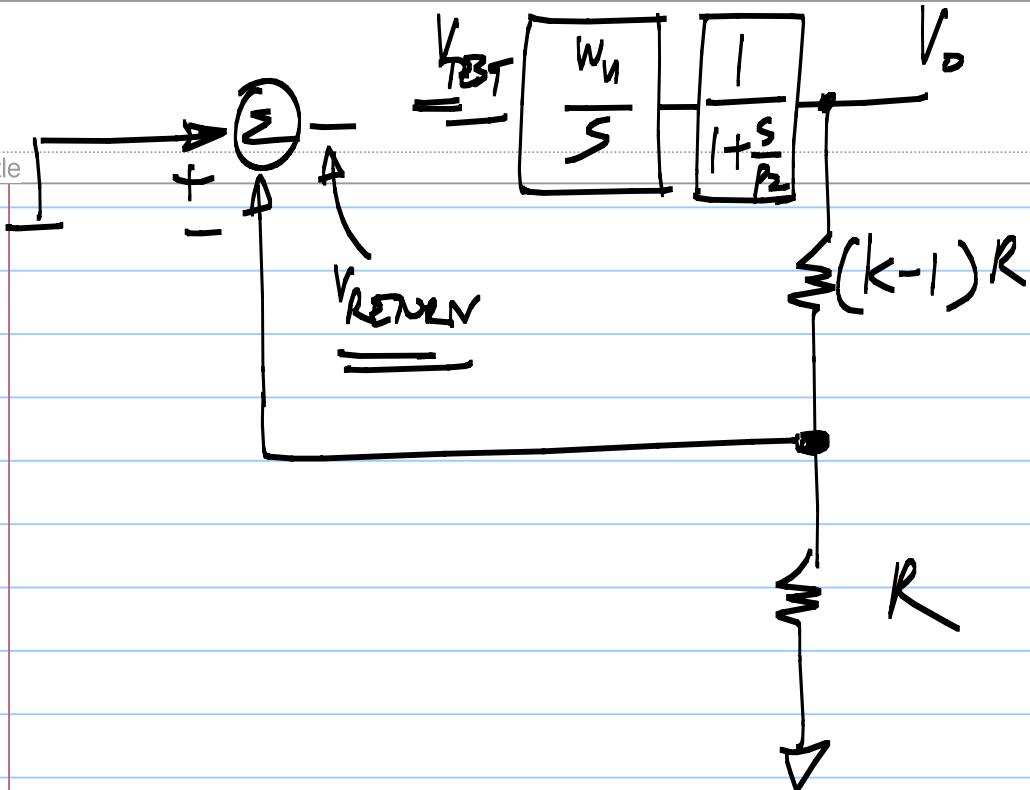

$$L(s) = -\frac{V_{RETURN}}{V_{TEST}}$$

$$= \frac{w_n}{s \cdot k}$$


$$L(s) = \frac{w_n}{s \cdot k} \frac{1}{1 + \sum p_z}$$

(w/ extra pole)

① No extra pole:

Note Title
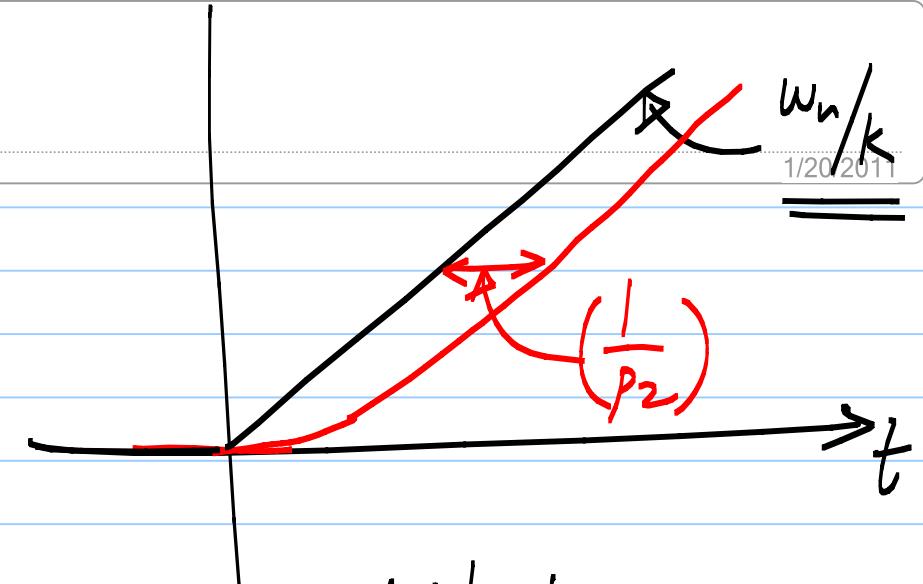
$$\text{Loop gain} = \frac{\omega_n/k}{s}$$



② 1 extra pole

$$\text{Loop gain} = \frac{\omega_n/k}{s} \cdot \frac{1}{1 + s/p_2}$$

Unit step response

of the loop gain

Step response is delayed by $\left(\frac{1}{p_2}\right)$

$$L(s) = \frac{\omega_n/k}{s} \cdot \frac{1}{1 + s/p_2}$$

1/20/2011

$$= \frac{\omega_n/k}{s} - \frac{\left[(\omega_n/k)/p_2 \right]}{1 + s/p_2}$$

$$\frac{1 - \exp(-p_2 t)}{1 + s/p_2}$$

