
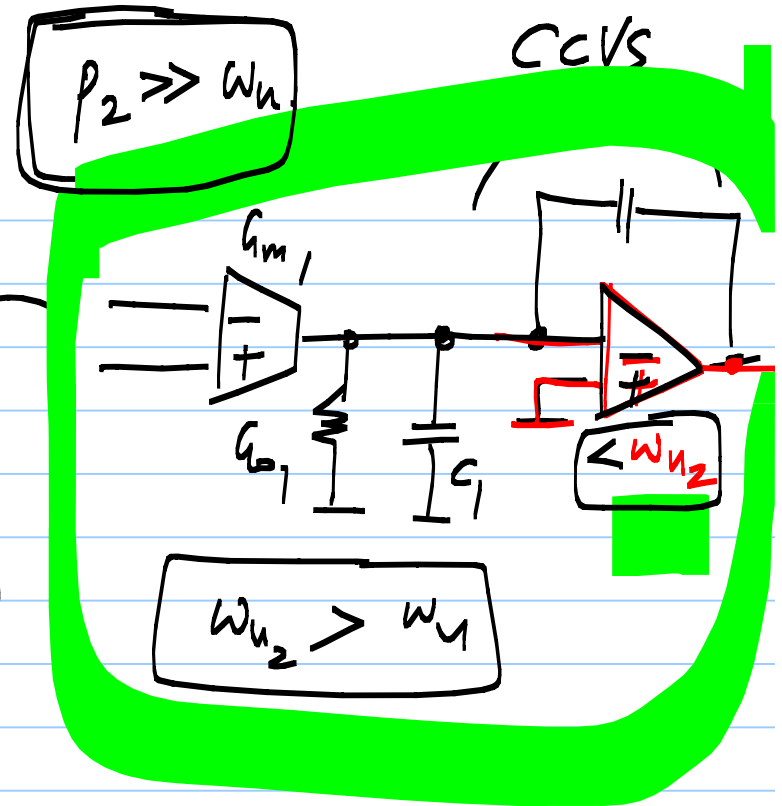


# Two stage ramp.

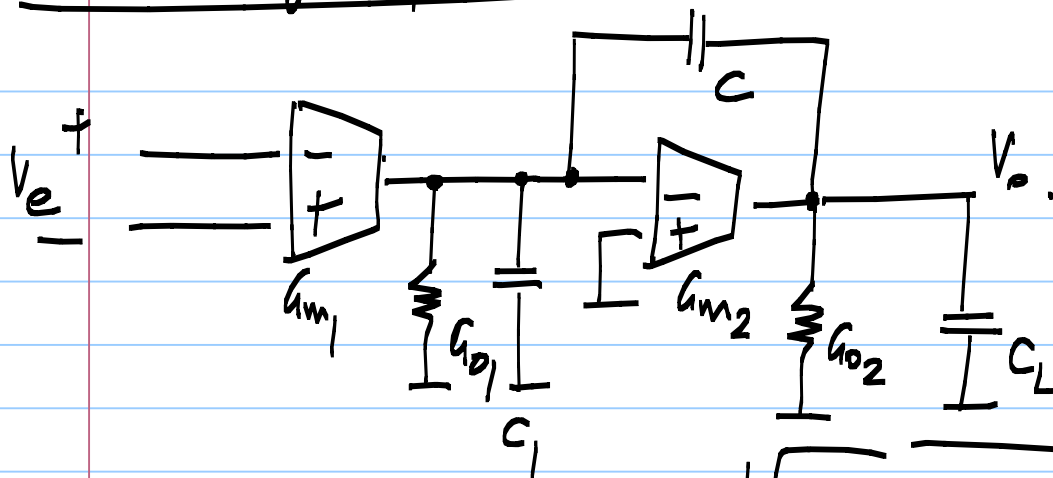

$$A_0 = \frac{g_{m1} g_{m2}}{g_{o1} g_{o2}} \quad \left| \quad \omega_u = \frac{g_{m1}}{C} \right.$$

$$p_1 = -\frac{g_{o1}}{C_1 + C \left( \frac{g_{m2}}{g_{o2}} + 1 \right)}$$


$$p_2 = -\left[ \frac{g_{m2} \cdot C}{C + C_1} + g_{o2} \right] / \left[ C_L + \frac{C C_1}{C + C_1} \right] \approx \frac{g_{m2} + g_{o2}}{C_L + C_1} \approx \frac{g_{m2}}{C_1}$$

$$z_1 = + \frac{g_{m2}}{C}$$

Right half plane zero  $\rightarrow$

phase lag
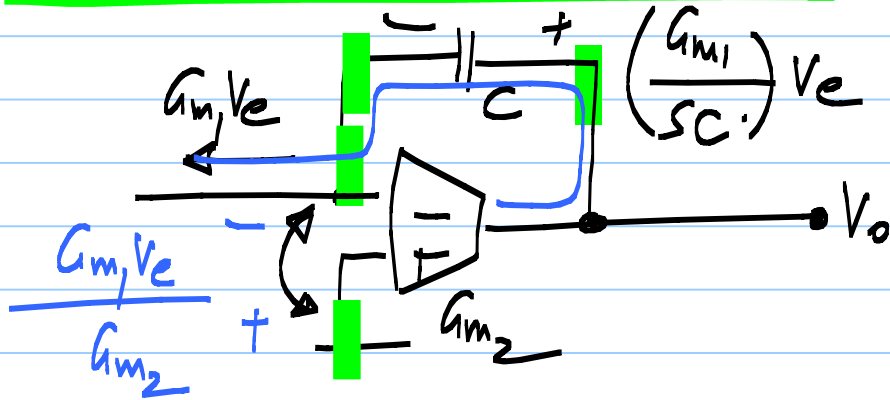
$$\left[ \frac{G_{m1} \cdot V_e}{G_{m2}} \right]$$




$$V_o = \left\{ G_{m1} V_e \left( \frac{1}{sC} - \frac{1}{G_{m2}} \right) \right\}$$

$$= G_{m1} V_e \left( \frac{G_{m2} - sC}{G_{m2} \cdot sC} \right)$$


$$G_{m1} V_e \left[ \frac{1}{sC} - \frac{1}{G_{m2}} + \frac{1}{G_{m2}} \right]$$

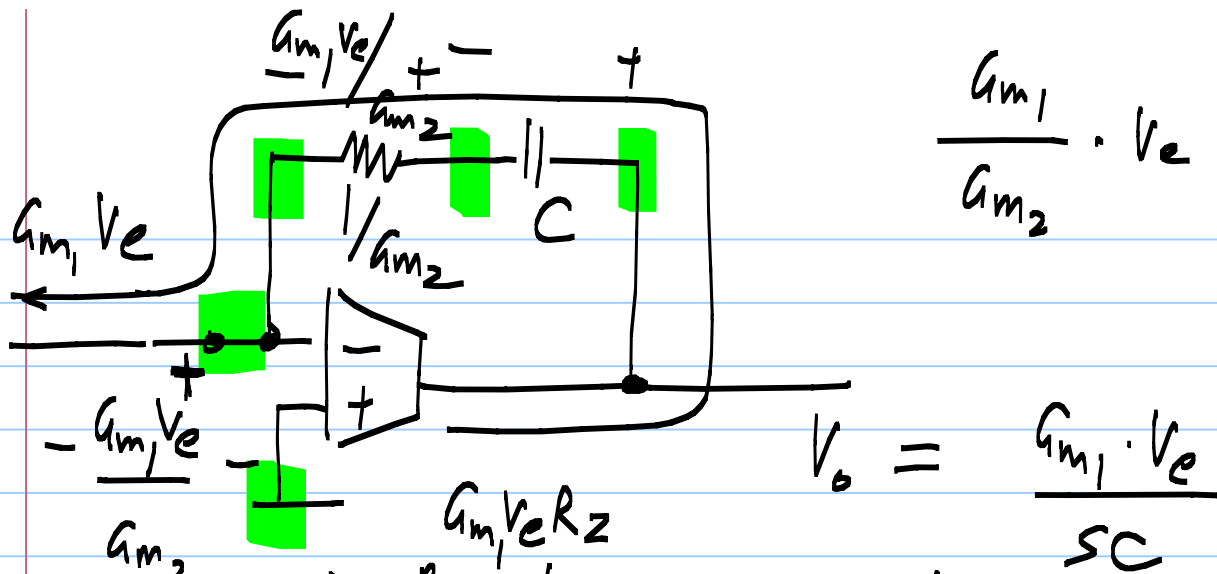Add this term for zero eliminating the RHP




Zero:
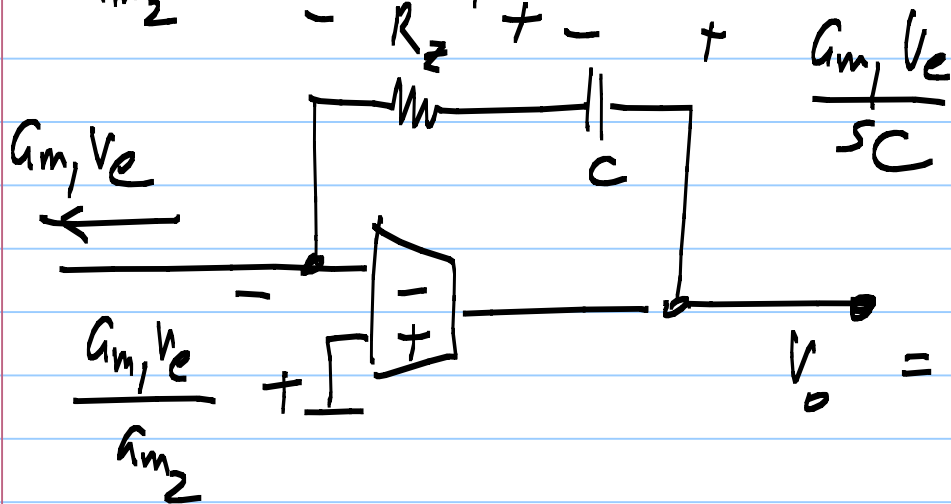
$$\frac{g_{m2}}{(g_{m2}R_2 - 1) \cdot C}$$



$$= g_{m1} \cdot v_e \left[ \frac{g_{m2} + (g_{m2}R_2 - 1) sC}{sC \cdot g_{m2}} \right]$$
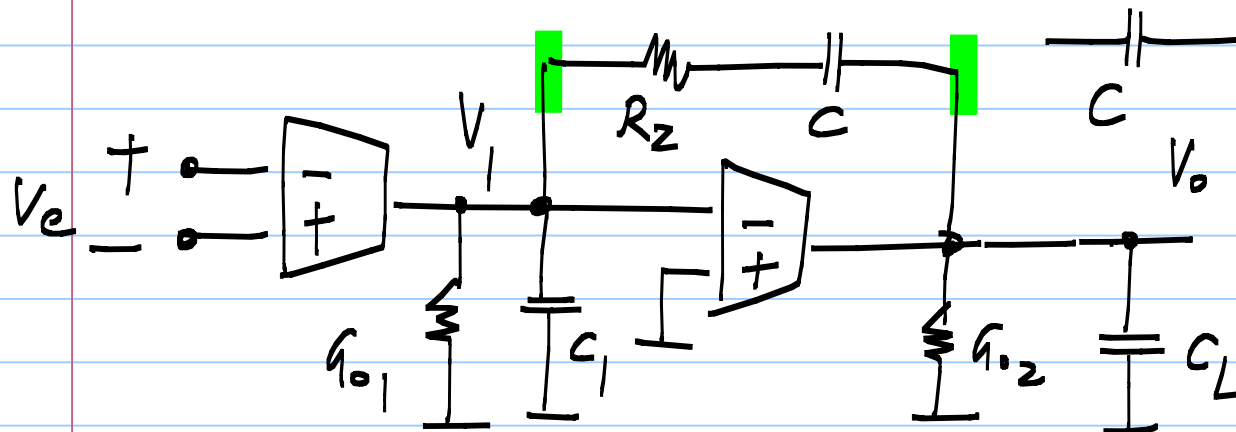
# Two stage opamp with RHP zero cancellation




3 poles

$$SC \rightarrow \frac{SC}{1 + SCR_z}$$


$$\begin{bmatrix} SC_1 + \frac{SC}{1 + SCR_z} + g_{o1} & -\frac{SC}{1 + SCR_z} \\ g_{m2} - \frac{SC}{1 + SCR_z} & SC_L + \frac{SC}{1 + SCR_z} + g_{o2} \end{bmatrix} \begin{bmatrix} V_1 \\ V_o \end{bmatrix} = \begin{bmatrix} -g_{m1}V_e \\ 0 \end{bmatrix}$$
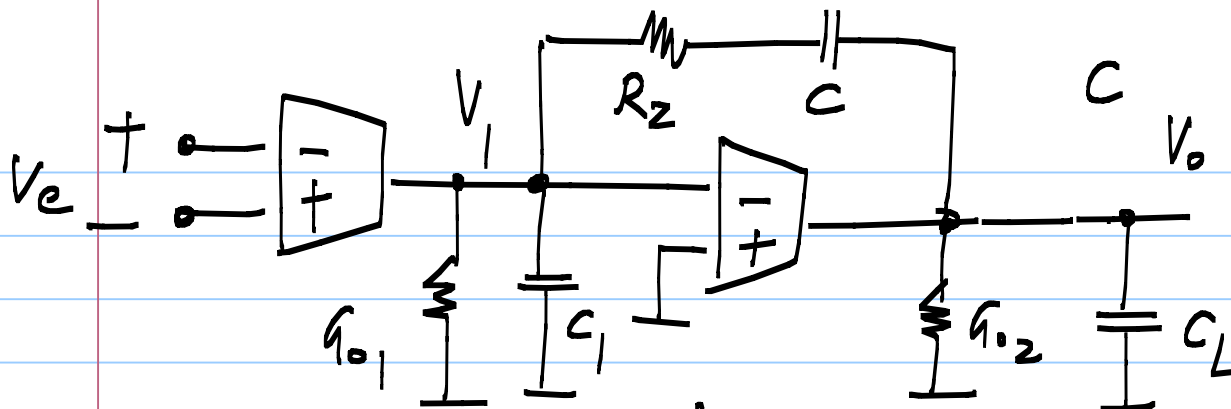
$$\begin{array}{l} R_z \quad z_1 \\ = \frac{1}{g_{m2}} \quad \infty \\ < \frac{1}{g_{m2}} \quad RHP \\ > \frac{1}{g_{m2}} \quad LHP \end{array}$$



$P_3 \approx$


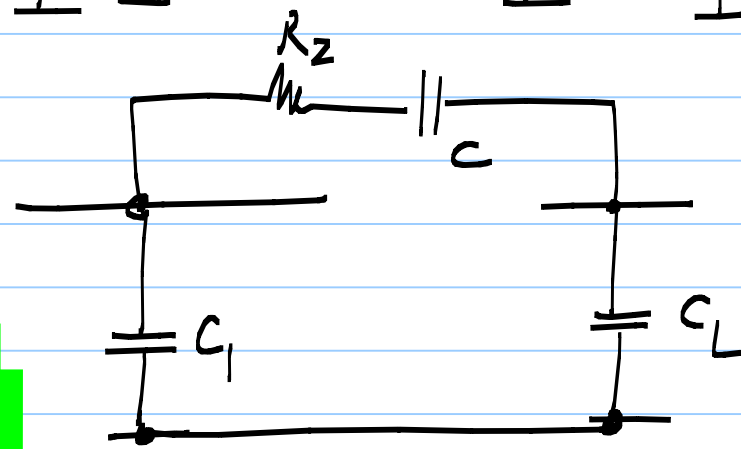
$$-\frac{1}{R_2} \left( \frac{1}{C} + \frac{1}{C_L} + \frac{1}{C_1} \right)$$




$$R_2 = \frac{1}{g_{m2}} \left( \frac{g_{m2}}{C} \right)$$

~~RH2 zero~~ ;  $-g_{m2} \left( \frac{1}{C} + \frac{1}{C_L} + \frac{1}{C_1} \right)$


Single stage opamp:

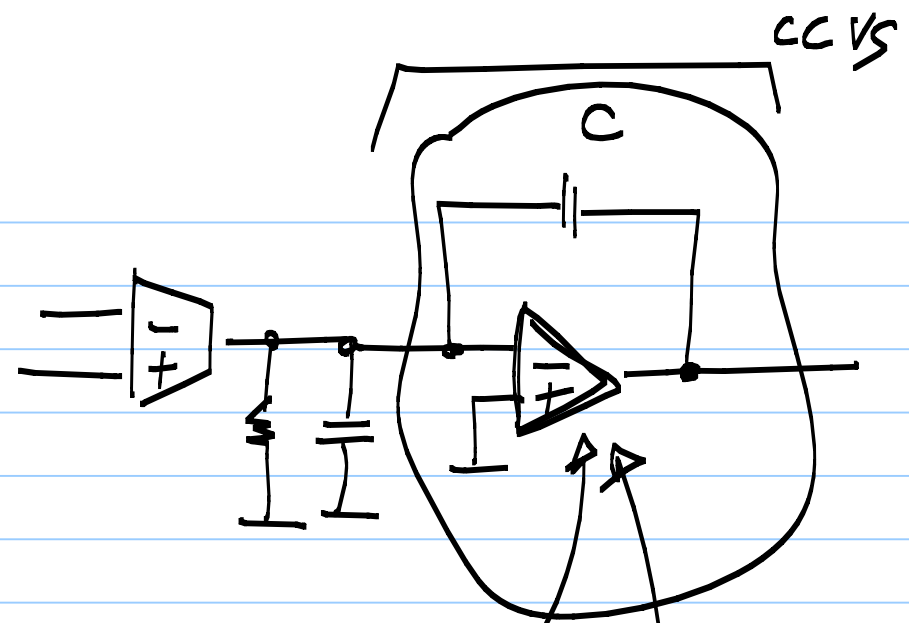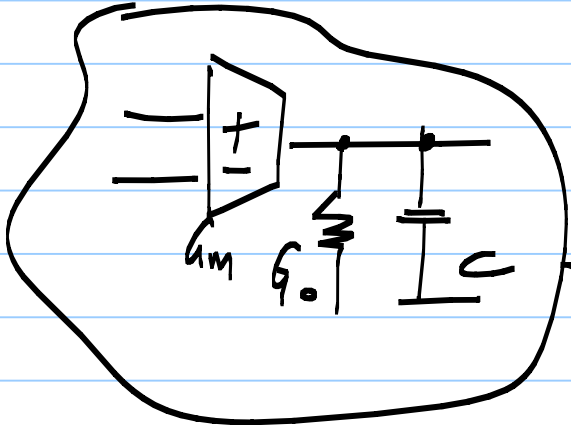

Two stage opamp:

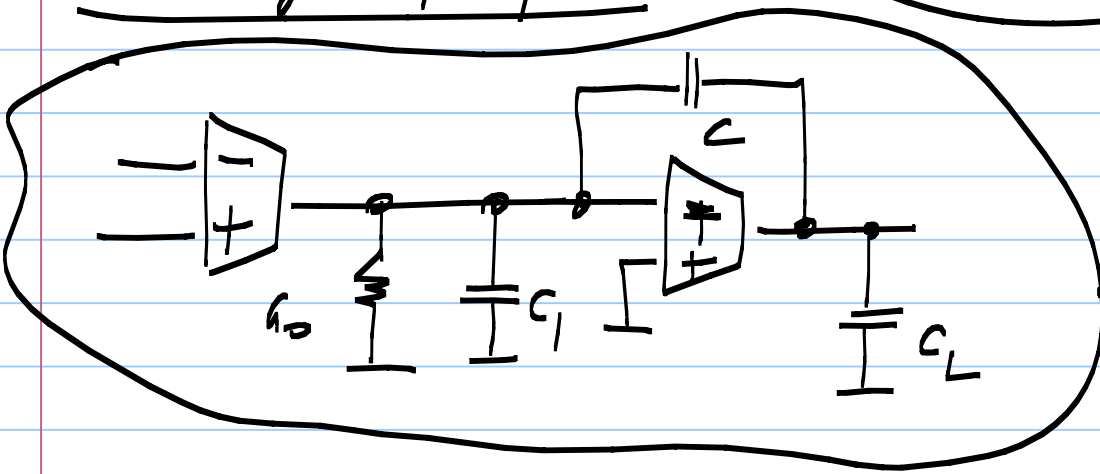

Nested miller  
3 stage opamp

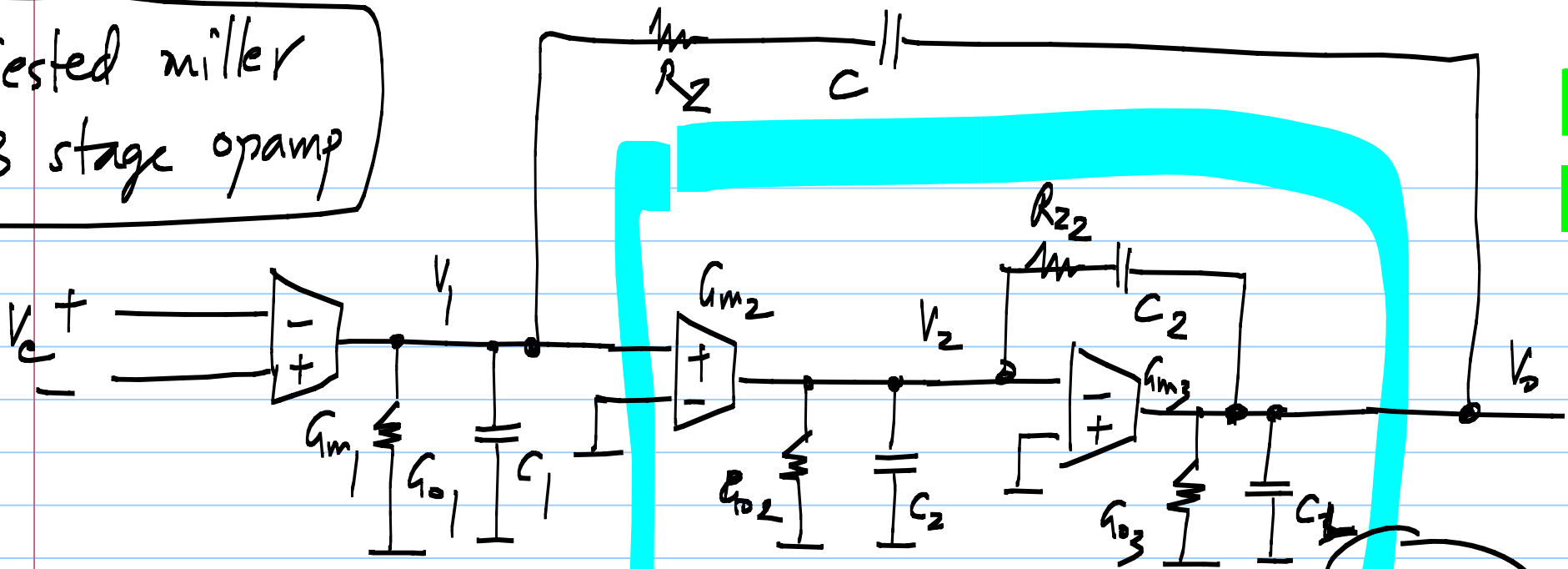

Three stage opamp

Two stage opamp

Miller  
Compensator  
2 stage  
opamp

$$A_D = \frac{g_{m1} g_{m2} g_{m3}}{g_{o1} g_{o2} g_{o3}}$$

\* Unity gain frequency of the opamp being realized  
$$= \frac{G_{m1}}{C}$$

\* Unity gain frequency of the two stage opamp  
used for the CCVS  $= \frac{G_{m2}}{C_2}$   
$$\frac{G_{m2}}{C_2} > \frac{G_{m1}}{C}$$

\* Unity gain frequency of the single stage opamp  
used for CCVS in the two stage opamp  $= \frac{G_{m3}}{C_L}$





$$\frac{G_{m3}}{C_L} \rightarrow \frac{G_{m2}}{C_2} \rightarrow \frac{G_{m1}}{C}$$



$$\left( \frac{G_{m5}}{C_5} \right) \rightarrow \frac{G_{m4}}{C_4} \rightarrow \frac{G_{m3}}{C_3} \rightarrow \frac{G_{m2}}{C_2} \rightarrow \frac{G_{m1}}{C}$$

—
—
—
—
—

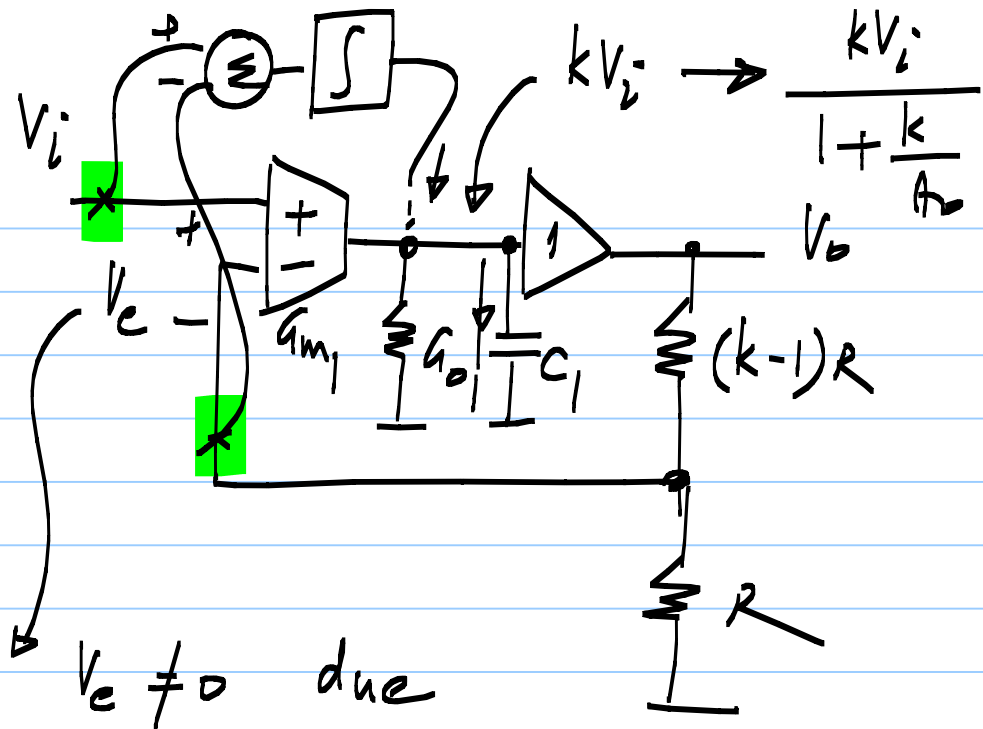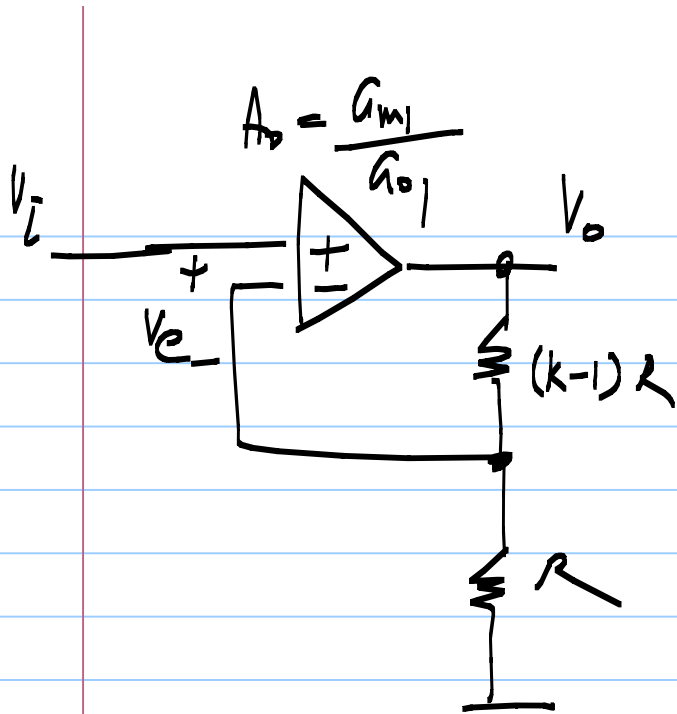

$V_e \neq 0$  due to finite dc gain