

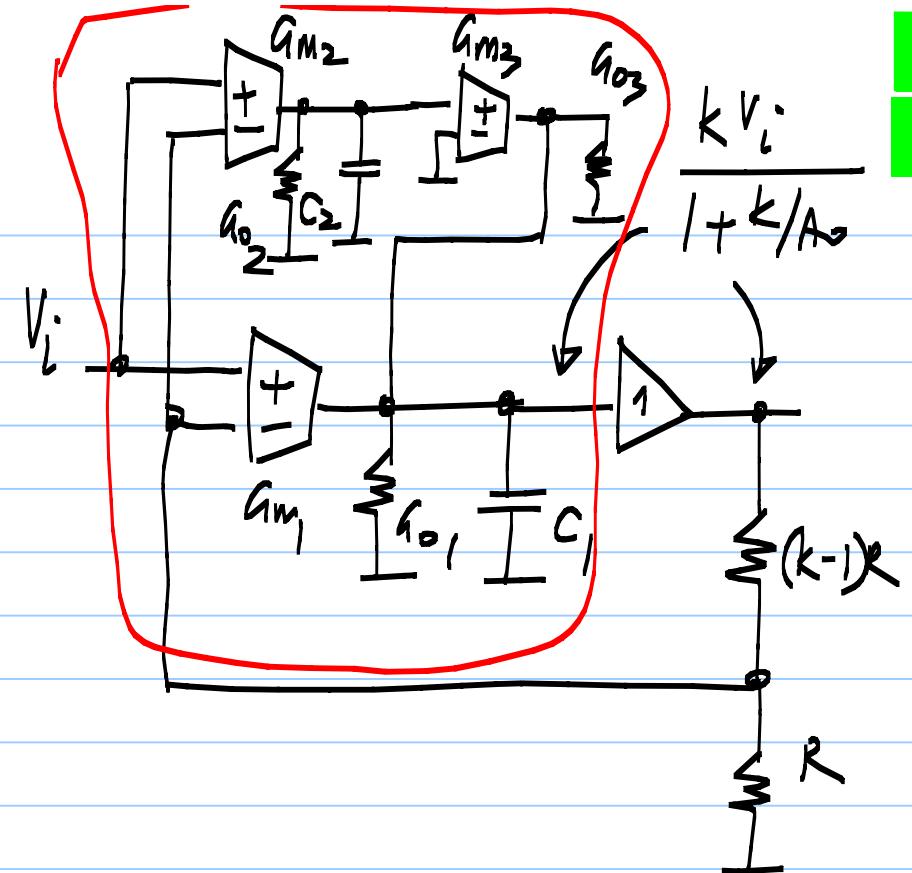


Lecture 16

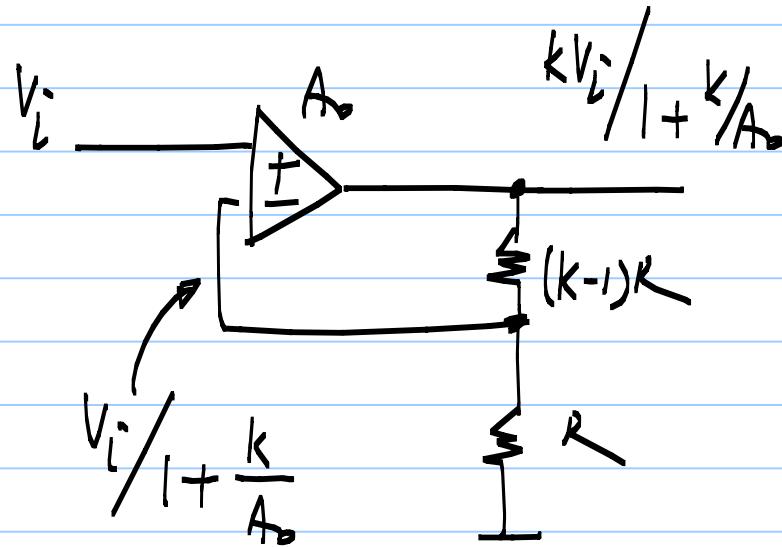

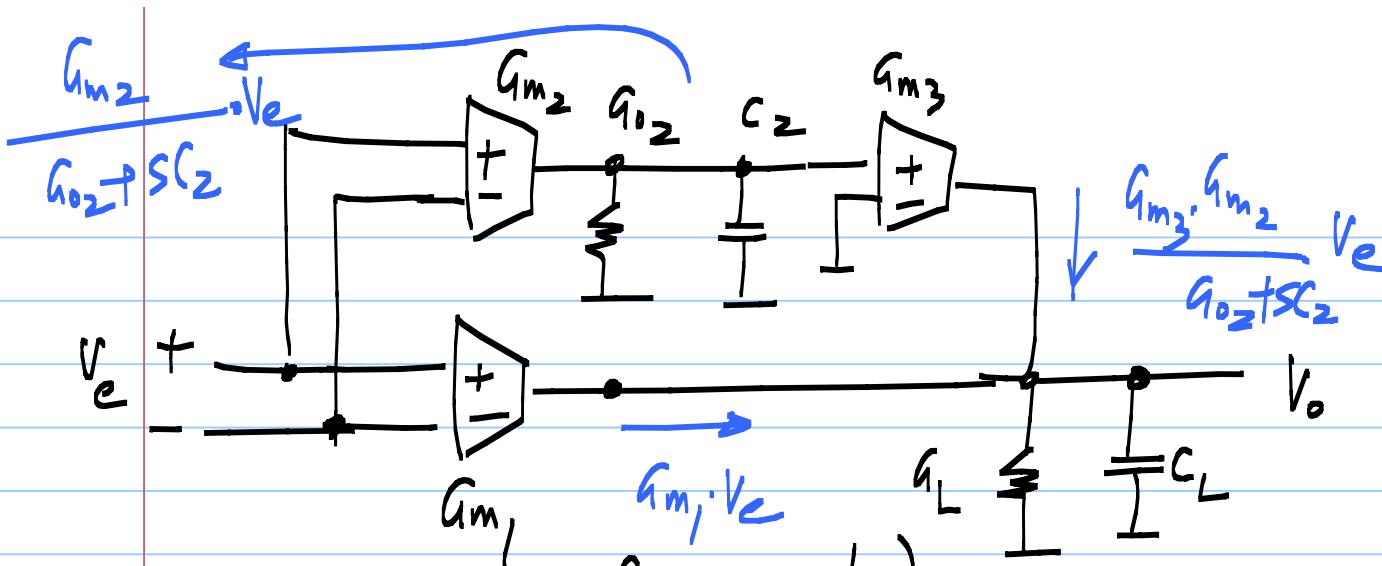

dc gain $A_{\text{dc}} =$



$$\left(\frac{G_{m_1}}{G_L} + \left(\frac{G_{m_3} G_{m_2}}{G_{o_2} G_L} \right) \right)$$



Feedforward opamp compensated.

$$\begin{aligned} \frac{V_o(s)}{V_e(s)} &= \left(G_{m_1} + \frac{G_{m_2} G_{m_3}}{G_{o_2} + sC_2} \right) \frac{1}{G_L + sC_L} \\ &= \frac{G_{m_1}}{G_L + sC_L} + \frac{G_{m_2} G_{m_3}}{(G_{o_2} + sC_2)(G_L + sC_L)} \end{aligned}$$

$$\begin{aligned}
 \frac{V_o(s)}{V_e(s)} &= \left(G_{m1} + \frac{G_{m2} G_{m3}}{G_{o2} + sC_2} \right) \frac{1}{G_L + sC_L} \\
 &= \frac{G_{m1}}{G_L + sC_L} + \frac{G_{m2} G_{m3}}{(G_{o2} + sC_2)(G_L + sC_L)} \\
 &= \frac{G_{m1} (G_{o2} + sC_2) + G_{m2} G_{m3}}{(G_{o2} + sC_2)(G_L + sC_L)} = A_D \cdot \frac{\left(1 + \frac{s}{Z_1} \right)}{\left(1 + \frac{s}{P_1} \right) \left(1 + \frac{s}{P_2} \right)}
 \end{aligned}$$
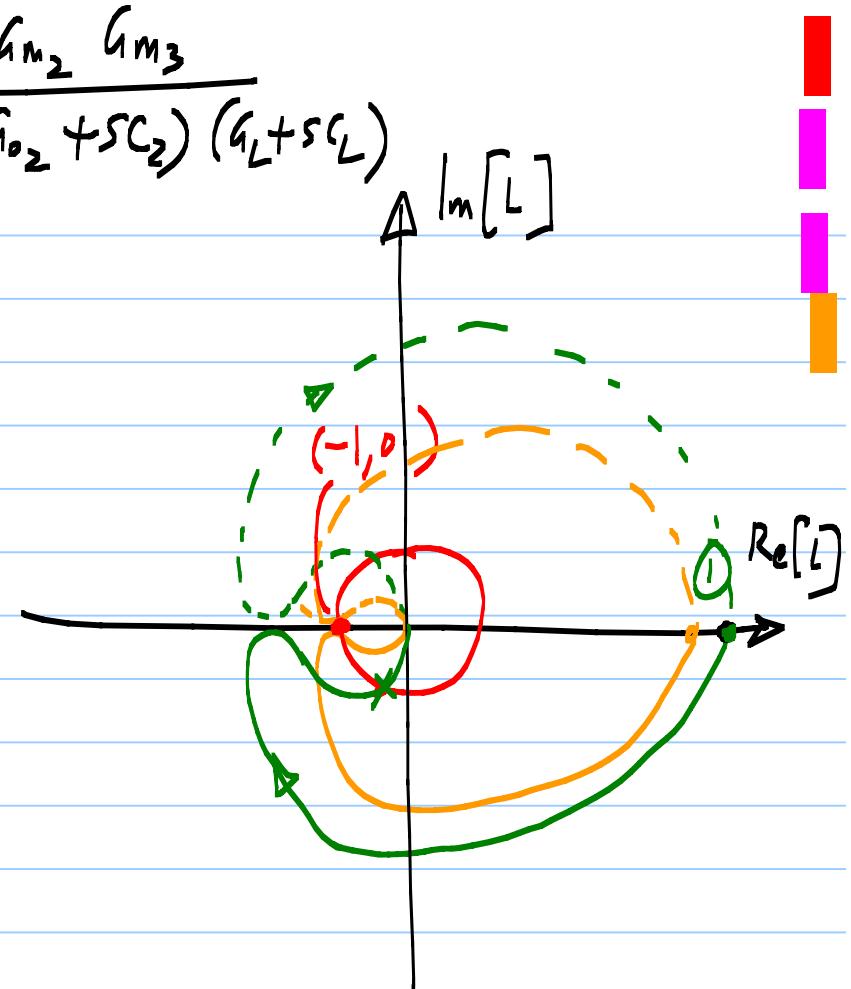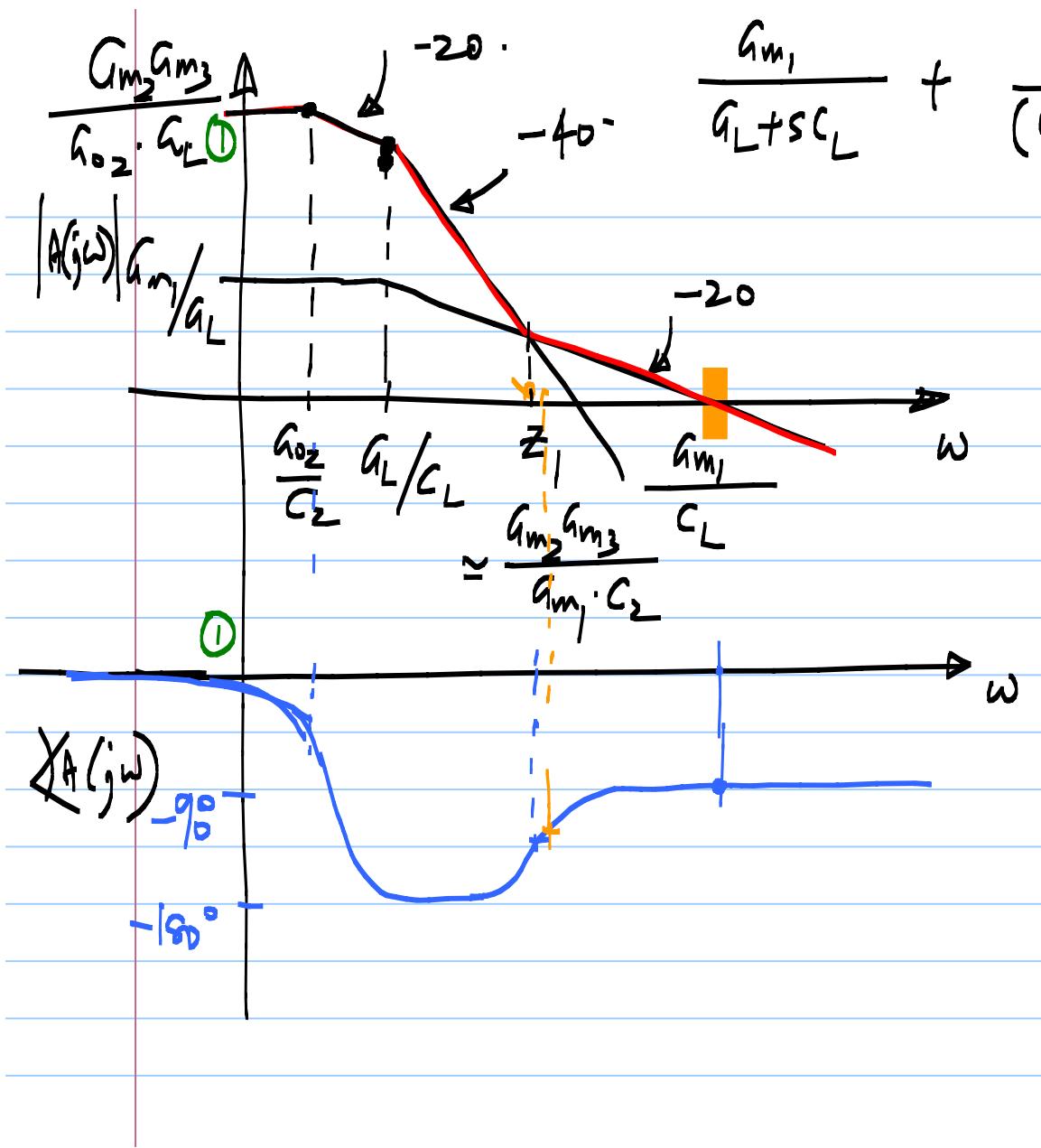
$$P_1 = \frac{G_L}{C_L}; \quad P_2 = \frac{G_{o2}}{C_2}; \quad Z_1 = \frac{G_{m1} G_{o2} + G_{m2} G_{m3}}{G_{m1} \cdot C_2} \simeq \frac{G_{m2} G_{m3}}{G_{m1} \cdot C_2}$$



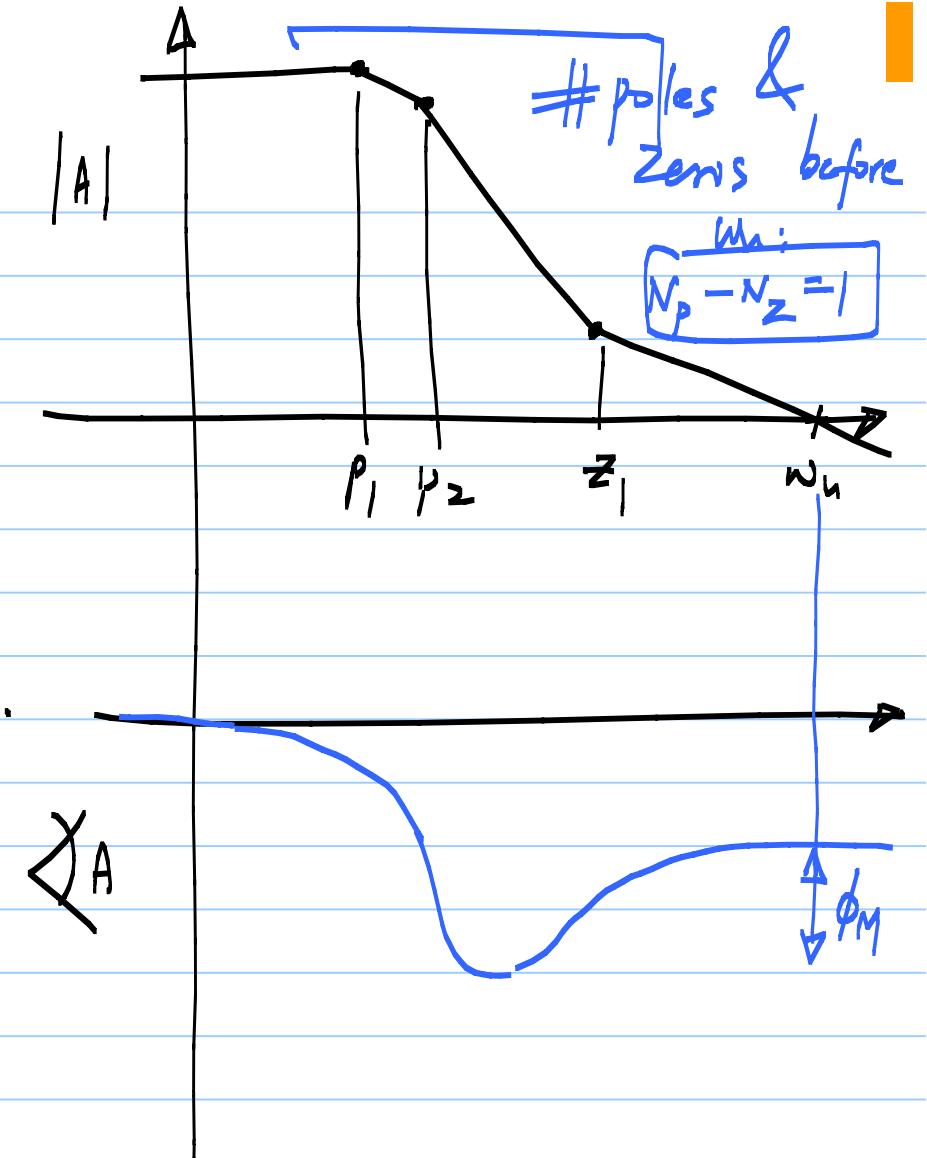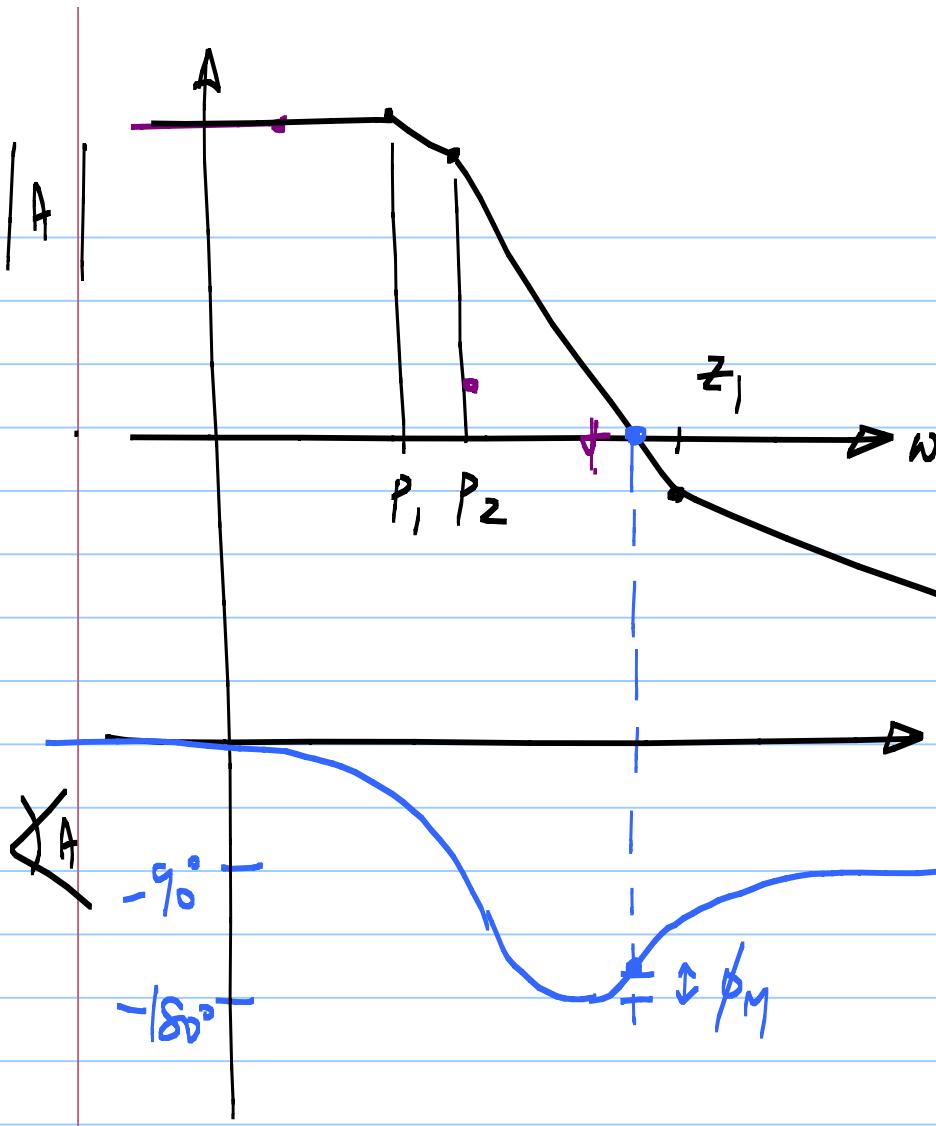

Feedforward Compensated opamp:

- * 2 poles & 1 zero
- * Both the poles & zero must occur before the unity loop gain frequency — for stability.

