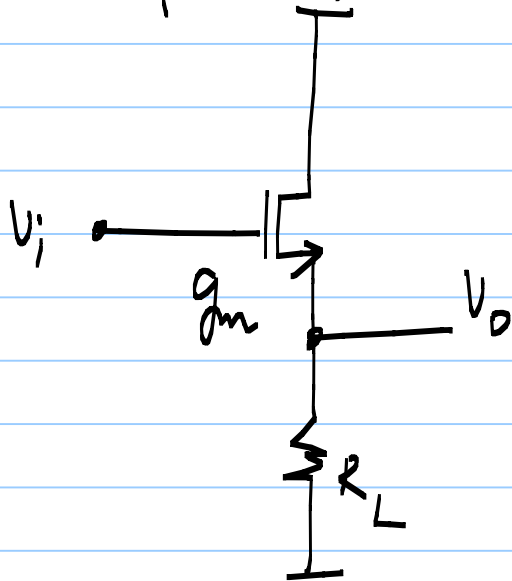


## Lecture 27:

Common drain amplifier:  
(Source follower)




\* Voltage buffer  $v_o = v_i$

$$* R_i = \infty ; R_o = \frac{1}{g_m} \frac{1}{g_m + g_{ds}}$$

$$* \left. \frac{v_o}{v_i} \right|_{R_L = \infty} = 1 ; \frac{v_o}{v_i} = \frac{g_m R_L}{1 + g_m R_L}$$

$\approx 1$  if  $g_m R_L \gg 1$
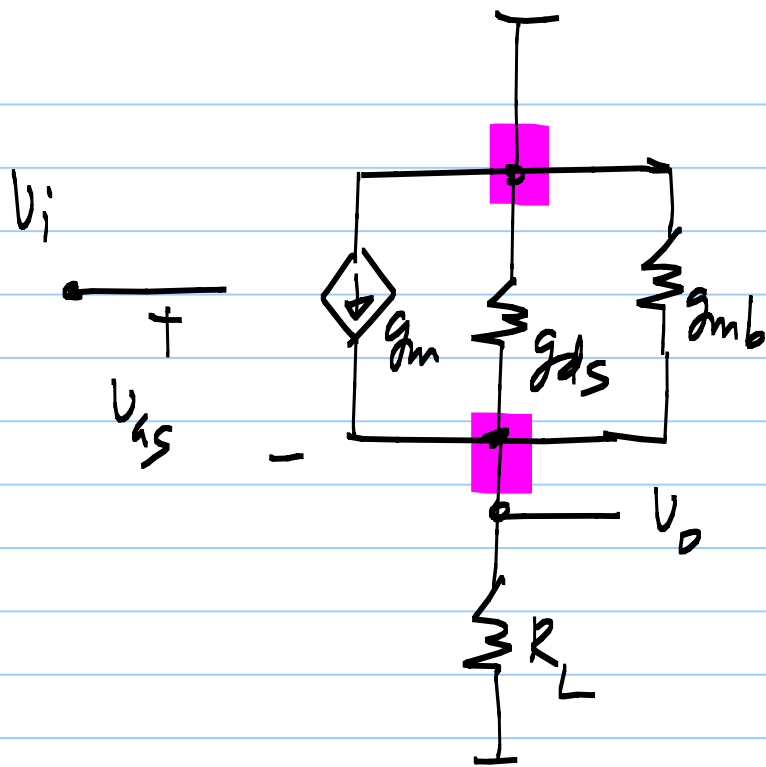
$$\frac{v_o}{v_i} = \frac{g_m}{g_m + g_L + g_{ds}}$$




$$\frac{v_o}{v_i} = \frac{g_m}{g_m + g_L + g_{mb} + g_{ds}}$$

$$R_L \rightarrow \infty, \quad r_{ds} \rightarrow \infty$$


$$(g_L \rightarrow 0, \quad g_{ds} \rightarrow 0)$$

$$\left[ \frac{v_o}{v_i} = \frac{g_m}{g_m + g_{mb}} < 1 \right]$$

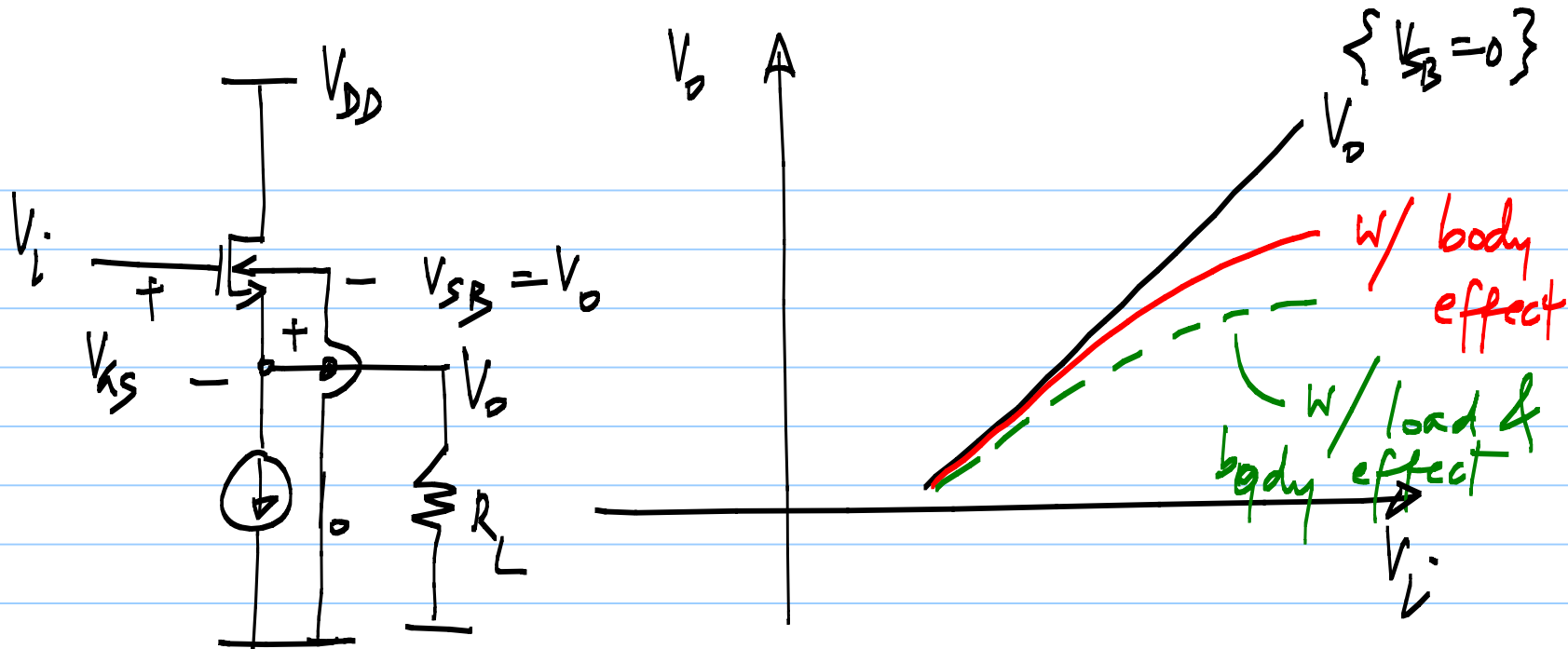
$$R_o \approx \frac{1}{g_m} \quad \underline{\underline{\frac{1}{g_m + g_{mb}}}}$$


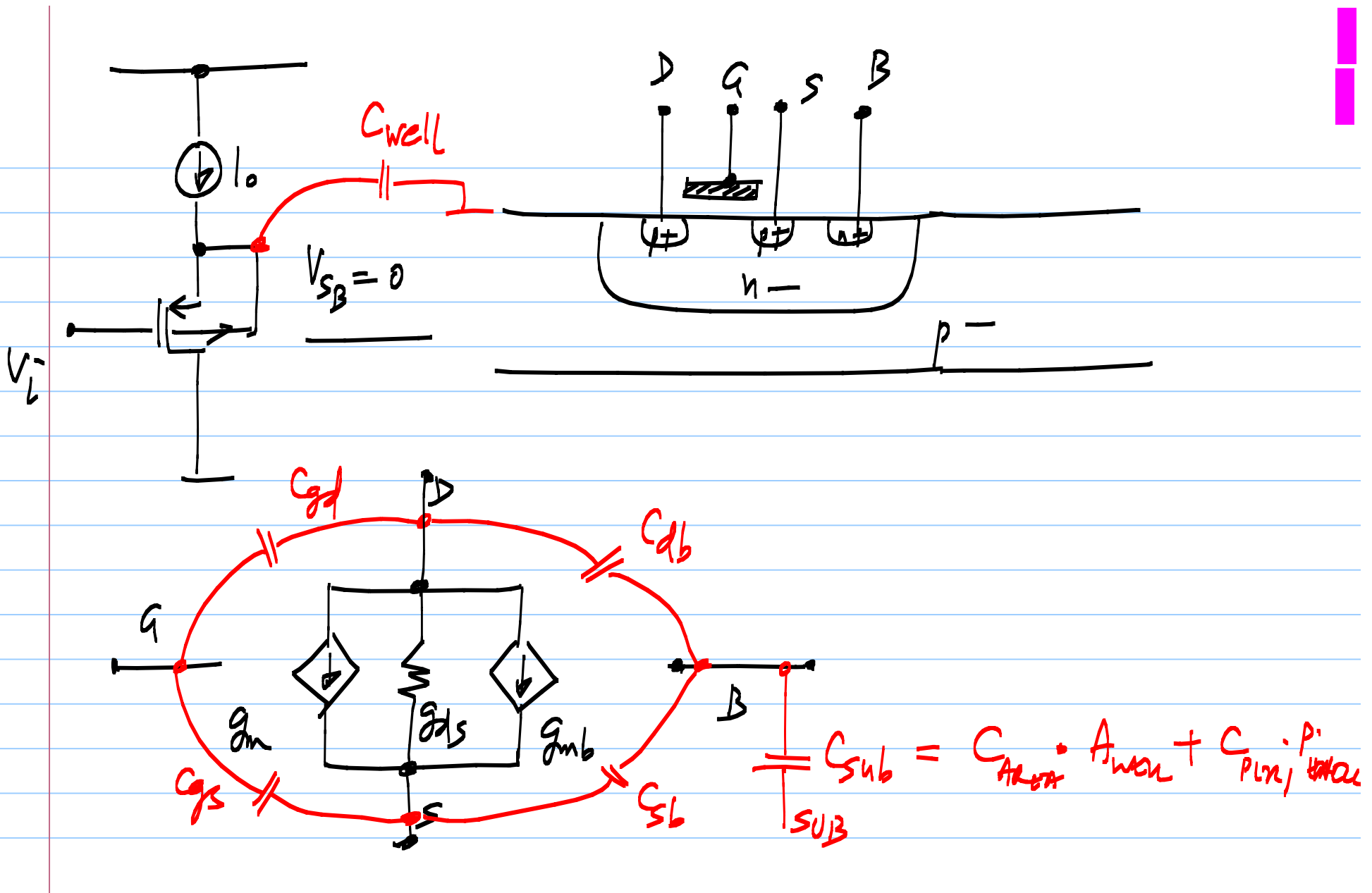
$$V_{gs} = V_T + \sqrt{\frac{2I_o}{\mu C_{ox} W/L}}$$



# C.D amplifier at high frequencies

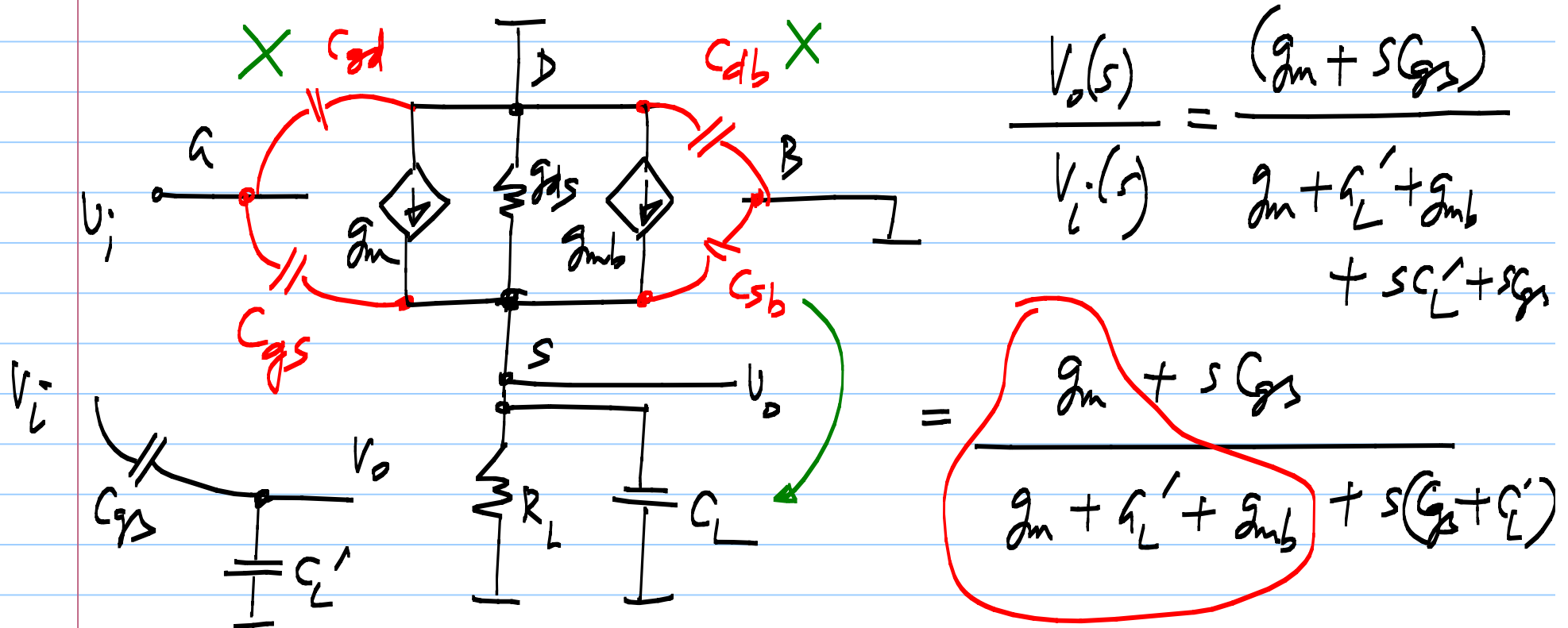



$$\frac{V_o(s)}{V_i(s)} = \frac{(g_m + sC_{gs})}{g_m + g_L' + g_{mb} + sC_L' + sC_{gs}}$$

$$= \frac{g_m + sC_{gs}}{g_m + g_L' + g_{mb} + s(C_L' + C_{gs})}$$

$$(V_i - V_o)(sC_{gs} + g_m) = V_o \left( \underbrace{g_L + g_{ds}}_{g_L'} + s \underbrace{(C_L + C_{sb})}_{C_L'} \right) + g_{mb} V_o$$
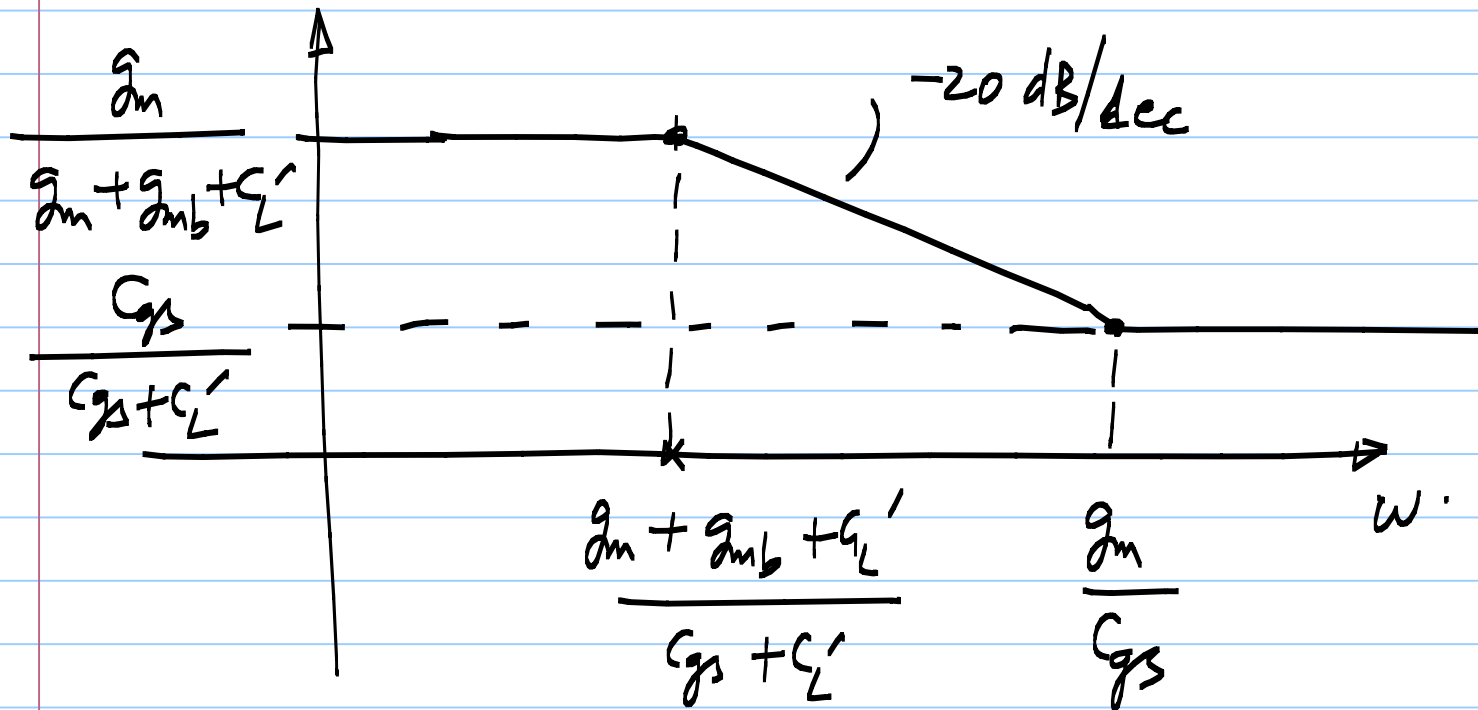
$$\frac{V_o}{V_i} = \frac{g_m + sC_{gs}}{g_m + g_{mb} + g_L' + s(C_{gs} + C_L')}$$



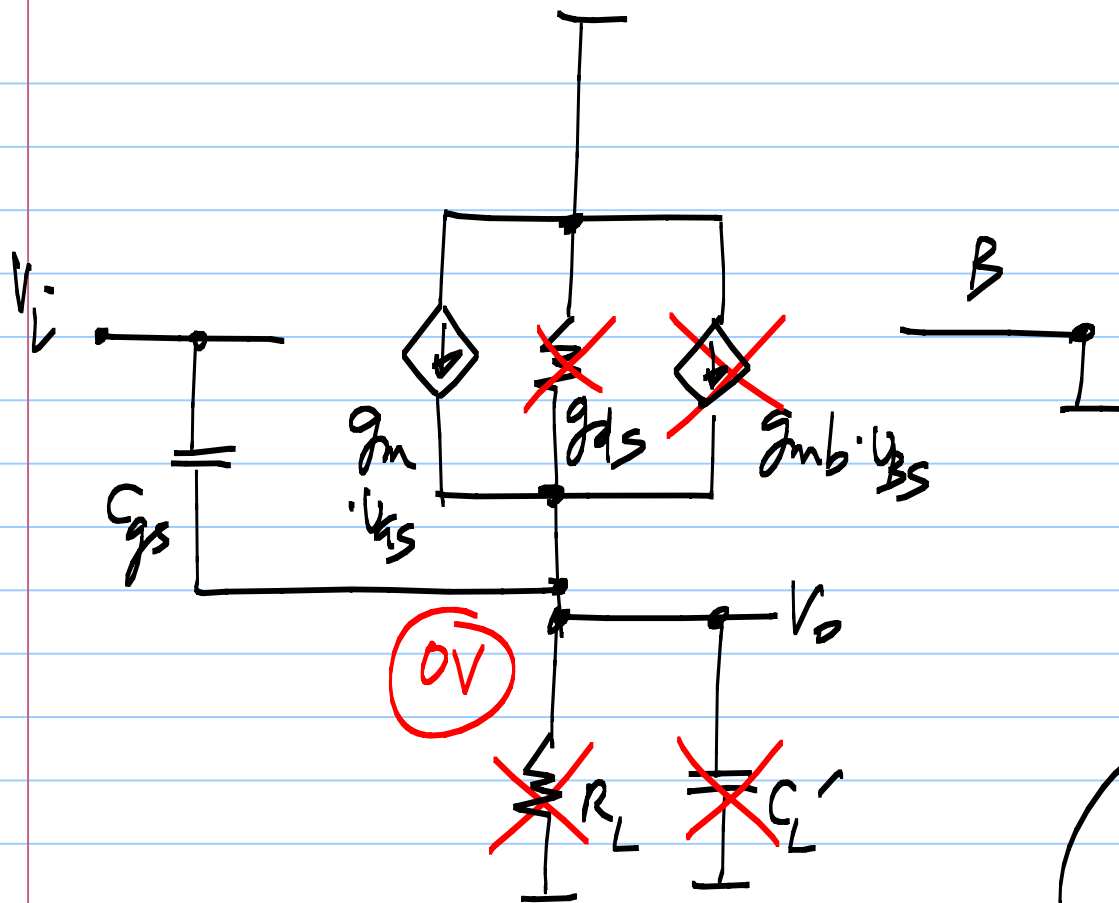

Poles:  $V_i = 0$

$$-\frac{g_m + g_{mb} + g_{ds} + g_L}{C_{gs} + C_L'}$$


Zero:

$$g_m \cdot V_i + sC_{gs} \cdot V_i = 0$$

$$s = z_1$$

$$z_1 = -\frac{g_m}{C_{gs}}$$

# Common gate amplifier:

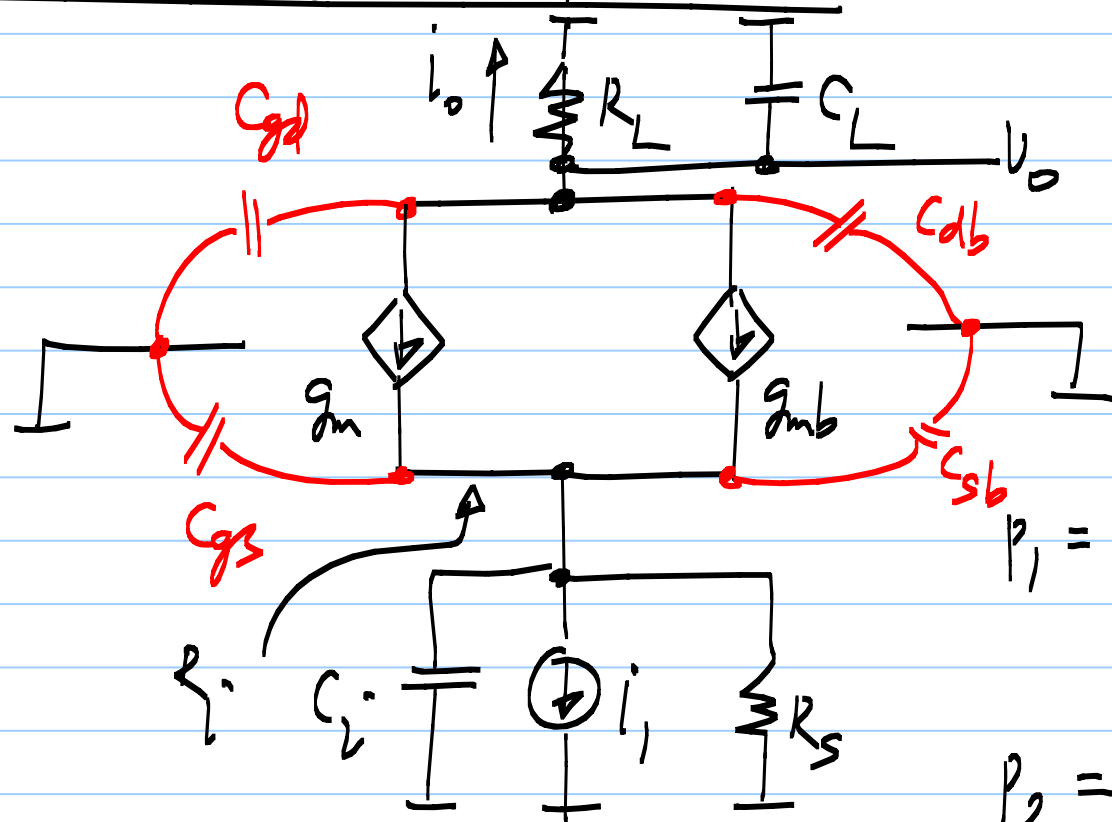

$$C_L' = C_L + C_{db} + C_g$$

$$C_i' = C_{gs} + C_{sb} + C_i$$


2 poles; No zeros

$$p_1 = - \frac{g_m + g_{mb} + g_s}{C_i}$$

$$p_2 = - \frac{1}{R_L C_L'} = - \frac{g_L}{C_L'}$$


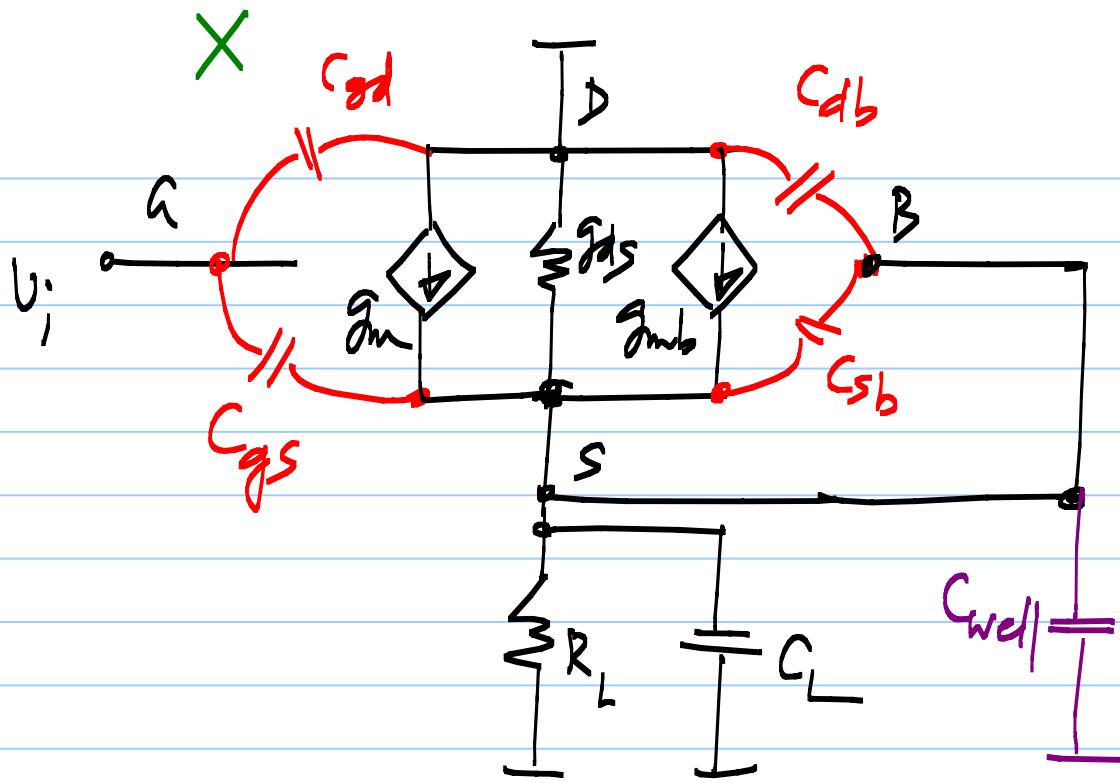
$$\frac{i_o}{i_i} = \frac{g_m + g_{mb}}{g_m + g_{mb} + g_s} \cdot \frac{1}{\left(1 + s \cdot \frac{C_{i'}}{g_s + g_m + g_{mb}}\right) \left(1 + \frac{s C_L'}{g_L}\right)}$$



Bulk was @ s.s. gnd

$$\underline{C_L' = C_L + C_{sb}}$$

Bulk: tied to source

$$\underline{C_L' = C_L + C_{db} + C_{well}}$$

PMOS CD amplifier;

CS amplifier:

$$C_L' = C_{db} + C_L$$

$$g_L' = g_L + g_{ds}$$

