

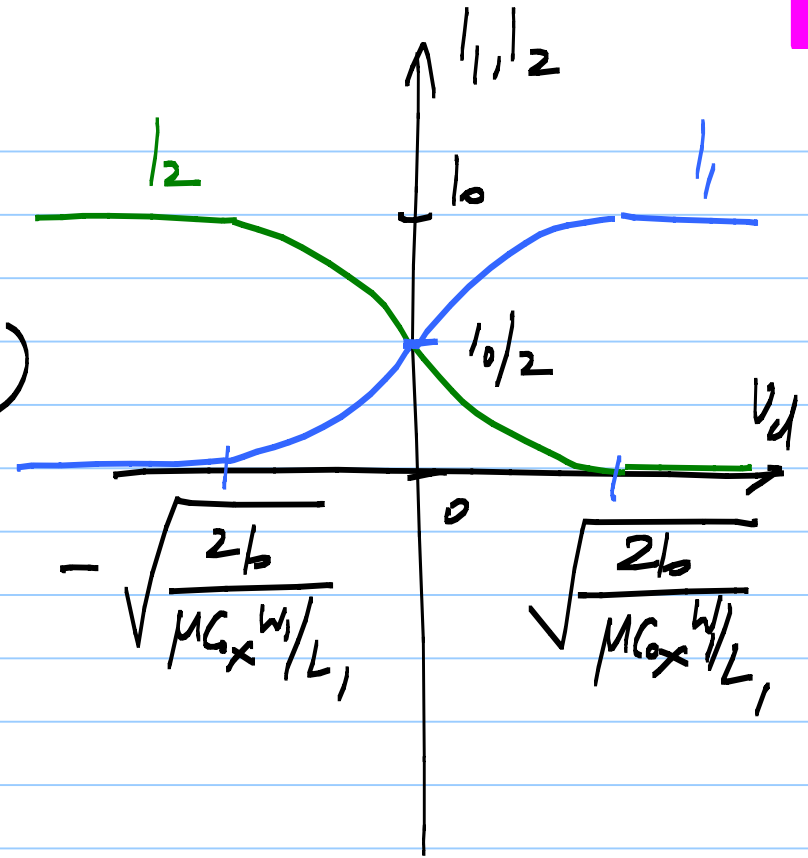
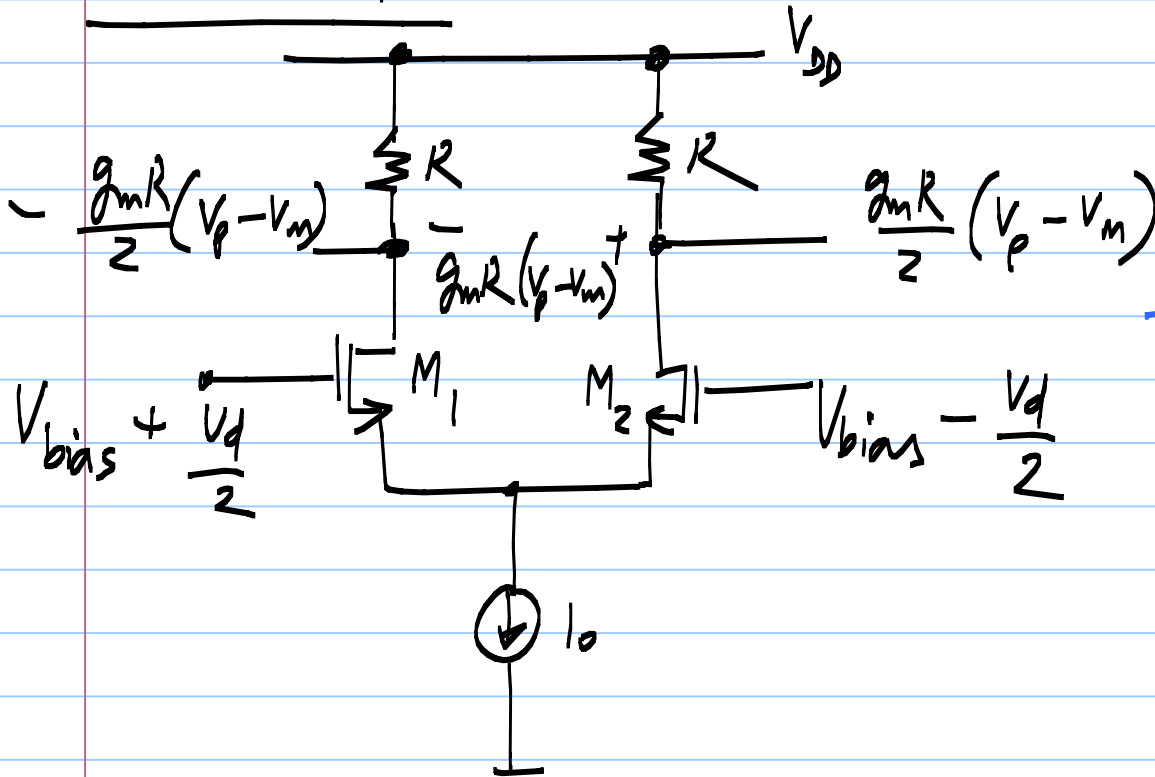



Lecture 29

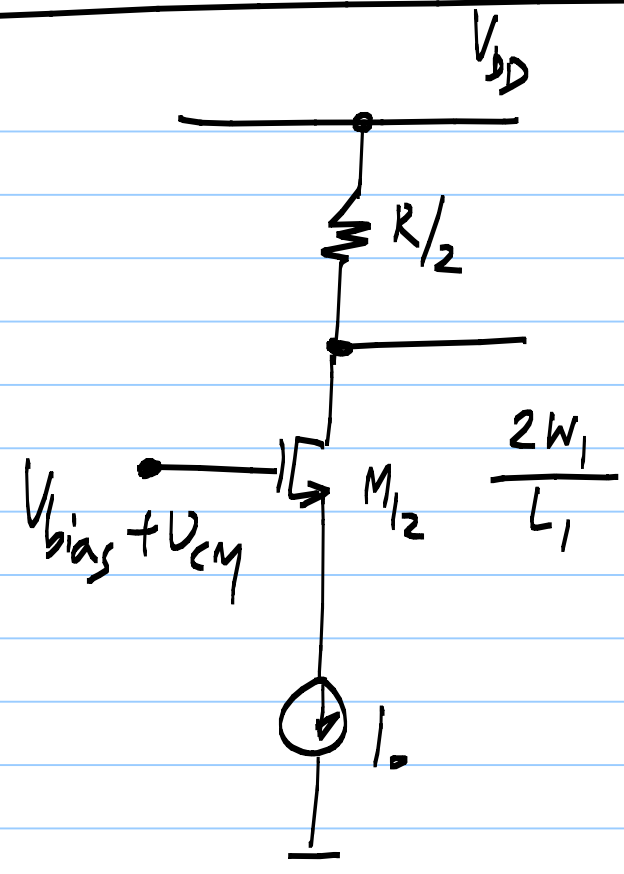


COMMON MODE EQ. CIRCUIT

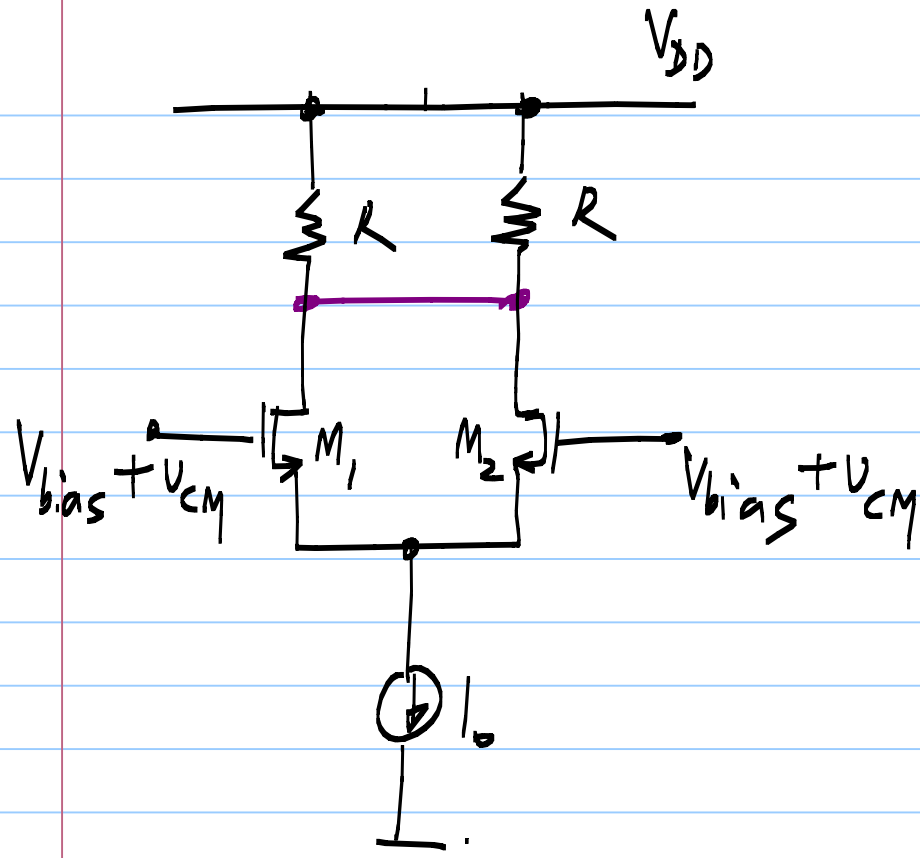


$$M_1 = M_2 \quad \frac{W_1}{L_1}$$

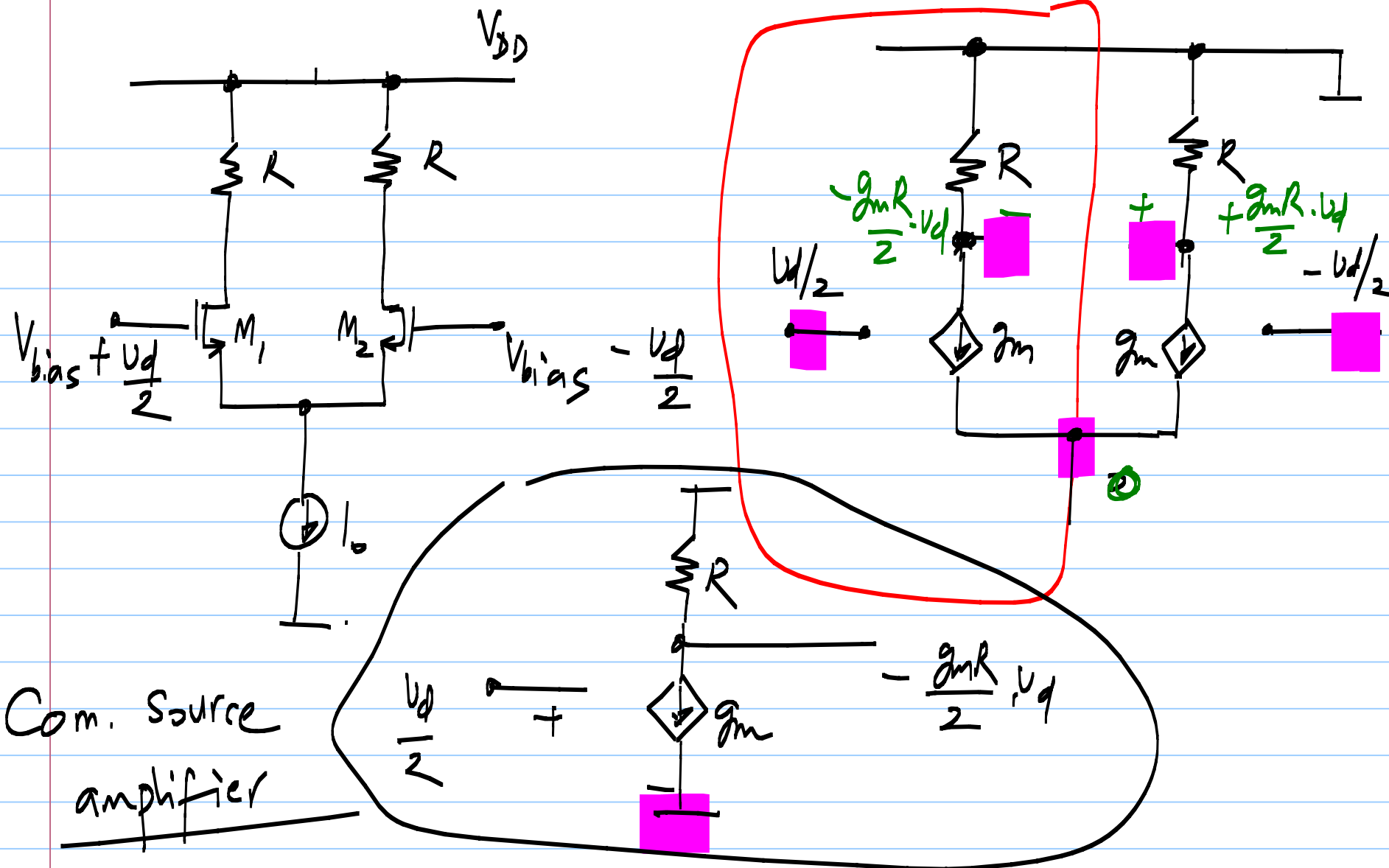

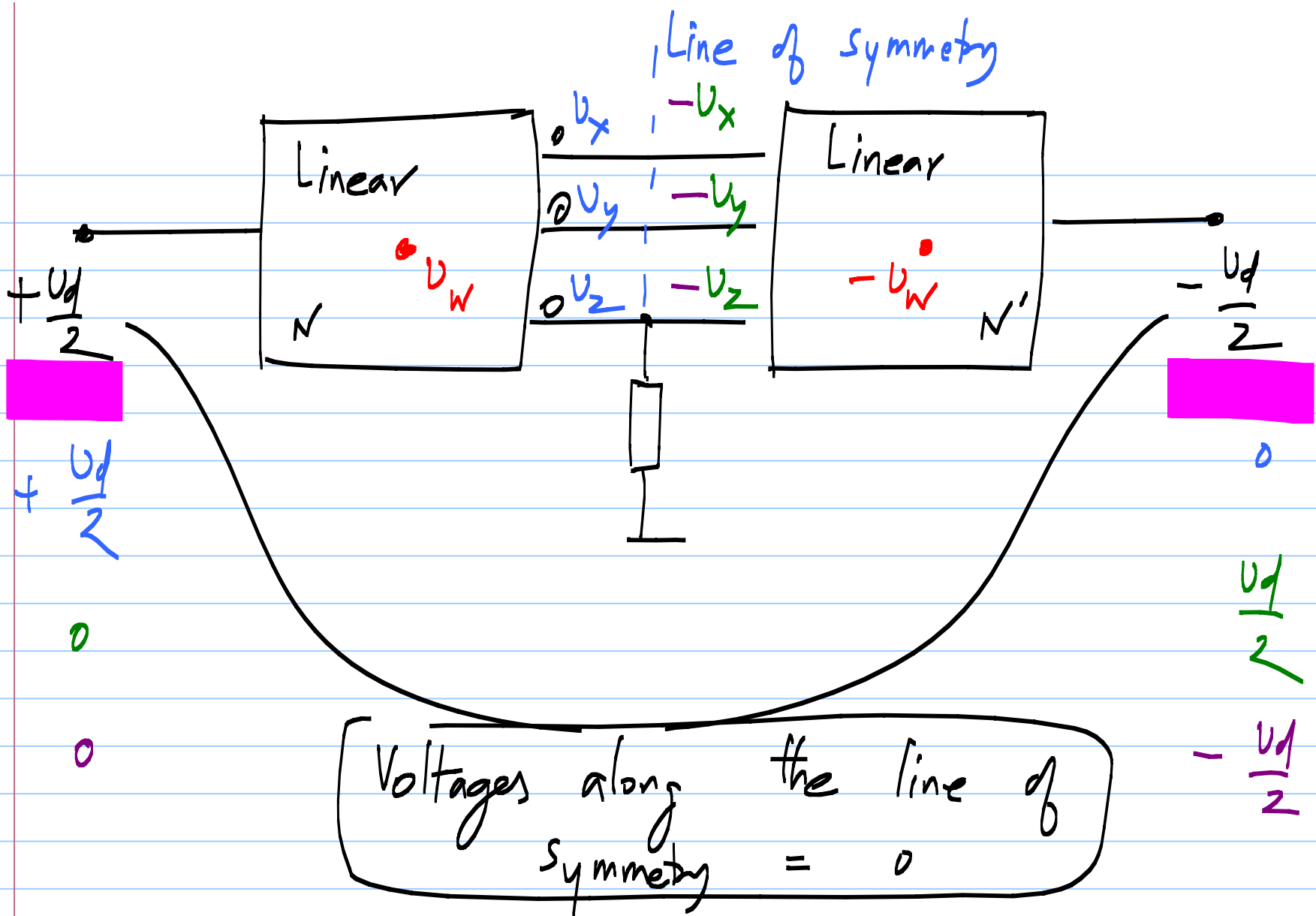

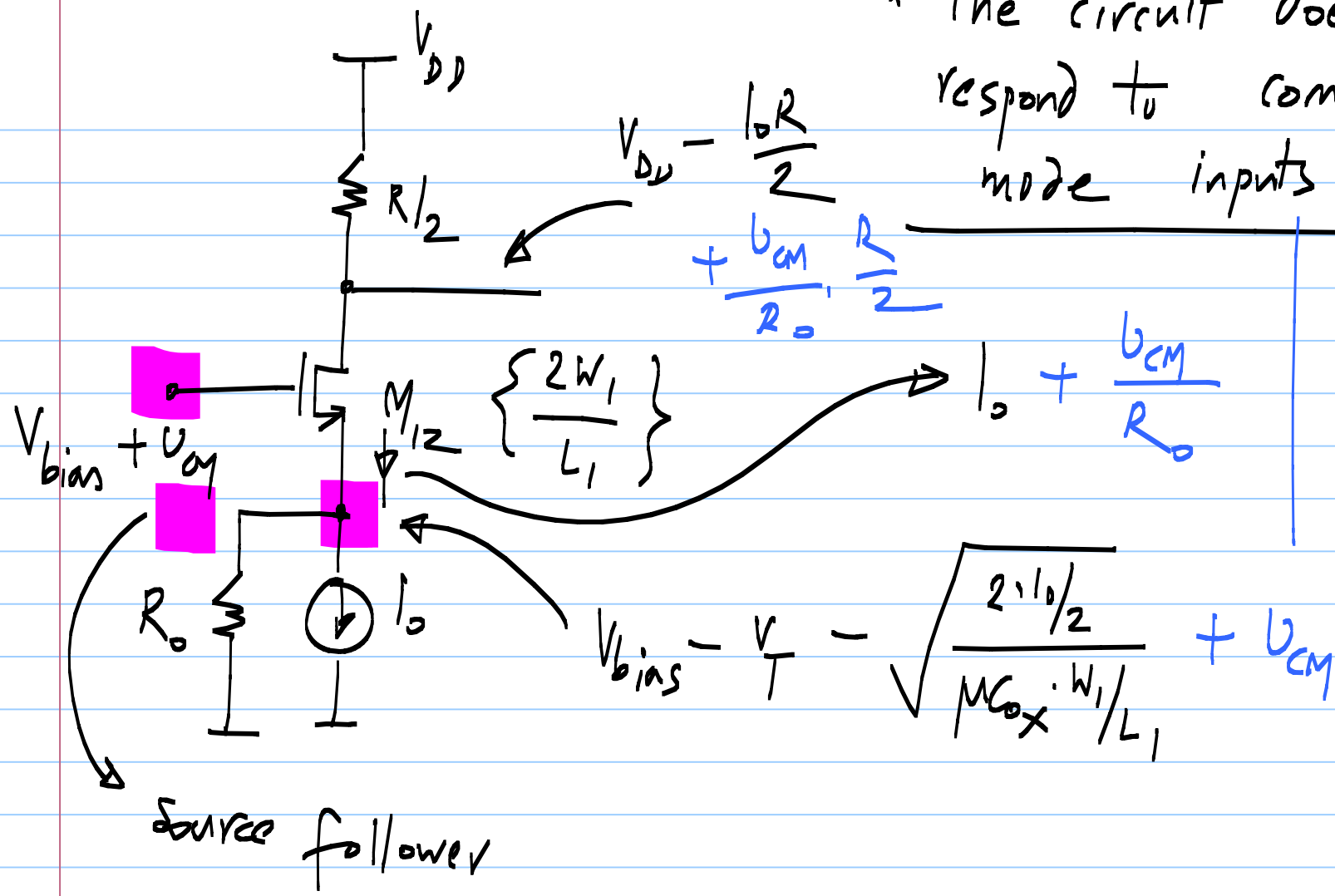* The circuit does not respond to common mode inputs



CM output
 $= \frac{V_{CM} \cdot R}{2R_o}$

CM gain
 $= \frac{R}{2R_o}$

Differential pair:

* Differential gain: $\frac{V_{op} - V_{om}}{V_p - V_m} = g_m R = A_d$
(differential input)

* CM gain = $\frac{(V_{op} + V_{om}) / 2}{(V_p + V_m) / 2} = \frac{R}{2R_o} = A_{cm}$
(CM input)


* CMRR = $\frac{A_d}{A_{cm}} = \frac{g_m R}{R / 2R_o} = 2 \cdot g_m \cdot R_o$

$$V_p = \frac{V_p + V_M}{2} + \frac{V_p - V_M}{2}$$


$$V_M = \frac{V_p + V_M}{2} - \frac{V_p - V_M}{2}$$

$$\frac{V_p + V_M}{2} = V_{CM}$$


$$V_p - V_M = V_d$$

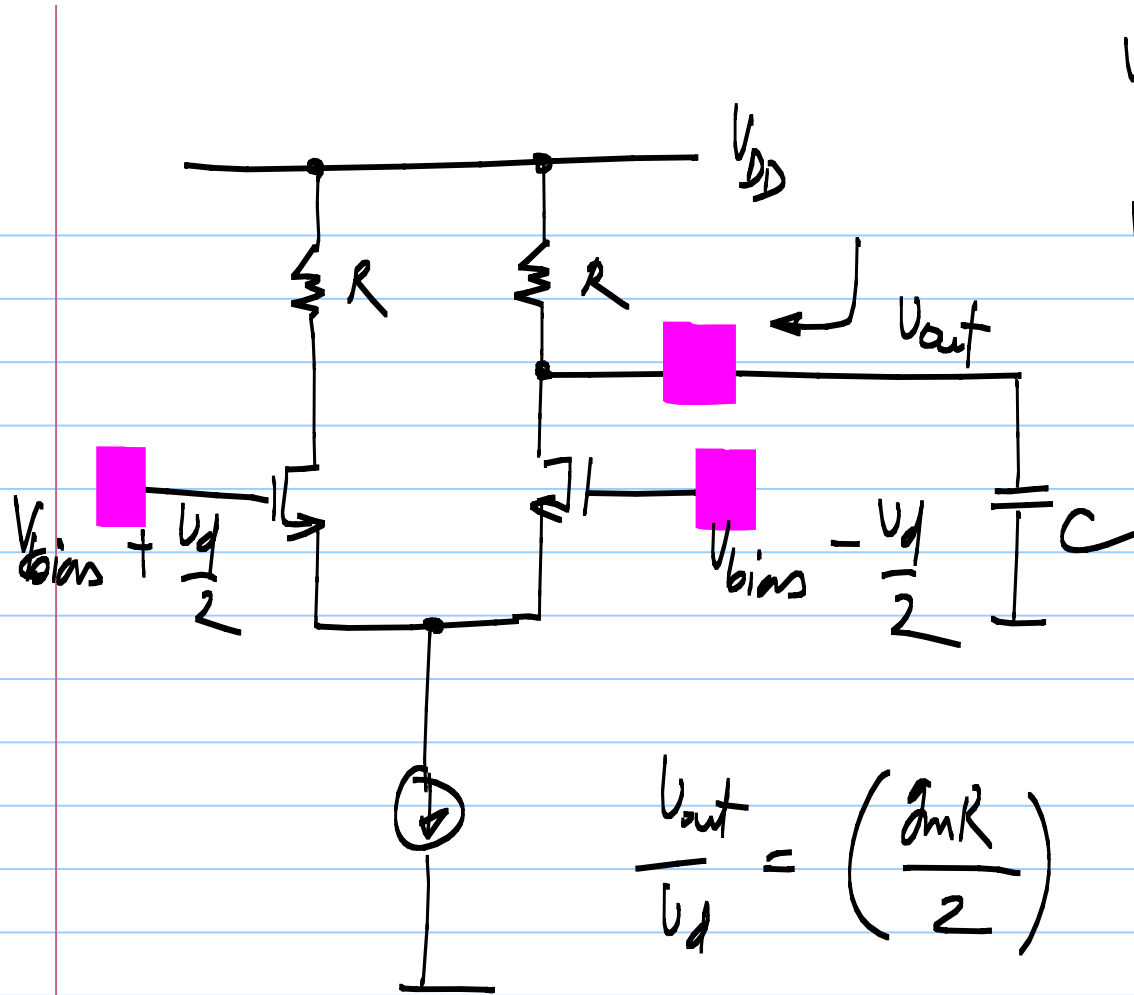
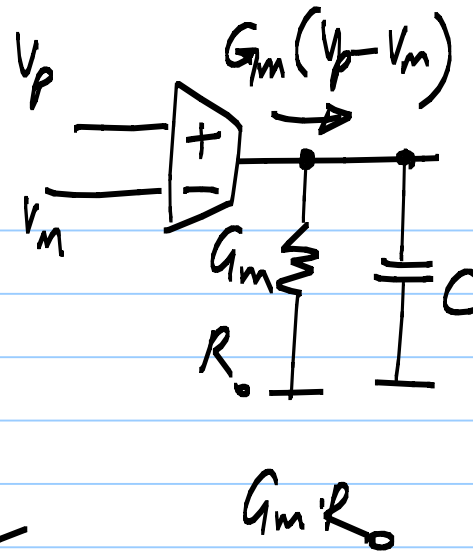
$$\frac{V_{out}}{V_d} = \left(\frac{g_m R}{2} \right)$$




Differential pair with an active load

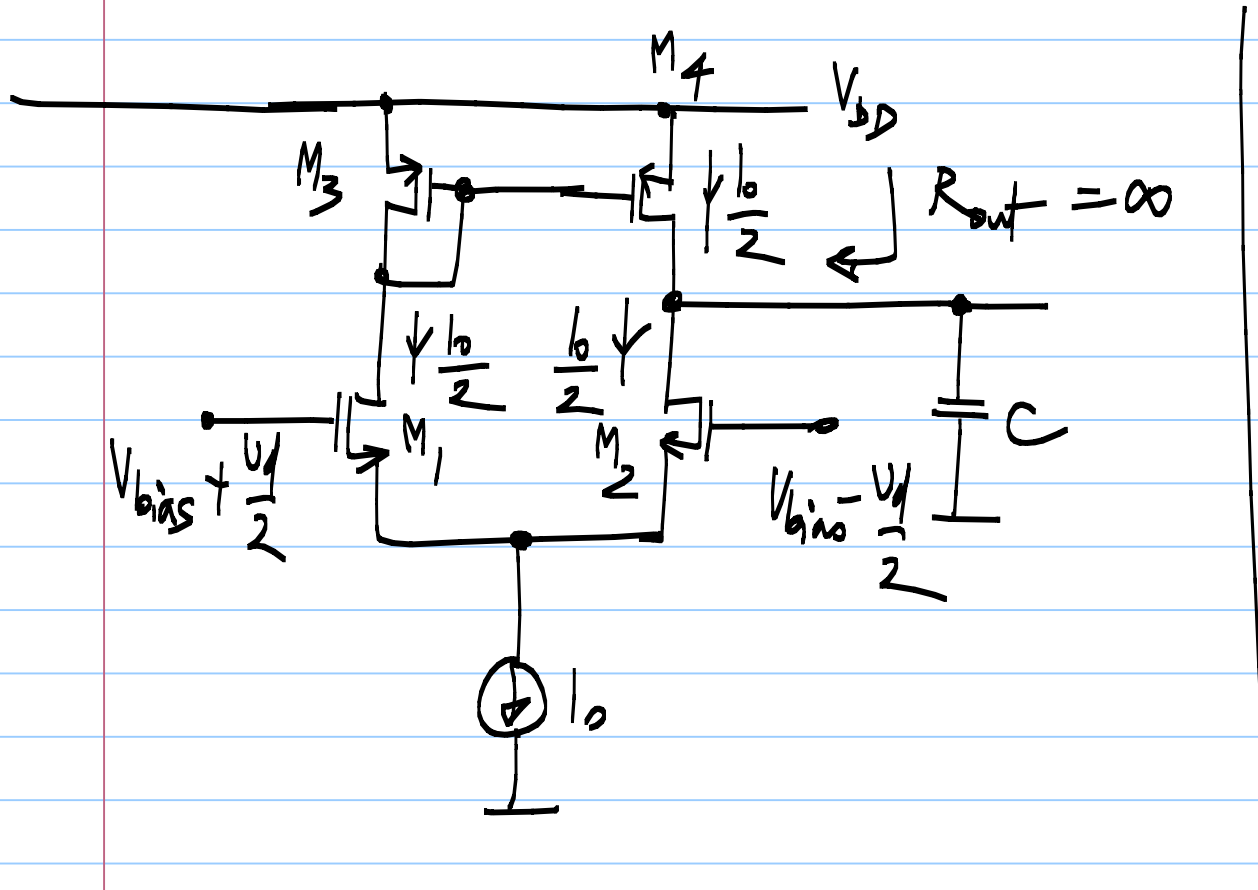

$R_{out} = \infty$ when
 $r_{ds1,2,3,4} = \infty$

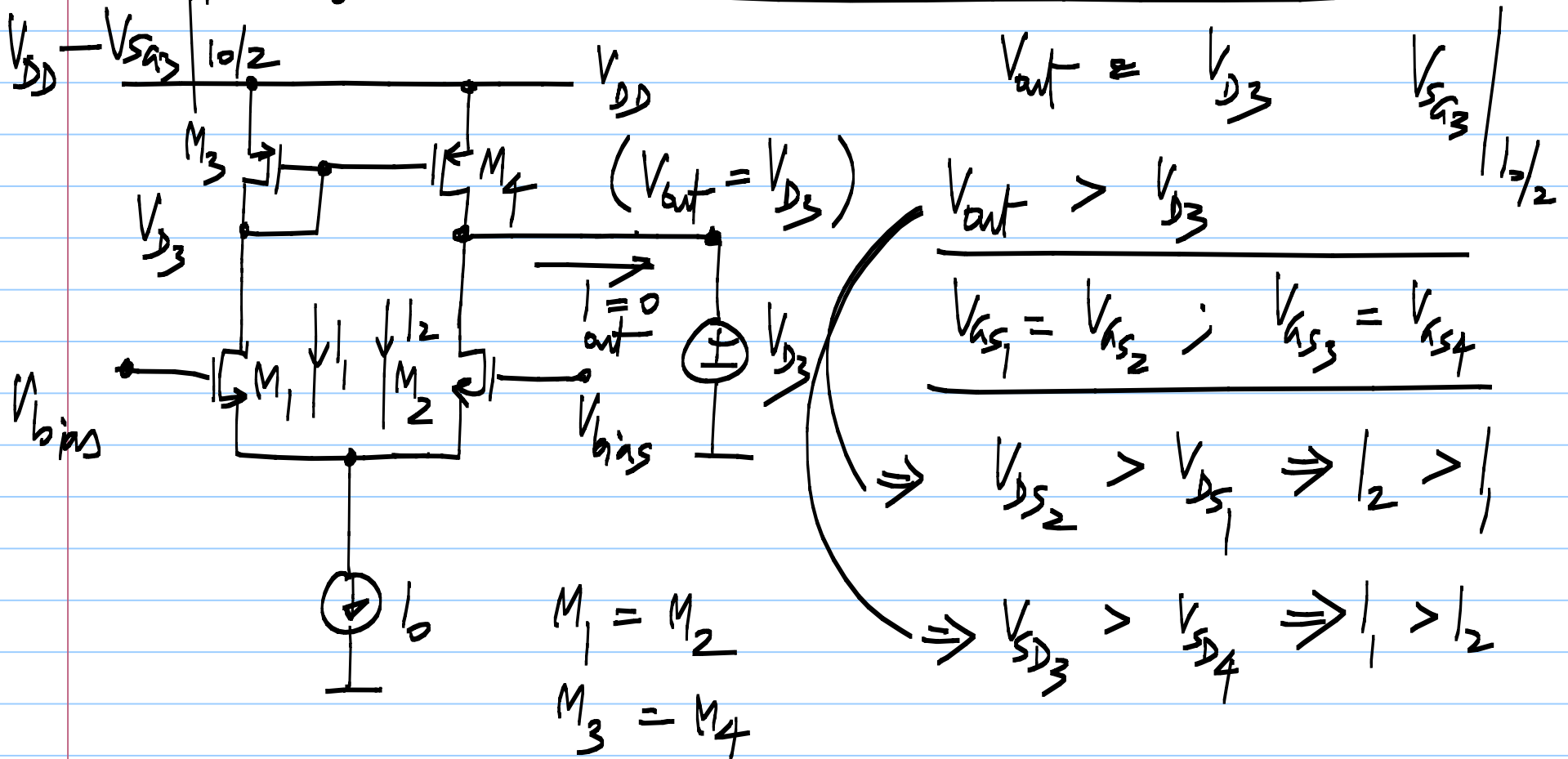Analysis of the differential pair with active load:



CM half circuit

Symmetric circuit w/ symmetric excitation:

* Identical voltages in the two halves of the circuit

* The two halves can be folded on top of each other

* $G \rightarrow 2G$; $W \rightarrow 2W$; $C \rightarrow 2C$
 $L \rightarrow L/2$; $R \rightarrow R/2$ [two halves]

* Components along the line of symmetry — $n=1$ changed

Symmetric circuit w/ anti-symmetric excitation

* (Linear circuit) Voltages along the line of symmetry $\rightarrow 0$

* Voltages in each half are antisymmetric

Differential half ckt