
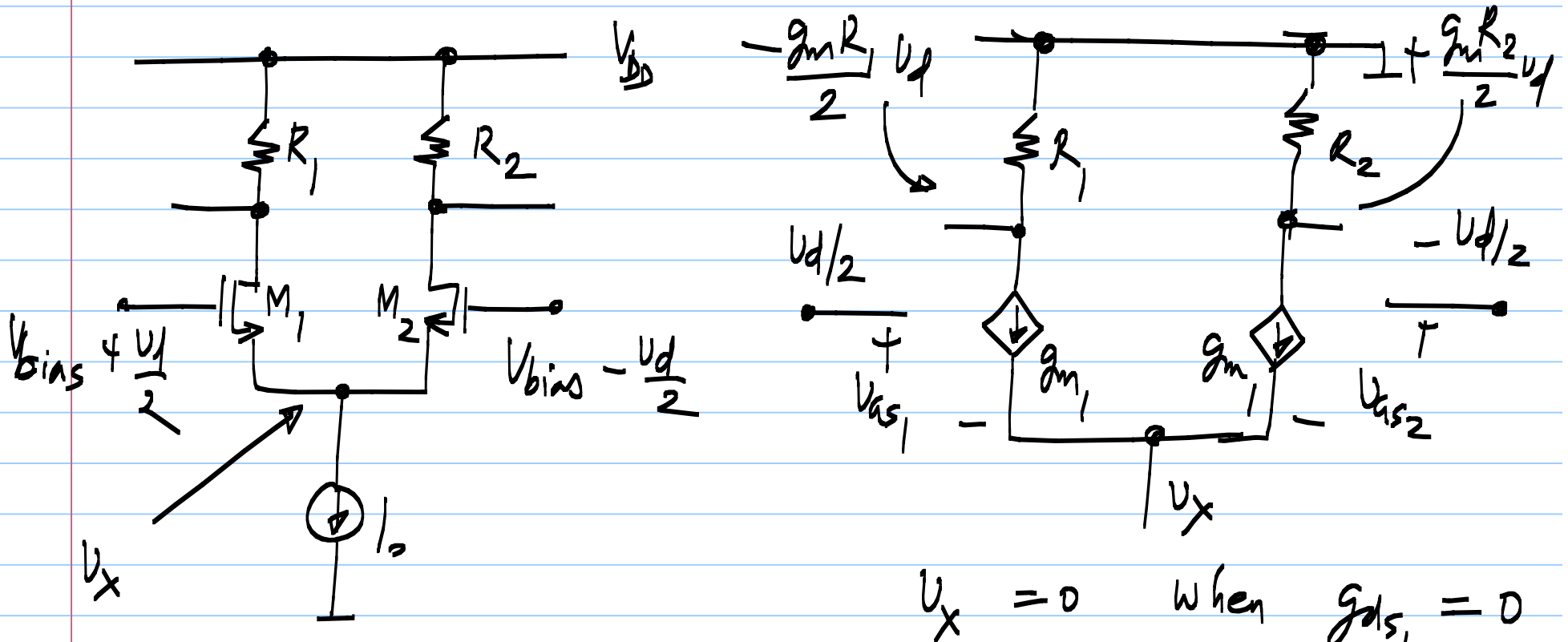

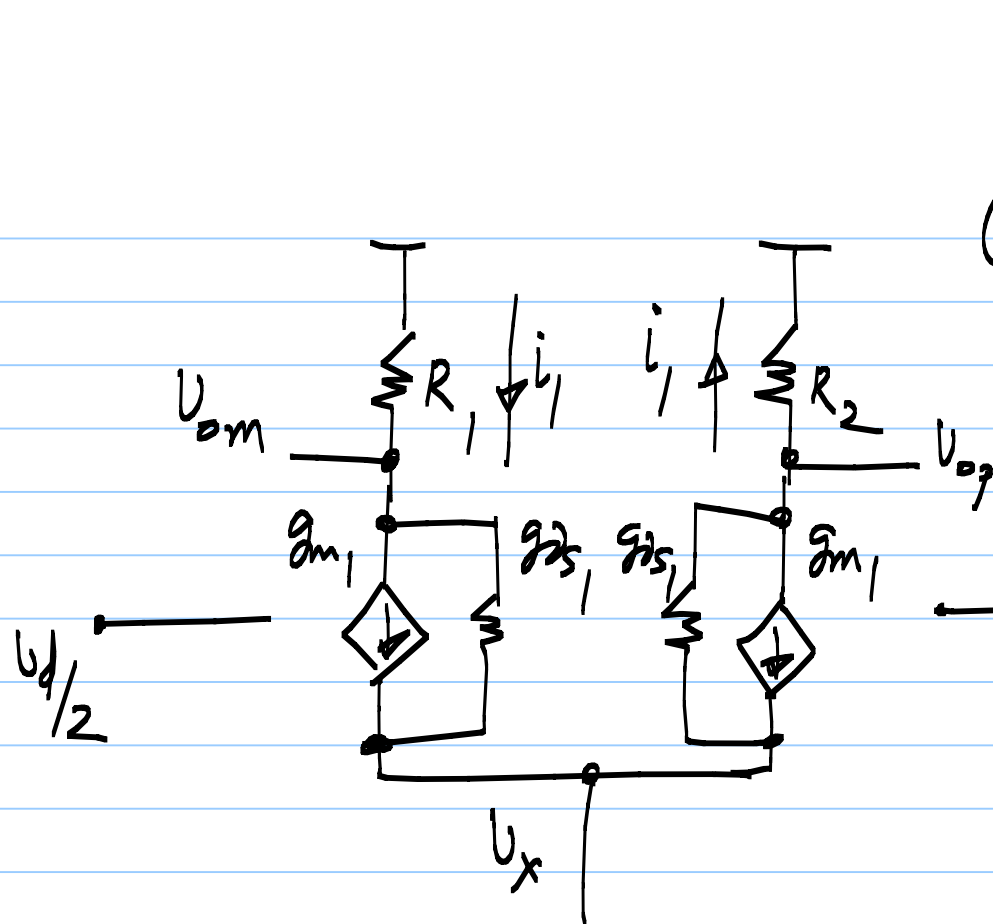
# Lecture 30: Differential pair w/ current mirror load.



$V_x = 0$  when  $g_{ds1} = 0$



$$\textcircled{1} \quad -\frac{V_{om}}{R_1} = \frac{V_{op}}{R_2} = i_1$$

$$\textcircled{2} \quad \frac{V_{om}}{R_1} + (V_{om} - v_x)g_{ds1} + \left(\frac{v_d}{2} - v_x\right)g_{m1} = 0$$

$$\textcircled{3} \quad \frac{V_{op}}{R_2} + (V_{op} - v_x)g_{ds1} + \left(-\frac{v_d}{2} - v_x\right)g_{m1} = 0$$

$$v_x = \frac{v_d}{2} \cdot \frac{g_{m1}}{g_{m1} + g_{ds1}} \cdot \left[ \frac{g_{ds1}(R_2 - R_1)}{1 + g_{ds1}(R_2 + R_1)} \right]$$

$$V_x = \frac{V_d}{2} \cdot \frac{g_{m1}}{g_{m1} + g_{ds1}} \cdot \left[ \frac{g_{ds1}(R_2 - R_1)}{1 + g_{ds1}(R_2 + R_1)} \right]$$

$\approx 1$

\*  $V_x = 0$  if  $R_2 = R_1$  OR  $g_{ds1} = 0$


\*  $V_x \approx 0$  if  $|g_{ds1} R_2|, |g_{ds1} R_1| \ll 1$

$$r_{ds1} \gg R_1 \text{ \& } R_2$$

\*  $V_x \neq 0$  if  $R_1$  &  $R_2$  are comparable to  $r_{ds1}$

$$G_m = g_{m1}$$

$$\approx g_{m1} \cdot V_d / 2$$

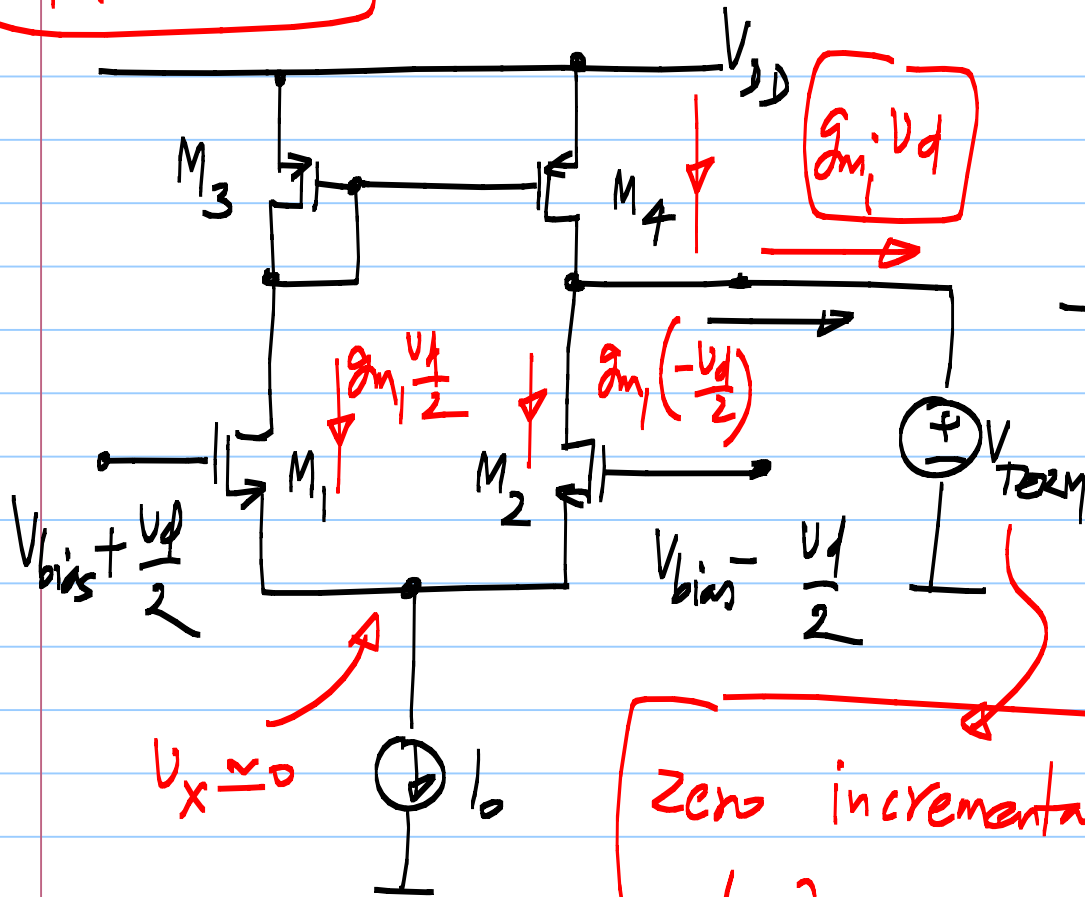

$$V_x \approx 0$$

Zero incremental load

$$V_x \approx 0$$



\* Load: asymmetrical


$$\frac{1}{g_{m3}}, \frac{1}{g_{ds3}}$$

\* Not  $\ll r_{ds1}$


$$\frac{1}{g_{m3}} \ll r_{ds1}$$
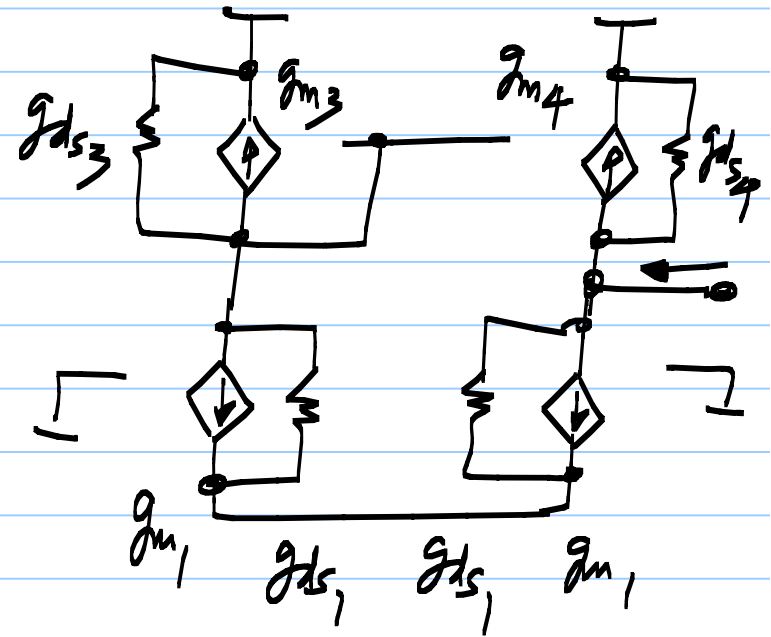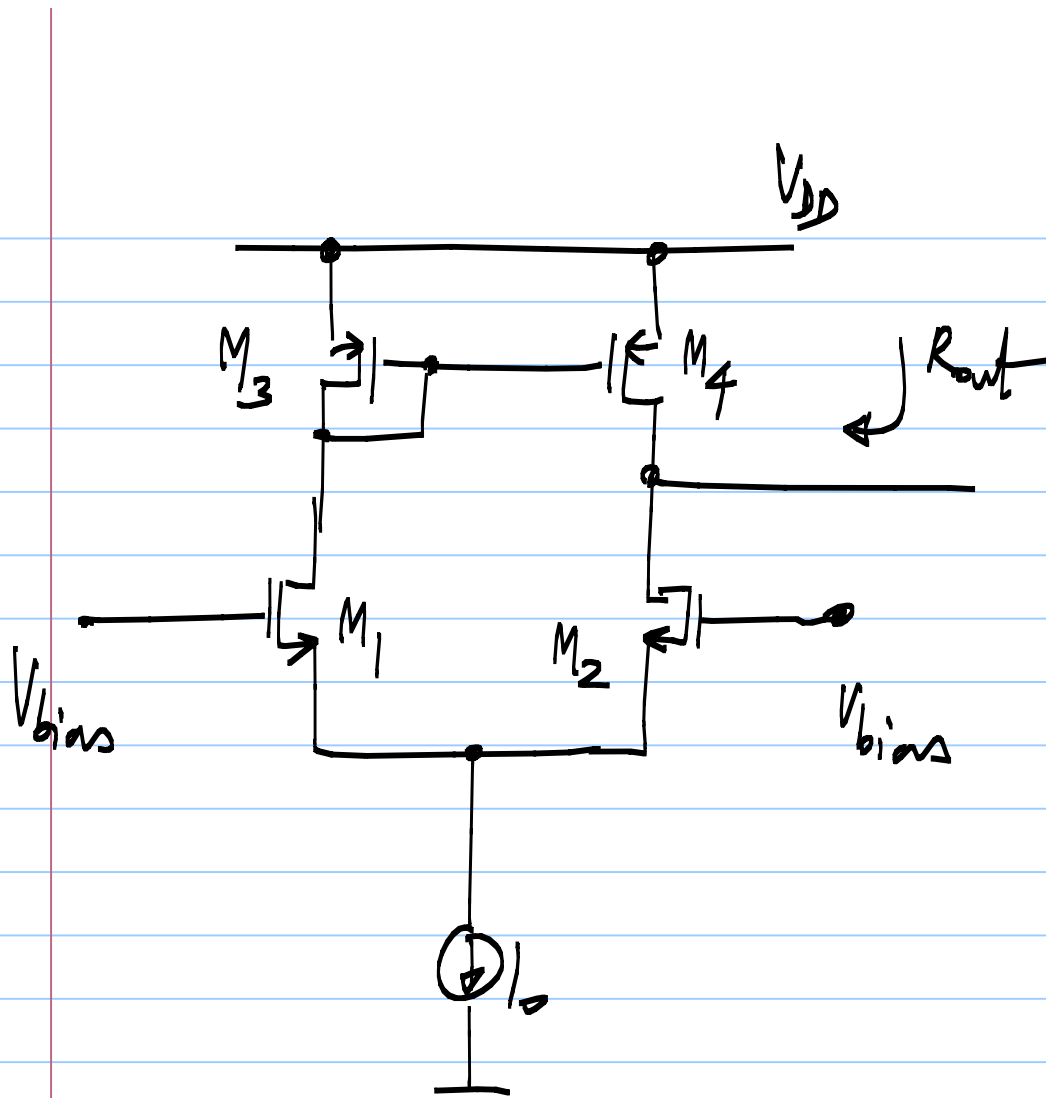
$$\frac{1}{g_{ds3}} = r_{ds3} \sim r_{ds1}$$




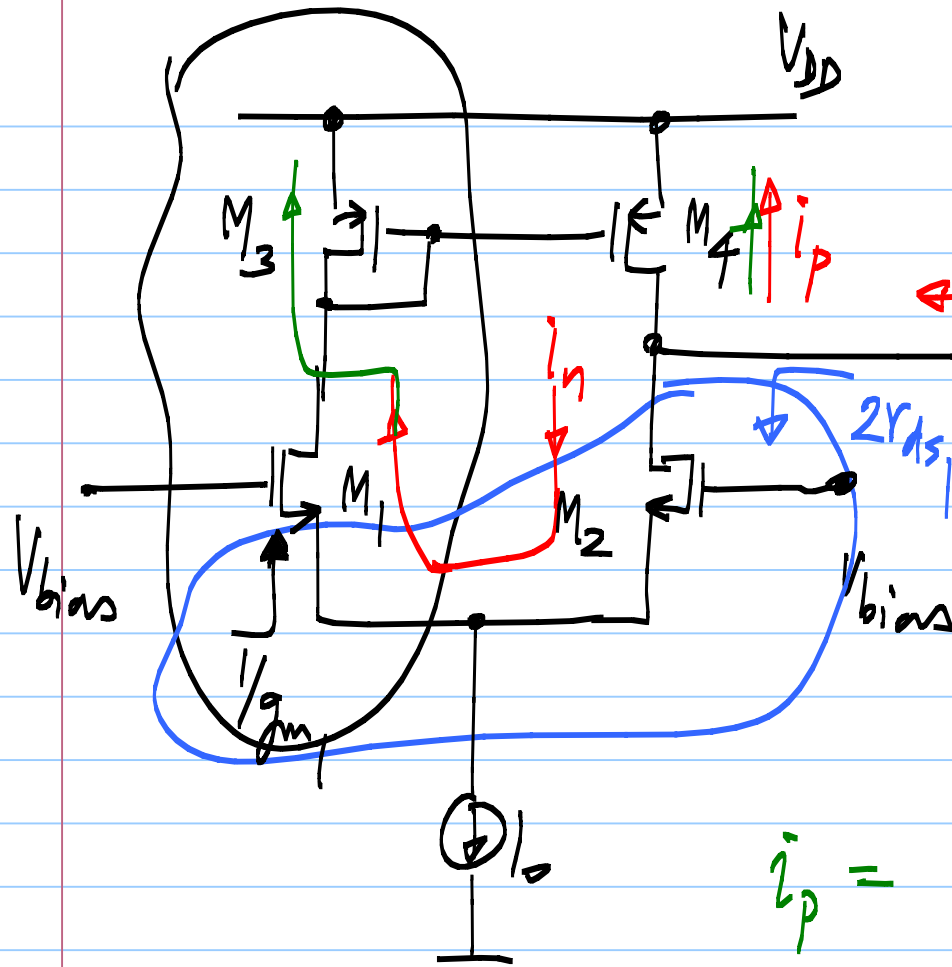
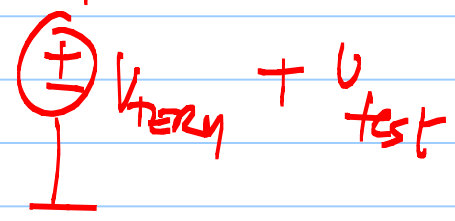
$$i_n = \frac{v_{test}}{2 \cdot r_{ds1}} = \frac{v_{test} \cdot g_{ds1}}{2}$$



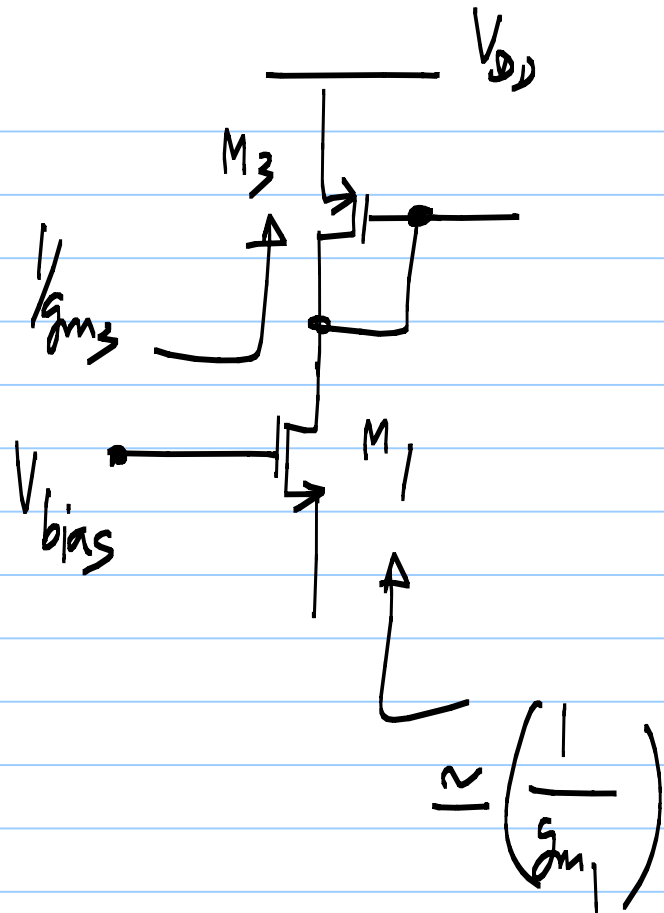
$$i_p = v_{test} \cdot g_{ds3} + v_{test} \cdot \frac{g_{ds1}}{2}$$



$$g_m r_{ds} R_S + r_{ds} + R_S$$
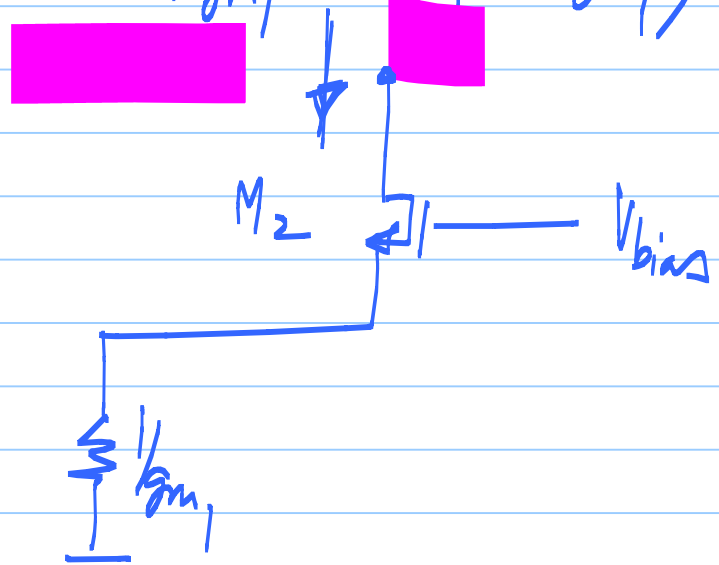
$$\left( g_{m1} r_{ds1} \frac{1}{g_{m1}} + r_{ds1} + \frac{1}{g_{m1}} \right)$$




$$\left[ 2 \cdot r_{ds1} + \cancel{\frac{1}{g_{m1}}} \right]$$

$$\begin{aligned} i_{\text{test}} &= i_p + i_n \\ &= v_{\text{test}} \left\{ \left[ g_{ds3} + \frac{g_{ds1}}{2} \right] + \frac{g_{ds1}}{2} \right\} \end{aligned}$$

$$= v_{\text{test}} \left[ g_{ds3} + g_{ds1} \right]$$
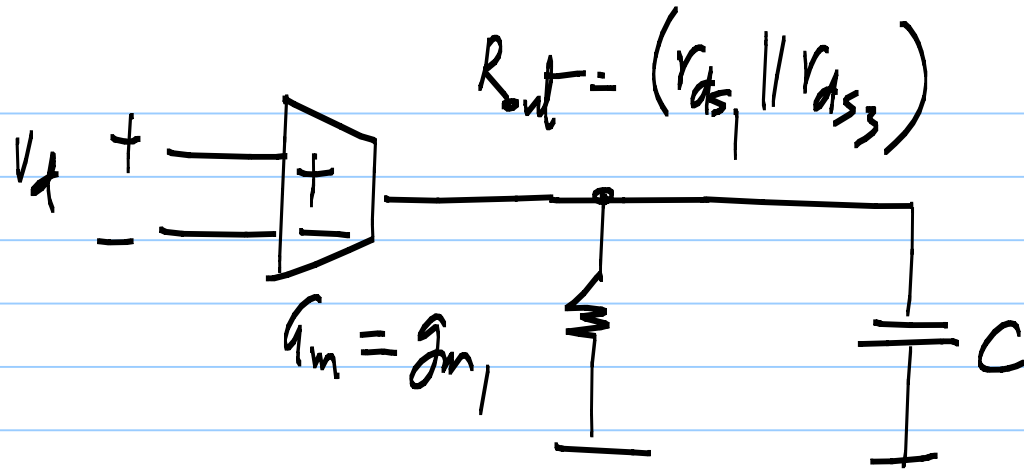
$$R_{\text{out}} = \frac{1}{g_{ds1} + g_{ds3}} = (r_{ds1} \parallel r_{ds3})$$







$$\omega_u = \frac{g_{m1}}{C} ; \quad A_o = g_{m1} (r_{ds1} || r_{ds3})$$


Single stage opamp
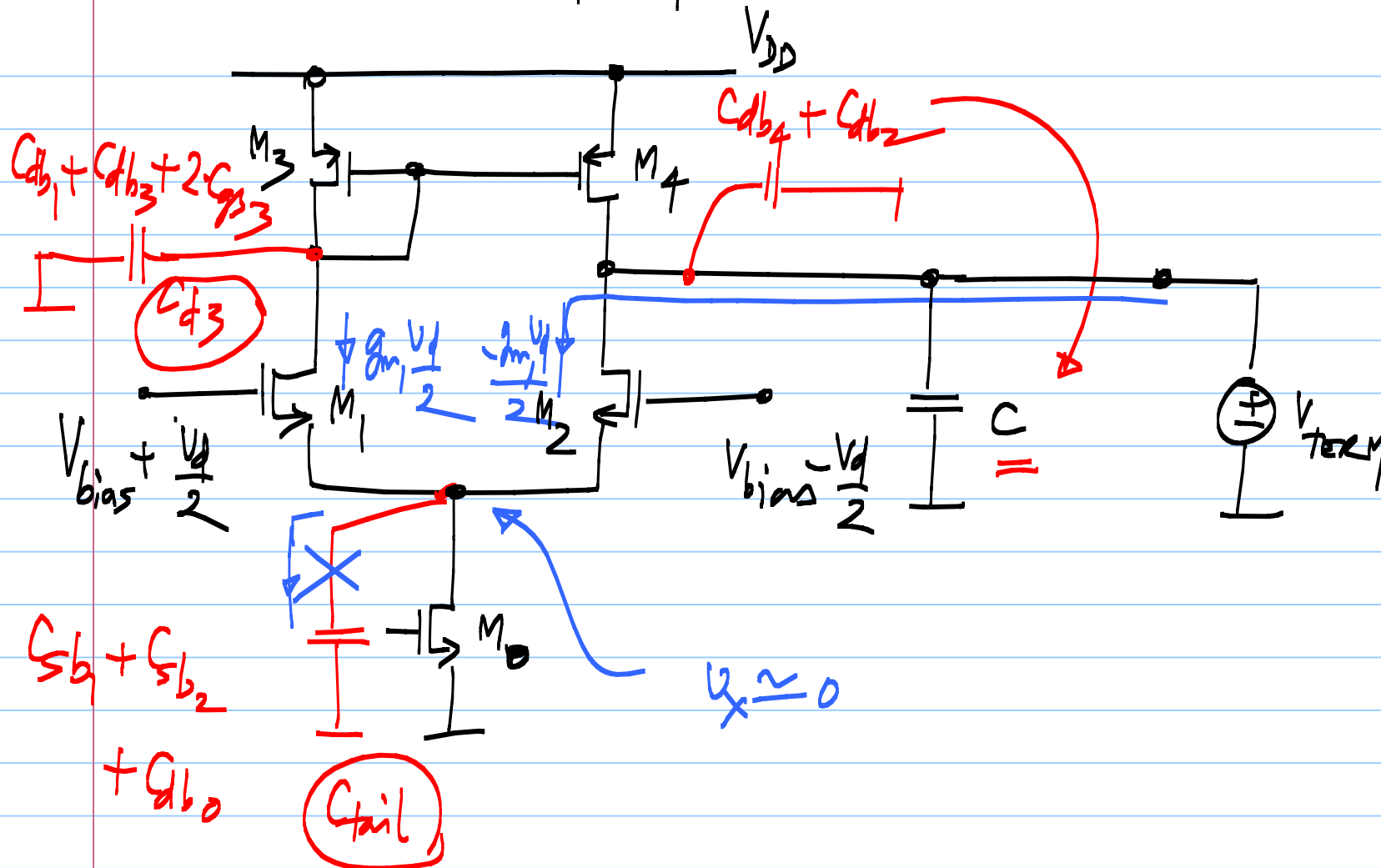
$$\omega_u = g_{m1} / C ; A_D = g_{m1} / (g_{ds1} + g_{ds3})$$



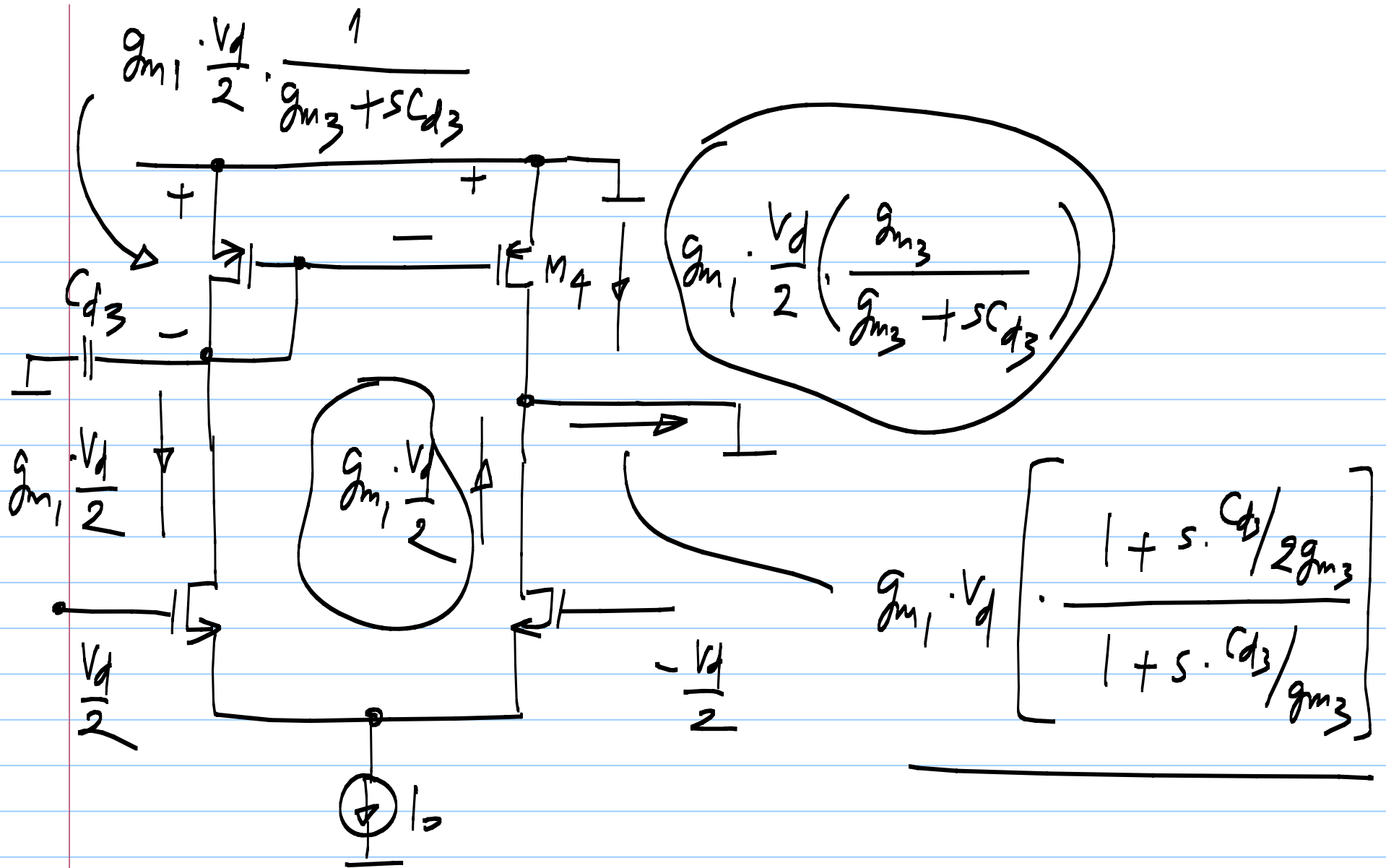
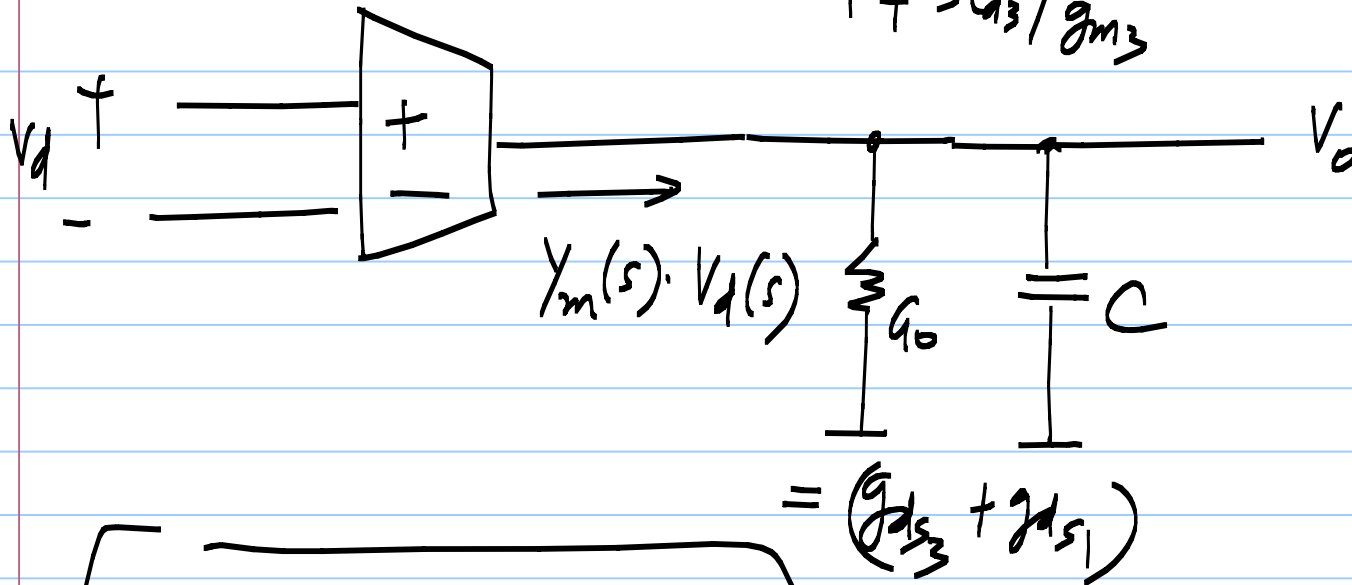
$$Y_m(s) = g_m \cdot \frac{1 + sC_{d3}/2g_{m3}}{1 + sC_{d3}/g_{m3}}$$



$$= (g_{ds3} + g_{ds1})$$

$$\frac{V_o}{V_d} = \frac{Y_m(s)}{(g_{ds3} + g_{ds1} + sC)}$$