

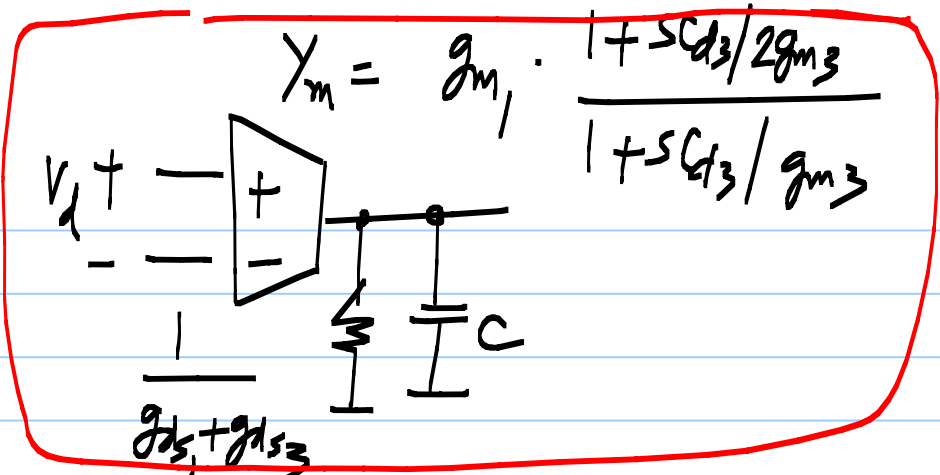


Lecture 31

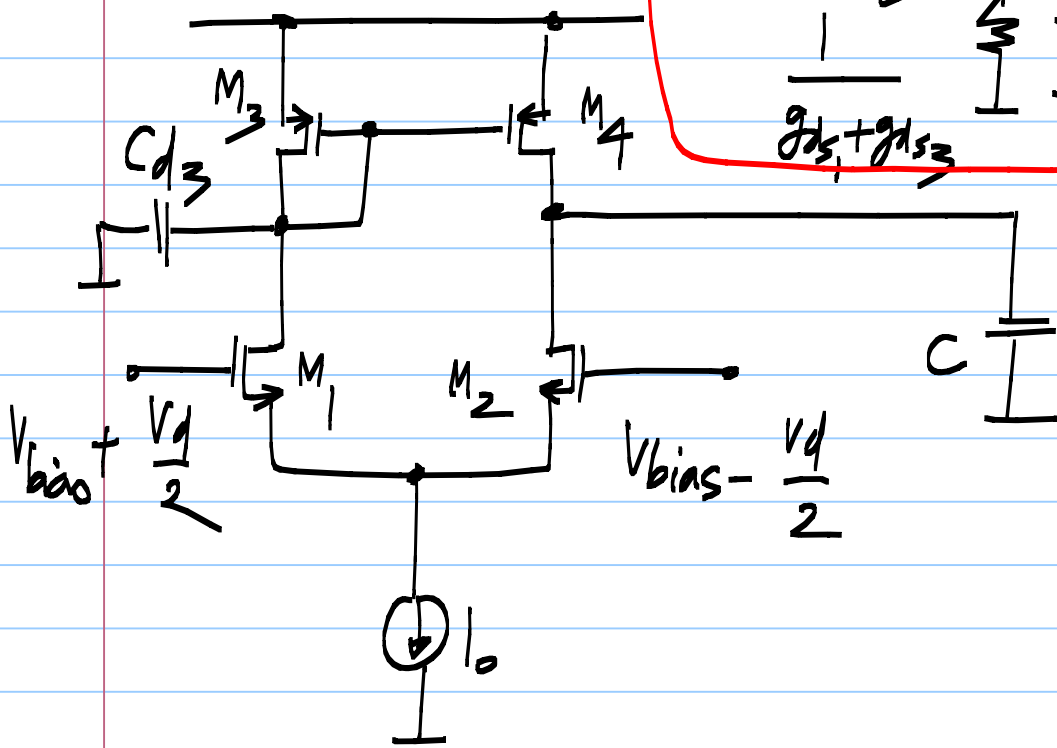

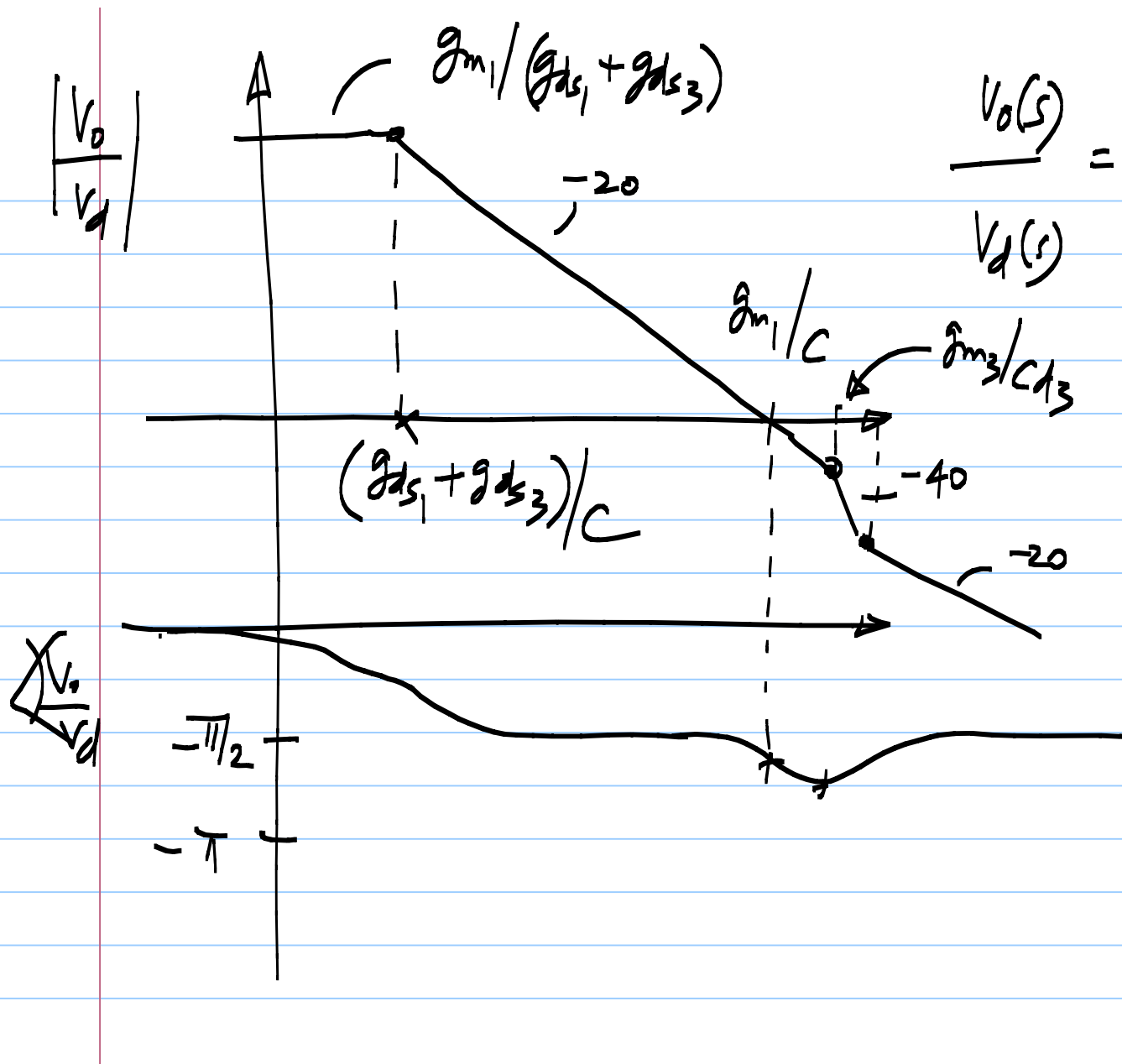
$$Y_m = g_{m1} \cdot \frac{1 + sC_{d3}/2g_{m3}}{1 + sC_{d3}/g_{m3}}$$



$$\frac{V_o(s)}{V_d(s)} = \frac{g_{m1}}{g_{ds1} + g_{ds3} + sC} \cdot \frac{1 + s \frac{C_{d3}}{2g_{m3}}}{1 + s \frac{C_{d3}}{g_{m3}}}$$

Single stage opamp: offset

$$V_{GS4} = \Delta V_{T34}$$

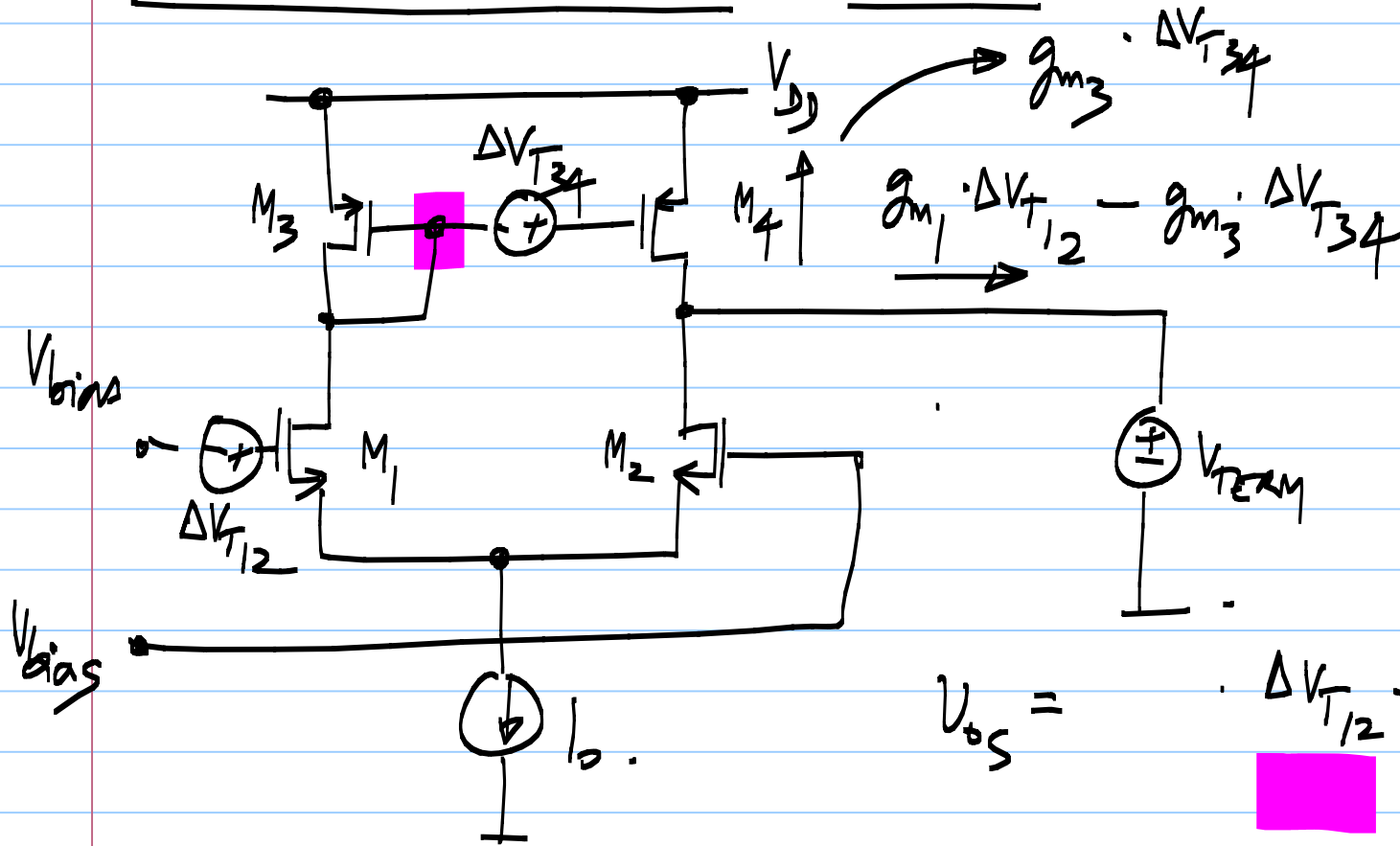


$$\sigma_{v_{os}}^2 = \sigma_{v_{T12}}^2 + \left(\frac{g_{m3}}{g_{m1}} \right)^2 \cdot \sigma_{v_{T34}}^2$$

$$\sigma_{v_{os}} = \sqrt{\sigma_{v_{T12}}^2 + \left(\frac{g_{m3}}{g_{m1}} \right)^2 \cdot \sigma_{v_{T34}}^2}$$


$$\sigma_{v_{os}}^2 = \frac{A_{v_{T12}}^2}{W_1 L_1} + \left(\frac{g_{m3}}{g_{m1}} \right)^2 \cdot \frac{A_{v_{T34}}^2}{W_3 L_3}$$


Single stage opamp: Noise

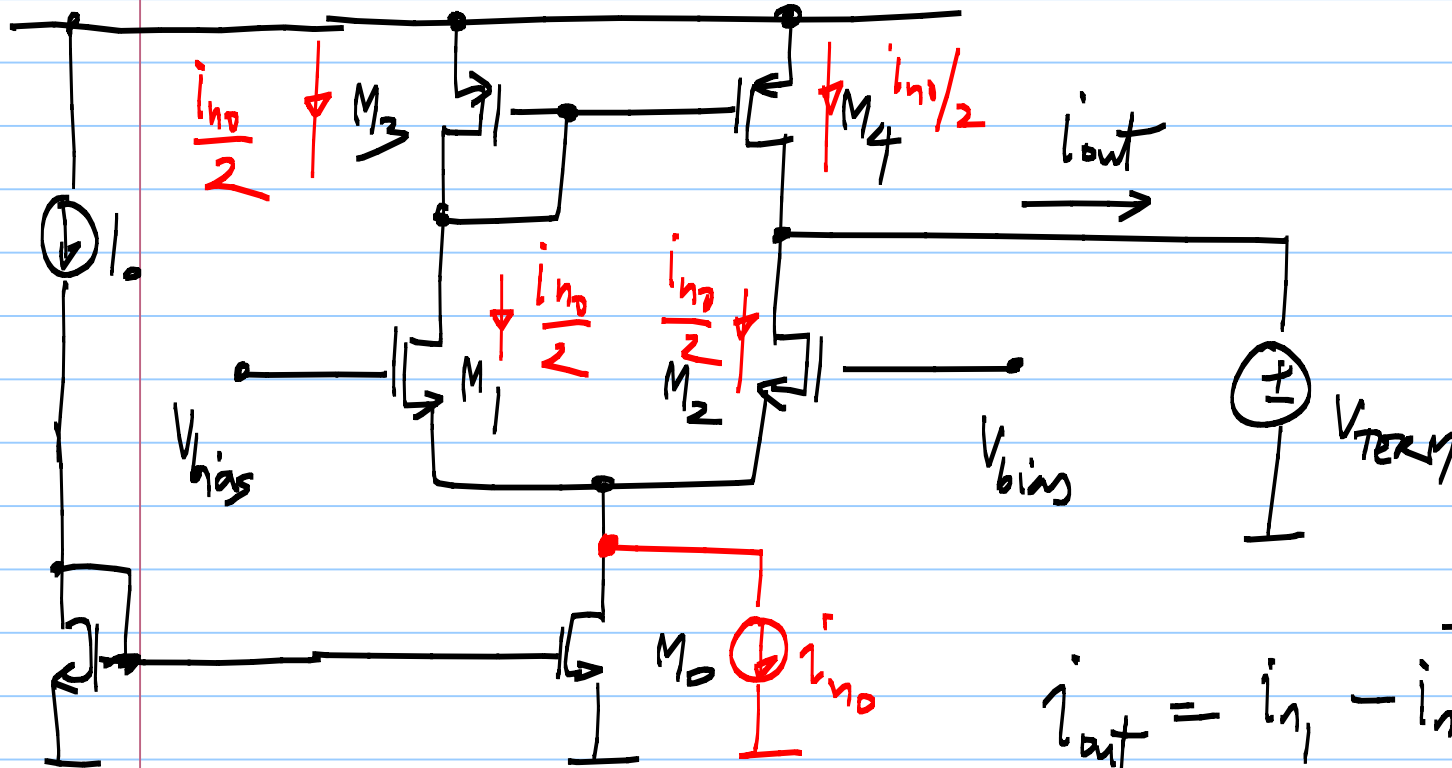

	i_{out}
M ₀ :	0
M ₁ :	i_{n1}
M ₂ :	$-i_{n2}$
M ₃ :	i_{n3}
M ₄ :	$-i_{n4}$
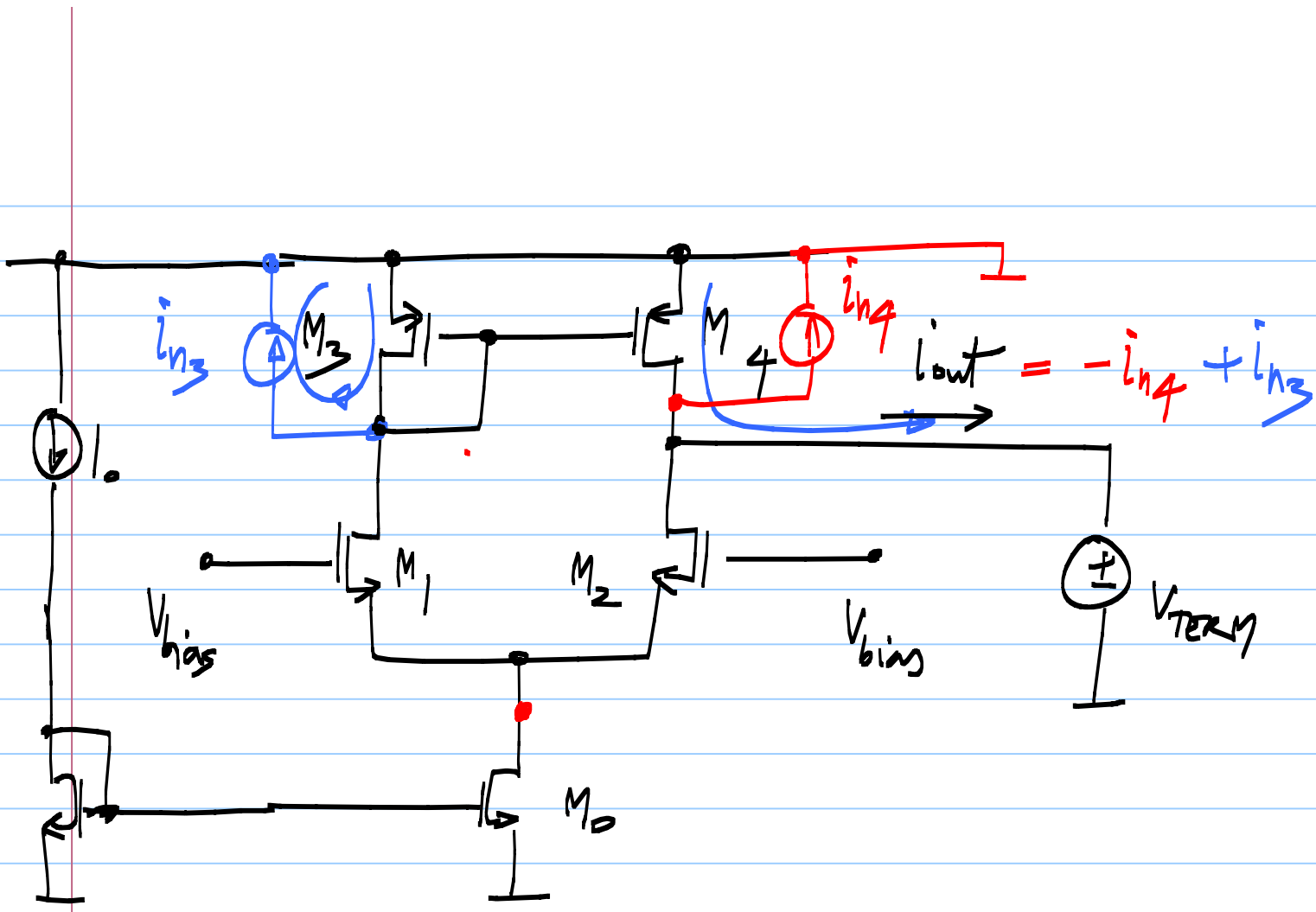
$$i_{out} = i_{n1} - i_{n2} + i_{n3} - i_{n4}$$



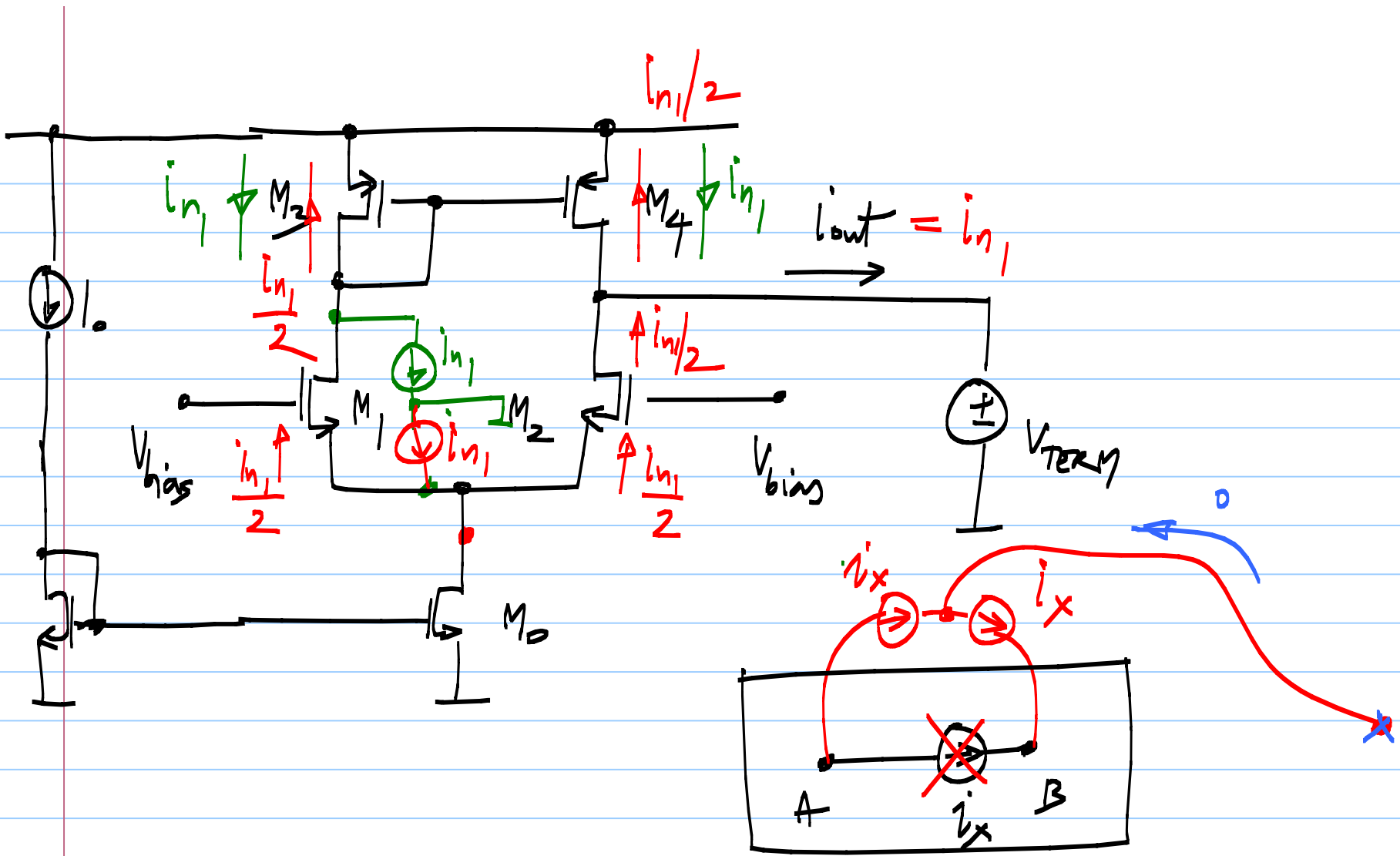

$$i_{out} = i_{n1} - i_{n2} + i_{n3} - i_{n4}$$


$$S_{iout} = S_{i_{n1}} + S_{i_{n2}} + S_{i_{n3}} + S_{i_{n4}}$$

$$= \frac{8}{3} kT (g_{m1} + g_{m1} + g_{m3} + g_{m3})$$

$$= \frac{16}{3} kT (g_{m1} + g_{m3})$$

$$S_{v_{in}} = \frac{S_{iout}}{g_{m1}^2} = \frac{16}{3} \frac{kT}{g_m} \left(1 + \frac{g_{m3}}{g_{m1}} \right)$$

Large signal limits:

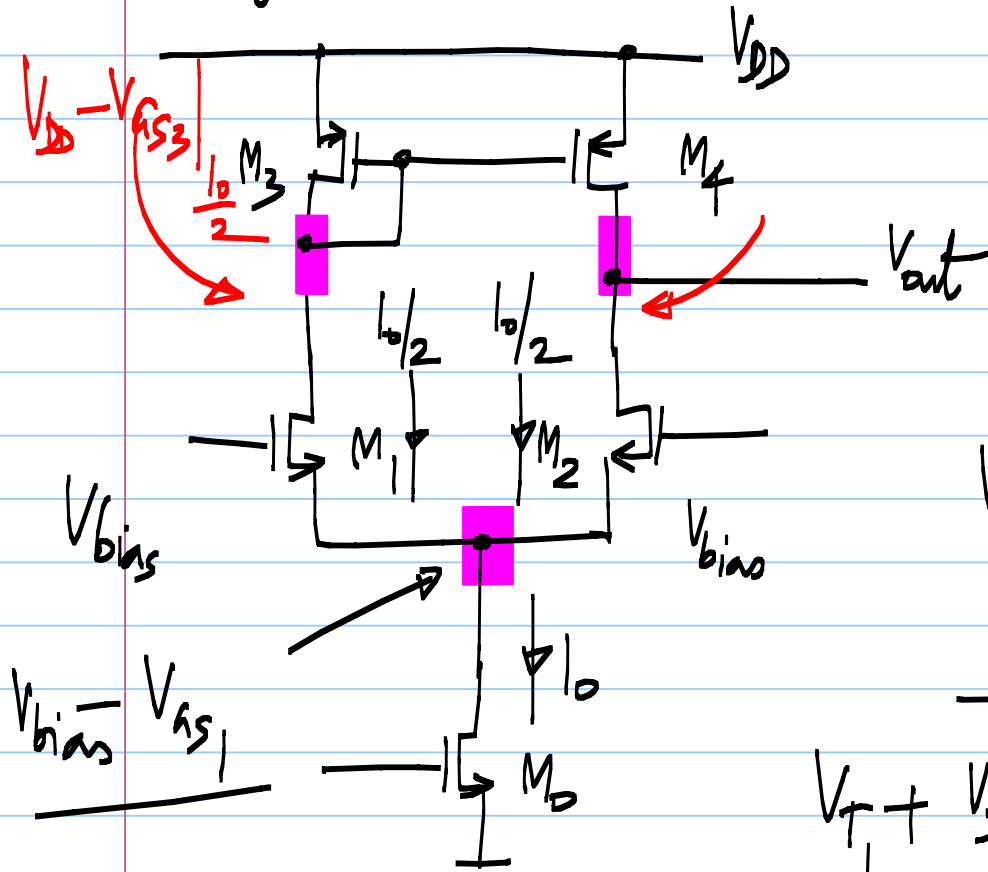

Find the limits on V_{out} & V_{bias}

Assume $V_d \approx 0$

$$V_{bias} - V_{T1} < V_{out} < V_{DD} - V_{DSAT4} \cdot \frac{l_0}{2}$$

$$V_{T1} + V_{DSAT1} + V_{DSAT0} < V_{bias} < V_{DD} - V_{T3} - V_{DSAT3} + V_{T1}$$

output range:

$$V_{bias} - V_{T1} < V_{out} < V_{DD} - V_{DSAT3} \Big|_{10/2}$$

Input common mode range:

$$V_{T1} + V_{DSAT1} \Big|_{10/2} + V_{DSAT6} \Big|_0 < V_{bias} < V_{DD} - V_{T3} - V_{DSAT3} \Big|_{10/2} + V_{T1}$$

