
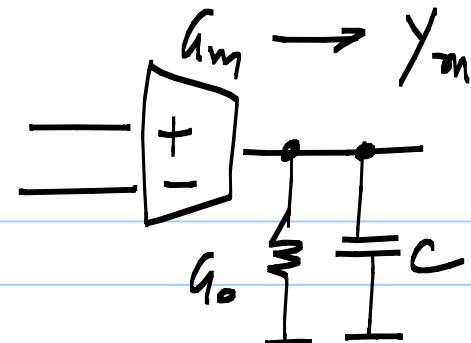


Lecture 32

Single stage opamp.

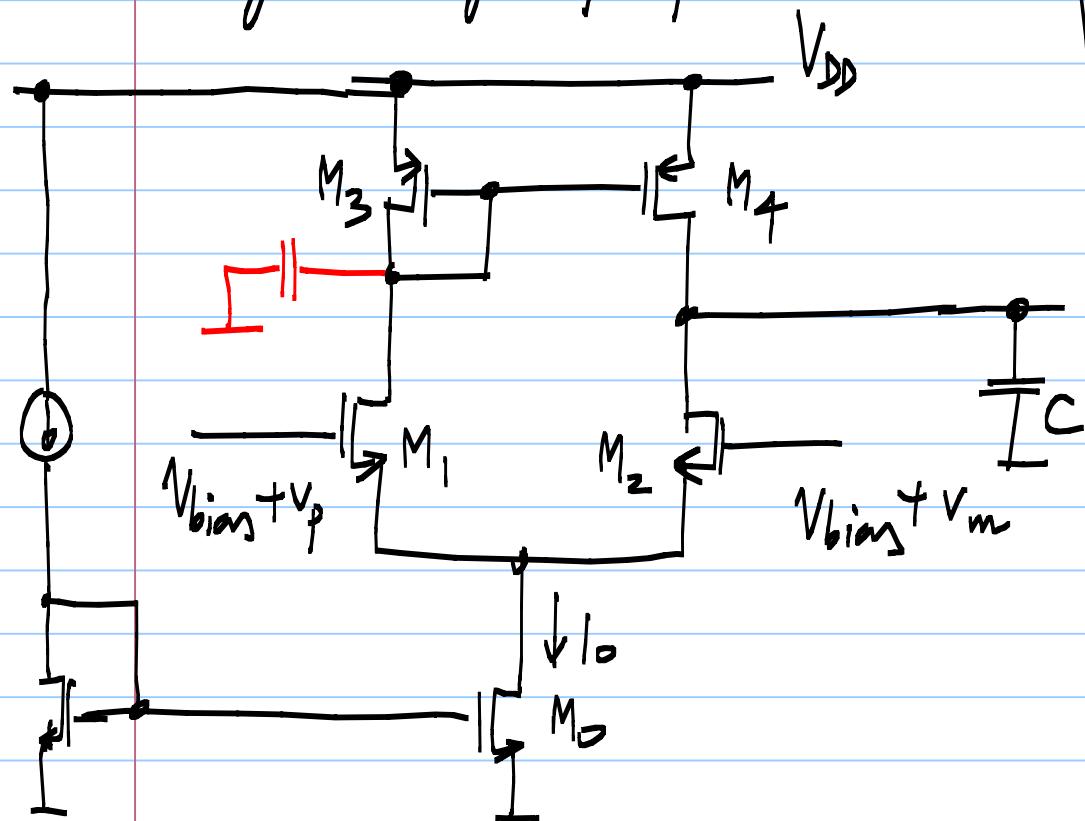

$$A_o = g_{m_1} / (g_{d_{s_1}} + g_{d_{s_3}})$$

$$Z_i = 2g_{m_3} / C_{d_3}$$

$$P_2 = g_{m_3} / C_{d_3}$$

$$\sigma_{v_{os}}^2 = \sigma_{v_{T_{12}}}^2 + \sigma_{v_{T_{34}}}^2 \cdot \left(\frac{g_{m_3}}{g_{m_1}} \right)^2$$

$$S_{v_{in}} = \frac{16}{3} \frac{kT}{g_{m_1}} \left(1 + \frac{g_{m_3}}{g_{m_1}} \right)$$

$$V_{in} - V_{T_1} < V_{out} < V_{DD} - V_{DSAT_3}$$


$$V_{DSAT_0} + V_{DSAT_1} + V_{T_1} < V_{bias} < V_{DD} - V_{T_3} + V_{T_1} - V_{DSAT_3}$$

$$SR_+ = \frac{I_o}{C} ; SR_- = \frac{I_o}{C}$$

To increase SR_+ , increase I_o (& reduce $\frac{W_1}{L_1}$ so that g_m doesn't change)


$$V_{DSAT_1} \uparrow \quad g_m = \frac{2I_o}{V_{DSAT_1}}$$

Opamp with dual supply & single supply


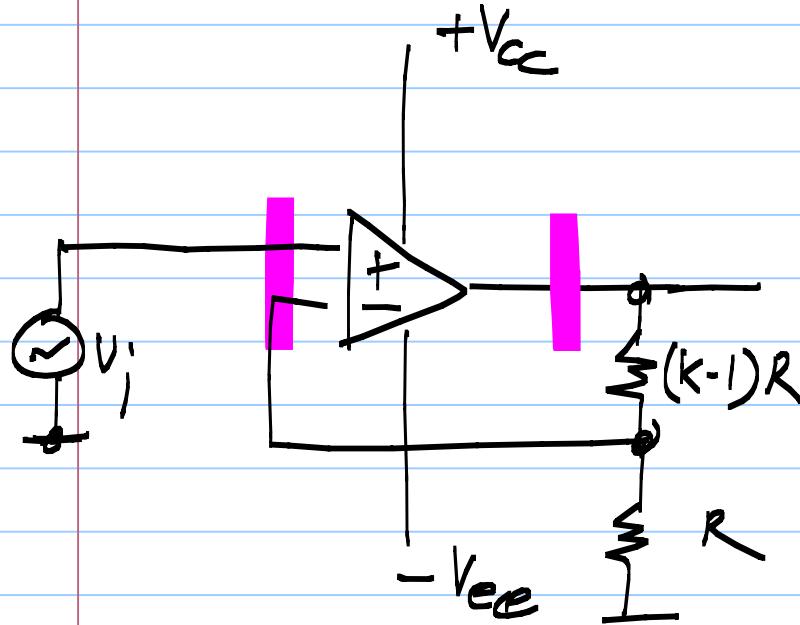


Dual supplies


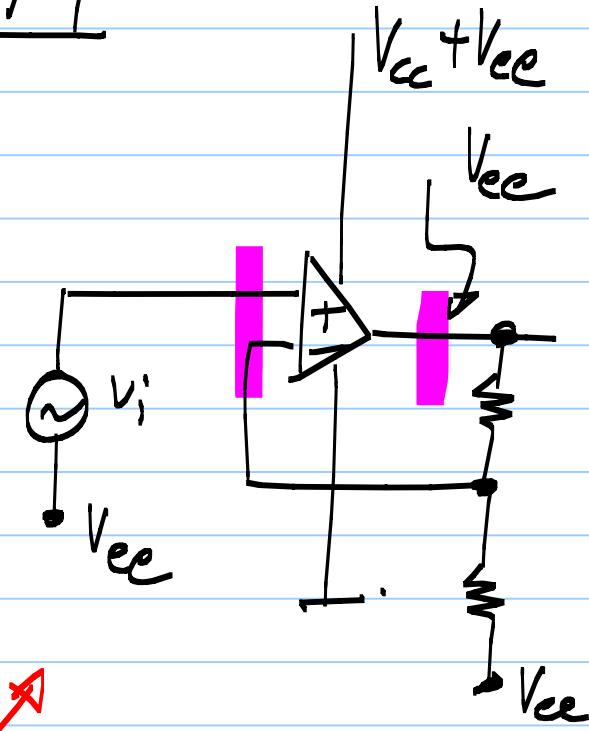
all the
voltages
in the
circuit -
 $+V_{ee}$




Single supply

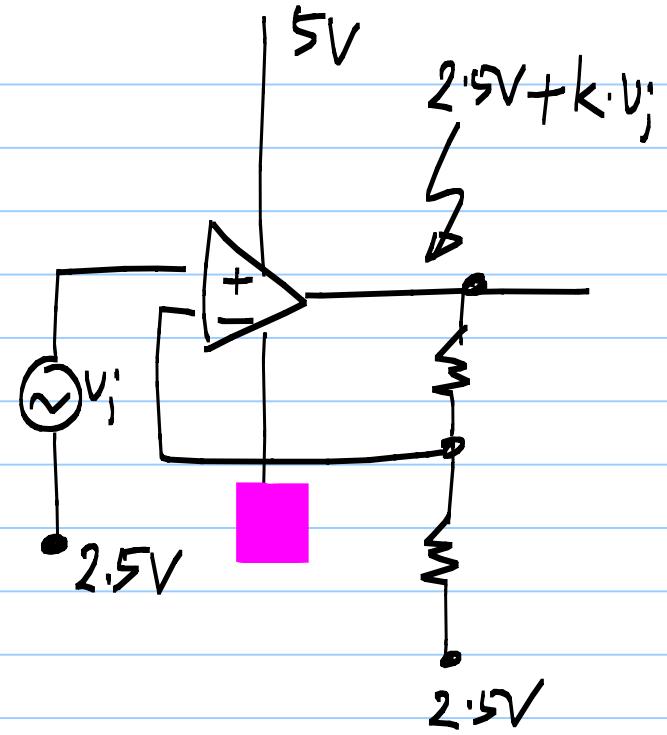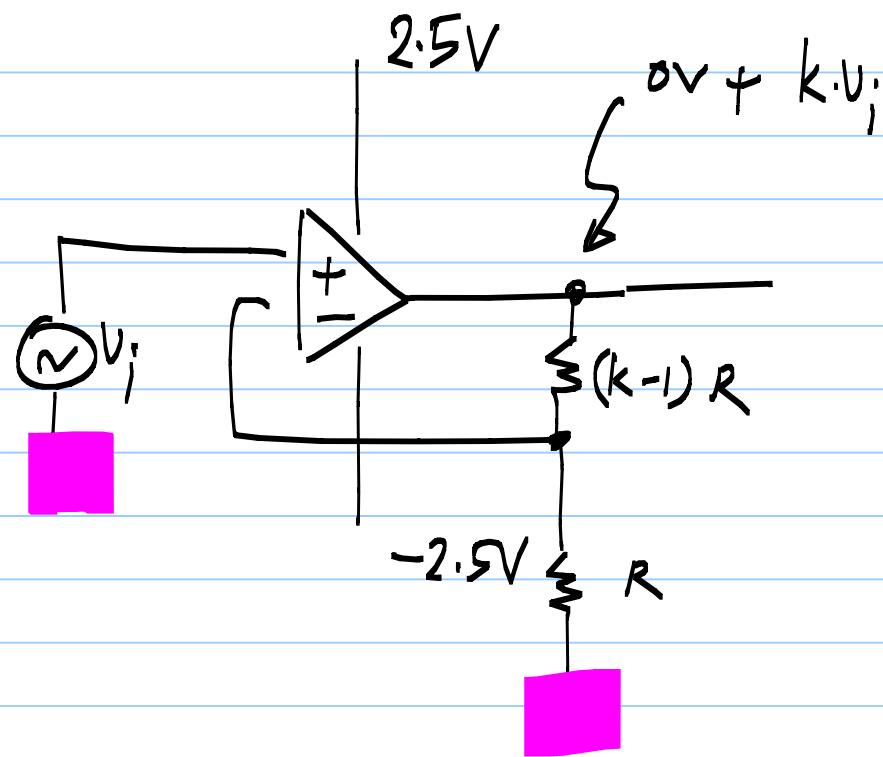

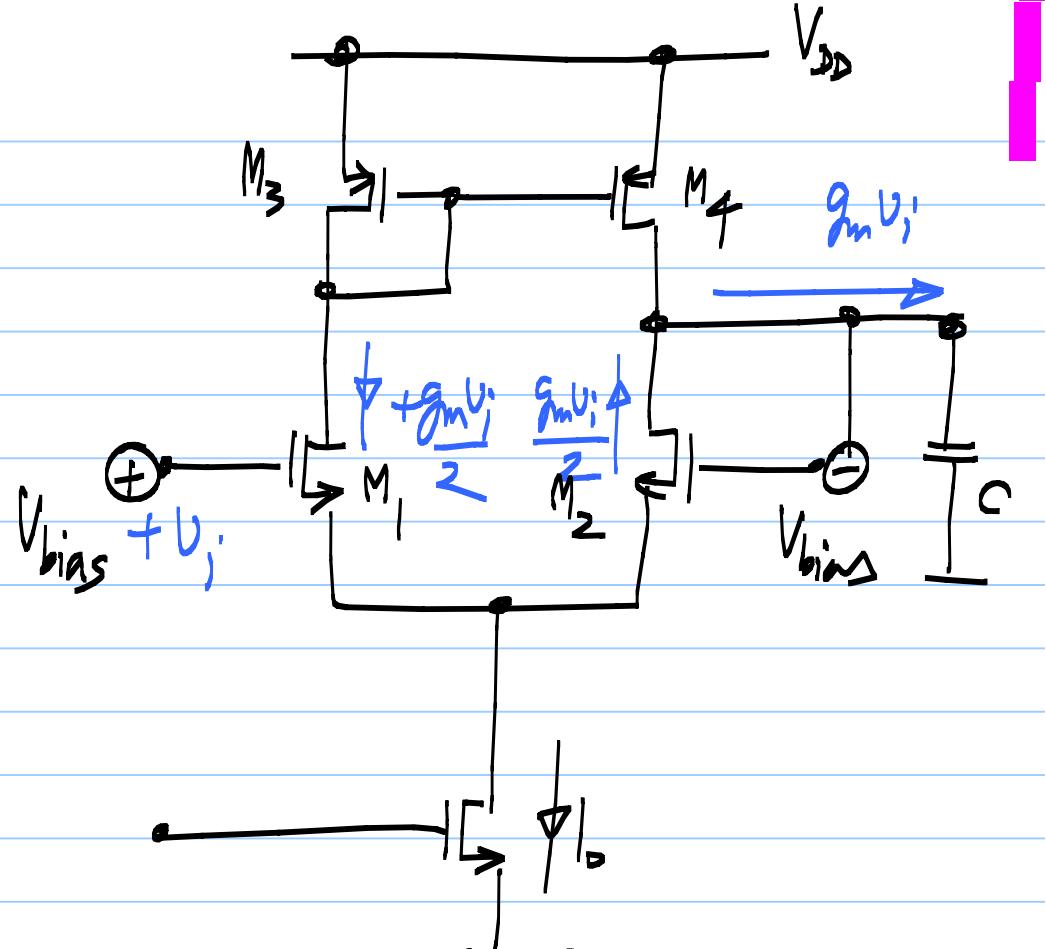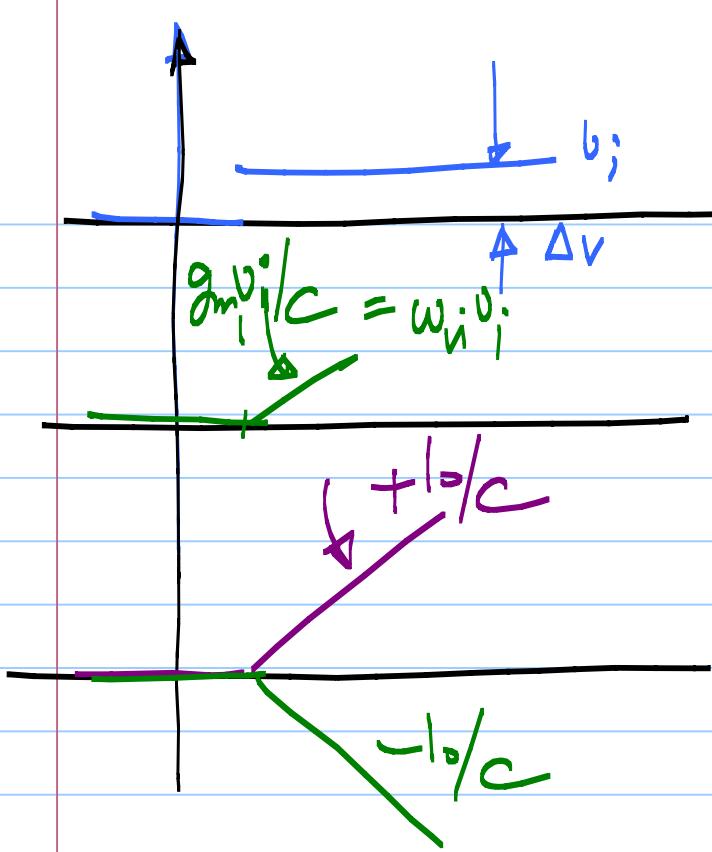- * Opamps can be operated from single or dual supplies \leftrightarrow just a voltage shift
- * Input common mode voltage & the output voltage within the respective limits.



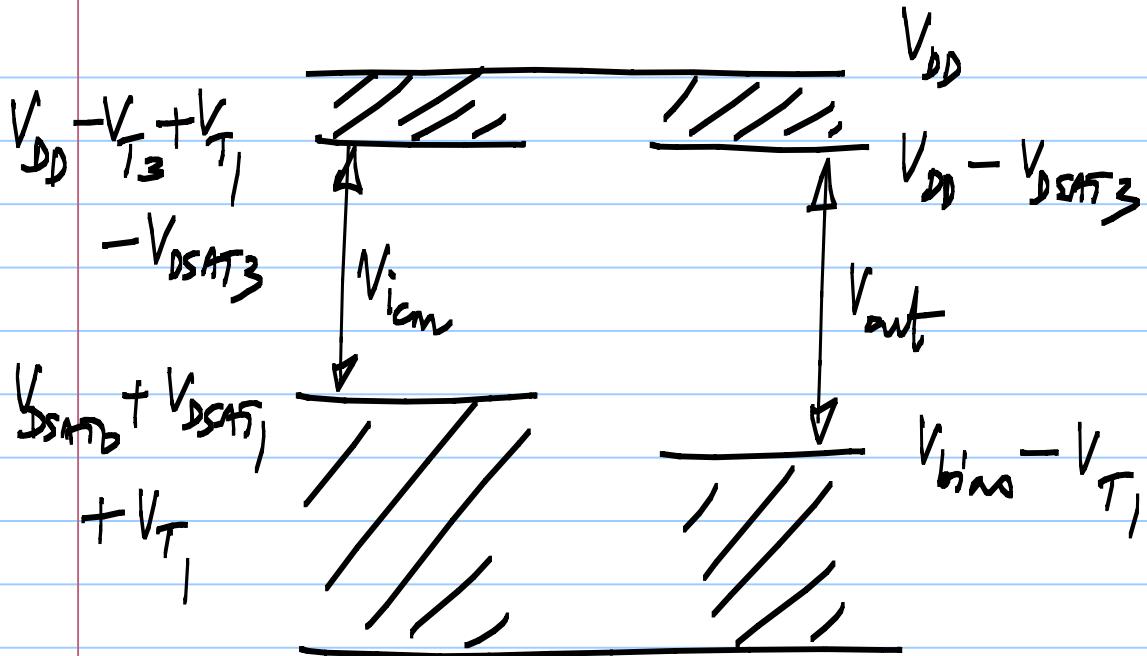Voltage follower using
the single stage opamp -



$$V_{i_{em}, \min} < V_{bias} + V_i < V_{i_{em}, \max}$$

$$V_{b, \min} < V_{bias} + V_i < V_{b, \max}$$

V_{bias} for maximum
signal swing
(V_i)

$$V_{DD} = 5V ; V_1 = V_{T3} = V_{T0} = 0.7V$$

$$V_{DSAT0,1,2,3,4} = 0.2V$$

[signal swing

Offset :

$$\sigma_{V_{DS}}^2 = \sigma_{V_{T12}}^2 + \sigma_{V_{T34}}^2 \cdot \left(\frac{g_{m_3}}{g_{m_1}} \right)^2$$

* $\frac{g_{m_3}}{g_{m_1}}$ mismatch contribution reduced by reducing
 \rightarrow increase V_{DSAT3} $g_{m_3} = \frac{2l_0/2}{V_{DSAT3}}$

* Increase the size of all transistors :

To reduce the offset by 2x Area \uparrow 4x

$C_{GS}, C_{DL} \dots \uparrow$

Noise :

$$S_{V_{in}} = \frac{16}{3} \frac{kT}{g_{m_1}} \left(1 + \frac{g_{m_3}}{g_{m_1}} \right)$$

* M_{34} contribution reduced by reducing g_{m_3}

$\Rightarrow V_{DSAT3} \uparrow \cdot \Rightarrow$ reduced swing

* Increase g_{m_1} , g_{m_3} (Noise scaling)

Increases power dissipation.

Offset, Noise reduction

Reduce the swing

Reduce the speed

Increase the power dissipation

$$A_o = \frac{g_{m1}}{g_{ds1} + g_{ds3}} = \frac{g_{m1}}{\frac{k_1 \cdot l_0}{L_1} + \frac{k'_1 \cdot l_0}{L_3}}$$

Increasing the dc gain:

Transconductance : g_m , o/p conductance: $g_{ds1} + g_{ds3}$

Reduce the o/p conductance:

Use a current buffer / common gate
amplifier

