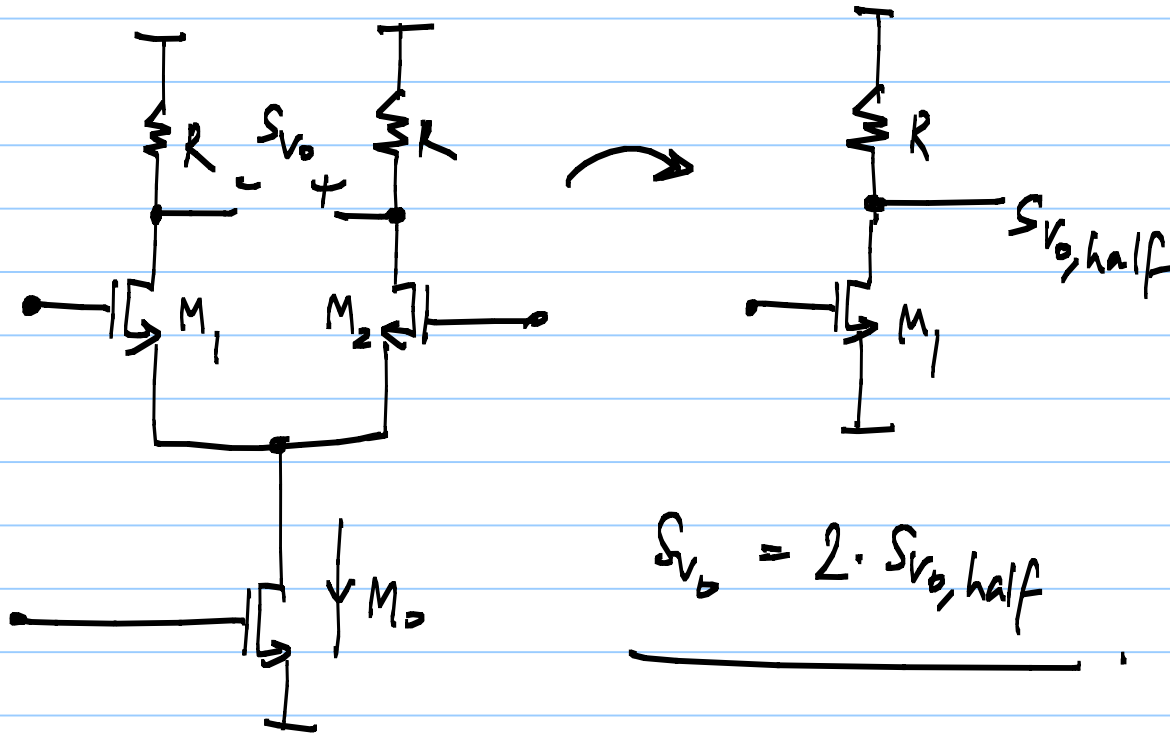



# Lecture 40

offset in fully differential circuits:



$$\Delta I_{D12} = \frac{I_0}{2} \cdot \Delta \beta$$


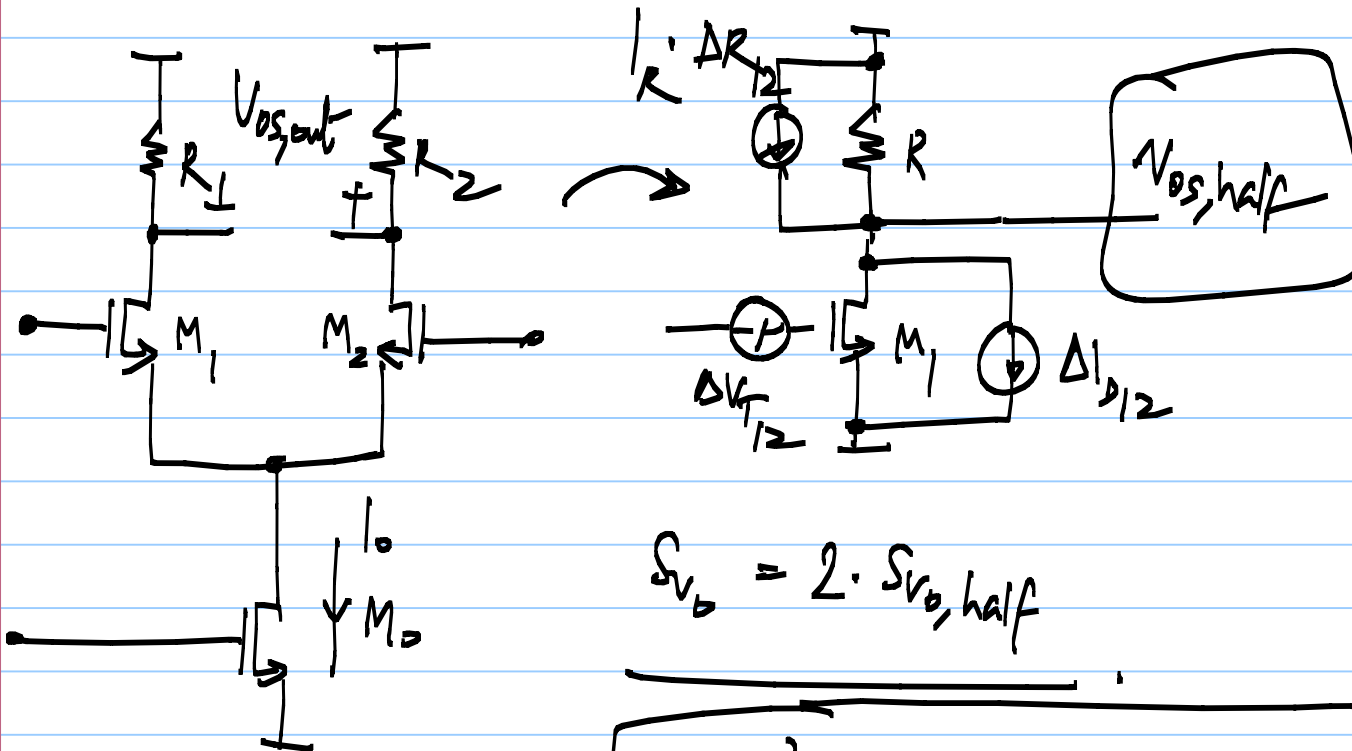
$$\frac{\Delta \beta}{\beta} ; \frac{\Delta R}{R}$$





$$S_{V_o} = 2 \cdot S_{V_o,half}$$


$$\sigma_{V_{os,out}}^2 = \sigma_{V_{os,half}}^2$$





# Single ended opamp.

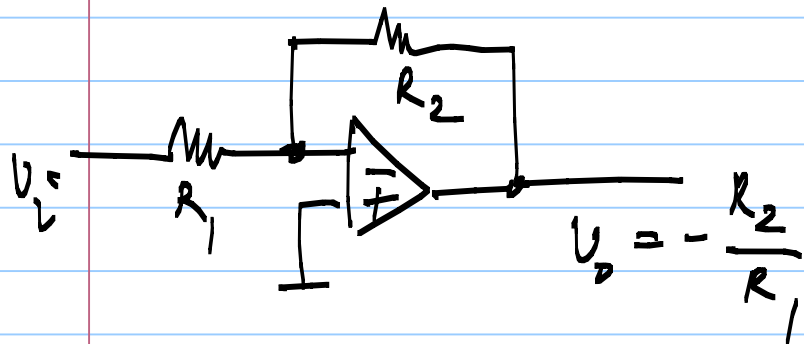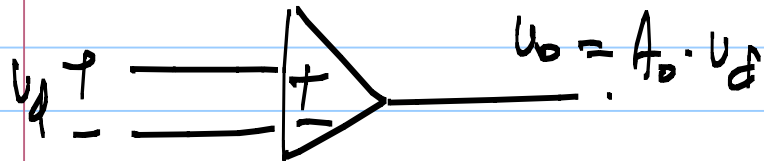

# Fully differential opamp

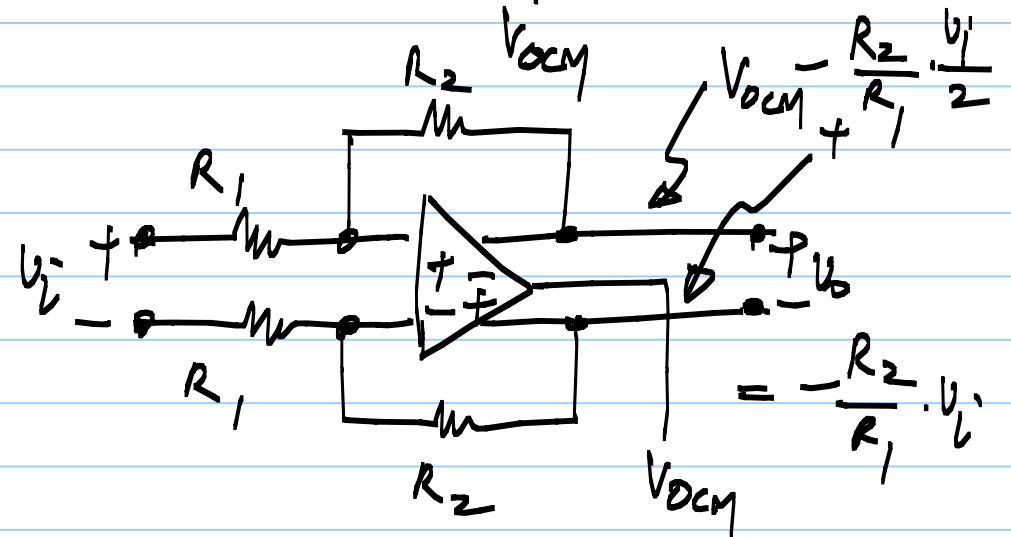
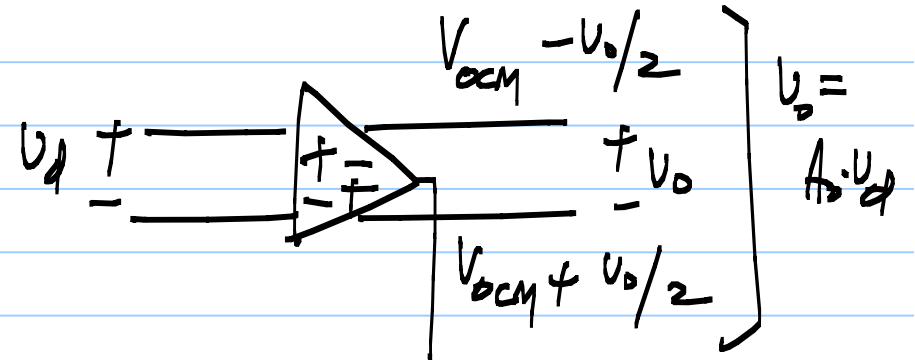


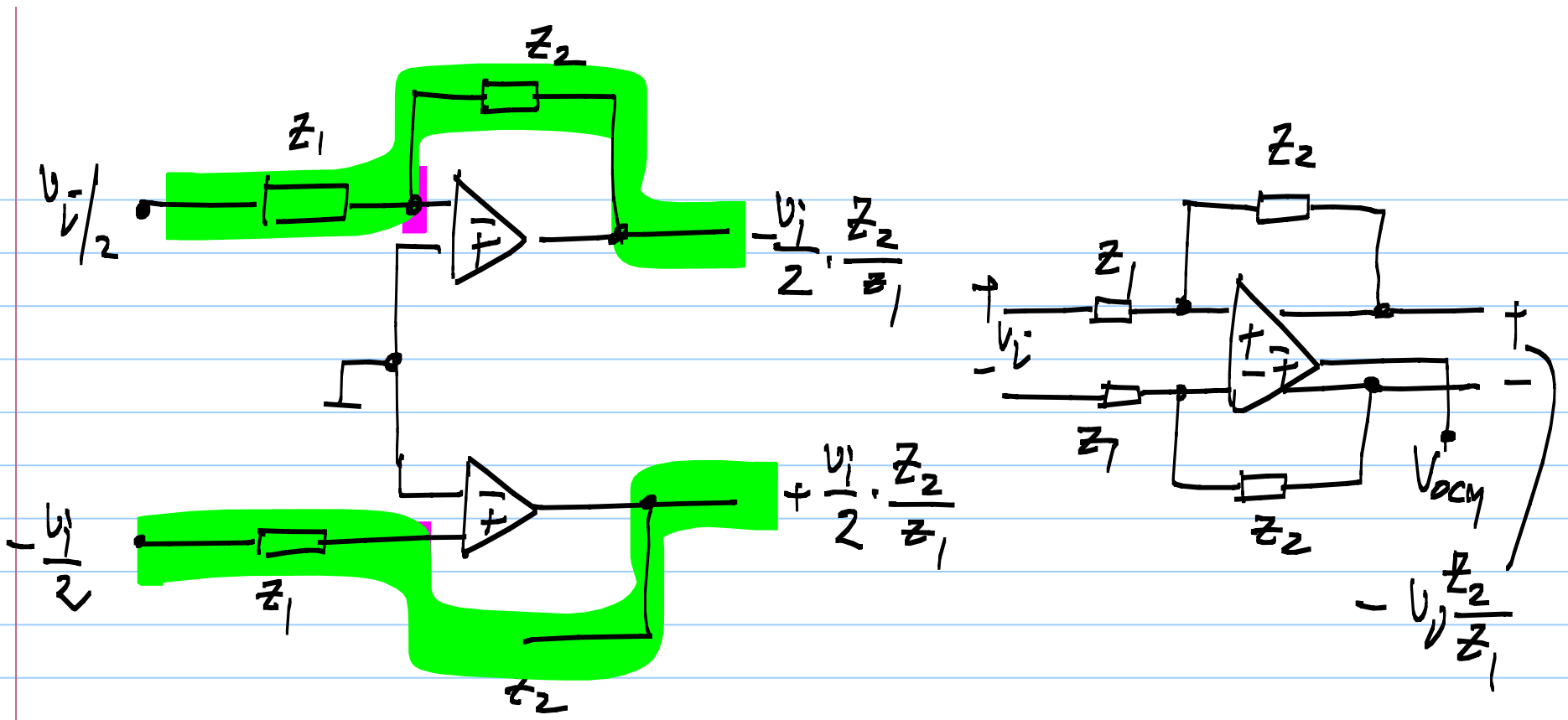


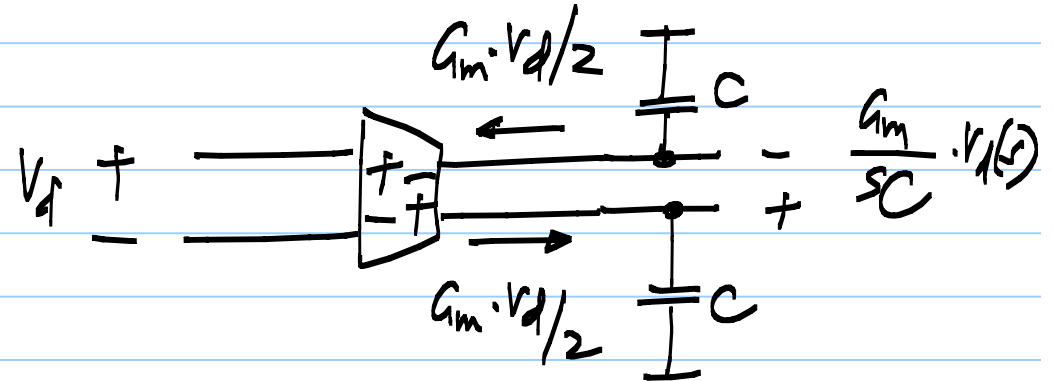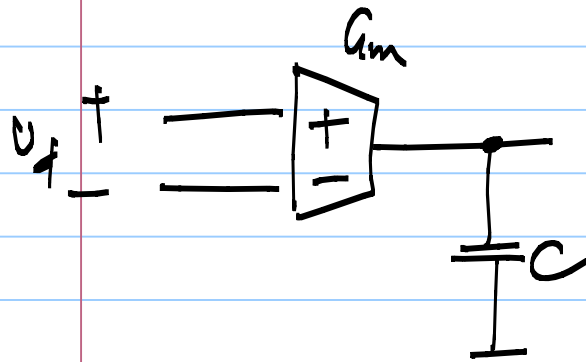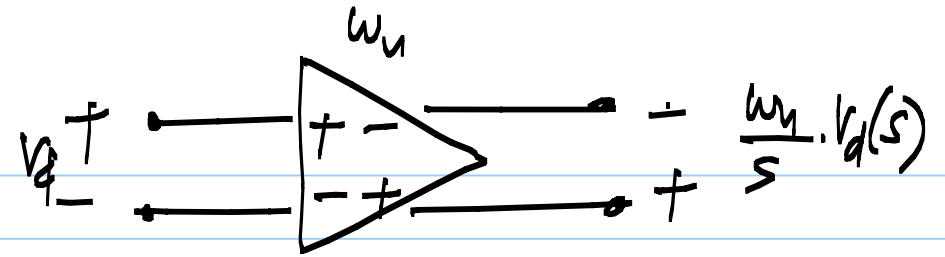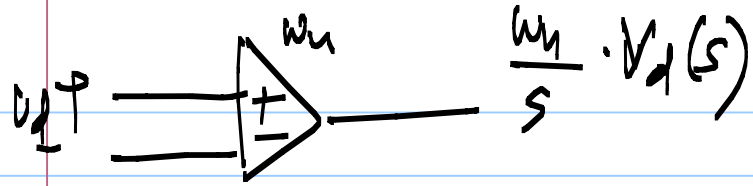


$$\omega_n = \frac{G_m}{C}$$

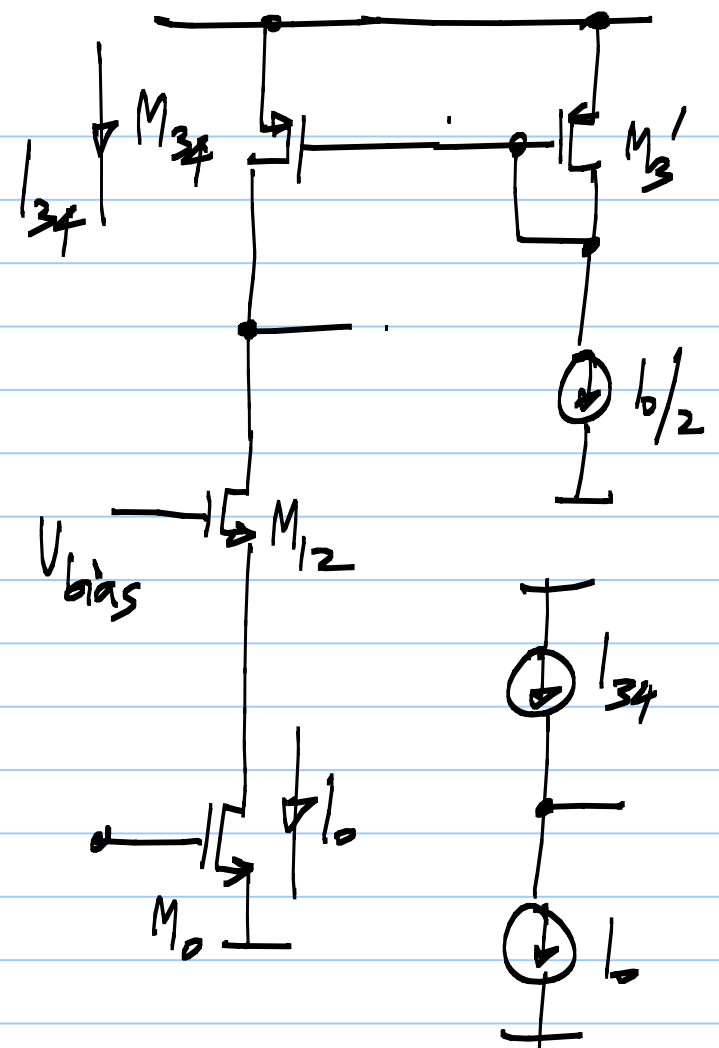
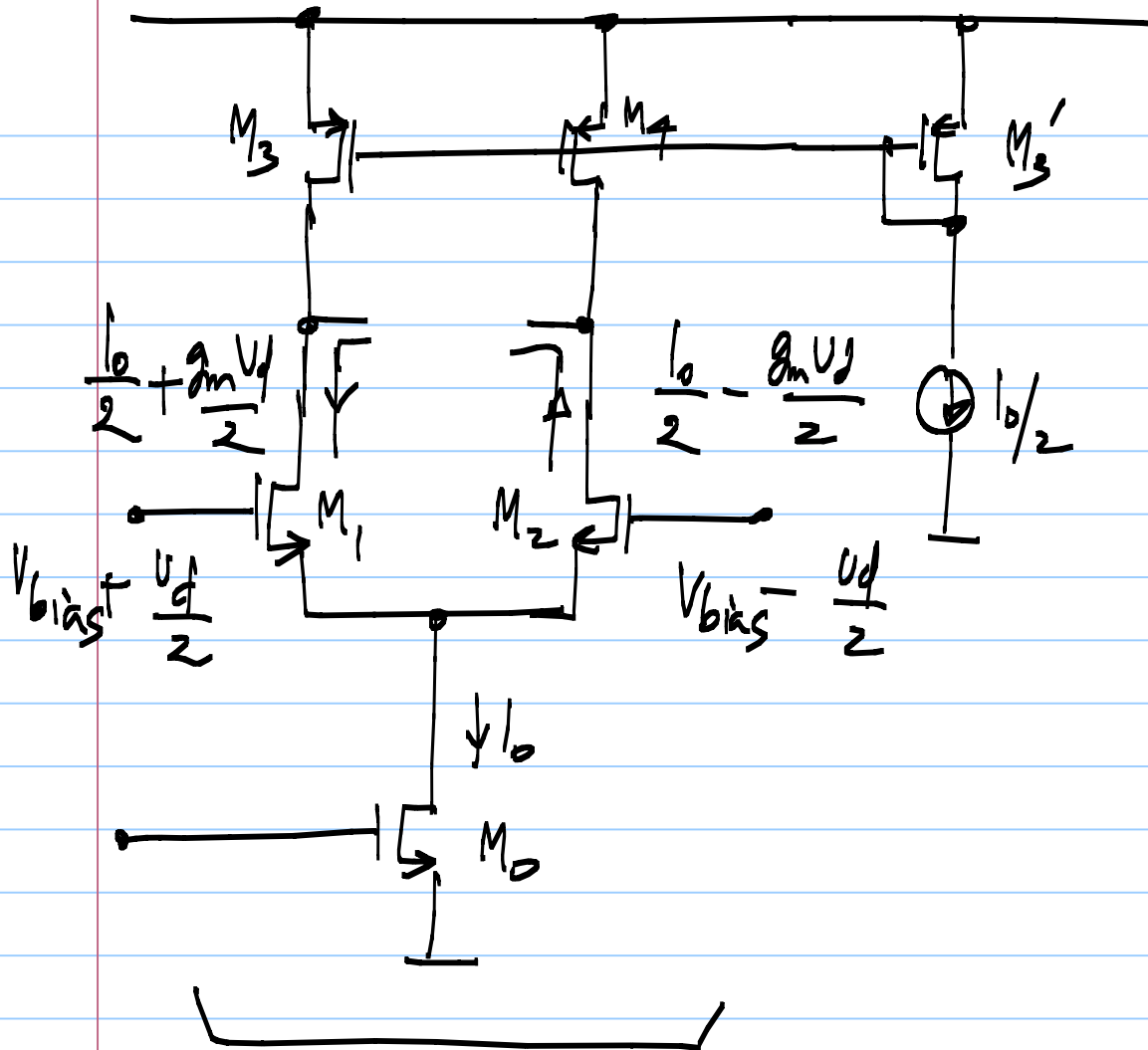
- Fully differential  $G_m$
- Two capacitors  $C$



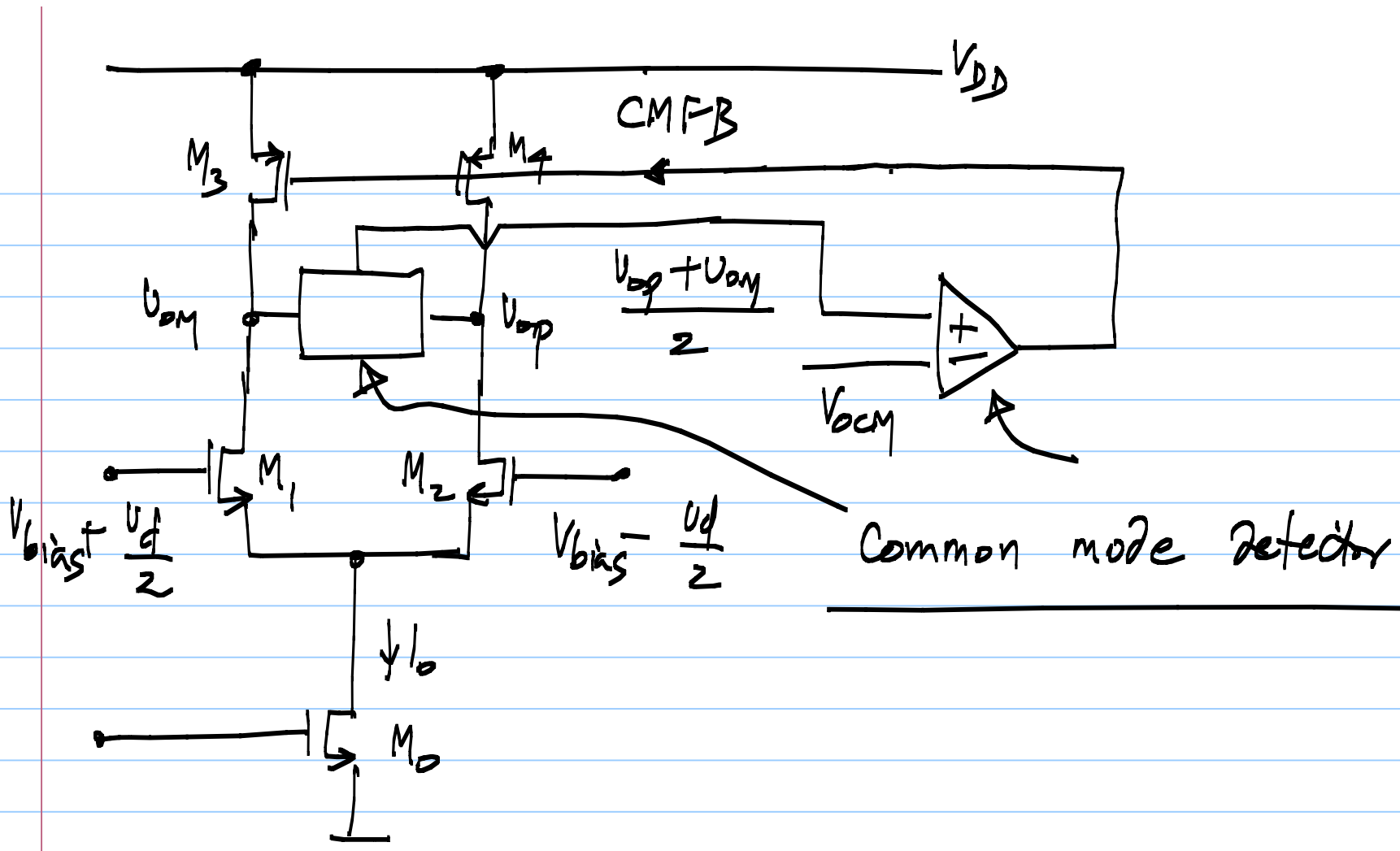

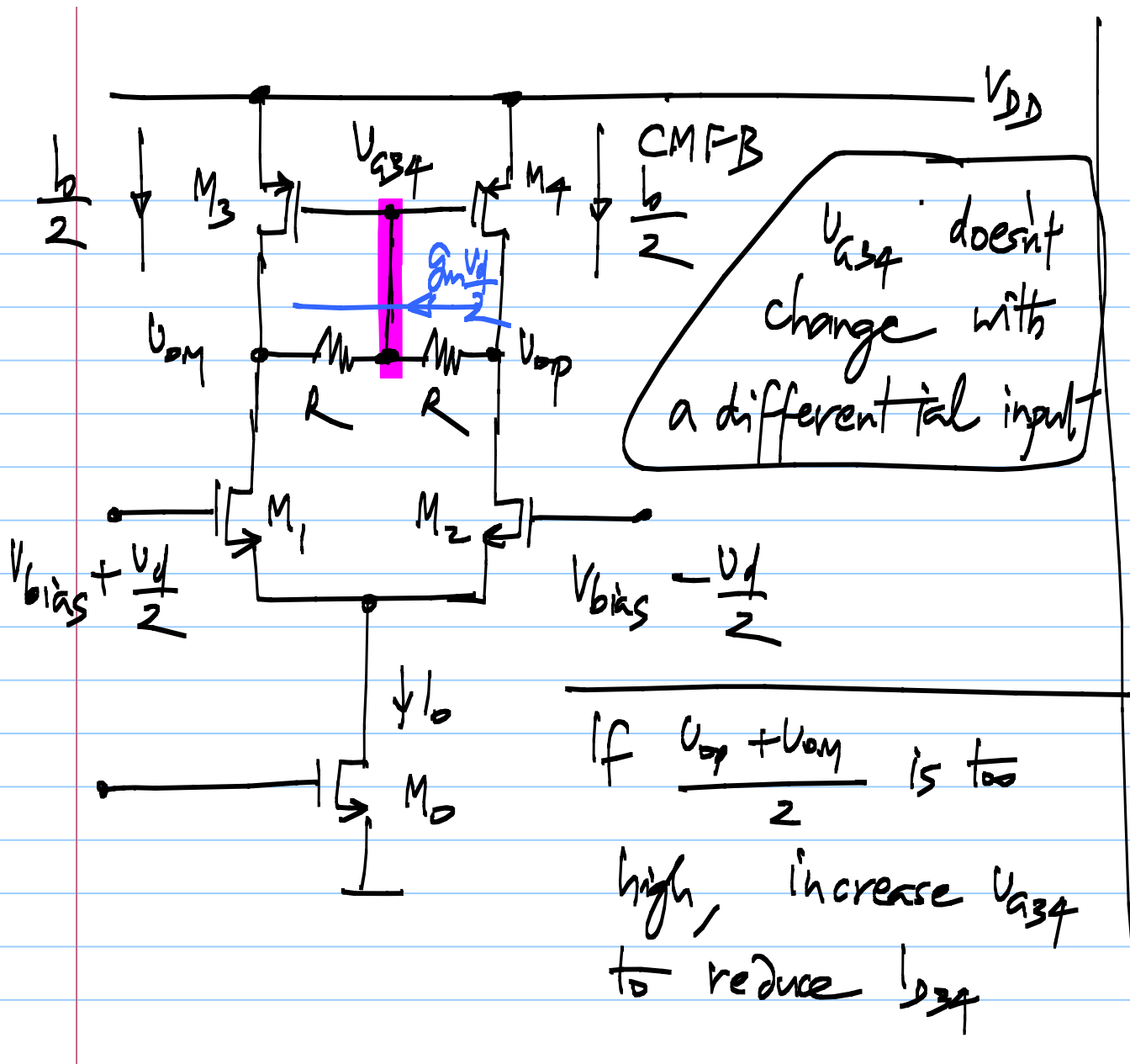

Common mode detector:

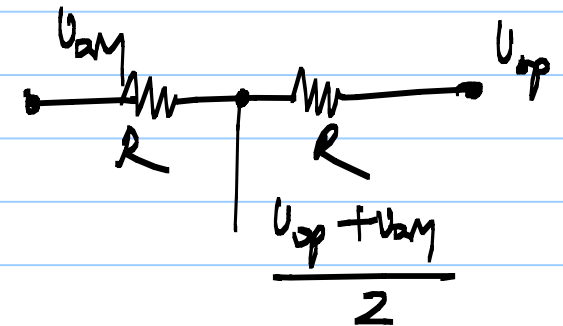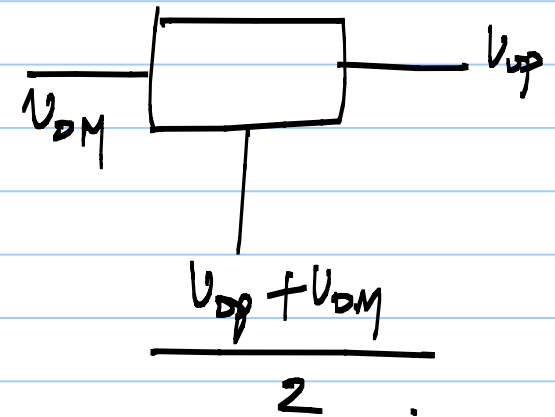



$$\text{Output CM voltage} = \frac{V_{DD} - V_{SG3}}{1/2} = V_{OCM}$$

$$\frac{V_{DD} - V_{TP} - \sqrt{\frac{2 \cdot I_D}{\mu_p C_{ox} W_3/L_3}}}{1}$$

