
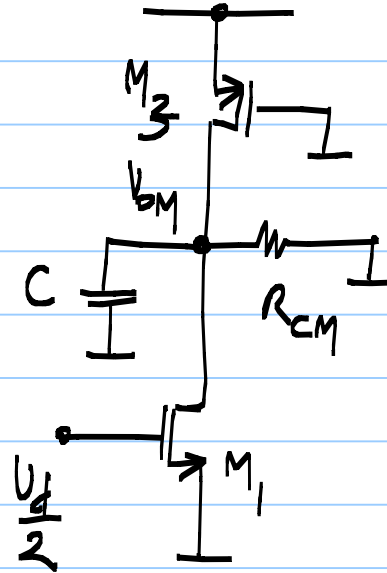


Lecture 42.

Diff. half ckt

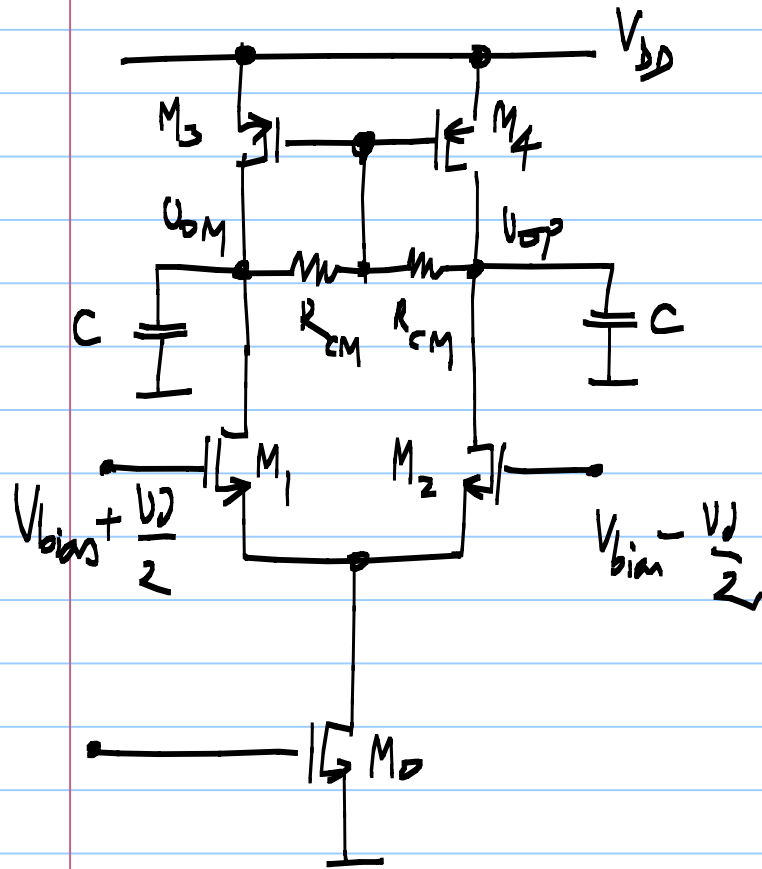

$$A_o = - \frac{g_{m1}}{g_{ds1} + g_{ds3} + g_{cm}}$$

$$\frac{U_{op} - U_{om}}{U_d} = \frac{g_{m1}}{g_{ds1} + g_{ds3} + g_{cm}}$$


$$\omega_u = \frac{g_{m1}}{C}$$

No mirror pole/zeros

$$S_{v_i} = \frac{16}{3} \frac{kT}{g_{m1}} \left(1 + \frac{g_{m3}}{g_{m1}} \right); \quad SR = \frac{I_o}{C};$$

Noise from R_{cm} neglected.
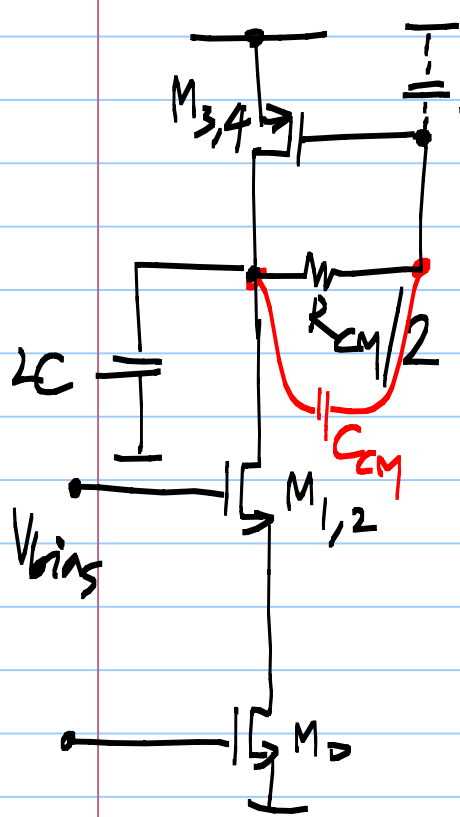
$$\sigma_{V_{OS}}^2 = \sigma_{V_{T1,2}}^2 + \sigma_{V_{T3,4}}^2 \cdot \left(\frac{g_{m3}}{g_{m1}}\right)^2 \quad \left\{ \begin{array}{l} \text{Neglecting} \\ R_{CM} \text{ mismatch} \end{array} \right\}$$





$$2C_{gs3} \quad \omega_{n,loop,cm} = \frac{2g_{m3}}{2C} = \frac{g_{m3}}{C}$$


$$P_{2,cm} = -\frac{1}{R_{cm} \cdot C_{gs3}} \quad |P_{2,cm}| \gg \omega_{n,loop,cm}$$

$$R_{cm}/2, \frac{1}{\omega C_{cm}} \Rightarrow \frac{1}{\omega C}$$

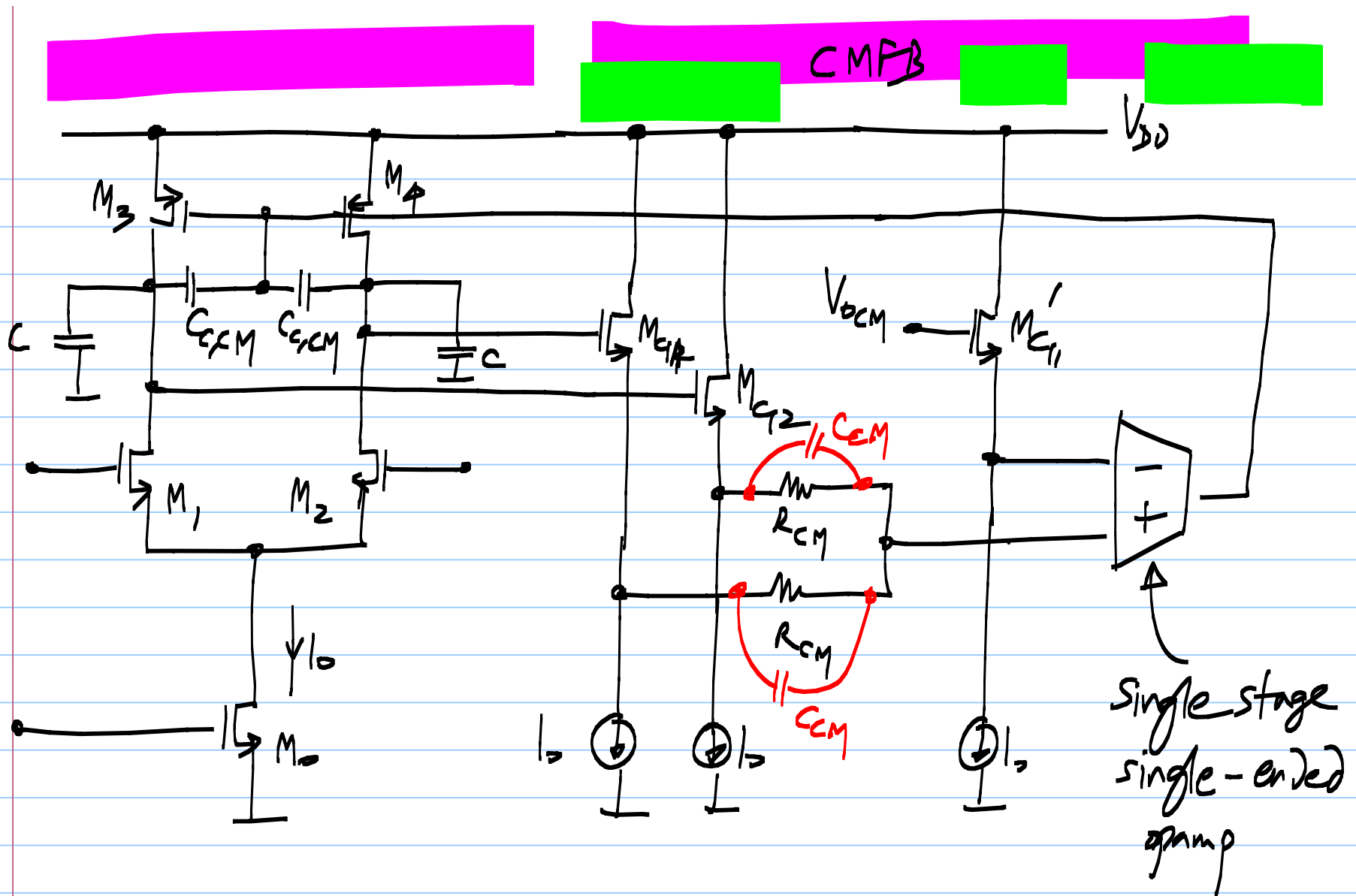
$$P_{2,cm} = -\frac{1}{R_{cm}(C_{gs3} + C_{cm}/2)}; \quad Z_1 = -\frac{1}{R_{cm}/2 \cdot C_{cm}}$$



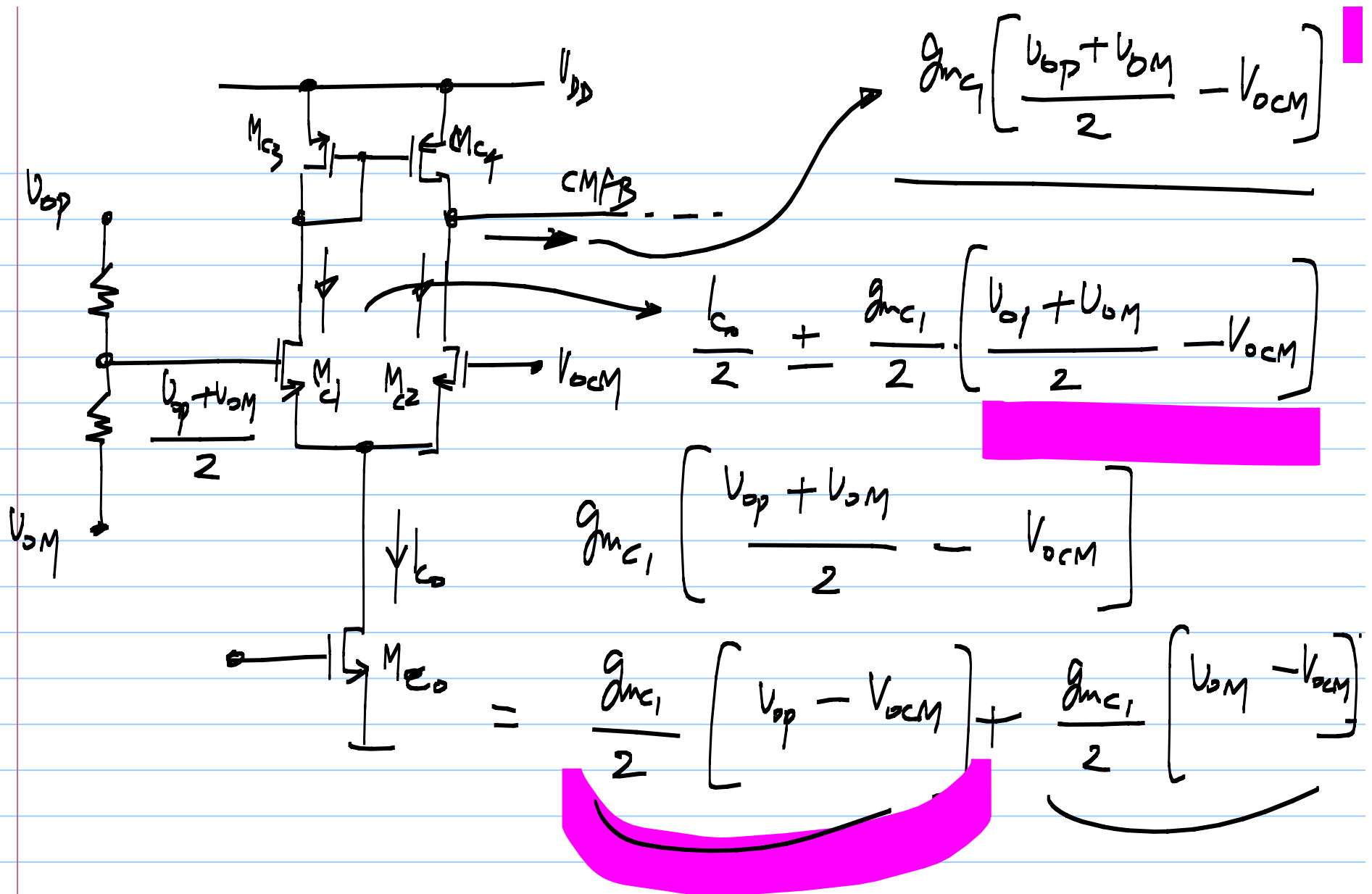


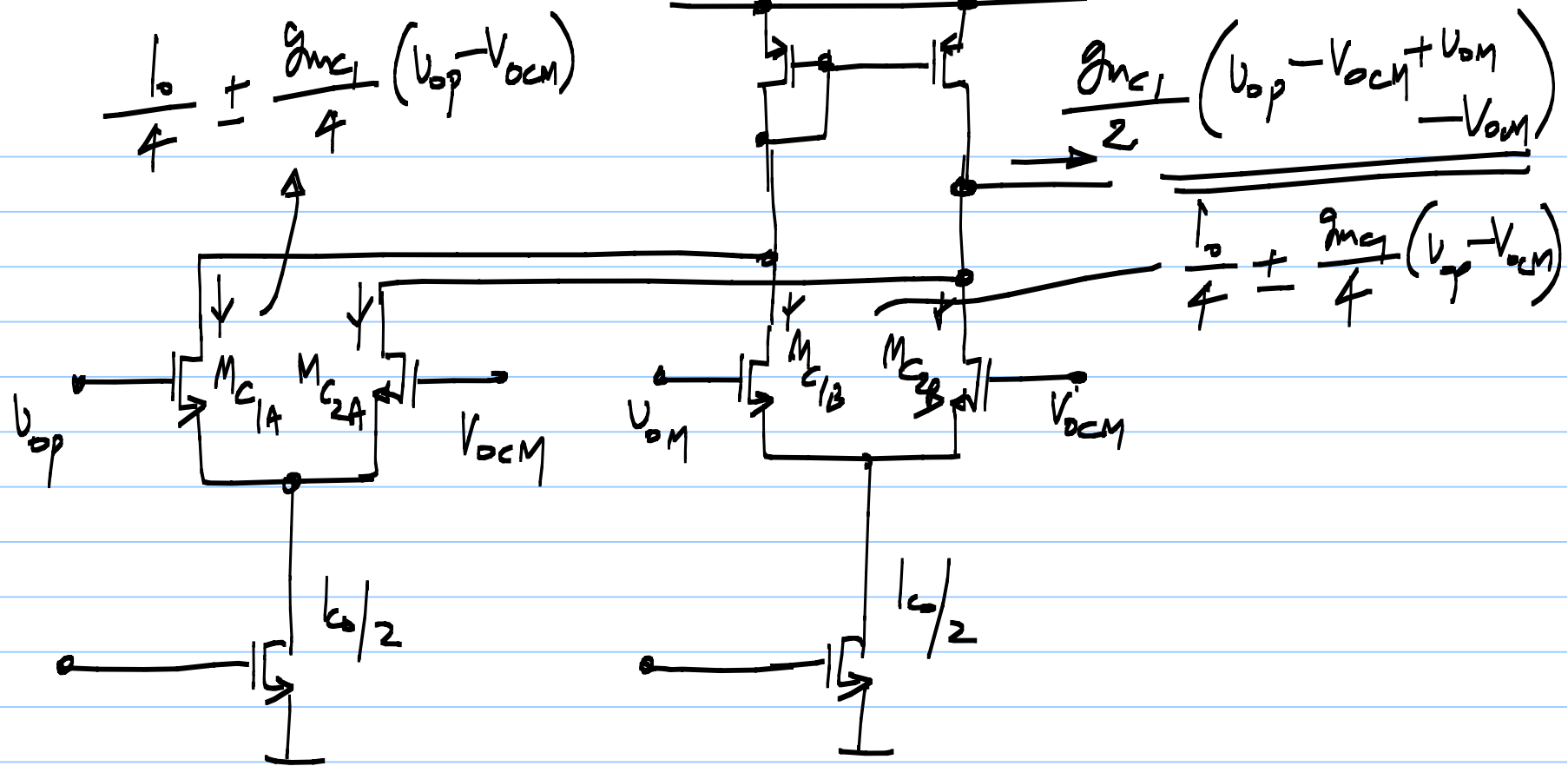

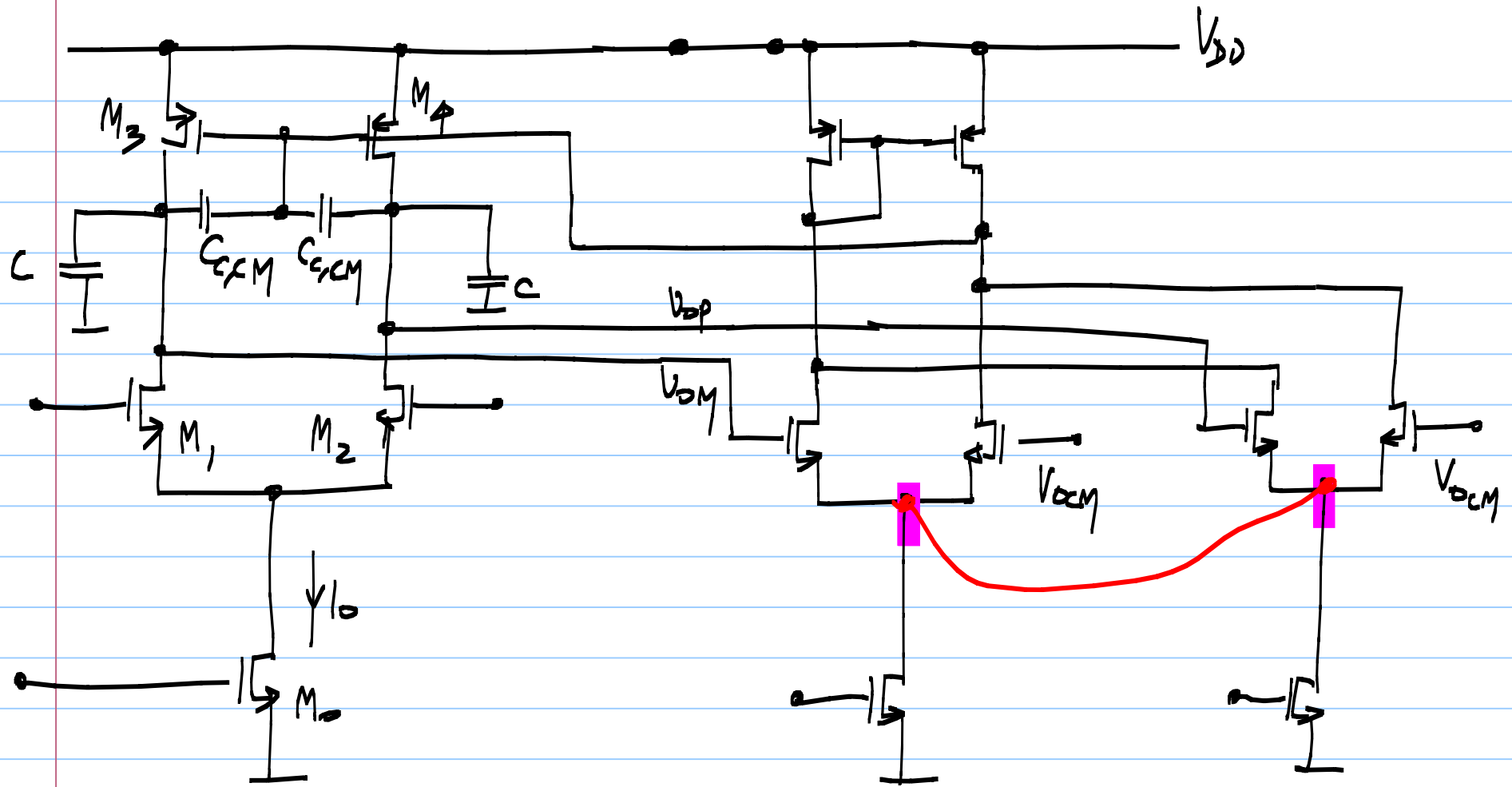
$$M_{C1A, 1B, 2A, 2B} = \frac{1}{2} M_{C1}$$




Fully differential two stage opamp.

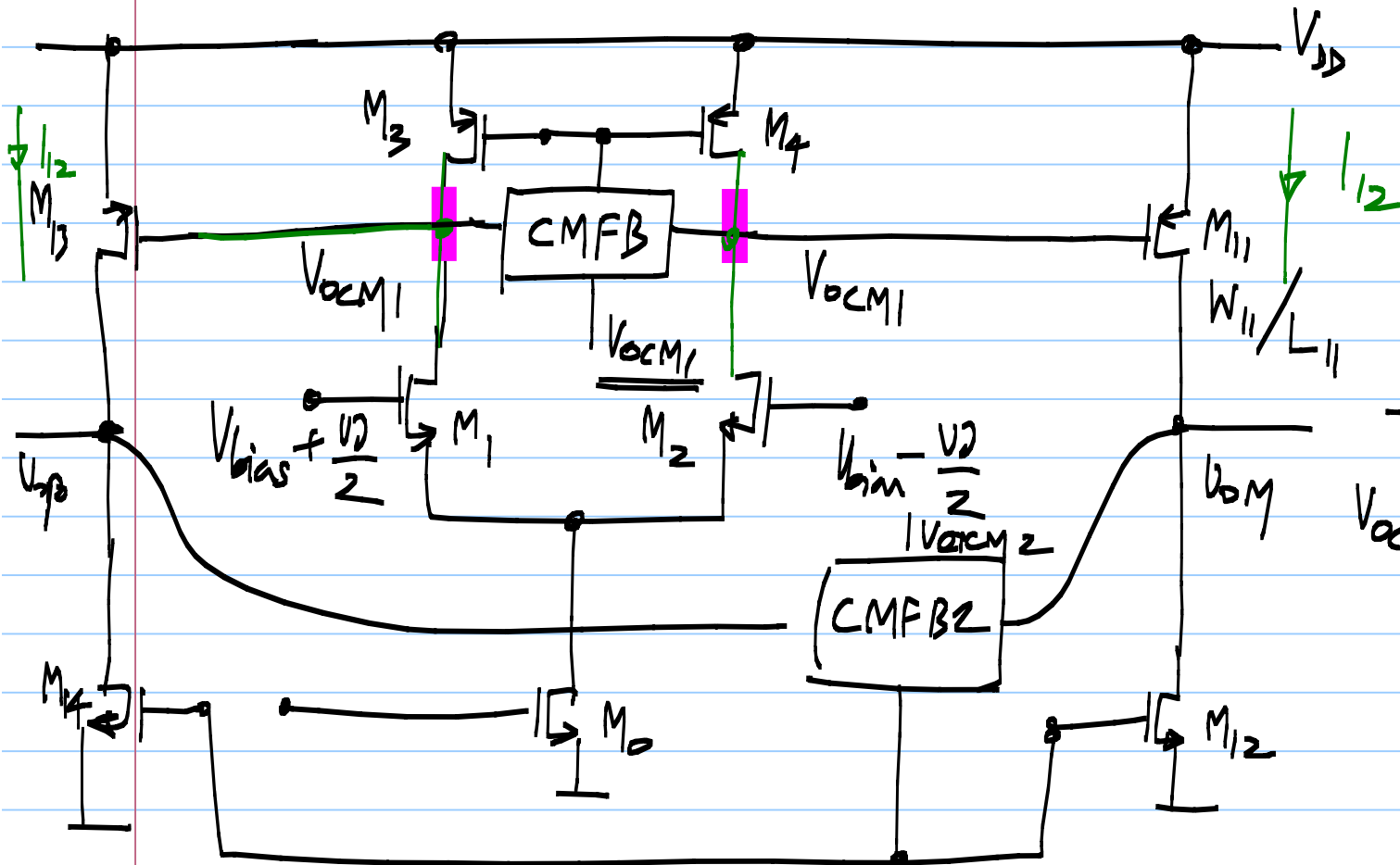

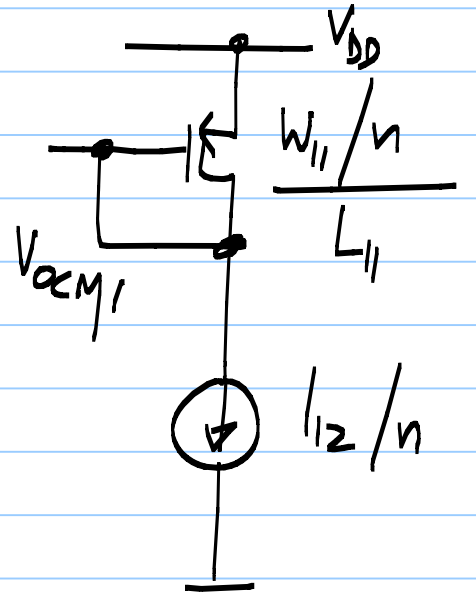
V_{ocM1} :
Desired quiescent current I_{12} flows in M_{11}




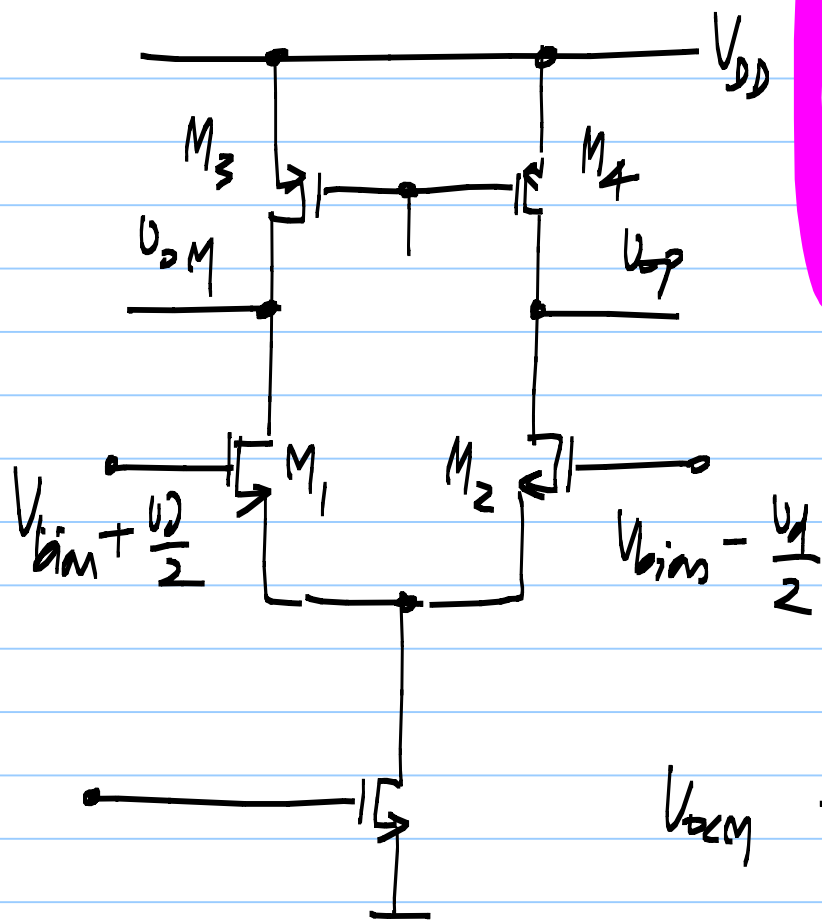


$$V_{bim} + V_{T1} < U_{op} < V_{DD} - V_{DSAT3}$$



V_{ocm} in the middle of this range

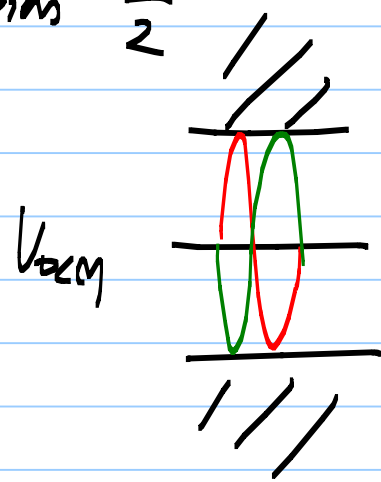

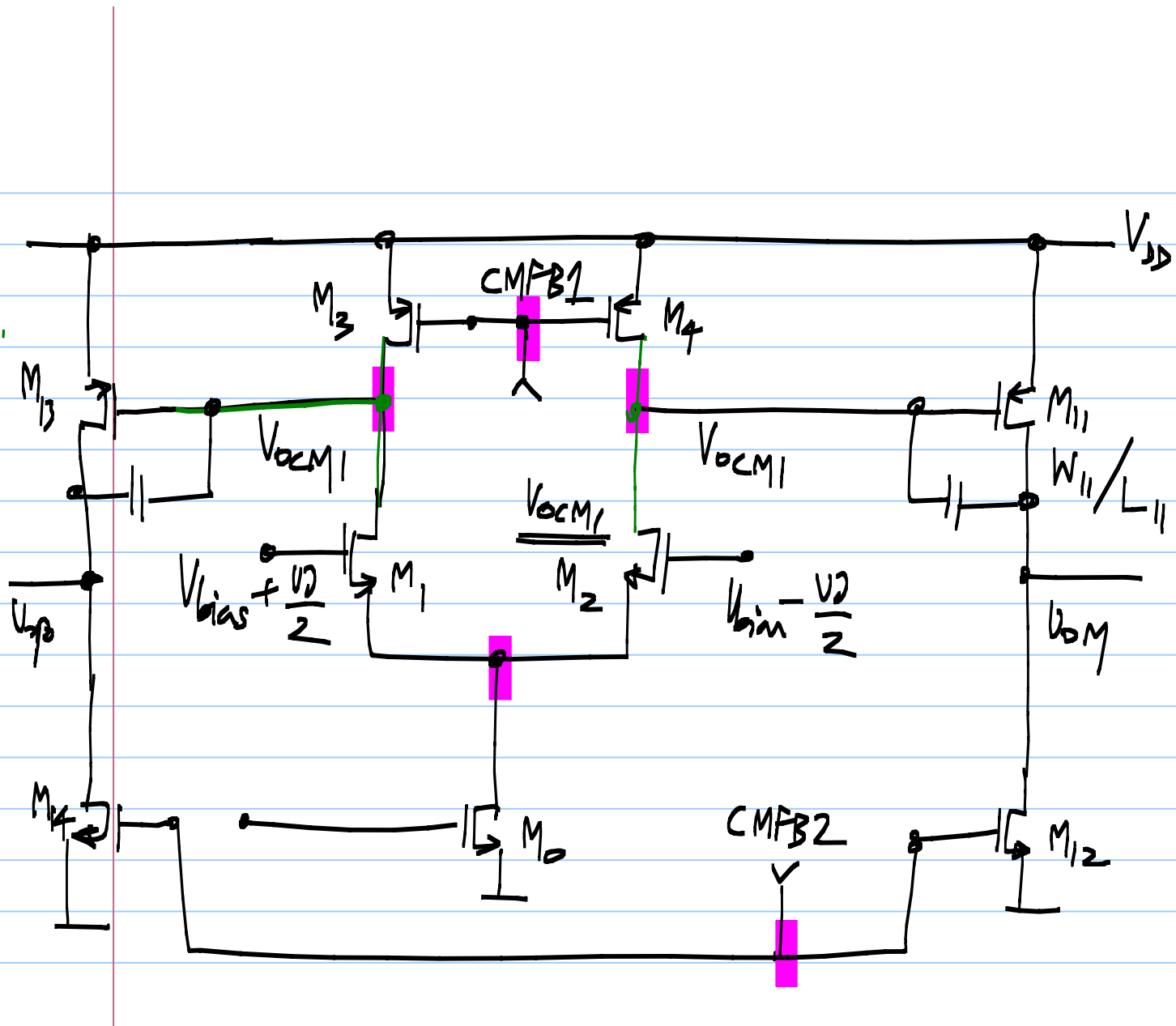

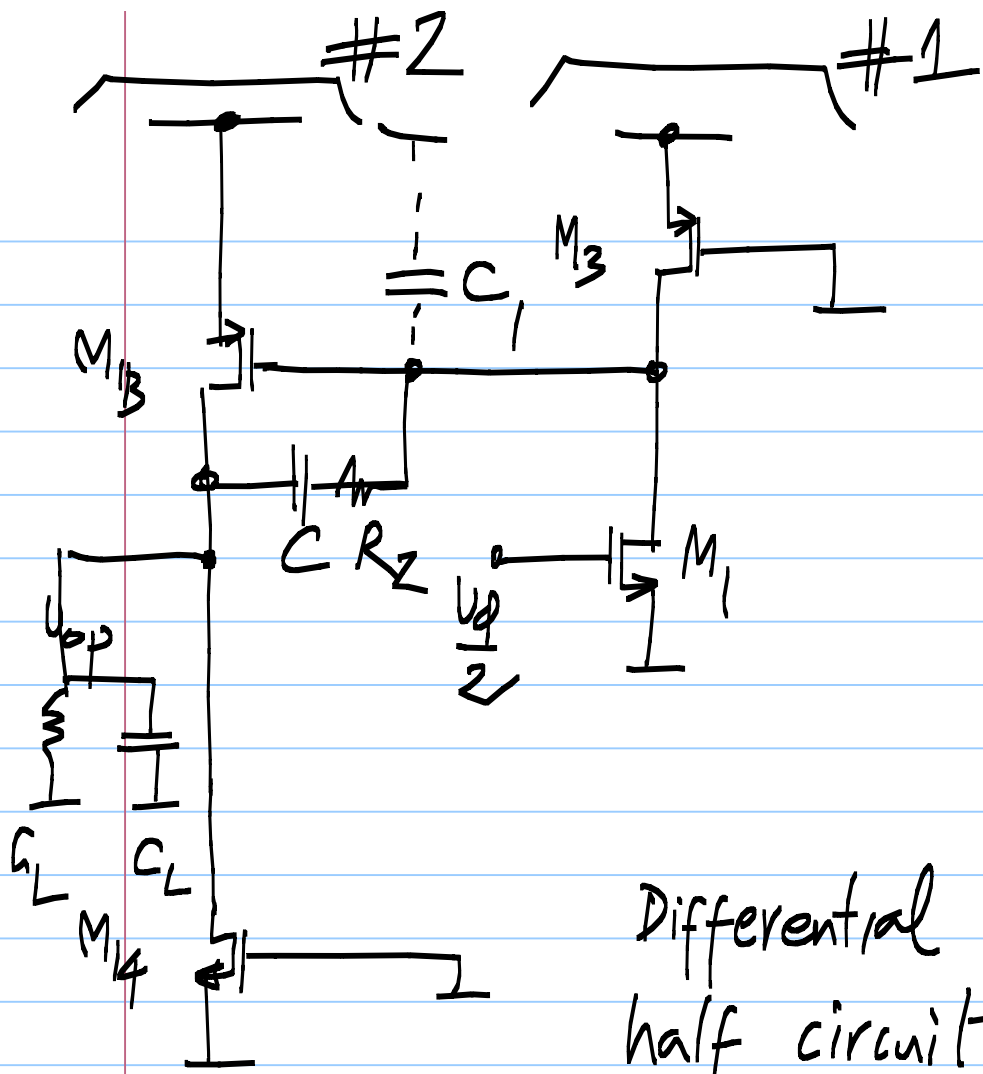

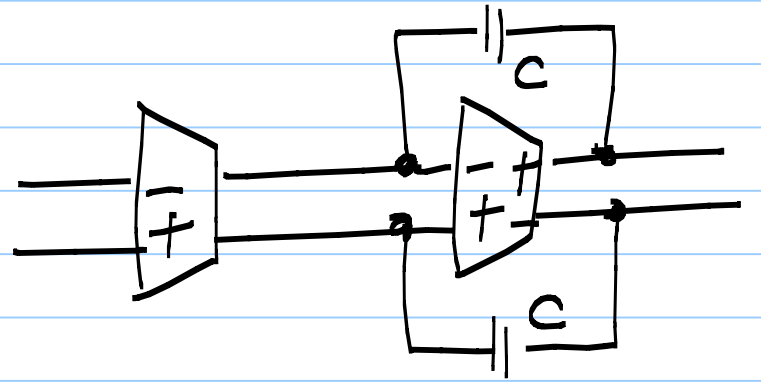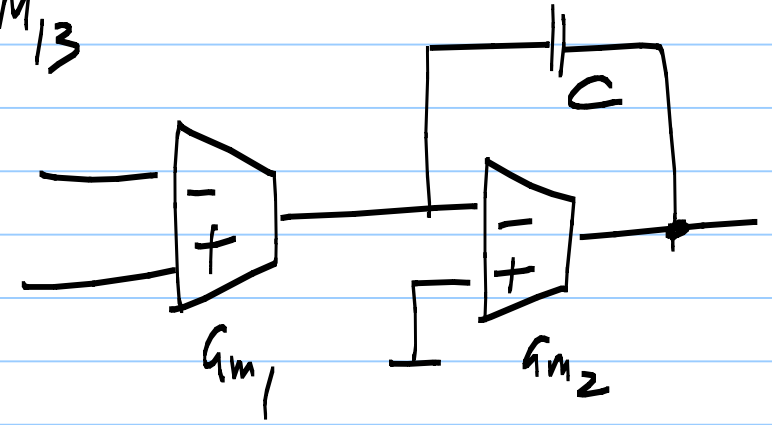CS amplifier M_1
 followed by CS amp.
 M_{13}



Differential
 half circuit

$$A_{DC} = \frac{g_{m1}}{g_{ds1} + g_{ds3}} \cdot \frac{g_{m13}}{g_{ds13} + g_{ds14} + g_L}$$

$$W_u = \frac{g_{m1}}{C}$$

$$P_2 = \frac{g_{m3} \cdot \frac{C}{C+C_1}}{\frac{C \cdot C_1}{C+C_1} + C_L}$$

$$Z_1 = \frac{g_{m13}}{C} \rightsquigarrow \text{cancelled using } R_2$$