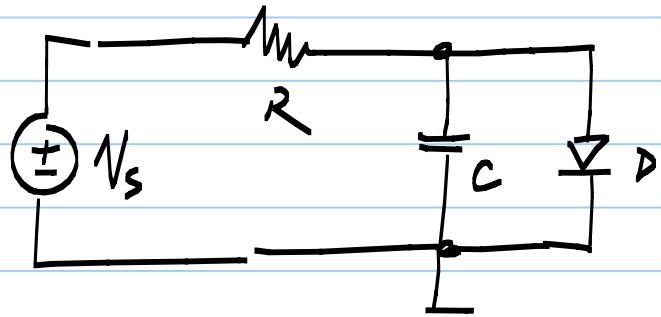


Lecture 44: Circuit simulators




dC_{Op} - op. point

ac - small signal
incr. analysis

transient - large signal
+
time-varying signals.

- ✓ * DC operating point
- ✓ * Small signal incremental analysis
- ✗ * Large signal analysis with time-varying inputs

Need a simulator

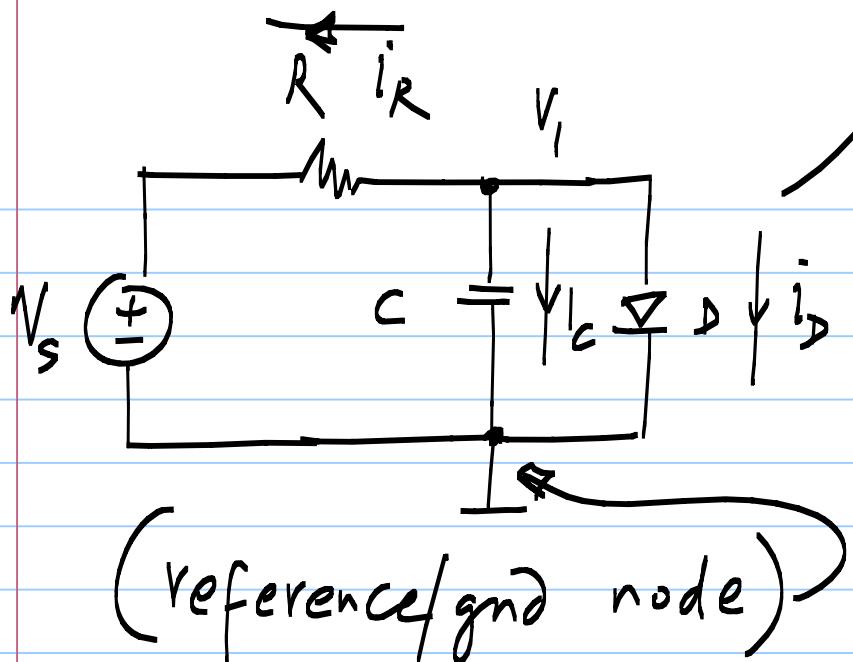

Schematic / netlist

Simulator set up


Modified nodal analysis
equations (nonlinear) &
solve the equations

$$C \cdot \frac{dv_1}{dt} + f(v_1) + \frac{v_1}{R} = \frac{V_s}{R}$$

device models




dc operating point:

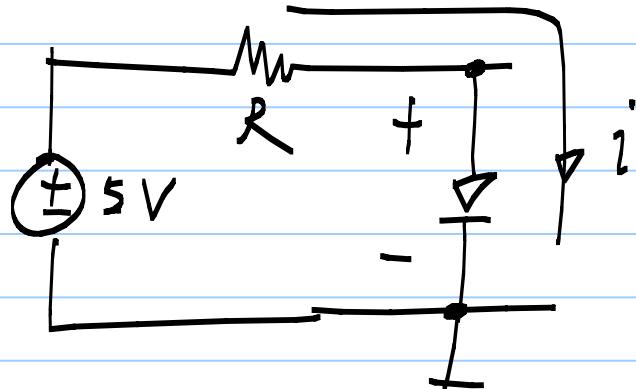- * open circuit capacitors, short circuit inductors
 - Nonlinear analysis




ac analysis - small signal incremental eq. circuit
increments: sinusoids at ω

Sinusoidal steady state

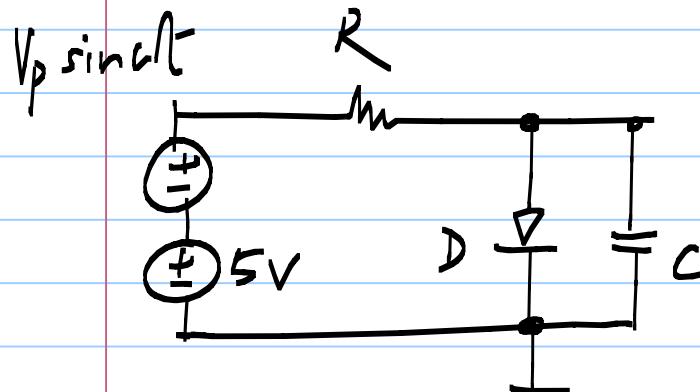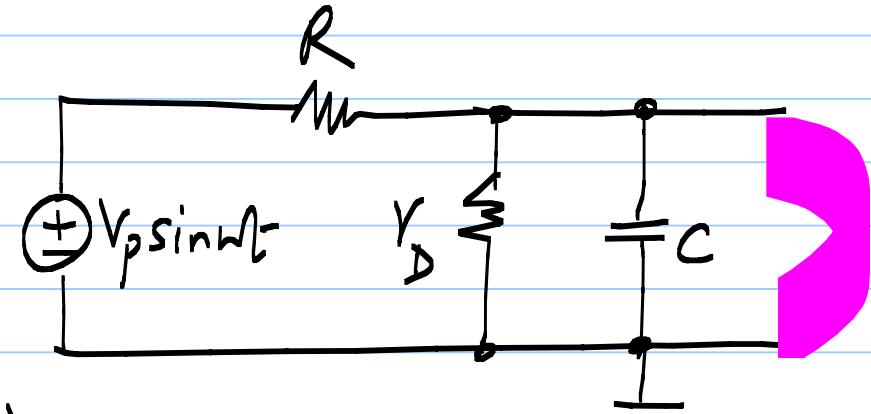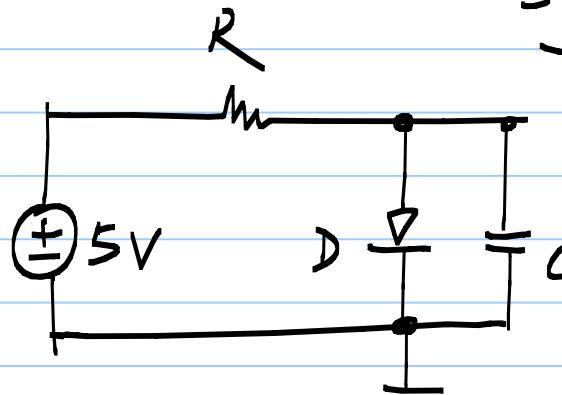

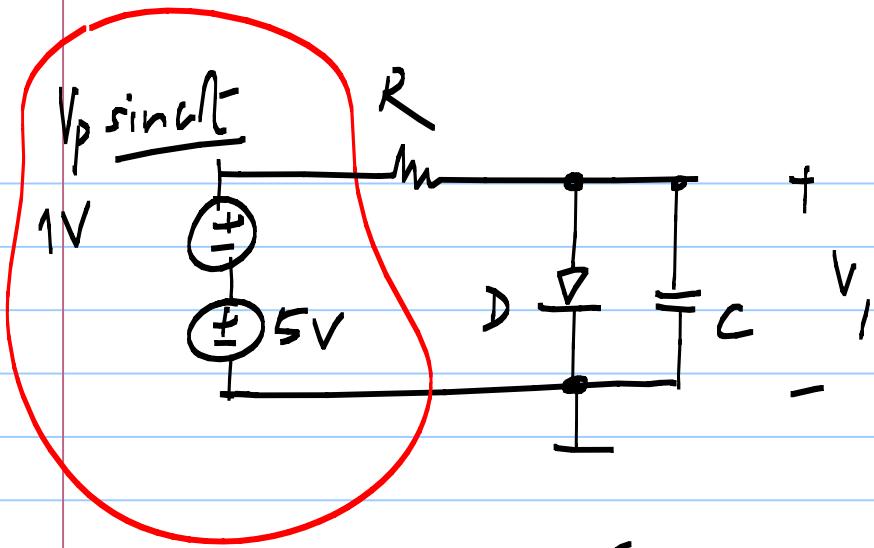
linear circuit
Signals $\propto V_p$ $V_p = 1 \angle 0^\circ V$




$$dc = 5V$$

$$\alpha_{cm} = 1 \quad \equiv$$

$$\alpha_{cp} = 0$$

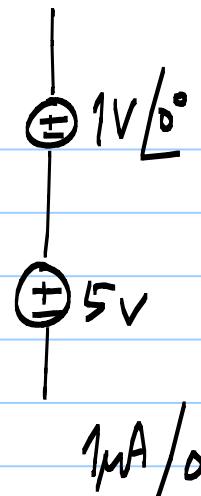

AC; sweep ω (linear / log)

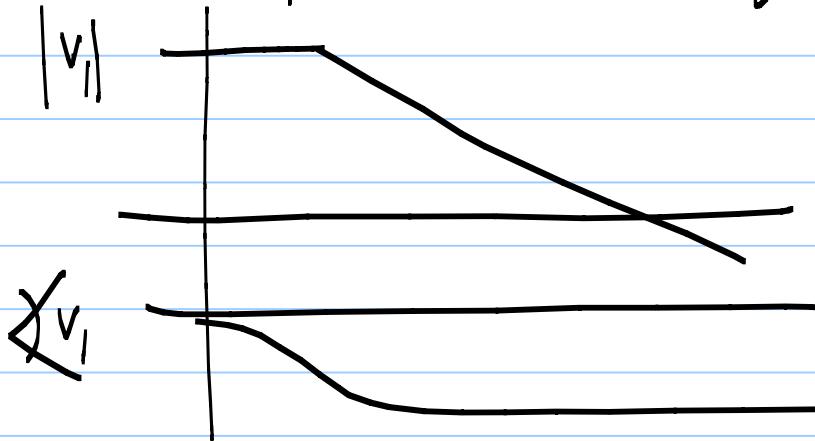


$$dc = 1mA$$

$$\alpha_{cm} = 1\mu A \quad \equiv$$

$$\alpha_{cp} = 0$$

Transient analysis :



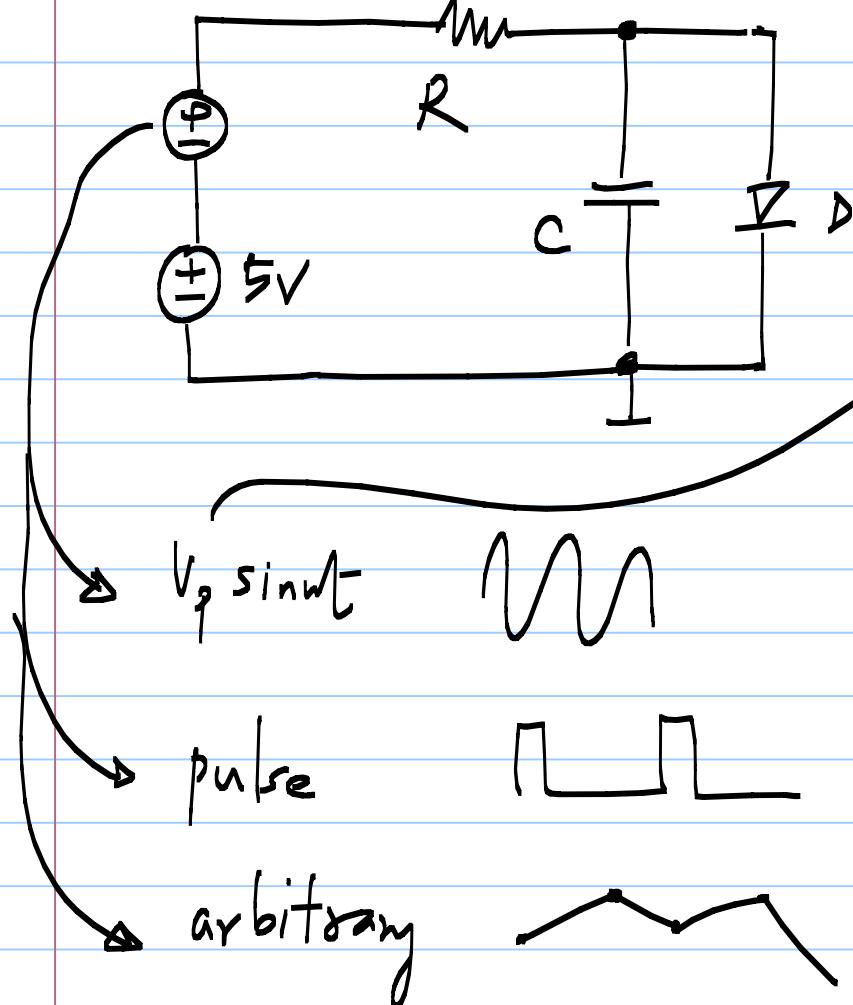



Solve the nonlinear differential equations w/ time varying inputs

v_p will make a difference

Sinusoidal i/p : Distortion

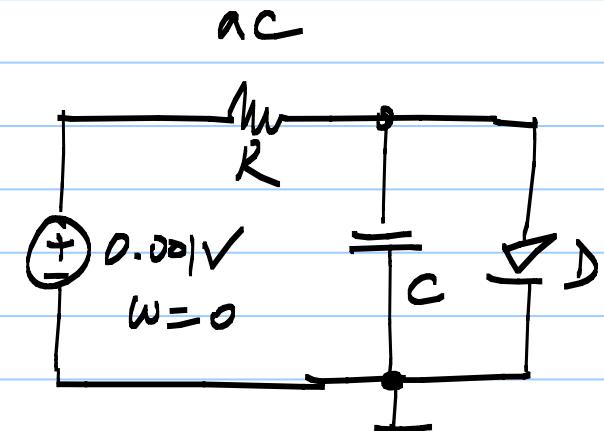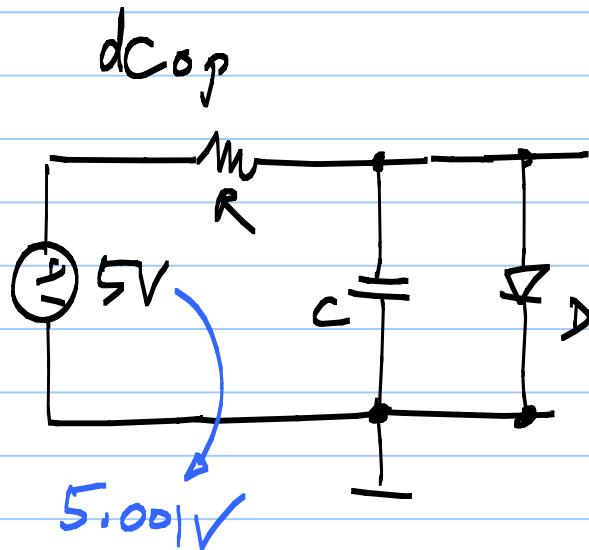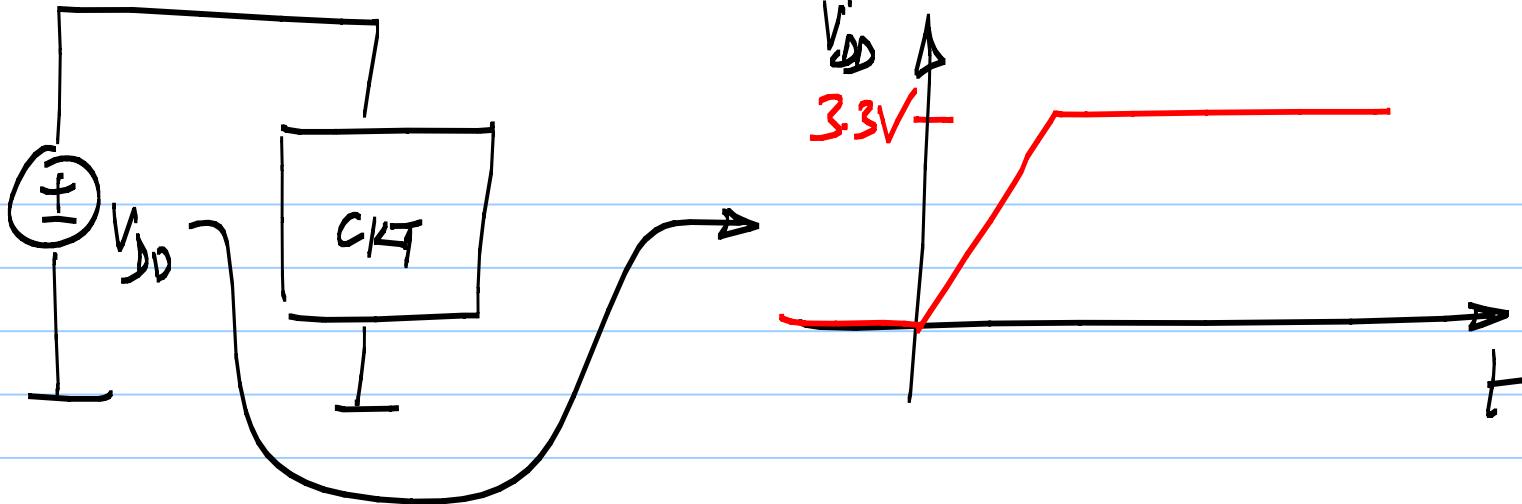Step response : small/large signal
linear / nonlinear ckt.



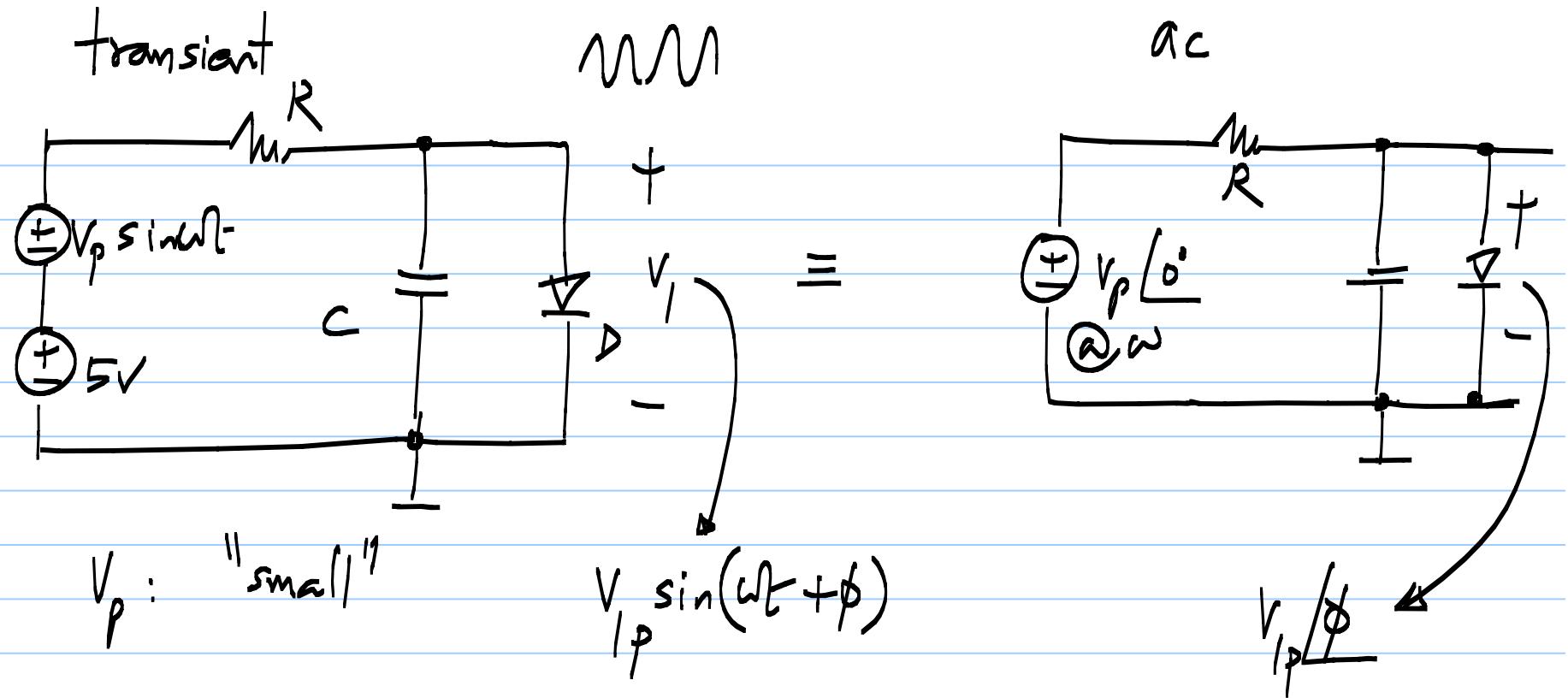


Sweep

dc value

component parameter

design variables

3V, 4V, 5V

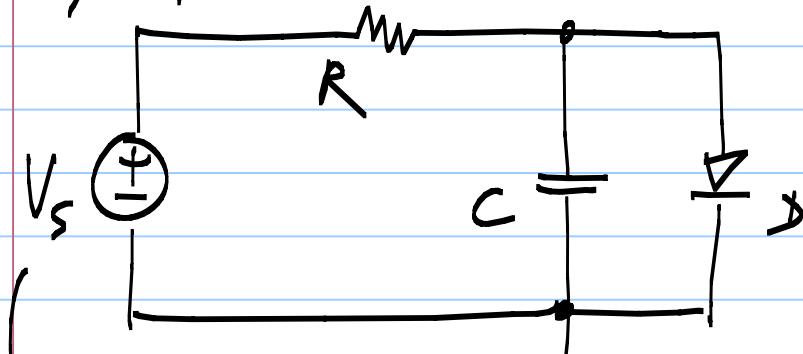


$$V_s = \{3V, 4V, 5V\}$$

Sophisticated analysis
PSS,

Post-processing:

- DFT
- plot results
- rise / fall times

Noise analysis

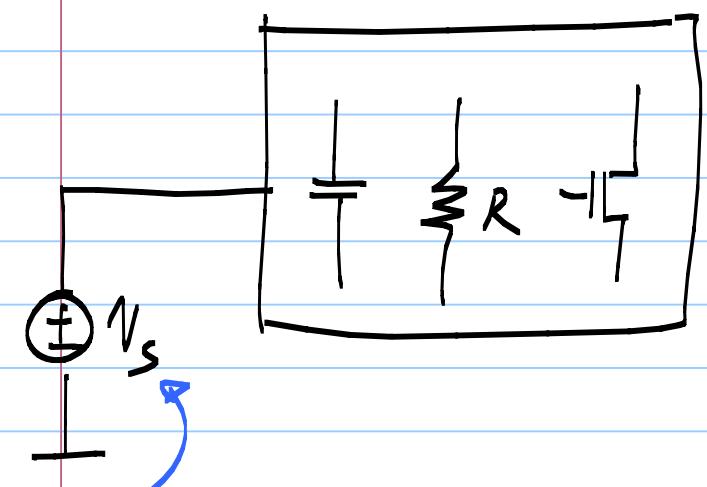

Add appropriate noise sources to each component

{ current sources in parallel with R , Mos }

* Output noise (at the specified o/p)

* Input referred noise (to the specified input)