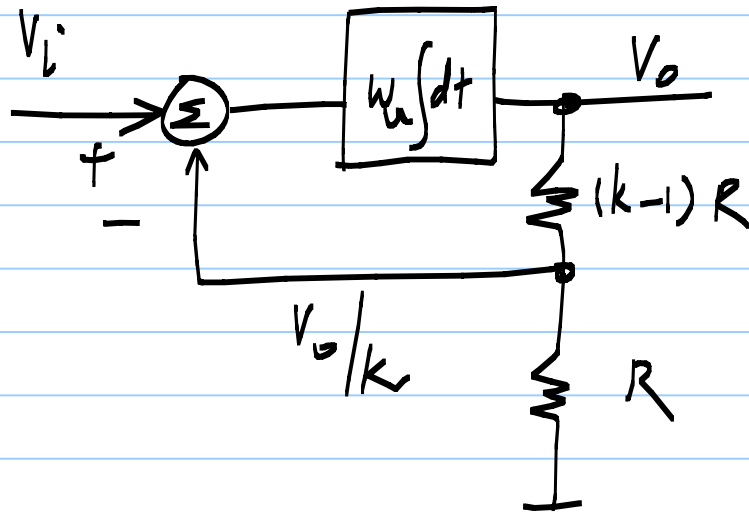


Lecture 45


Voltage amplifier



$$V_o = kV_i$$

(for constant V_i)

Frequency multiplier

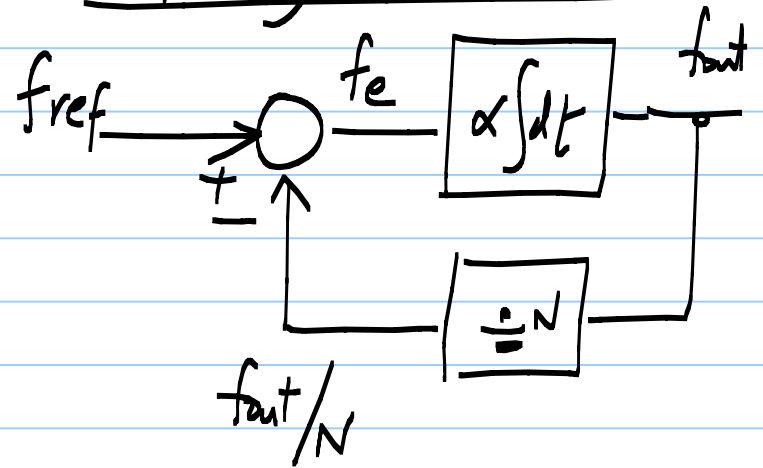

$$f_{out} = N \cdot f_{ref}$$

(Constant f_{ref})

Frequency and phase:

$$\cdot \cos(2\pi f_0 t)$$

$\cos(\theta)$: periodic in θ with a period 2π

$$\cos(\theta + n \cdot 2\pi) = \cos(\theta)$$

$$\theta = 2\pi f_0 t$$

$\cos(2\pi f_0 t)$: periodic in t with a period $\frac{1}{f_0}$

$\cos(\theta)$

$$\theta = 2\pi f_0 t$$


Periodic signal in time:

phase: \wedge ramp { linearly with time }

$$\theta = 2\pi f_0 t + \Phi_0$$

Constant offset Φ_0
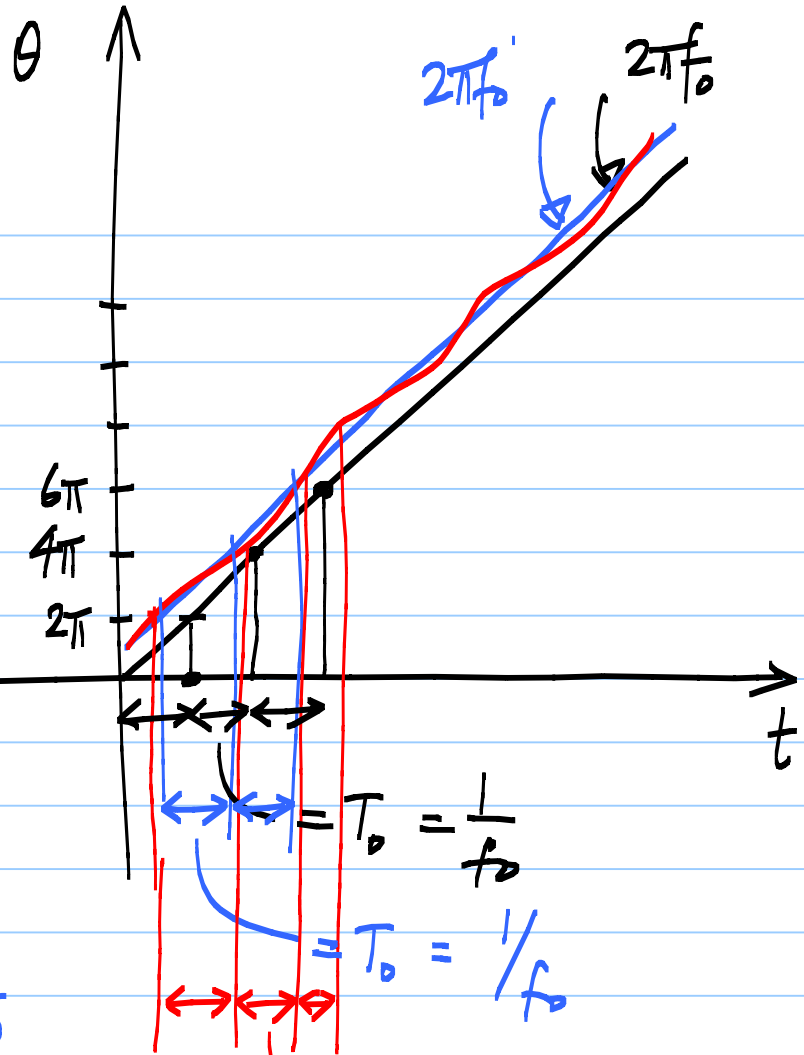
$$\theta = 2\pi f_0 t + \Phi_0 + \phi(t)$$



Not equal to each other
zero average

$p(\theta)$: periodic in θ , with a period 2π
 $\cos(\theta)$: periodic in θ , with a period 2π

$$\theta = 2\pi f_0 t + \Phi_0 + \phi(t)$$

(excluding the ramp)
 time varying part
 average (dc) phase shift





Only specify
 the frequency
 f_0

Ramp, represents the average slope

f_0 : average frequency

$\frac{1}{f_0} = T_0$: average period

$p(-)$

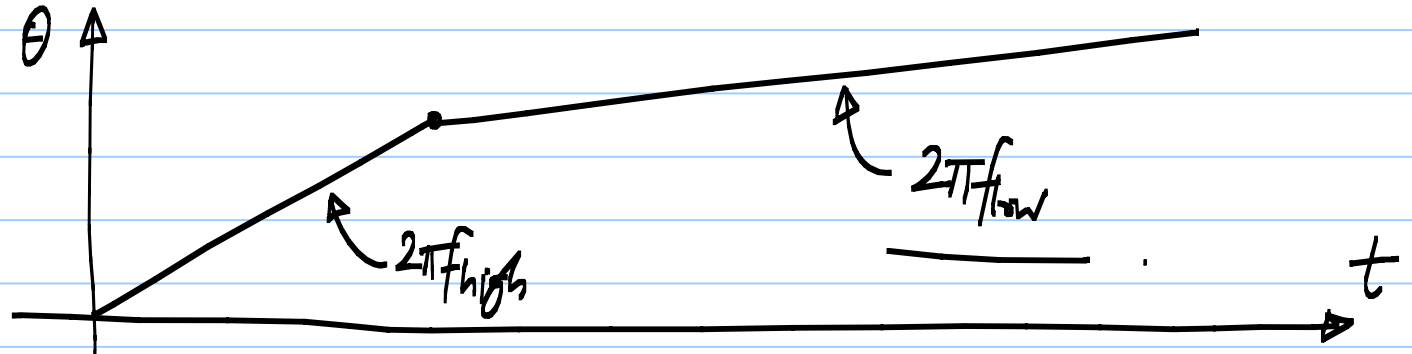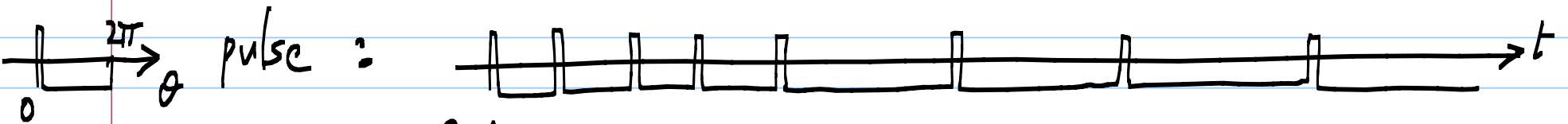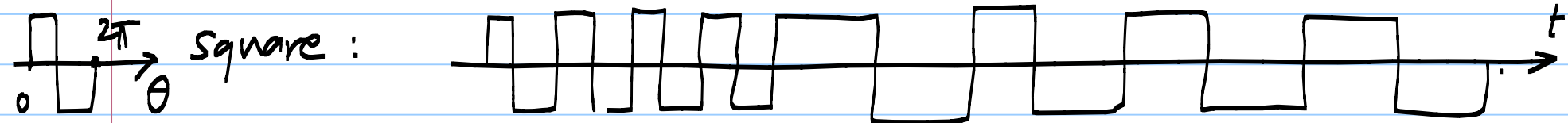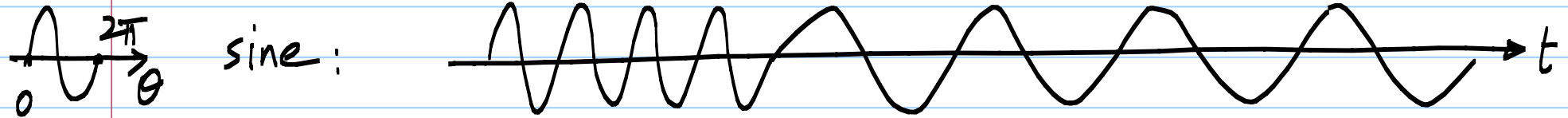


Phase $\theta(t) = 2\pi f_0 t + \Phi_0 + \phi(t)$ ↗ average frequency


Instantaneous Frequency $f = \frac{1}{2\pi} \cdot \frac{d\theta}{dt} = f_0 + \underbrace{\frac{1}{2\pi} \frac{d}{dt} \phi(t)}_{\text{average} = 0}$

Instantaneous phase $\theta(t) = 2\pi f_0 t + \Phi_0 + \phi(t)$ ↗ frequency (avg.) average = 0

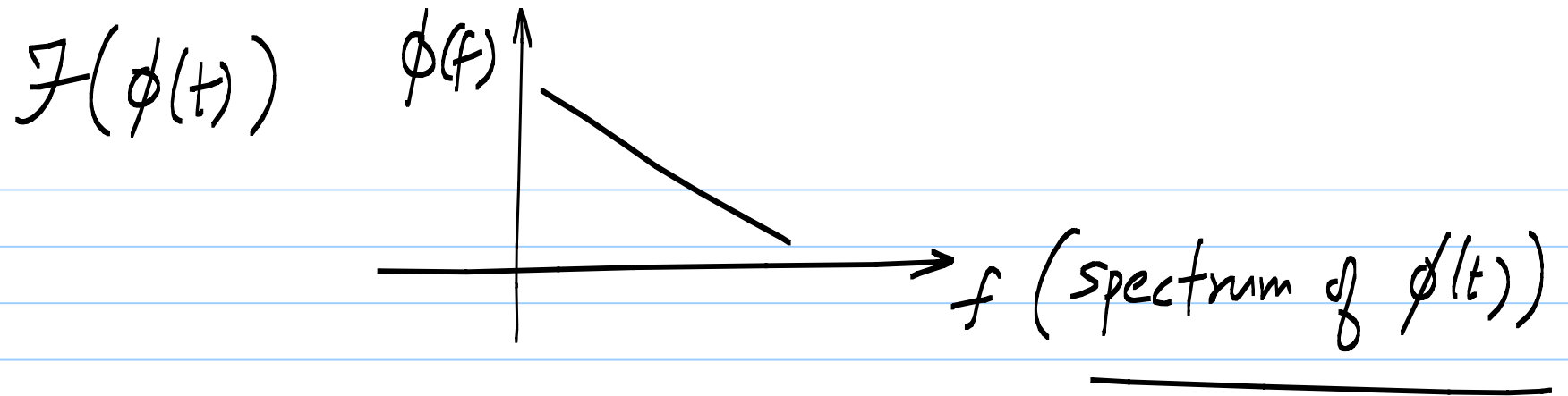Instantaneous frequency $f(t) = f_0 + \underbrace{\frac{1}{2\pi} \cdot \frac{d\phi(t)}{dt}}_{\text{frequency of } \frac{1}{2\pi} \frac{d\phi(t)}{dt}}$ ↗ frequency of $\phi(t)$



Frequency multiplier:

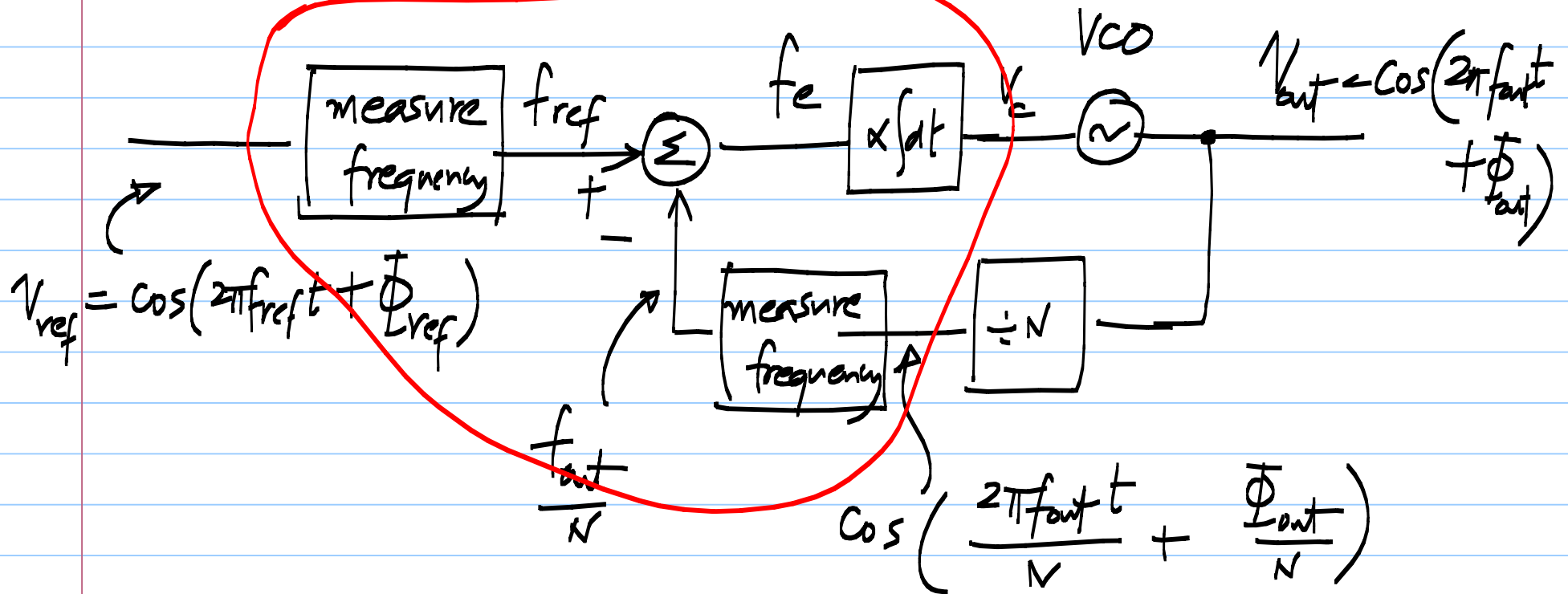


Steady state when $f_e = 0$

$$\frac{f_{out}}{N} = f_{ref} \quad \text{or} \quad \underline{\underline{f_{out} = N \cdot f_{ref}}}$$

To control the o/p frequency f_{out}:

Voltage controlled oscillator (VCO)

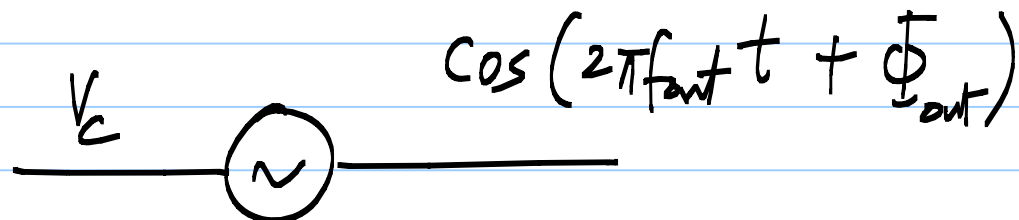

$$f_{out} = K_{VCO} \cdot V_c + f_0$$

VCO gain
Hz/V


free running
frequency
(freq. when $V_c = 0$)

VCO output: $\cos(\theta_{out}(t))$


$$\theta_{out} = 2\pi f_0 t + 2\pi K_{VCO} \int v_c(t) dt$$

$$= 2\pi (f_0 + K_{VCO} \cdot v_c) \cdot t$$

(constant v_c)





Frequency divider?

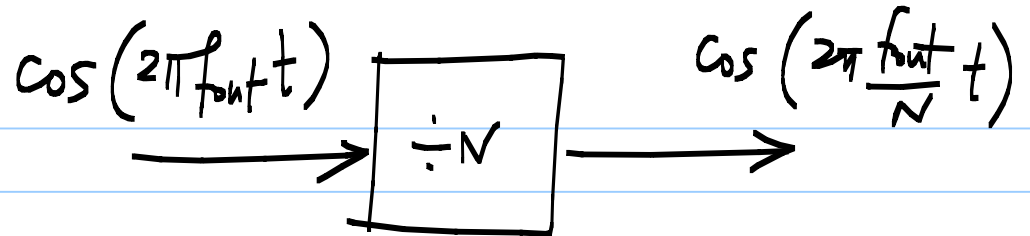

When N is an integer:


Digital counter

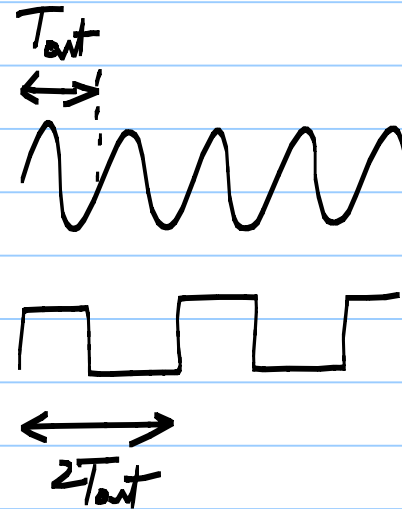

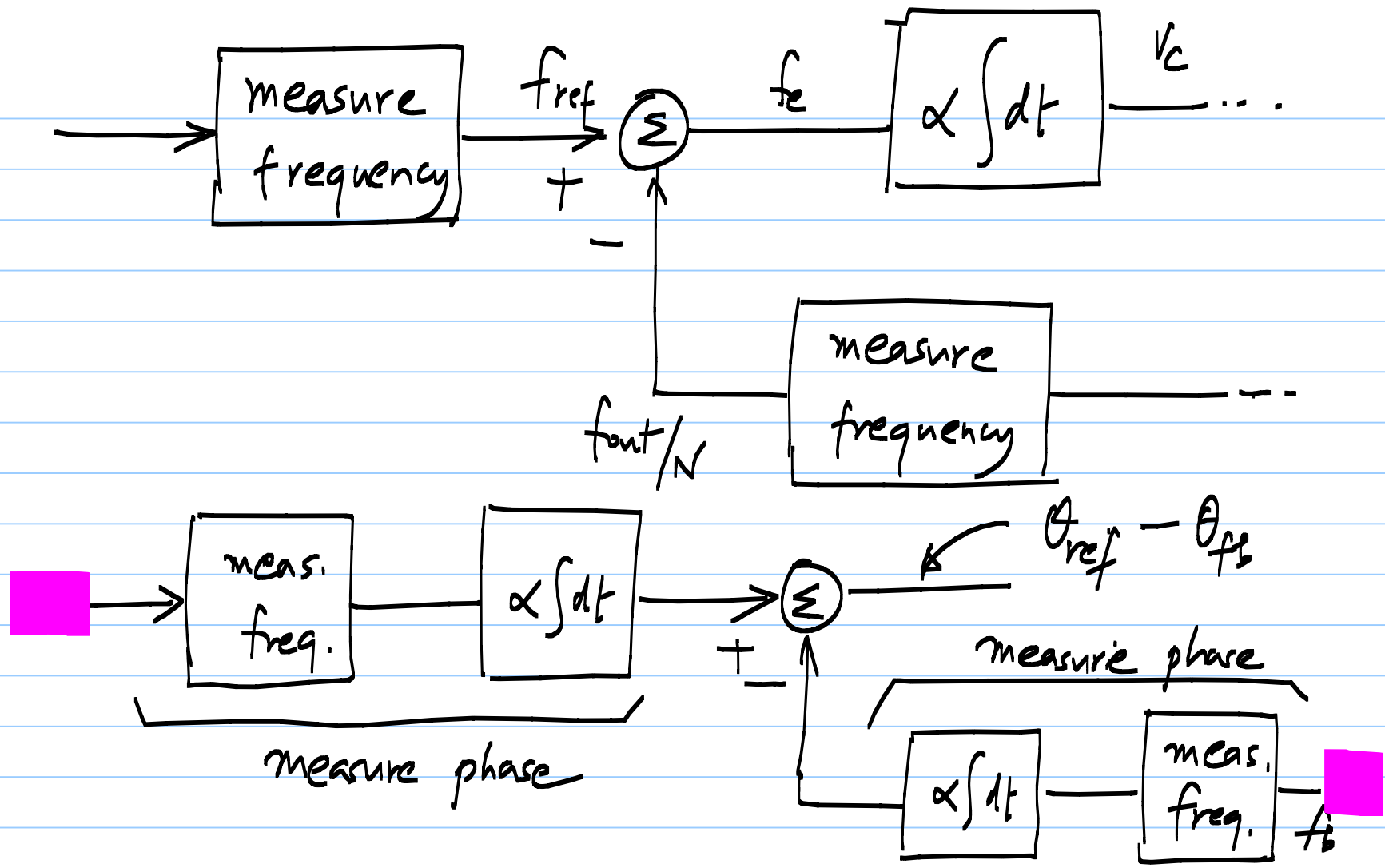

$$f_i(t) = \frac{1}{2\pi} \frac{d\theta(t)}{dt}$$

$$\theta(t) = 2\pi \int f_i(t) dt$$

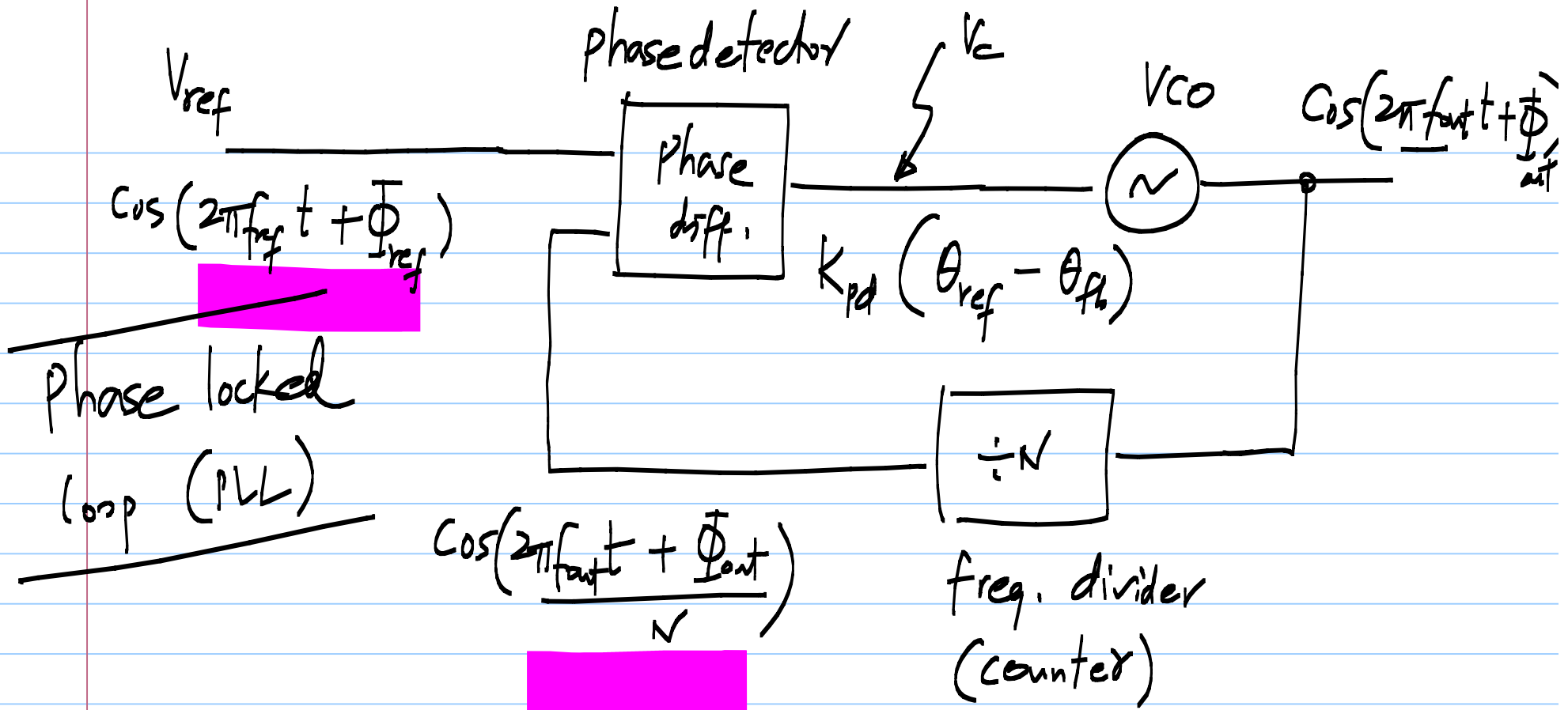

$$V_c = K_{pd} \left[2\pi \left(f_{ref} - \frac{f_{out}}{N} \right) t + \Phi_{ref} - \frac{\Phi_{out}}{N} \right]$$