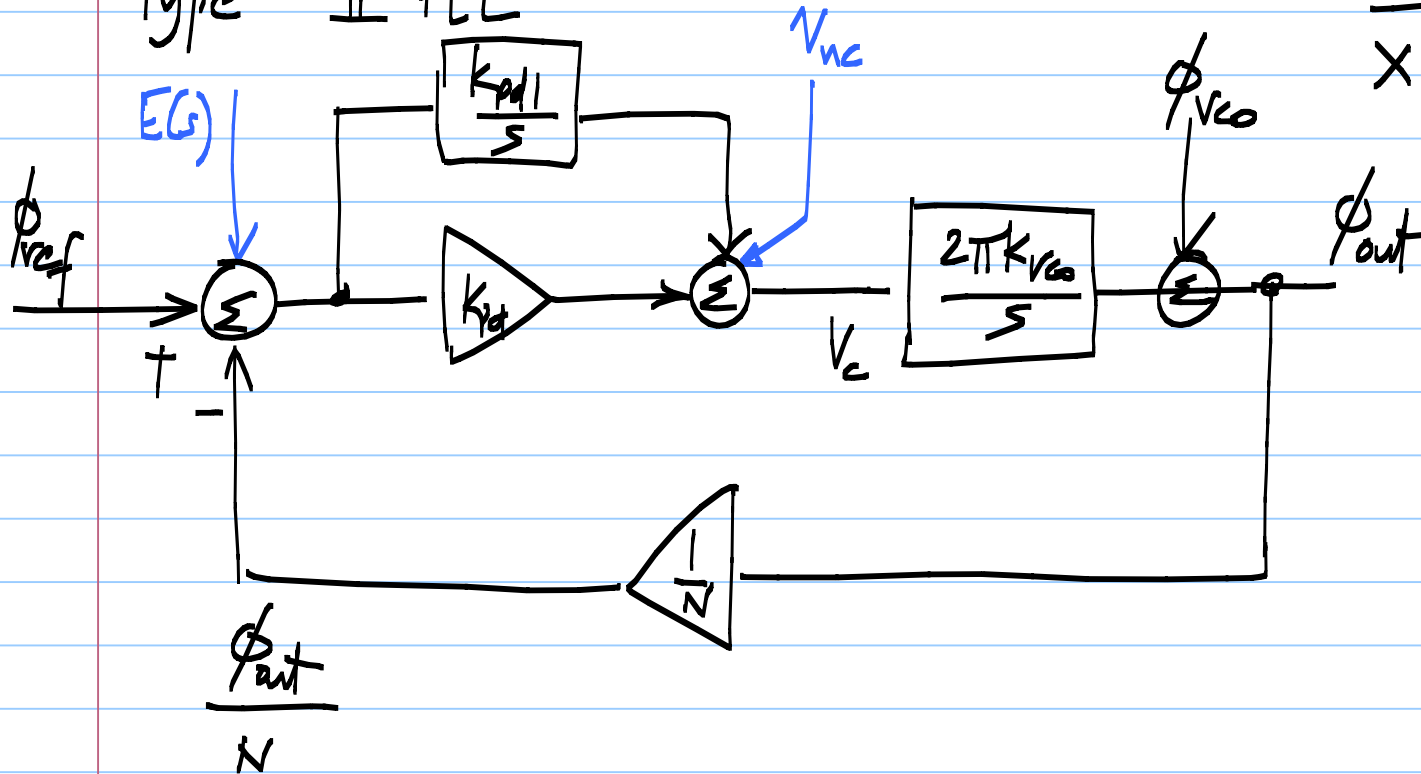


# Lecture 49:

Type II PLL



"forward path"

$$\frac{Y}{X} = \frac{G}{1 + GH}$$

loop gain

Lowpass

$$\frac{\phi_{out}(s)}{\phi_{ref}(s)} = N \cdot \frac{1 + \frac{s}{z_1}}{1 + \frac{s}{z_1} + \frac{s^2}{\omega_{n,loop} z_1}}$$

$$z_1 = \frac{K_{pd,1}}{K_{pd}}$$


$$\omega_{n,loop} = \frac{2\pi K_{pd} K_{vco}}{N}$$

Bandpass

$$\frac{\phi_{out}(s)}{V_{nc}(s)} = \frac{2\pi K_{vco}}{s} \cdot \frac{1}{1 + \frac{2\pi K_{vco}}{N \cdot s} \left( K_{pd} + \frac{K_{pd,1}}{s} \right)} = \frac{N}{K_{pd}} \cdot \frac{s/z_1}{1 + \frac{s}{z_1} + \frac{s^2}{\omega_{n,loop} z_1}}$$

Highpass
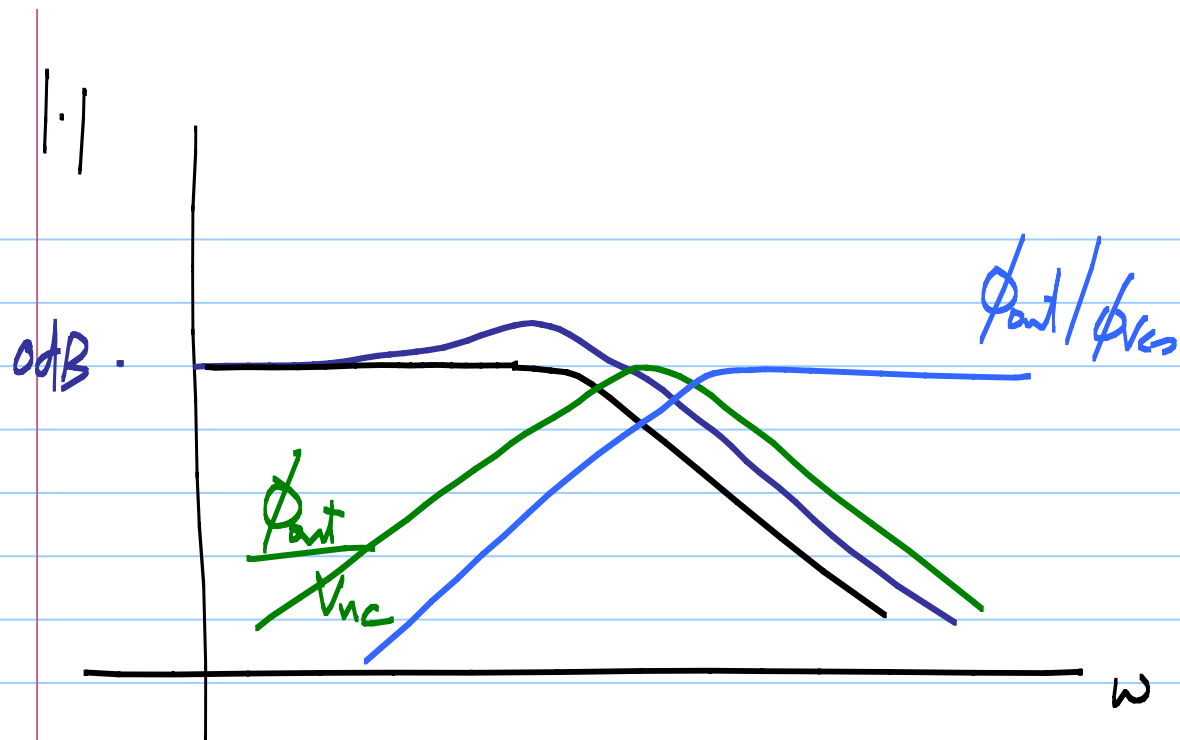
$$\frac{\phi_{out}(s)}{\phi_{vco}(s)} = \frac{1}{1 + \frac{2\pi K_{vco}}{N \cdot s} \left( K_{pd} + \frac{K_{pd,1}}{s} \right)} = \frac{\frac{s^2}{\omega_{n,loop} z_1}}{1 + \frac{s}{z_1} + \frac{s^2}{\omega_{n,loop} z_1}}$$



$$\frac{1}{N} \cdot \frac{\phi_{out}}{\phi_{ref}}$$

$$\frac{K_{pd}}{N} \cdot \frac{\phi_{out}}{V_{inc}}$$

$$\frac{\phi_{out}}{\phi_{vco}}$$

$\frac{\phi_{out}}{\phi_{ref}}$  : Lowpass with dc gain =  $N$  ;  $\frac{\phi_{out}}{\phi_{vco}}$  : Highpass

$\frac{\phi_{out}}{\phi_{vco}}$  : Bandpass with a peak gain  $\frac{N}{K_{pd}}$

Clean up the jitter of the reference oscillator:

\* Low bandwidth PLL; More filtering of  $\phi_{ref}$

Clean up the jitter of the VCO: (reduce contribution of  $\phi_{vco}$ )


\* High bandwidth PLL

Follow the jitter of the reference oscillator:


\* High bandwidth PLL.
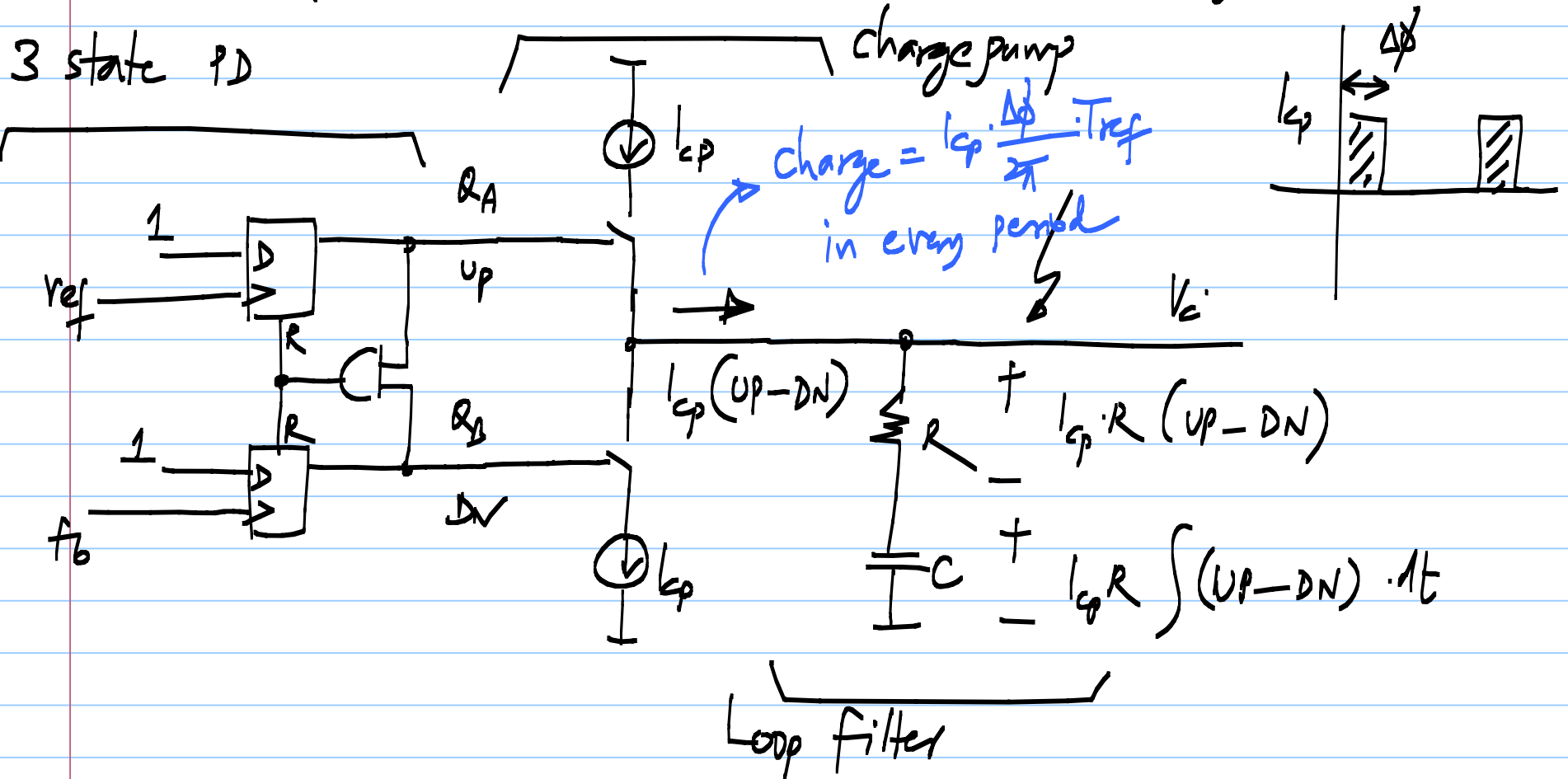
# Reference feedthrough in a type II PLL

3 state phase detector  $\leftarrow$  proportional & integral paths.



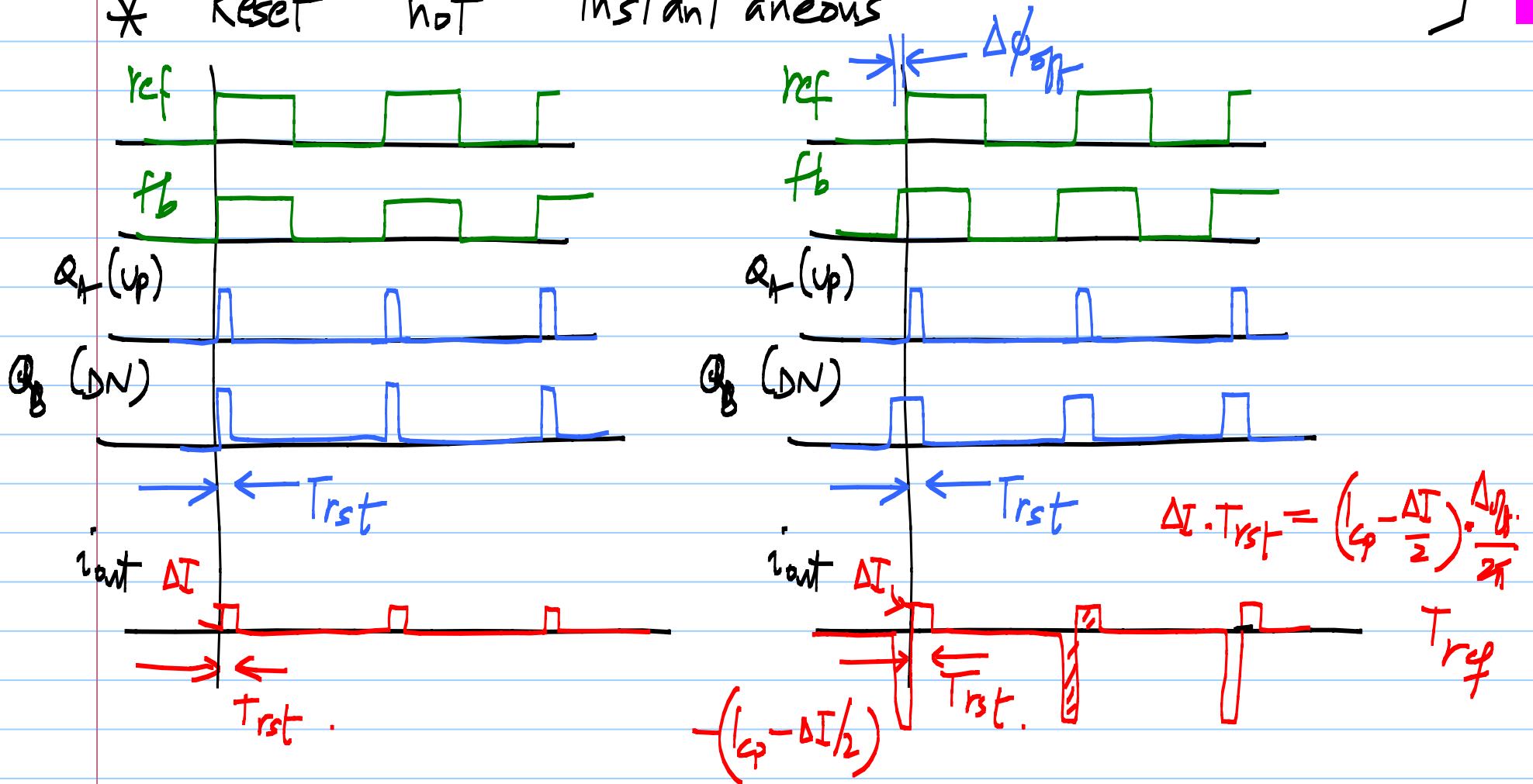- \* upper and lower currents not equal to each other
- \* Reset not instantaneous




# Type II PLL locks with a phase offset $\Delta\phi_{off}$

$$\Delta I \cdot T_{rst} = + \left( I_{cp} - \frac{\Delta I}{2} \right) \cdot \frac{\Delta\phi_{off}}{2\pi} \cdot T_{ref}$$

$$\Delta\phi_{off} = 2\pi \cdot \frac{T_{rst}}{T_{ref}} \cdot \frac{\Delta I}{\left( I_{cp} - \frac{\Delta I}{2} \right)} \approx 2\pi \cdot \left( \frac{T_{rst}}{T_{ref}} \right) \cdot \left( \frac{\Delta I}{I_{cp}} \right)$$


P.D + charge pump d/p:

input referred  
 $e(t)$

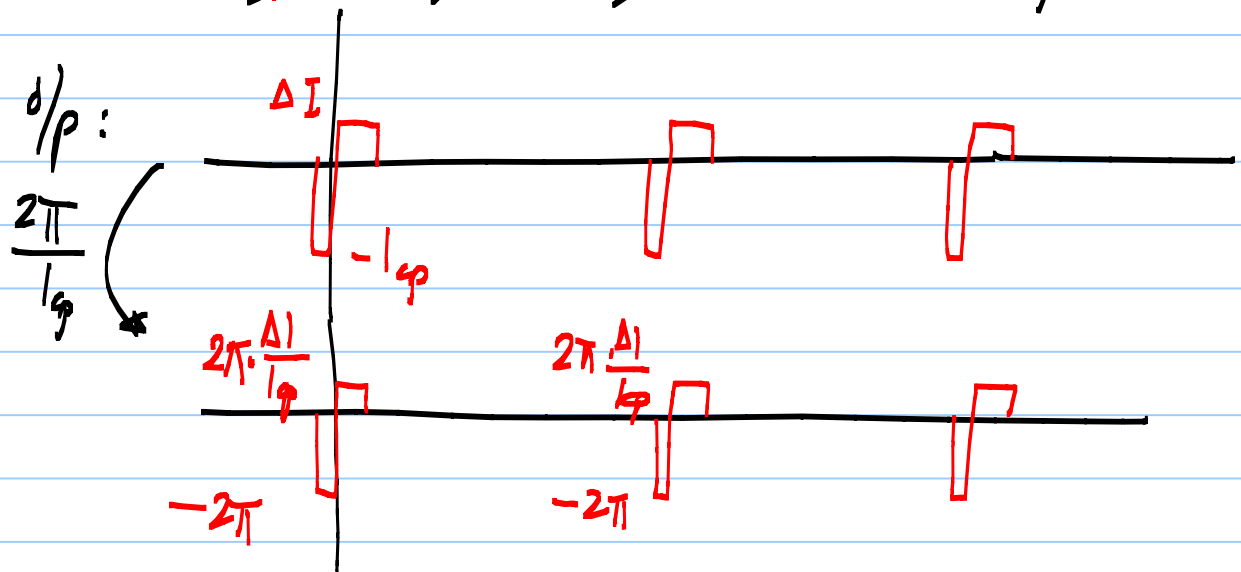
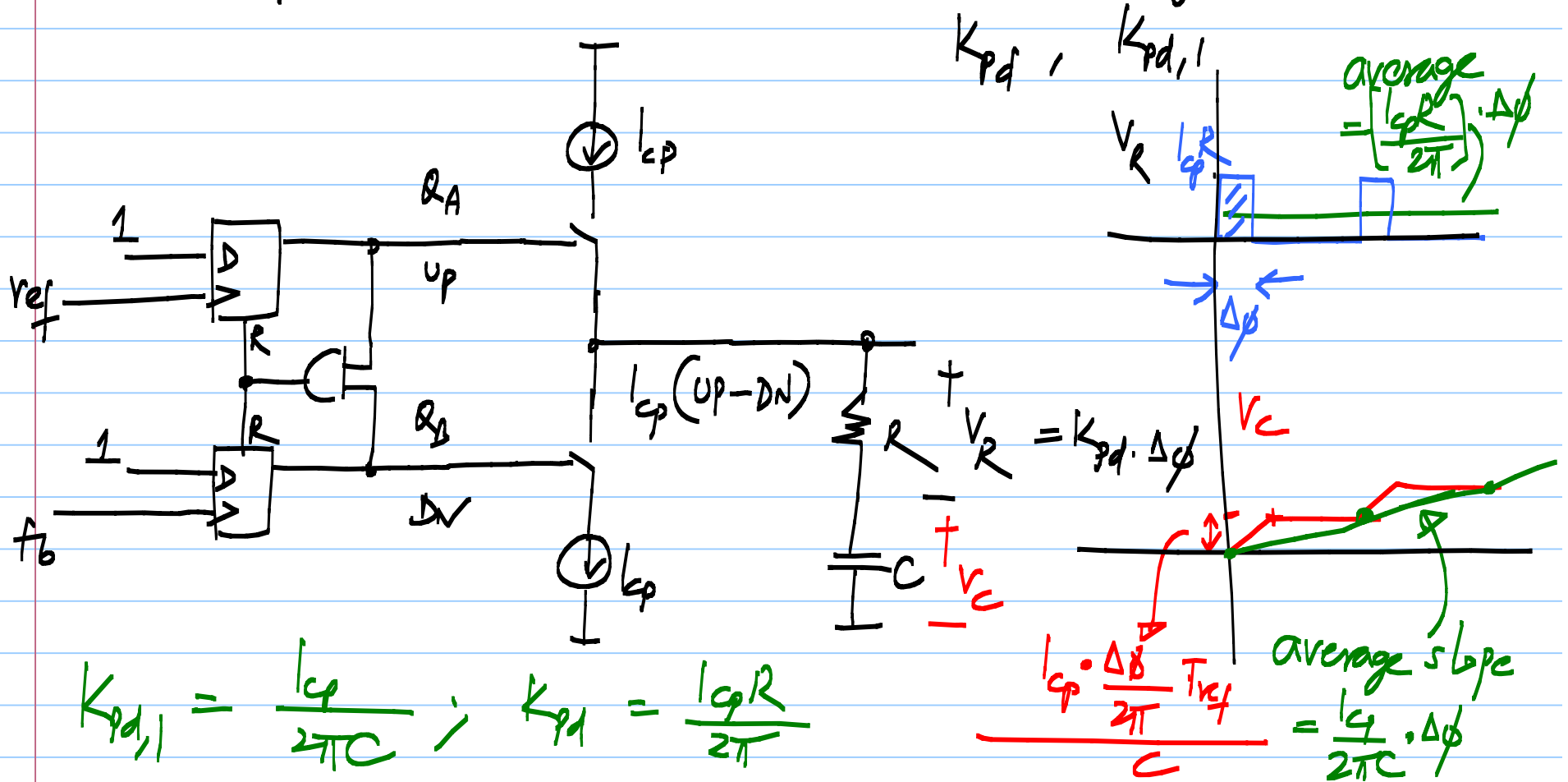
# Reference feedthrough in a type II PLL

3 state phase detector  $\leftarrow$  proportional & integral paths.





$$\omega_{u,loop} = \frac{2\pi k_{pd} k_{vco}}{N} = \frac{2\pi \cdot \frac{I_{cp} R}{2\pi} \cdot k_{vco}}{N}$$

$$\omega_{u,loop} = \frac{I_{cp} R \cdot k_{vco}}{N} \quad ;$$

(rad/s) (Hz)

$$z_1 = \frac{k_{pd,1}}{k_{pd}} = \frac{1}{RC}$$

Periodic error  $e(t)$  added to the loop:

