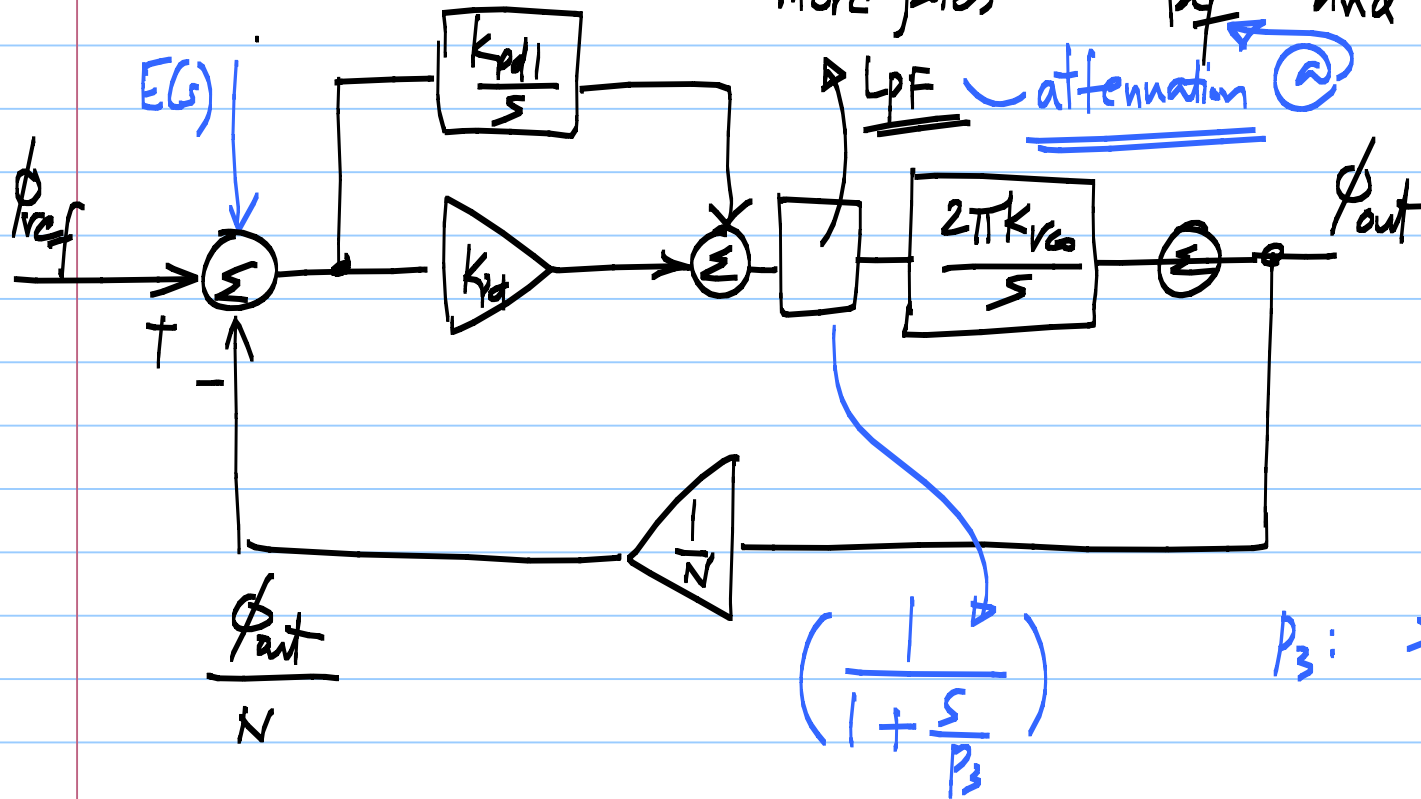


# Lecture 50:

$e(t)$ : contains components at more poles  $f_{ref}$  and its harmonics




well beyond the unity loop gain frequency

$P_3: \gg \omega_{u,loop}$

Phase:

$\phi_{ref}(t)$ : continuous-time

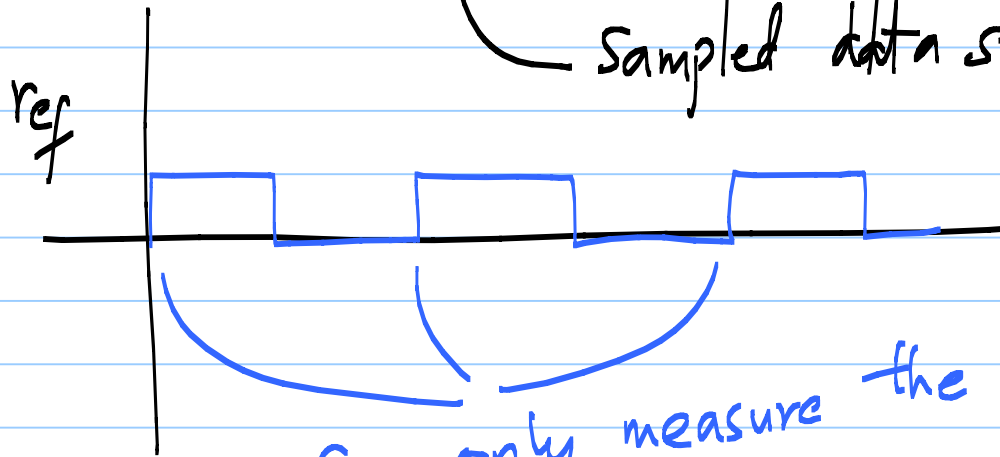
sampled data signal - sampled at  $f_{ref}$




Can only measure the phase  
at the zero crossings

Continuous-time approximation valid if
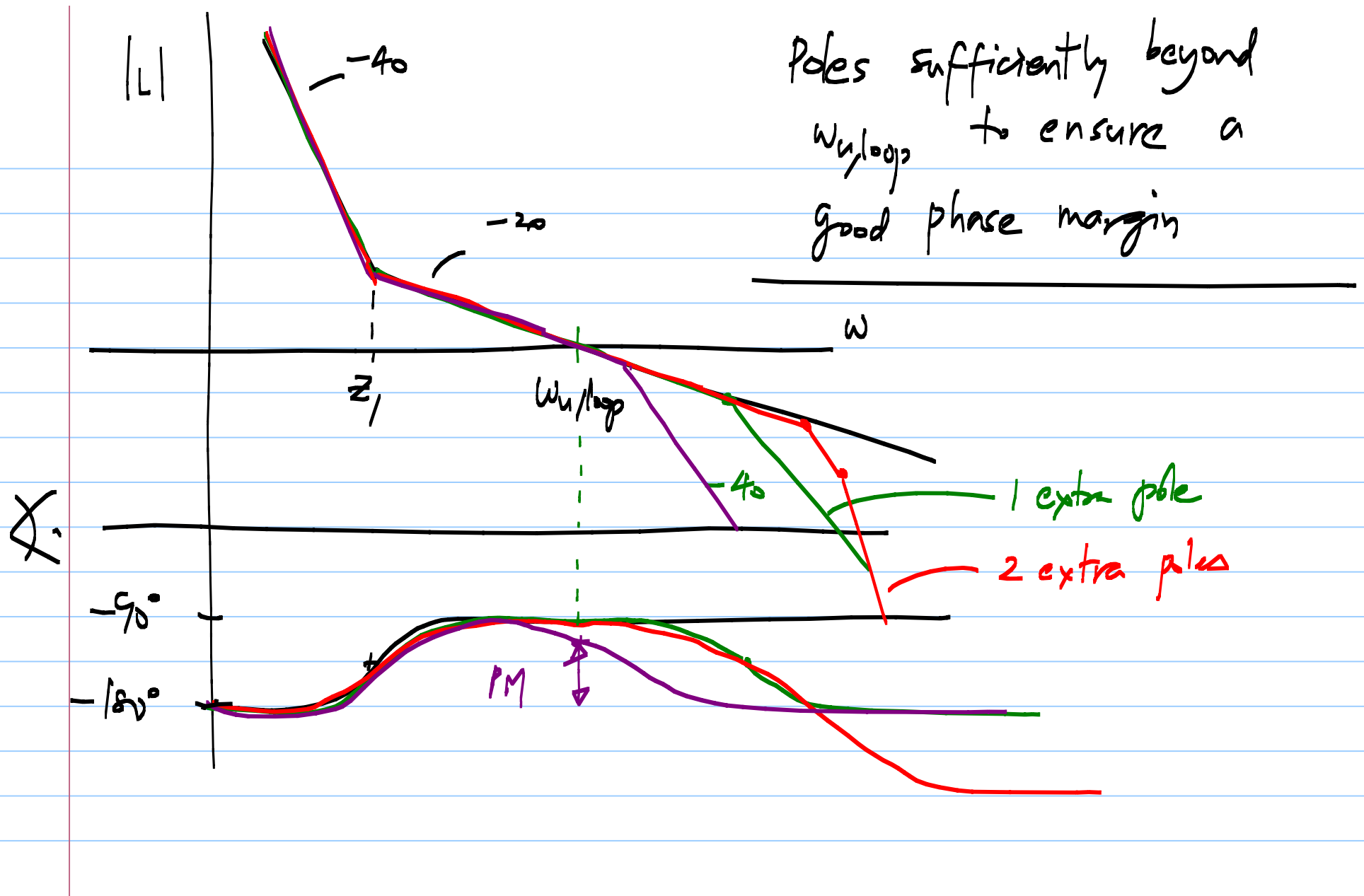
$$f_{ref} \gg \frac{\omega_{loop}}{2\pi}$$




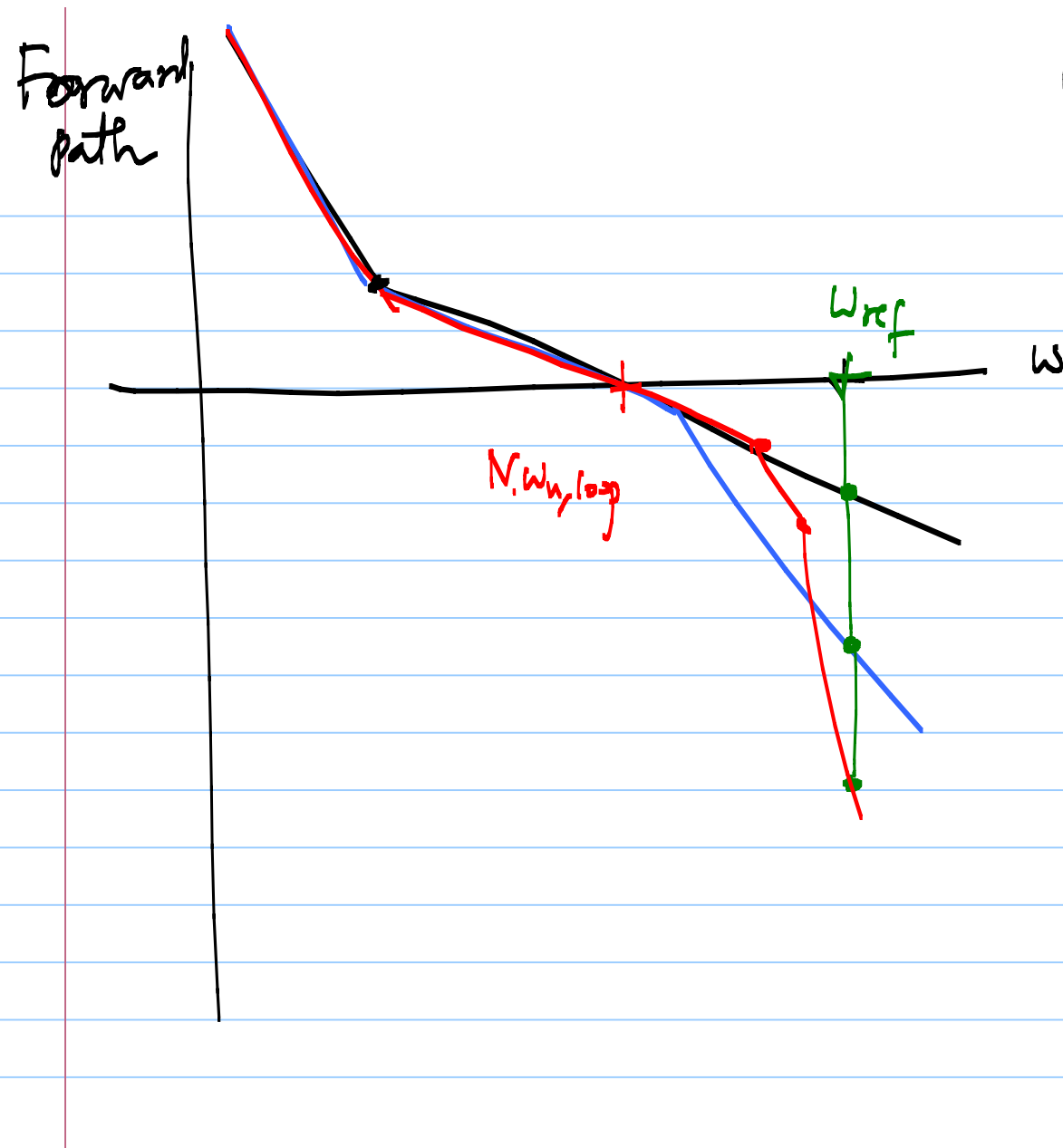

$$\left( K_{p1} + \frac{K_{p1,1}}{s} \right) \cdot \frac{2\pi K_{vco}}{s} \left( \frac{1}{1 + \frac{s}{p_3}} \right)$$

Poles have to be below the reference frequency in order to attenuate feedthrough components.

# Type II PLL w/ charge pump:

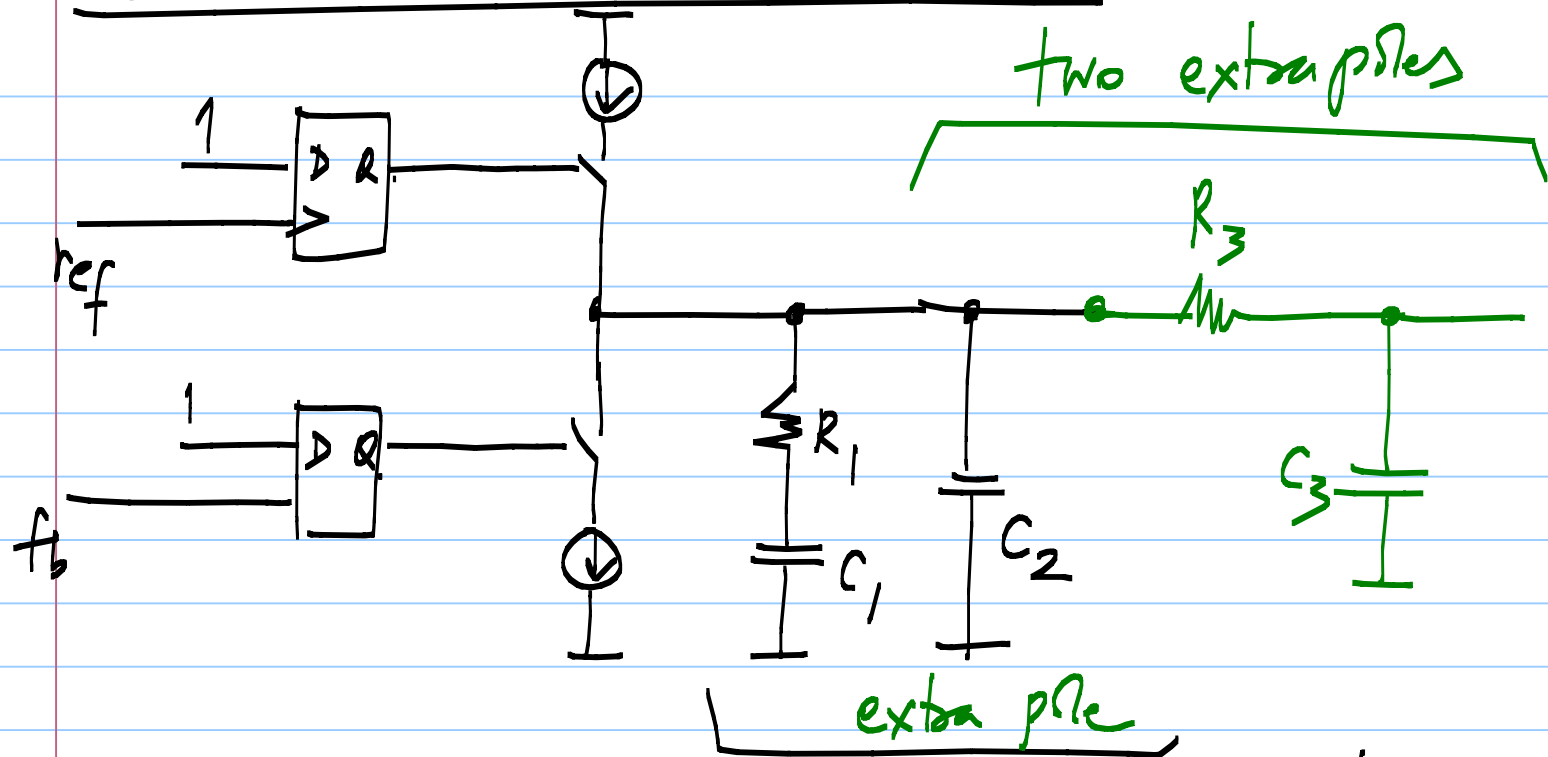


1 extra pole: add  $C_2$  . pole @  $\frac{1}{R_1 \frac{(C_1 \cdot C_2)}{C_1 + C_2}}$  rad/s


## Random noise in a PLL:

- \* Reference oscillator: phase noise ( $\phi_{ref}$ )
- \* VCO : phase noise ( $\phi_{VCO}$ )
- \* Charge pump noise (current source noise)
- \* Loop filter noise (e.g. resistor)

# Charge pump noise:

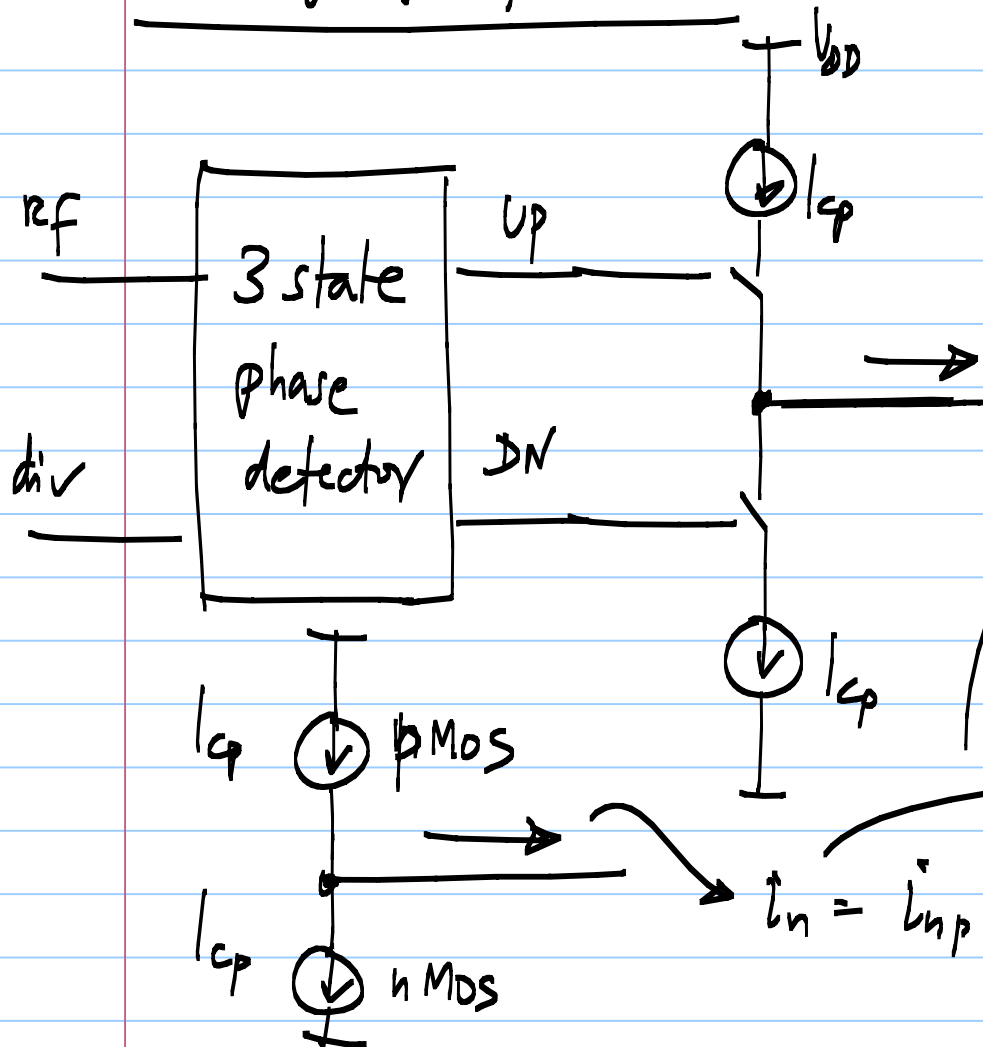

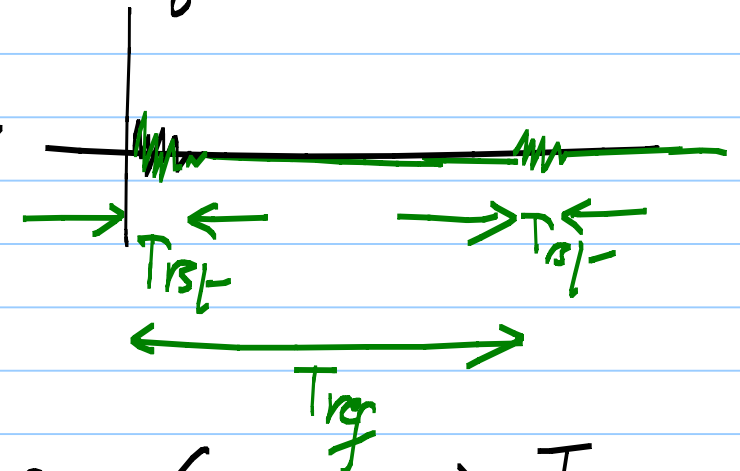\* UP, DN: on for a duration of  $T_{rst}$  (reset time of the PD)



$$f_n = (S_{inp} + S_{inn}) \cdot \frac{T_{rst}}{T_{ref}}$$

$$\frac{\phi_{out}}{\phi_{ref}} = N \cdot \frac{1 + s/z_1}{1 + \frac{s}{z_1} + \frac{s^2}{\omega_{hloop} z_1}} = \frac{\phi_{out}}{\phi_{n,cp}}$$

$$s_{in} = (s_{inp} + s_{inn}) \cdot \frac{T_{rst}}{T_{ref}}$$

input ref. noise  
of the charge pump

$$S_{\phi_{n,cp}} = \frac{s_{in}^2}{(I_{cp}/2\pi)^2} = \left(\frac{2\pi}{I_{cp}}\right)^2 \left[ s_{inp} + s_{inn} \left(\frac{T_{rst}}{T_{ref}}\right) \right]^2$$

$$S_{out,cp} = \left(\frac{2\pi}{I_{cp}}\right)^2 \left[ s_{inp} + s_{inn} \right]^2 \left(\frac{T_{rst}}{T_{ref}}\right)^2 \cdot \left| \frac{\phi_{out}}{\phi_{n,cp}} \right|^2$$



$$S_{out,CP} = \left( \frac{2\pi}{I_{CP}} \right)^2 \left[ g_{mp} + g_{mn} \right] \left( \frac{T_{rst}}{T_{ref}} \right) \left| \frac{\phi_{out}}{\phi_{in,CP}} \right|^2$$

\* Reduce  $T_{rst}/T_{ref}$

$$\frac{4\pi^2}{I_{CP}^2} \frac{8}{3} kT (g_{mp} + g_{mn}) \left( \frac{T_{rst}}{T_{ref}} \right) \left| \frac{\phi_{out}}{\phi_{in,CP}} \right|^2$$

\* Increase  $I_{CP}$

— reduce  $R$   $k_{pd} = \frac{I_{CP} R}{2\pi}$


— increase  $C$   $k_{pd,1} = \frac{I_{CP}}{2\pi C}$

$$= \frac{4\pi^2}{I_{CP}} \frac{8}{3} kT \left[ \frac{g_{mp}}{I_{CP}} + \frac{g_{mn}}{I_{CP}} \right] \left( \frac{T_{rst}}{T_{ref}} \right) \left| \frac{\phi_{out}}{\phi_{in,CP}} \right|^2$$

\* Increase  $\left\{ \begin{array}{l} V_{GS,P} - V_{TP} \\ V_{GS,N} - V_{TN} \end{array} \right.$

$$\left[ \frac{2}{V_{GS,P} - V_{TP}} + \frac{2}{V_{GS,N} - V_{TN}} \right]$$

# Contribution of the loop filter:

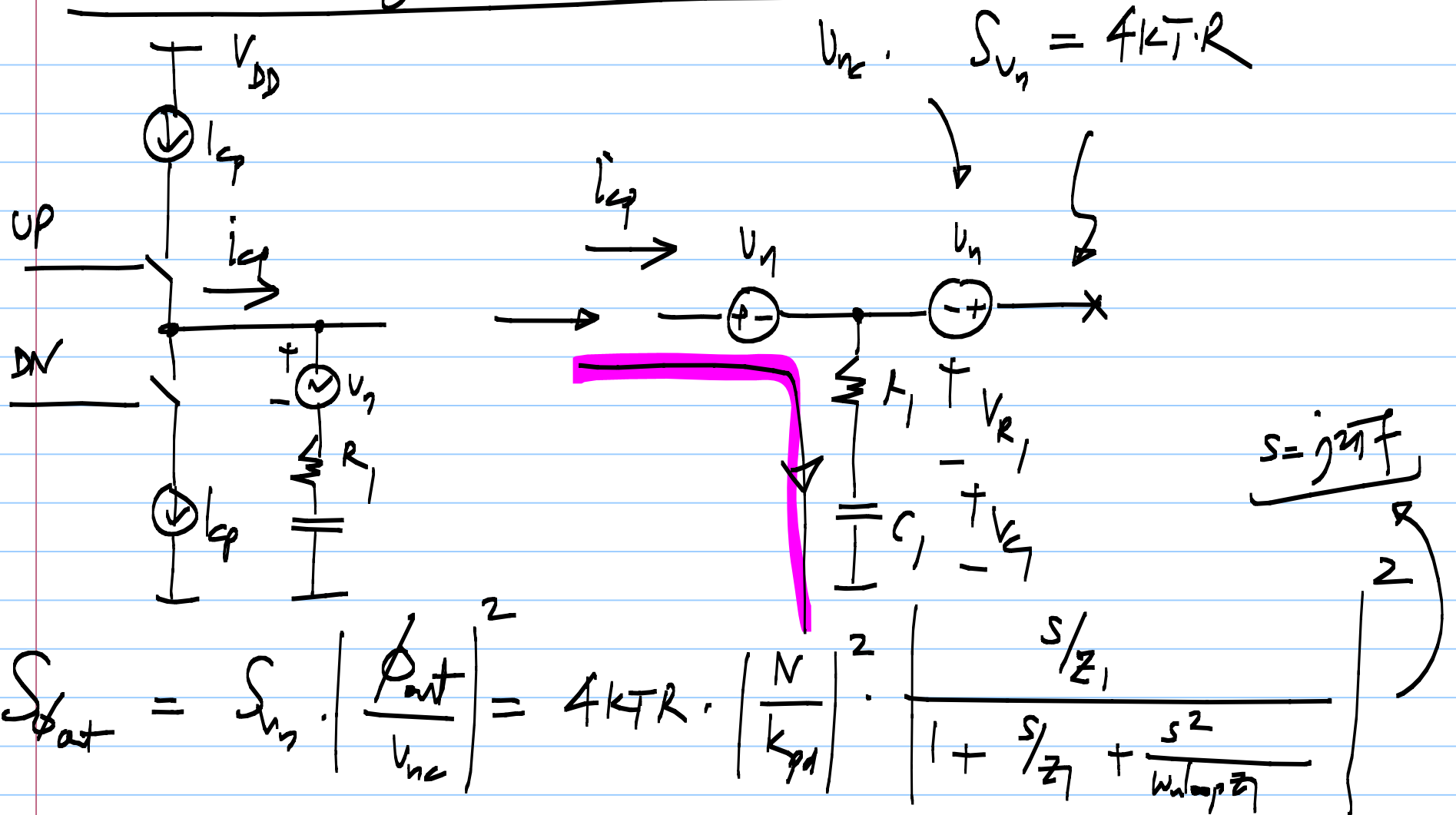

$$S_{\phi_{out}} = 4kTR \cdot \left| \frac{N}{k_{pd}} \right|^2 \cdot \left| \frac{s/z_1}{1 + \frac{s}{z_1} + \frac{s^2}{\omega_{n0}^2 z_1}} \right|^2$$


$s = j2\pi f$

\* Reduce R

Increase $\omega_p$	$k_{pd} = \omega_p R / 2\pi$	Increase C	$k_{pd,1} = \omega_p / 2\pi C$	} Impedance scaling

\* Increase  $k_{pd}$

└ Reduce  $k_{re}$

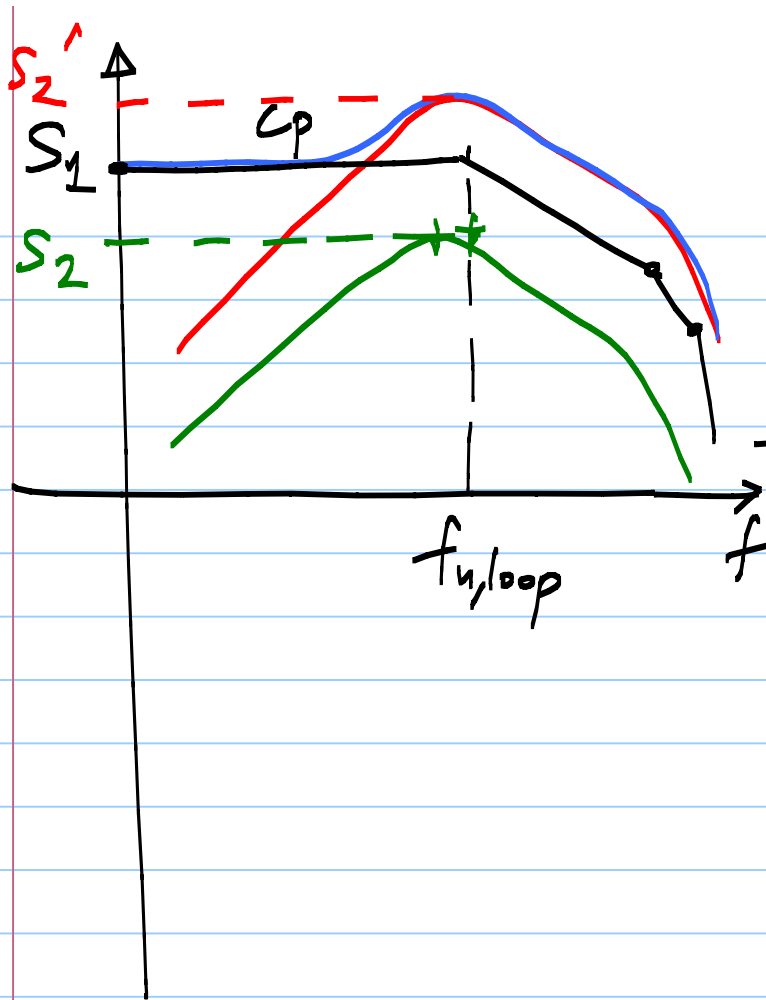

Noise in  $\phi_{out}$  due to charge pump:

$$S_1 = \frac{4\pi^2}{I_{CP}^2} \cdot \frac{8}{3} kT (g_{mp} + g_{mn}) \left( \frac{T_{VST}}{T_{ref}} \right) \left| \frac{\phi_{out}}{\phi_{ref}} \right|^2$$

$\text{rad}^2/\text{Hz} \quad \left\{ \frac{1}{\text{Hz}} \right\}$

$$S_2 = 4kTR \left| \frac{N}{K_{p1}} \right|^2$$

