
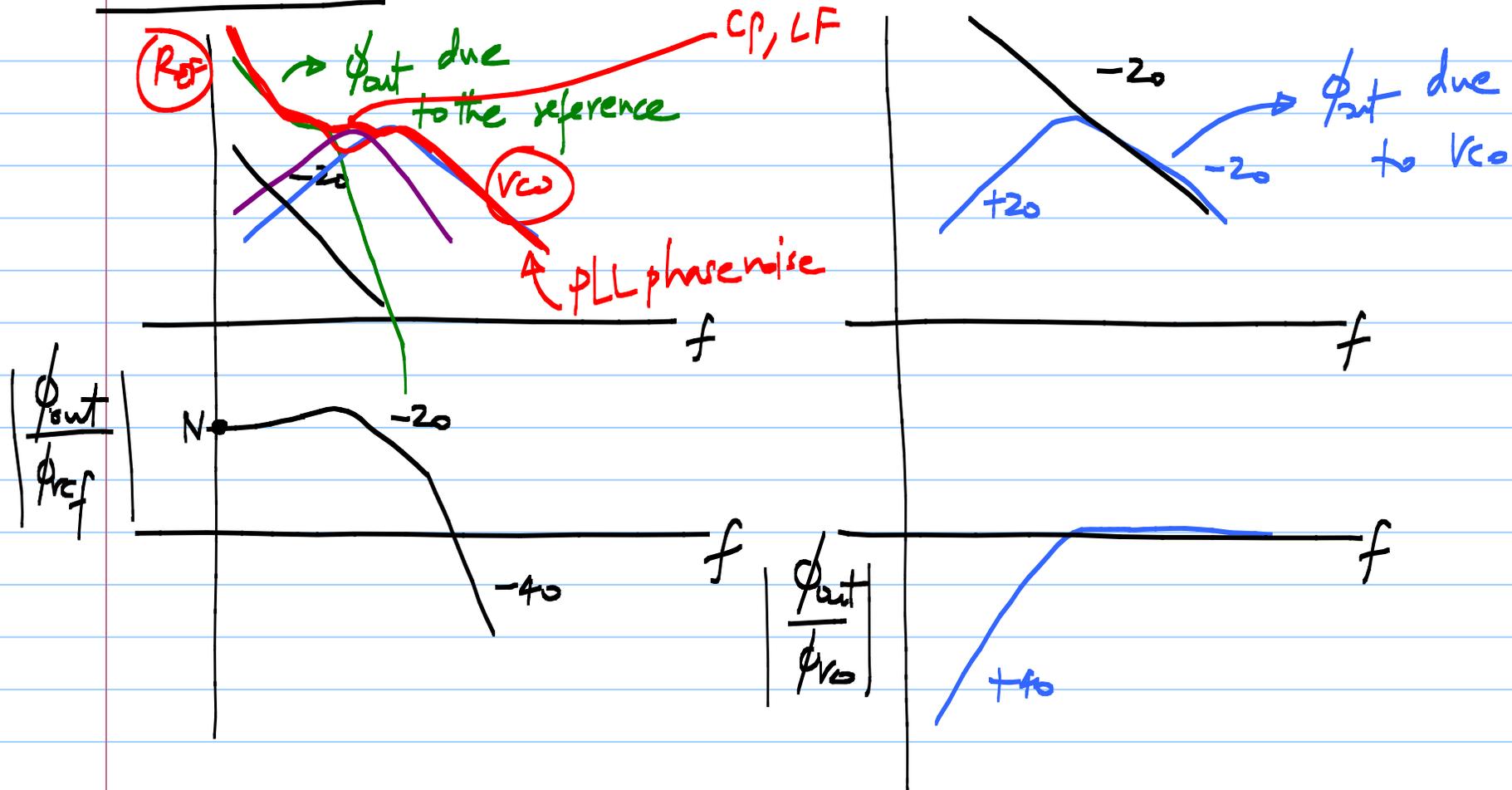


Lecture 52

PLL phase noise

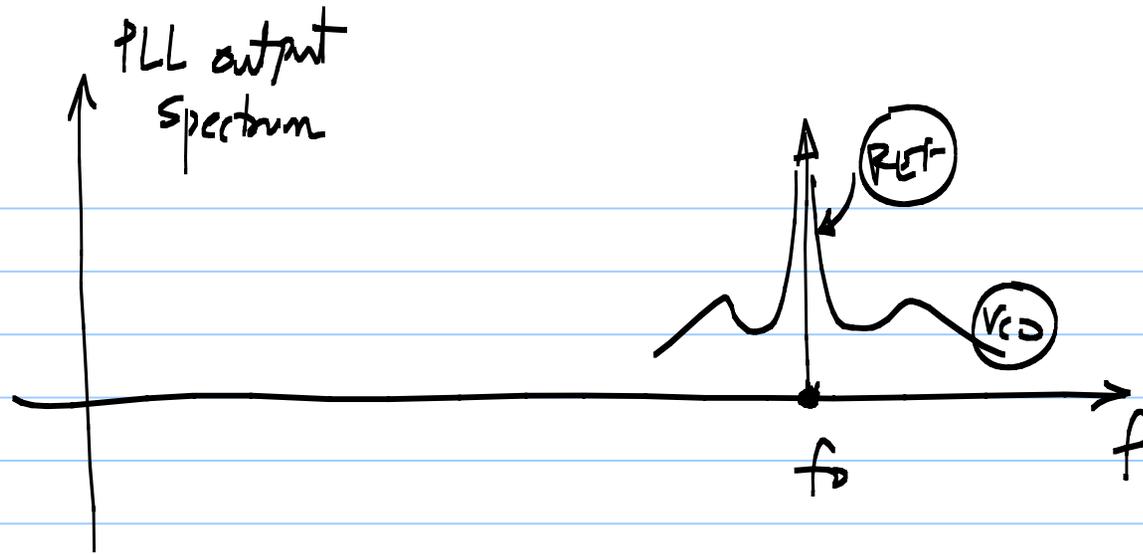




Voltage controlled oscillator

* L.C oscillators : cross coupled pair ✓
Colpitts, Hartley oscillators

* Ring oscillators :
• CMOS inverter ring oscillator
• current starved ring oscillator
• CML (differential) ring oscillator

LC oscillator:

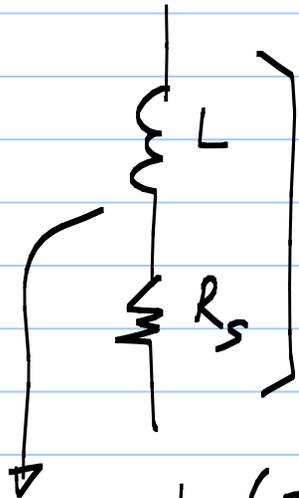


$$Z = R_s + j\omega L$$

$$Y = \frac{1}{R_s + j\omega L} = \frac{R_s - j\omega L}{R_s^2 + \omega^2 L^2} = \frac{R_s}{R_s^2 + \omega^2 L^2} - j \frac{\omega L}{R_s^2 + \omega^2 L^2}$$

If $Q \gg 1$ { $\omega L \gg R_s$ }

$$Q: \frac{\text{Im}(Z)}{\text{Re}(Z)} = \frac{\omega L}{R_s}$$
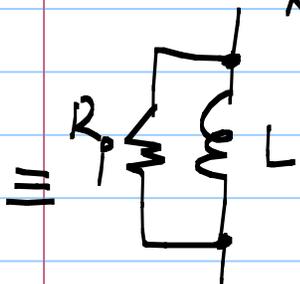
$$Y \approx \frac{R_s}{\omega^2 L^2} - \frac{j}{\omega L}$$



$$R_p = \frac{\omega_0^2 L^2}{R_s} = Q^2 R_s$$


$$R \quad \frac{1}{R_p} + \frac{1}{j\omega L}$$

$$Q = \omega L / R_s$$



≡

$$Q = R_p / \omega L$$

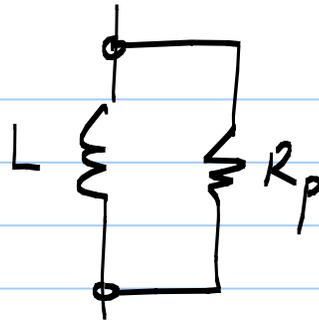


$$Q = \frac{1}{\omega C R_s}$$




≡


$$Q = \omega C R_p$$

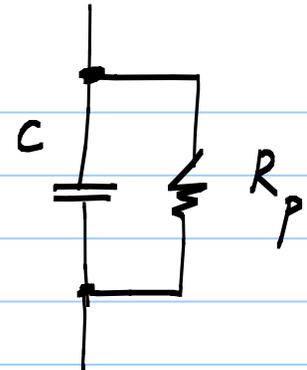

$$R_p = Q^2 \cdot R_s$$

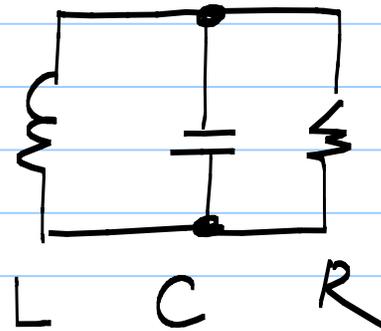

[loss of L, C]

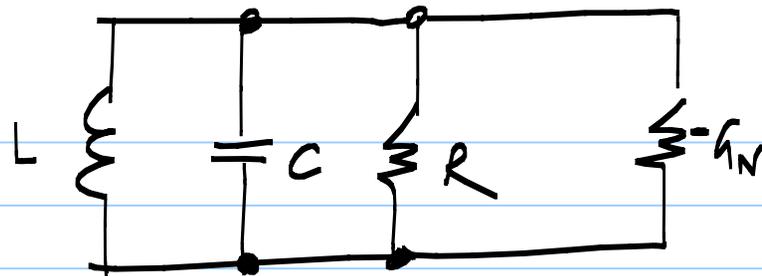


If $g_N = g_p$,
lossless LC

$$\frac{1}{R} = g_p$$

$g_N < g_p$: lossy ; oscillations die out




$g_N = g_p$: lossless ; sustained oscillations
 at a constant amplitude

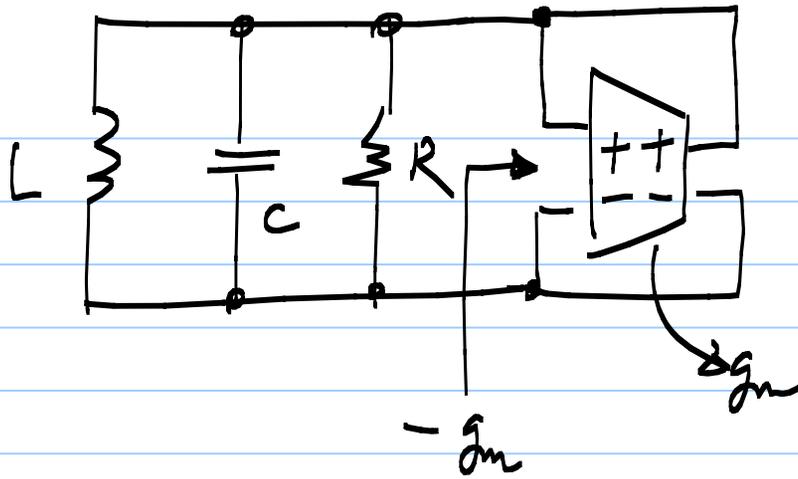$g_N > g_p$: regenerative ; Oscillations with
 increasing amplitude





$$g_m > g_p = \frac{1}{R}$$




For reliable start up

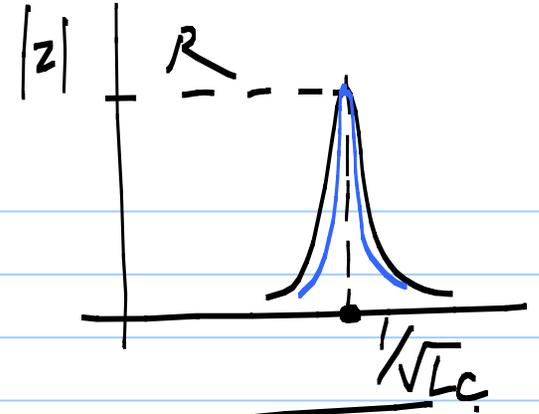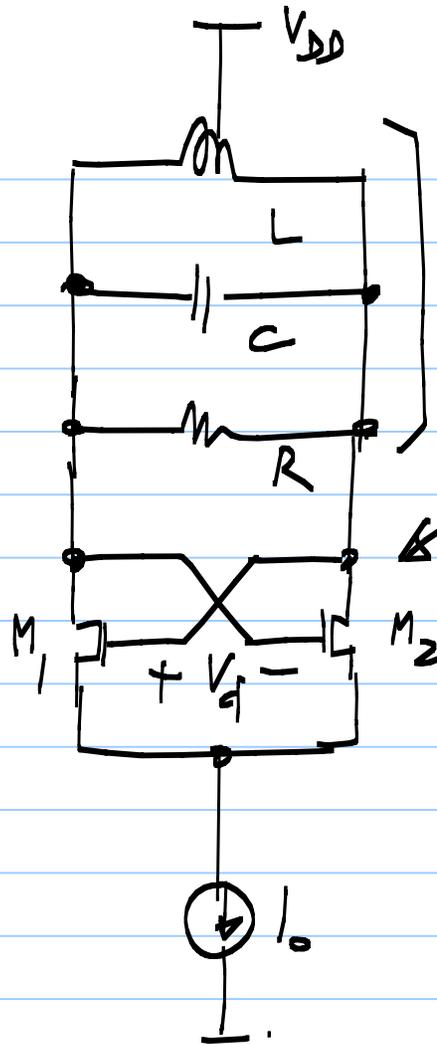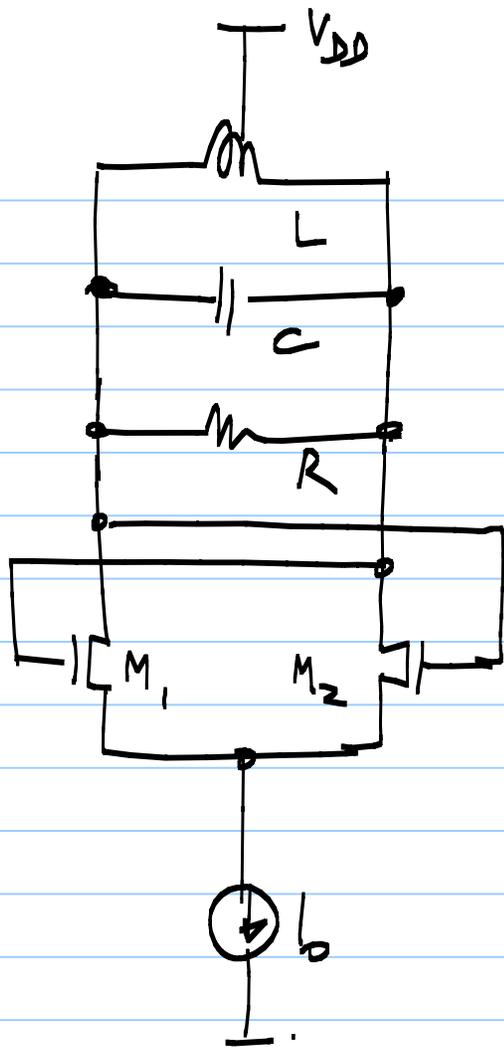

Cross coupled pair

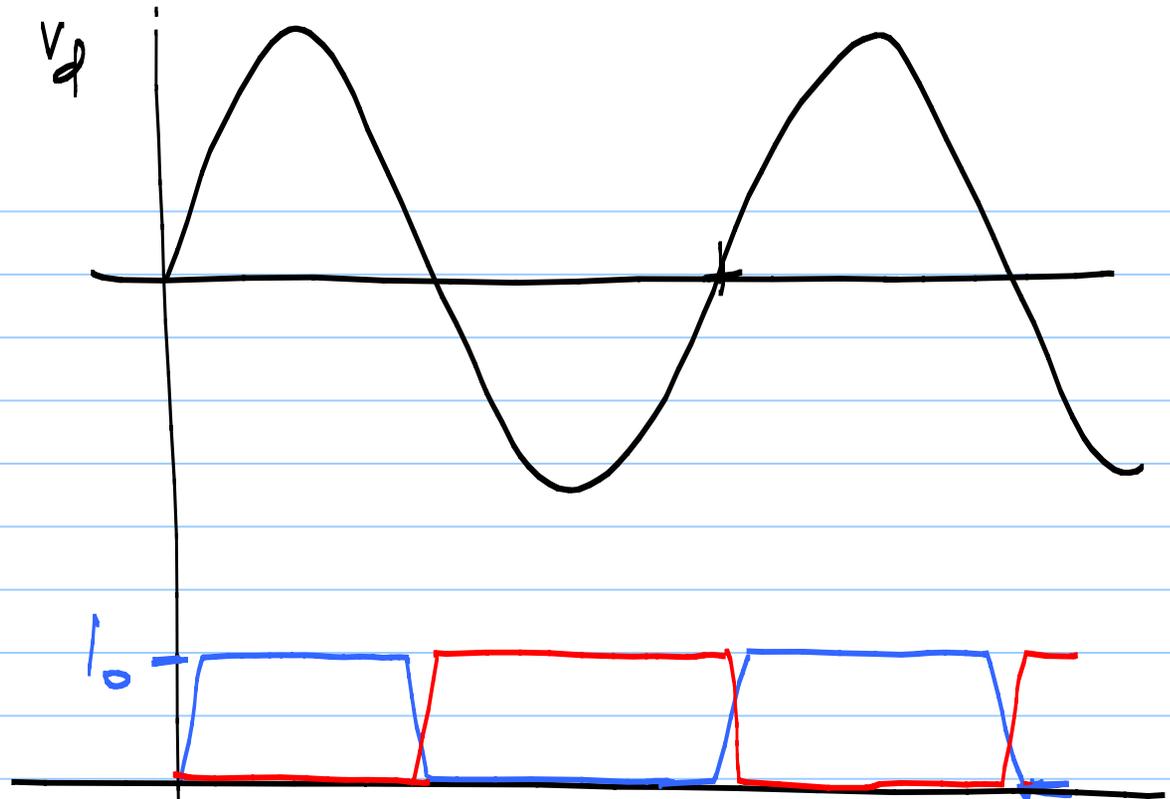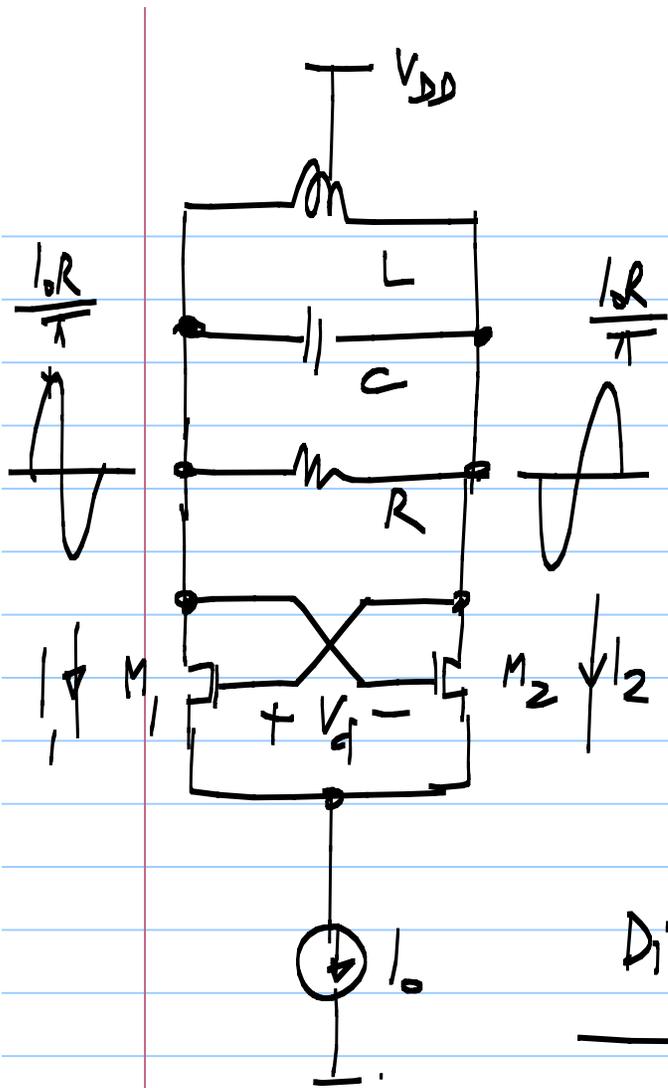

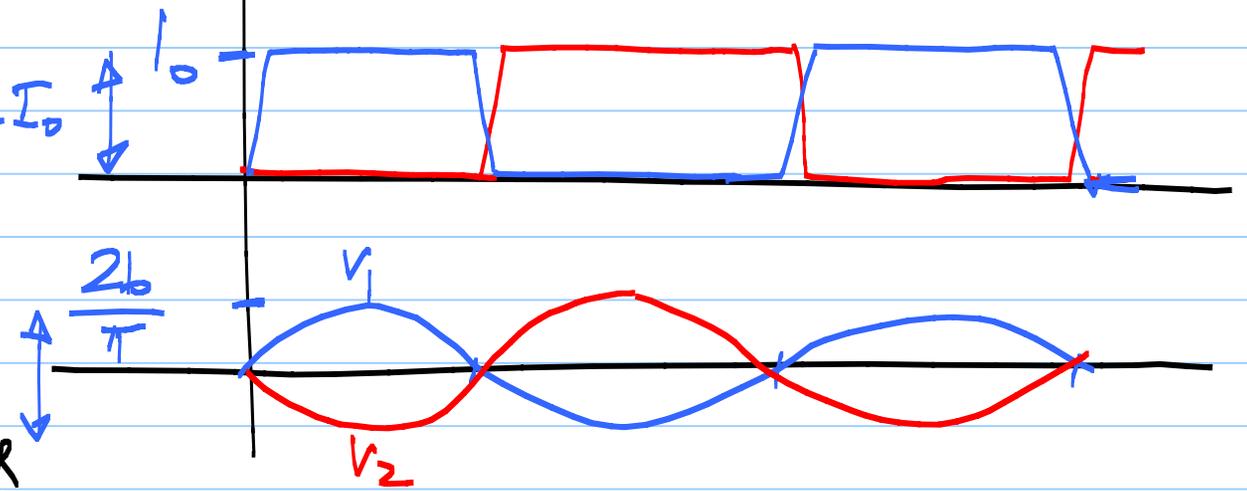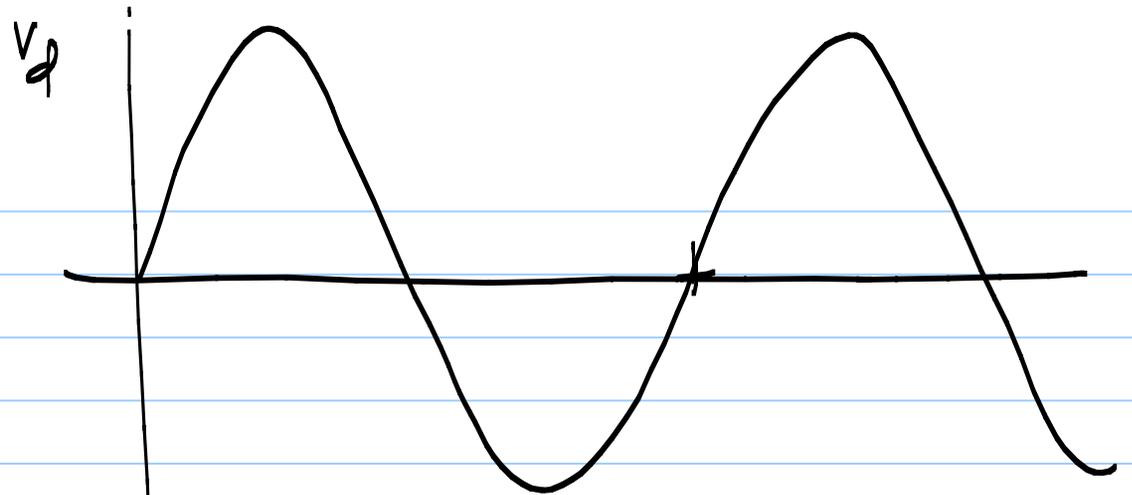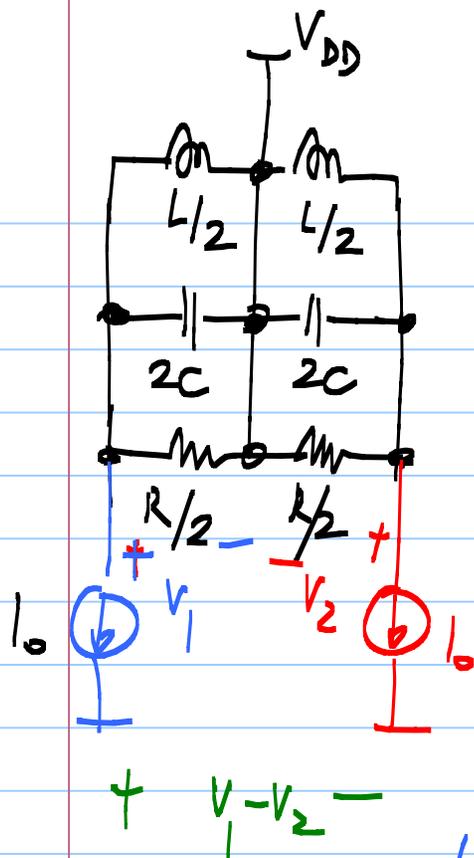Differential output: peak value of $\frac{2LR}{\pi}$
 $\frac{4LR}{\pi}$ Volts p-p



Amplitude of

$$v_1 : \frac{2I_0}{\pi} \cdot R/2$$

$$v_2 : \frac{2I_0}{\pi} \cdot R/2$$

$$\left(\frac{4}{\pi}\right) I_0$$

$$v_1 - v_2 : \frac{2I_0 R}{\pi}$$

Cross coupled pair LC oscillator:

* L, C for the desired frequency

$$f_0 = \frac{1}{2\pi\sqrt{LC}}; \quad L, C \text{ chosen based on}$$


- Quality factor,

- Area


$$* \text{ Amplitude} = \frac{4I_b R}{\pi} \cdot V_{pp} \rightarrow I_0$$

$$* g_m > G_p \rightarrow W/L$$


LC VCO:

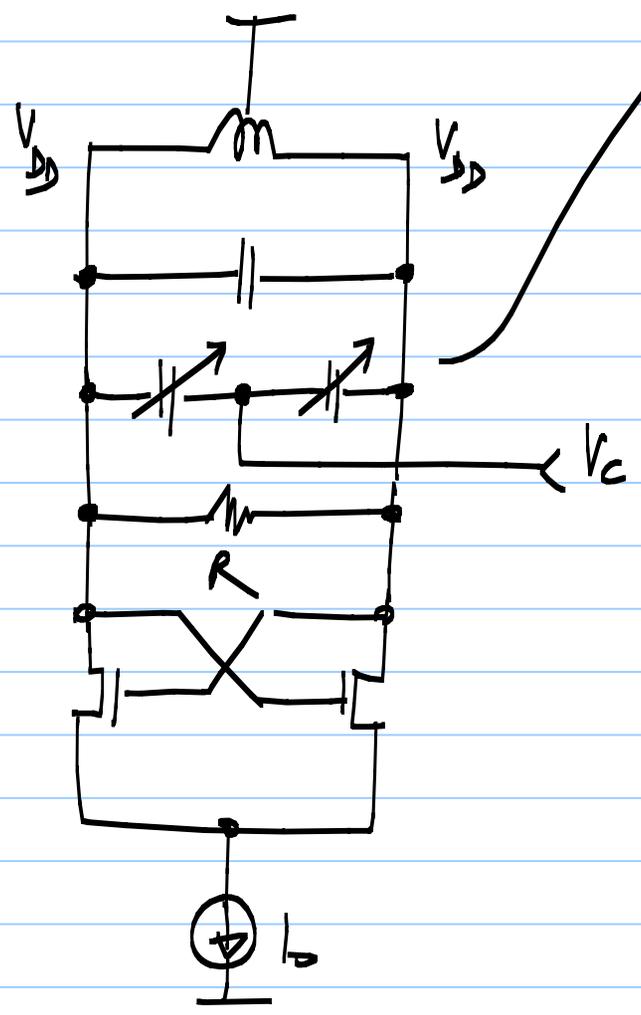


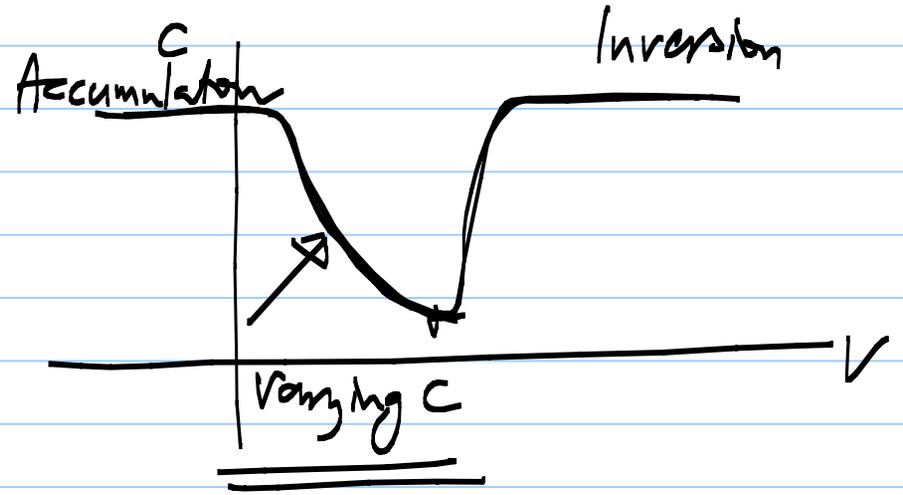
- variable capacitors (Varactors)
 - reverse biased p-n junctions
- MOS transistors



nMOS in an n-Well

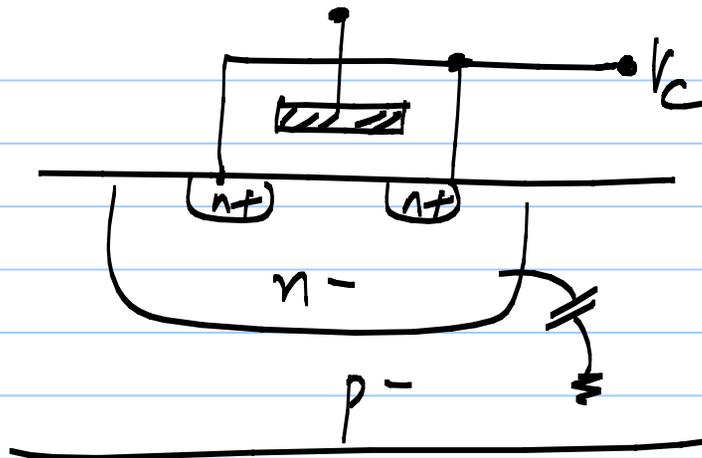


other variants:

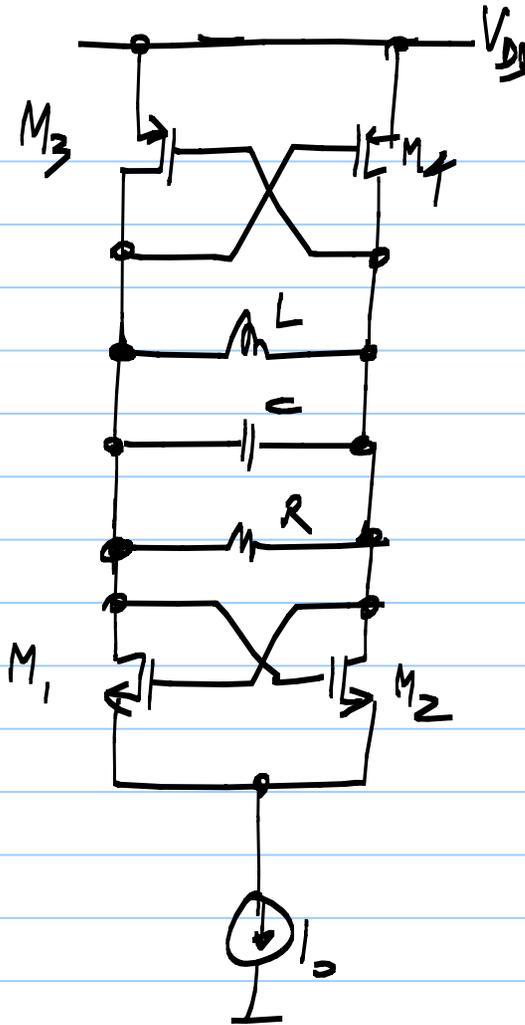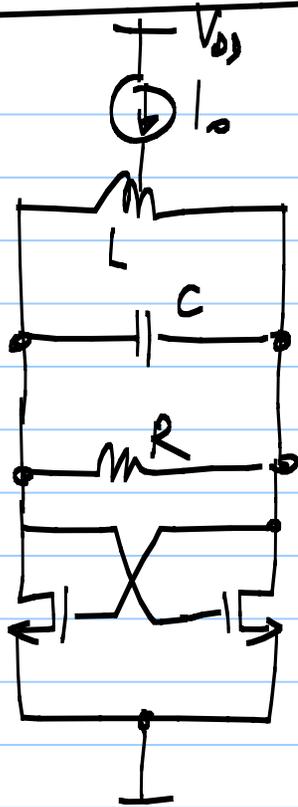

Ring oscillators:


odd # inverters

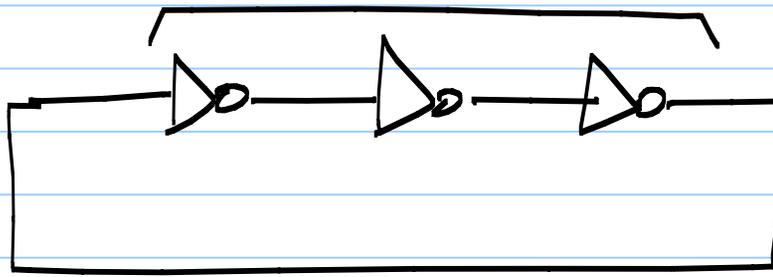

$$\text{Osc. period} = 2 \cdot N \cdot t_d$$


inverter delay

Inverter ring oscillator:

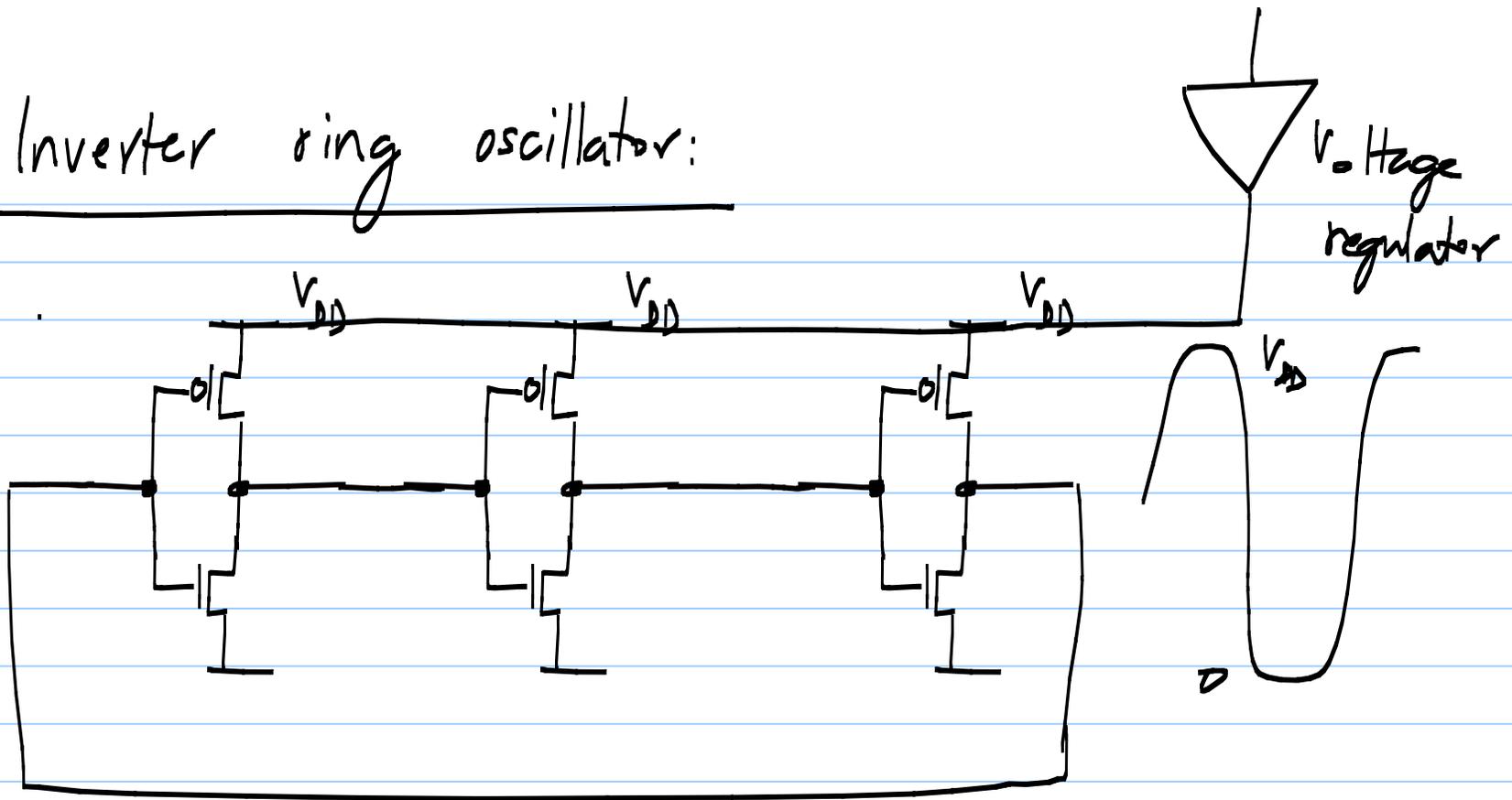



Osc. freq. \uparrow with reducing L
Phase noise \uparrow with reducing L

Current starved ring oscillator:

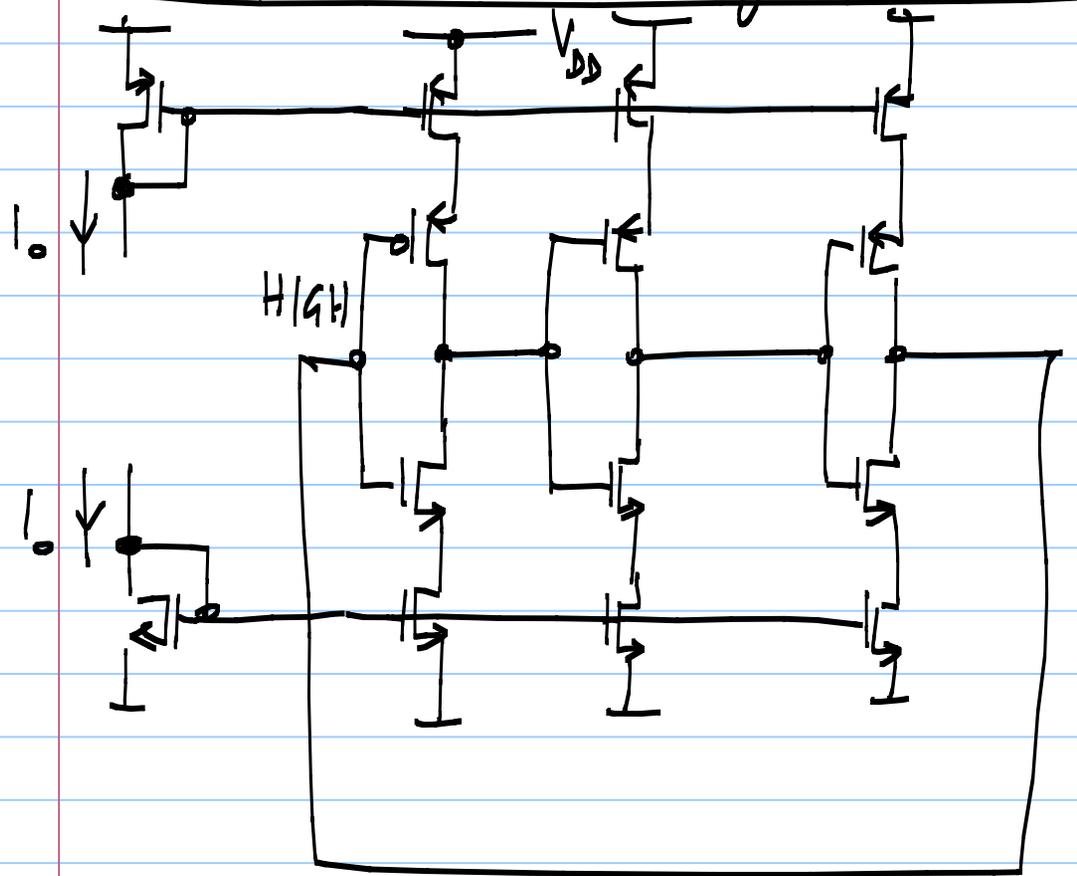


* Better (lower) sensitivity to the power supply

* I_0 controls the frequency.

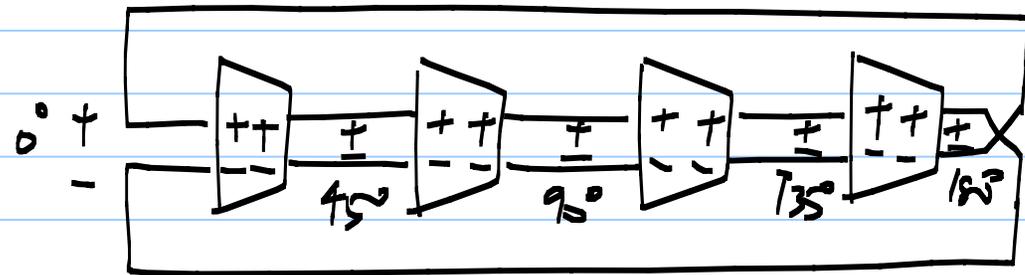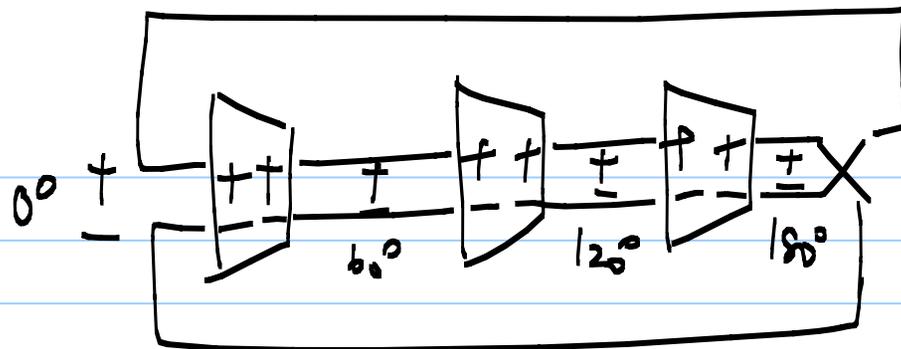

Can generate
quadrature
waveforms

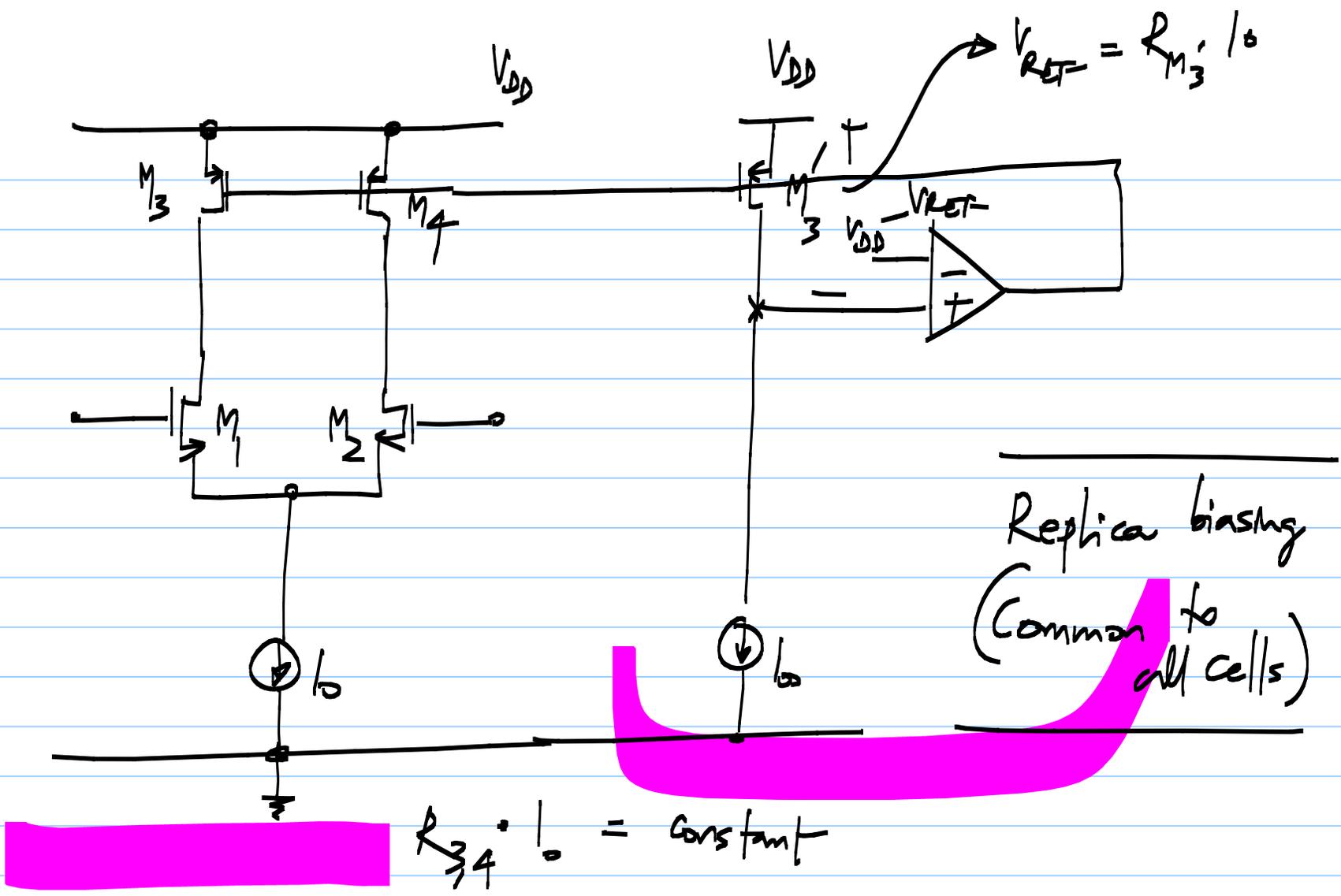

LC oscillators:

- * Low phase noise [Reduces with increasing Q]
- * Limited tuning range

Ring oscillators

- * Higher phase noise
- * Wider tuning range