
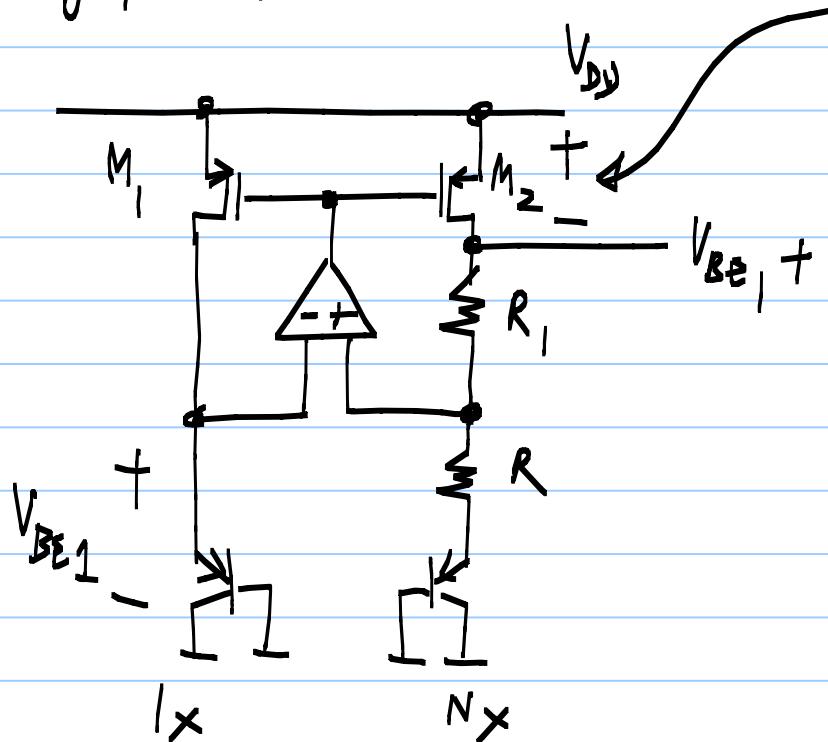


# Lecture 55

## Bandgap reference

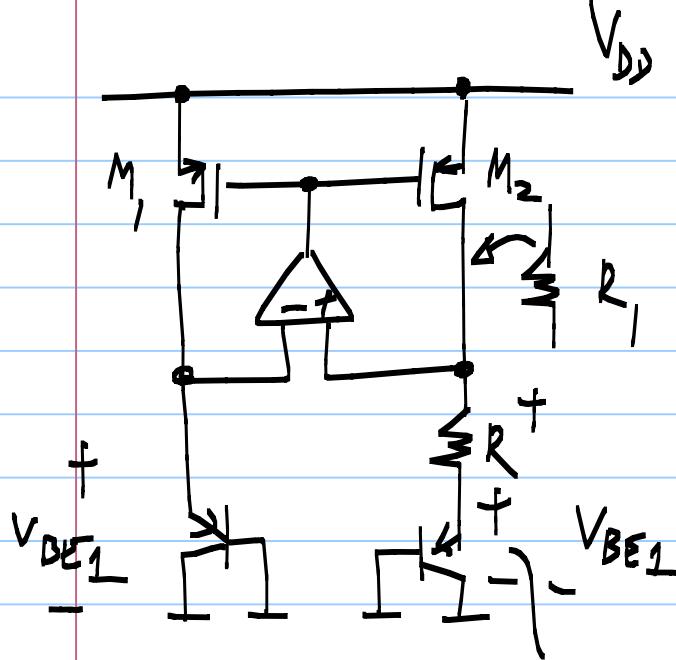


$$\begin{aligned}
 V_{DD, min} &= V_{out} + V_{DSAT, M_2} \\
 &= 1.2V + 0.2V = 1.4V \\
 V_{BE1} + V_T \ln(N) \cdot \frac{R_1}{R} &= \frac{E_{GP}}{2} \approx 1.2V
 \end{aligned}$$





Currents in  $M_{1,2}$ : PTAT

$$\left( V_T \frac{\ln N}{R} \right)$$

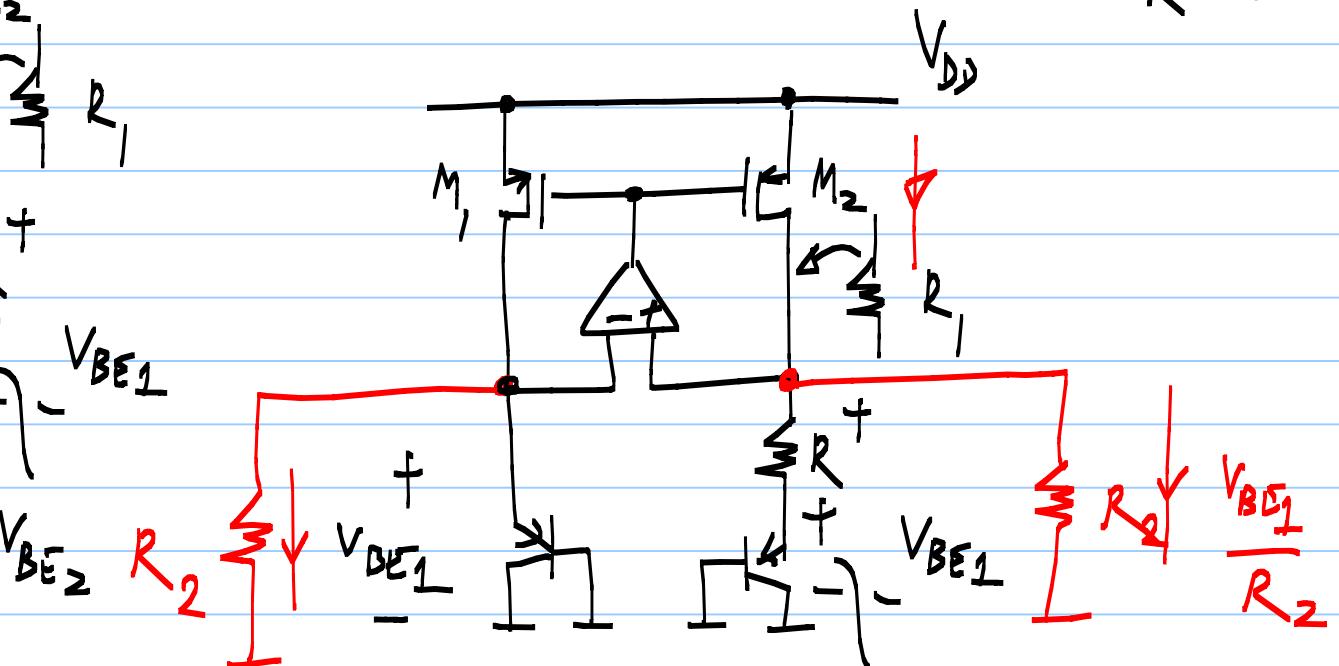

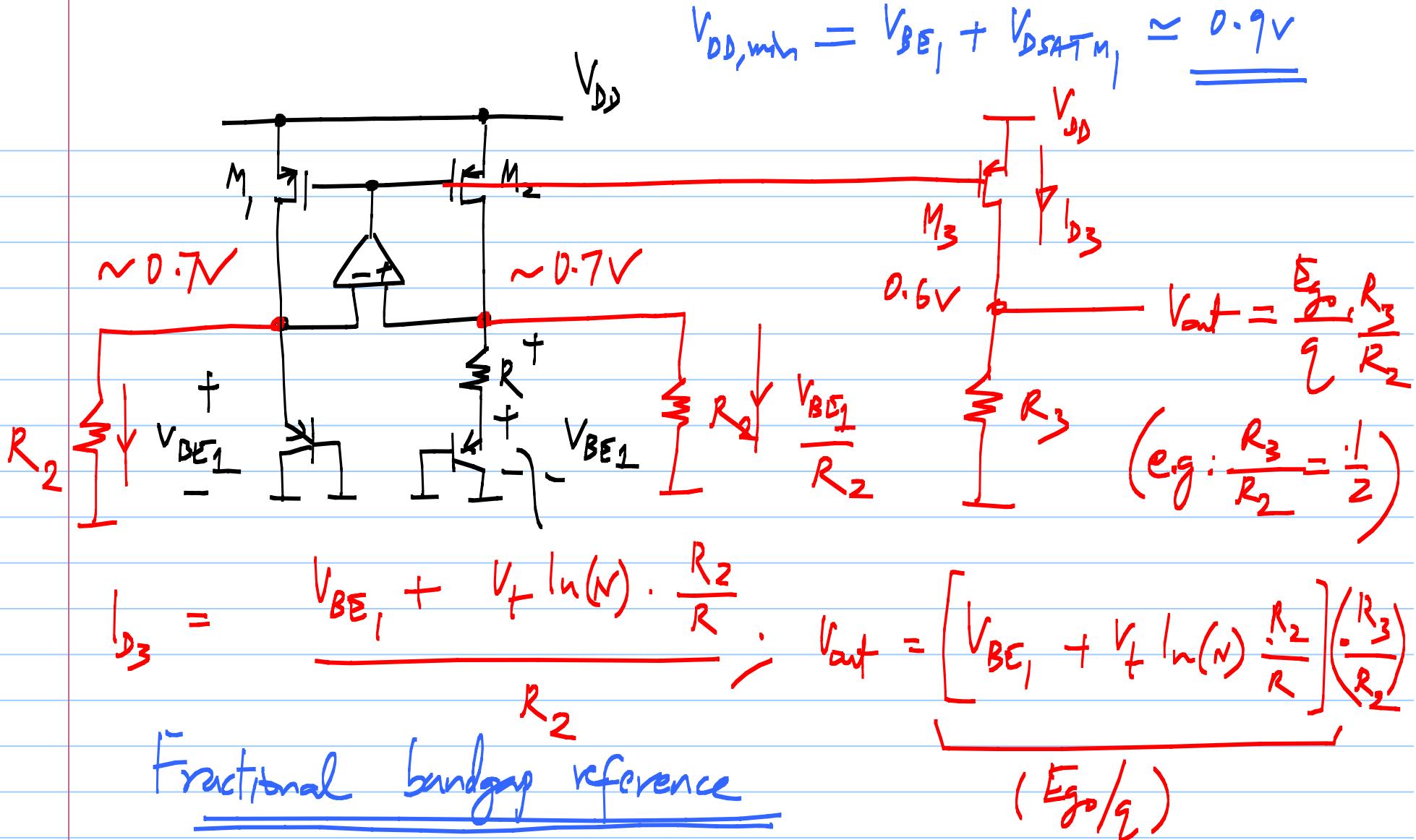Currents in  $M_{1,2}$ :  $\frac{V_T \ln(N)}{R} + \frac{V_{BE1}}{R_2} = \frac{V_{BE2} \left[ V_{BE1} + V_T \ln(N) \frac{R_2}{R} \right]}{R_2}$



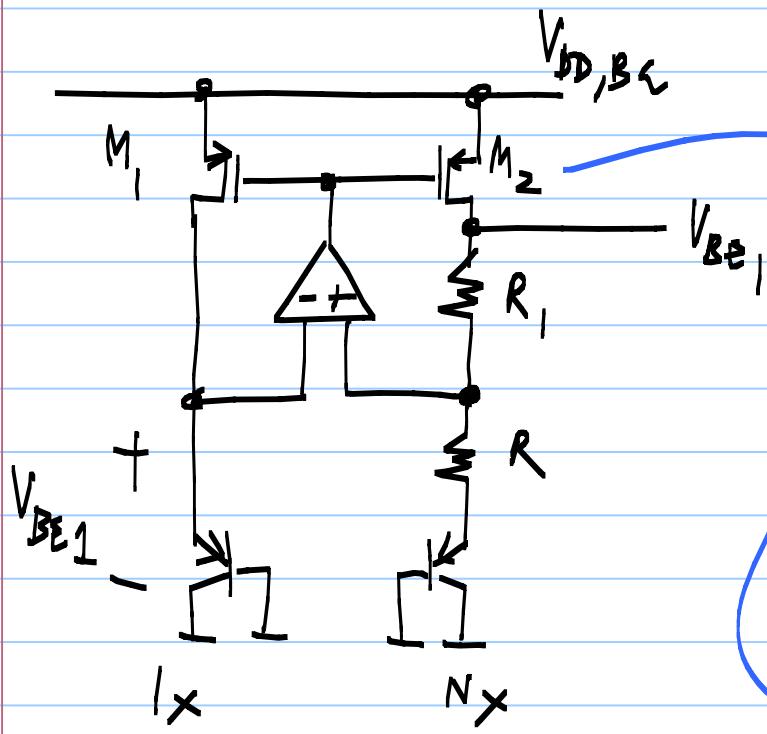


$M_{1,2}$  : different  $V_{SD}$

different

Cascode current mirror


\*  $V_{DD,BQ}$  : regulated

Reducing Ps sensitivity

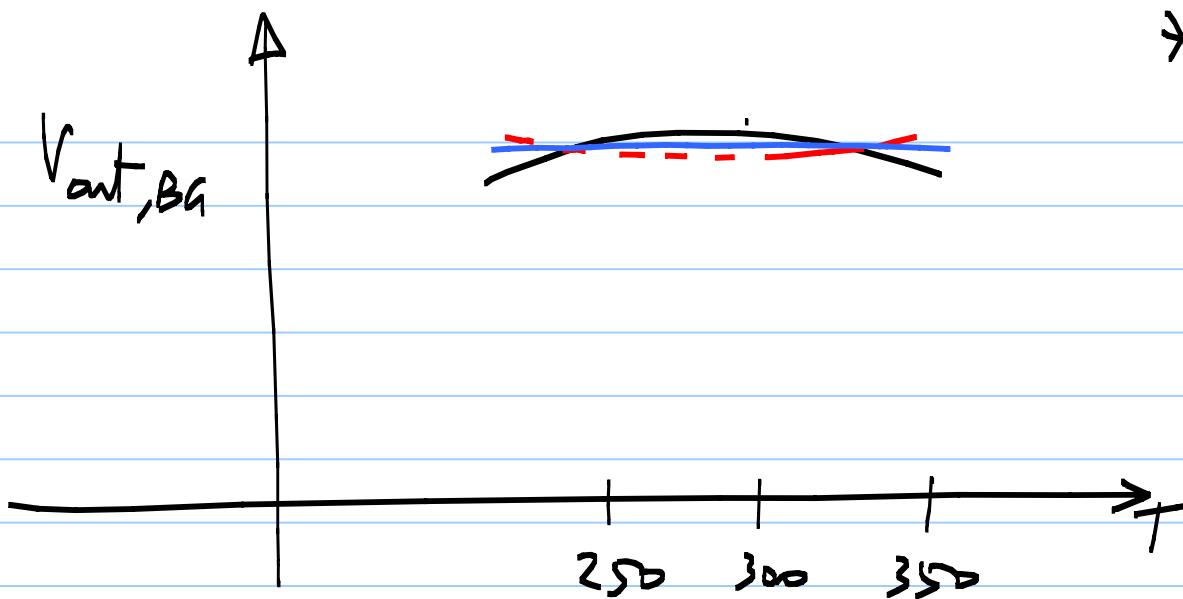

\* For reducing variations with temperature even further, use curvature compensation

## Voltage regulators:

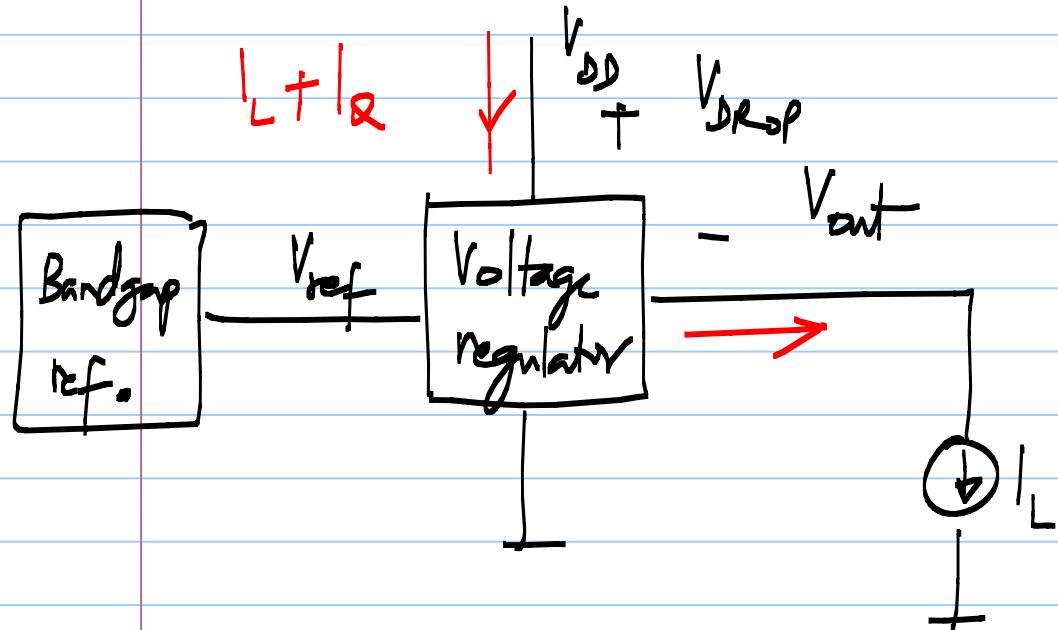


$$P_{out} = V_{out} \cdot I_L$$

$$P_{in} = V_{DD} \cdot (I_L + I_Q)$$

$$\eta = \frac{P_{out}}{P_{in}} = \frac{V_{out}}{V_{DD}} \cdot \frac{I_L}{I_L + I_Q}$$

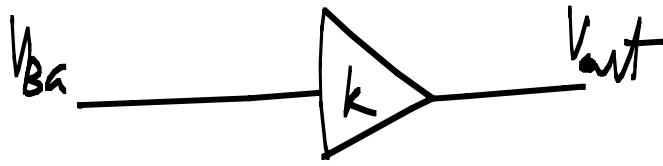
$$= \frac{V_{out}}{V_{out} + V_{drop}} \cdot \frac{I_L}{I_L + I_Q}$$



## Voltage regulator:

- \* Feedback controlled voltage source with a low  $R_{out}$
- \* Scaled version of the bandgap voltage
- \* "swing limit": must be close to  $V_{DD}$
- \*  $I_L > 0$  need be supported

\* Low dropout

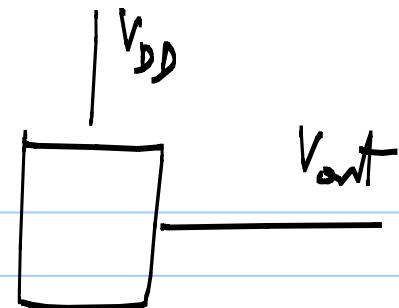

\*  $\frac{\Delta V_{out}}{\Delta I_L} = R_{out}$  must be small (load regulation)

\*  $\frac{\Delta V_{out}}{\Delta V_{DD}}$  : must be small (line regulation)

\* Output voltage must be accurately defined

\* Transient  $I_L$  (step) :  $\Delta V_{out}$  must be small


\*  $\left| \frac{V_{out}(f)}{V_{DD}(f)} \right|$  Transfer function (small signal)  
from  $V_{DD}$  to  $V_{out}$

$\ll 1$

$$\frac{1}{PSRR}$$

Power supply rejection  
ratio

Low dropout:

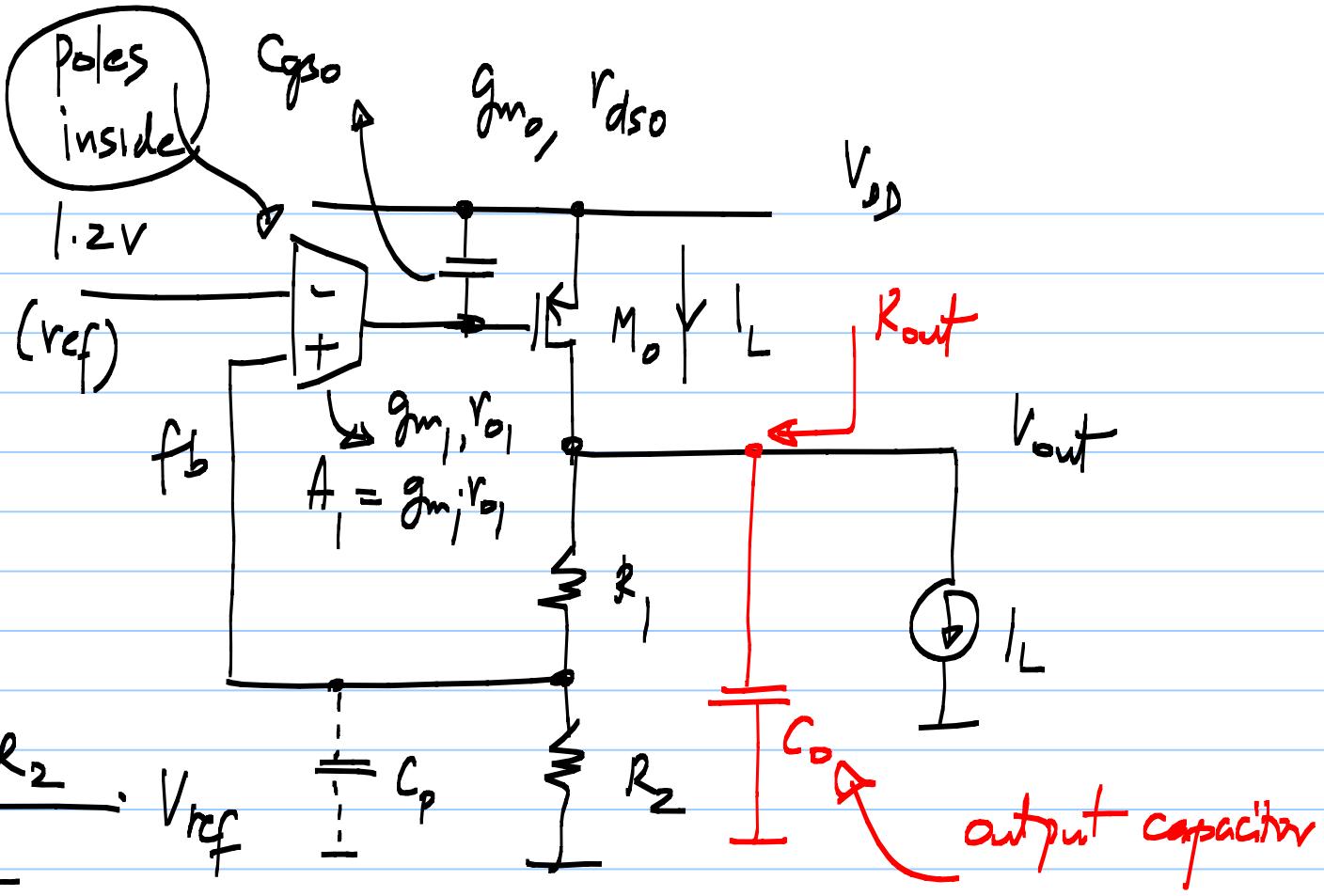

$$V_{out,L} = 2.4V$$

$$V_{ref} = 1.2V$$

In steady state,

$$V_{out} = \frac{R_1 + R_2}{R_2} \cdot V_{ref}$$

$A_D$ : dc loop gain:

$$R_{out} = \frac{r_{ds}}{1 + A_D}$$


gain, transconductor:  $g_{m_1} \cdot r_{o_1}$

$$M_o : g_{m_0} \left[ r_{ds_0} \parallel (R_1 + R_2) \right] \approx g_{m_0} \cdot r_{ds_0}$$


$$A_o = \underline{g_{m_1} r_{o_1} \cdot g_{m_0} \cdot r_{ds_0} \left( \frac{R_2}{R_1 + R_2} \right)}$$

$R_{out}$  small if  $A_o$  is large

| Step from low to high values  $\rightarrow$  large  
Change in the output.

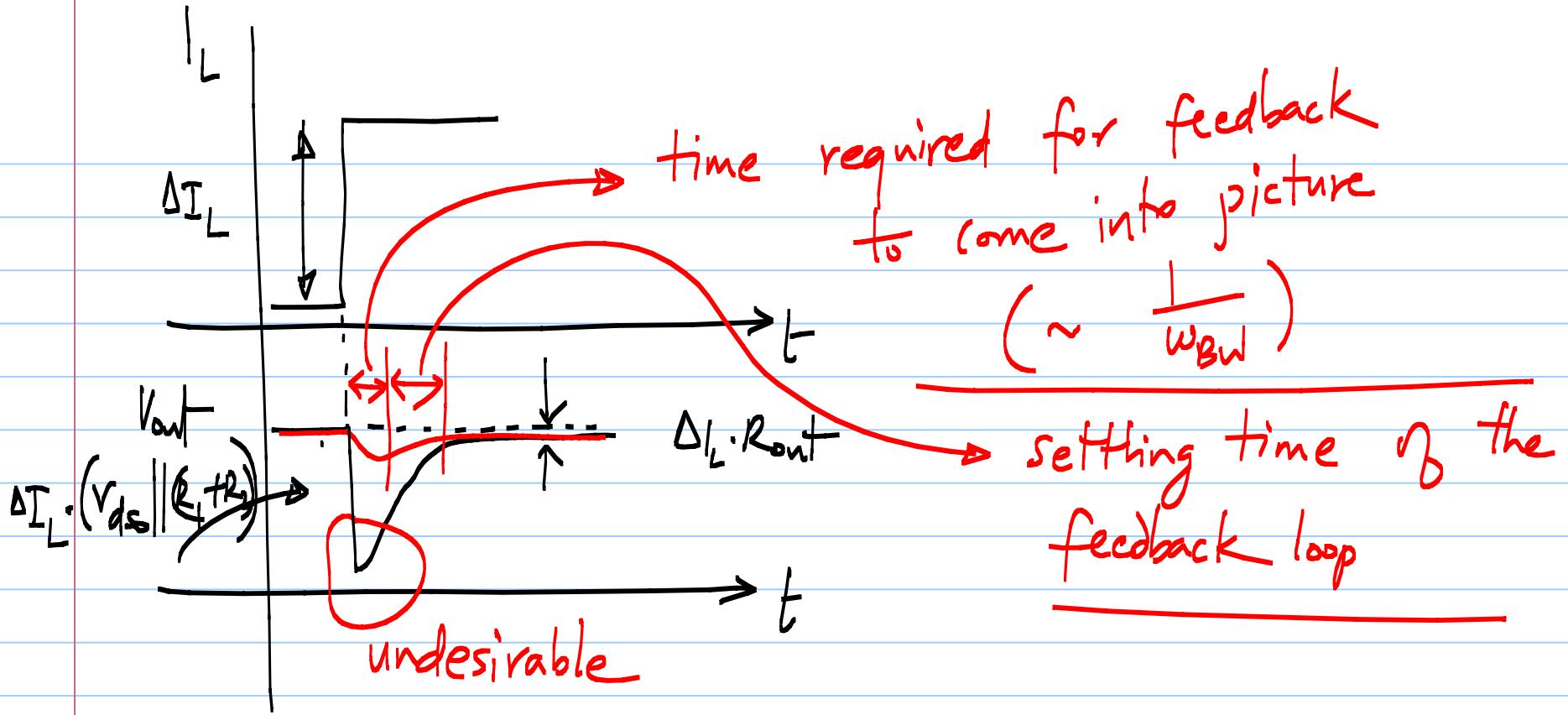

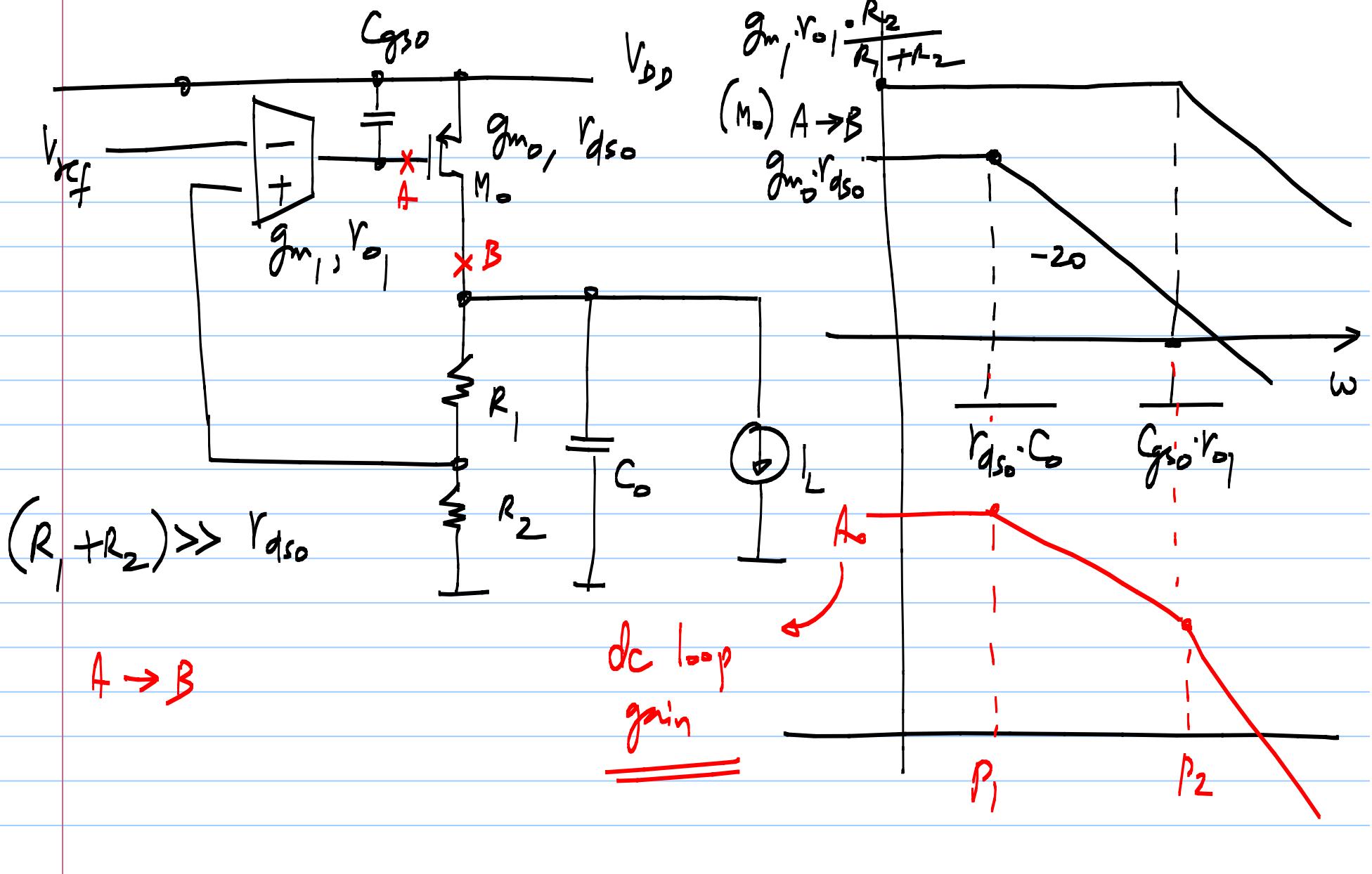Poles due to (i)  $s$   
 (ii)  $C_{gs}$   
 $\times$  (iii) poles in  $g_m$ , ; feedback divider



$$P_2 > \omega_{n,loop}$$

$$\left[ \frac{1}{C_{g_{SO}} \cdot r_{o1}} \right] > g_{m1} r_{o1} \cdot g_{mo} r_{ds0} \left( \frac{R_2}{R_1 + R_2} \right) \frac{1}{r_{ds0} C_0}$$

