
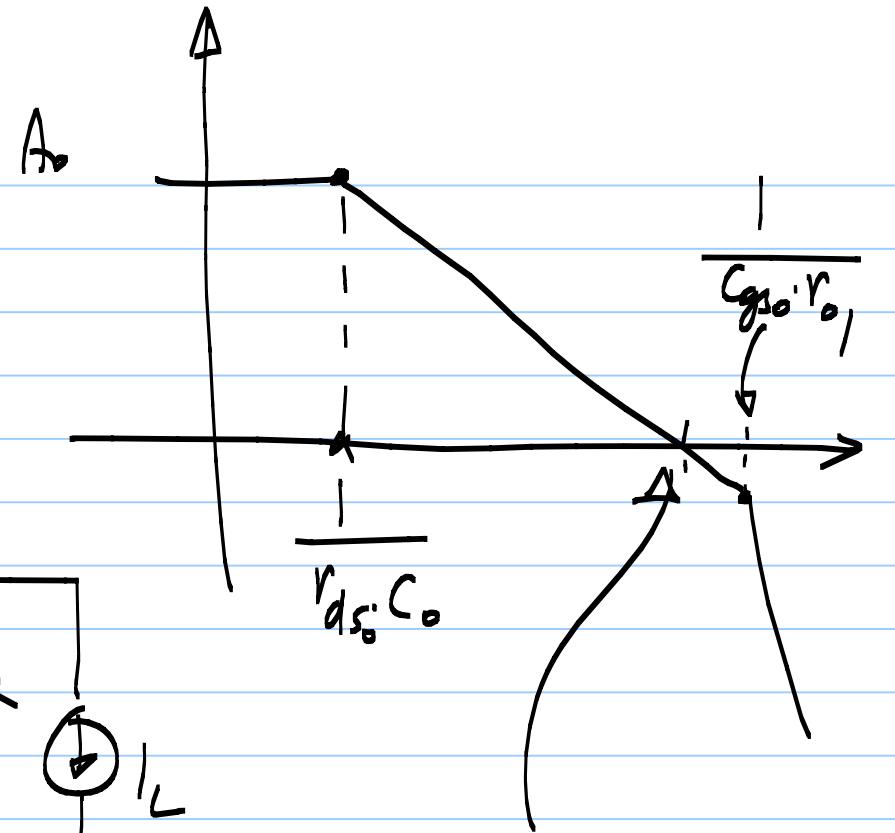


Voltage regulators:

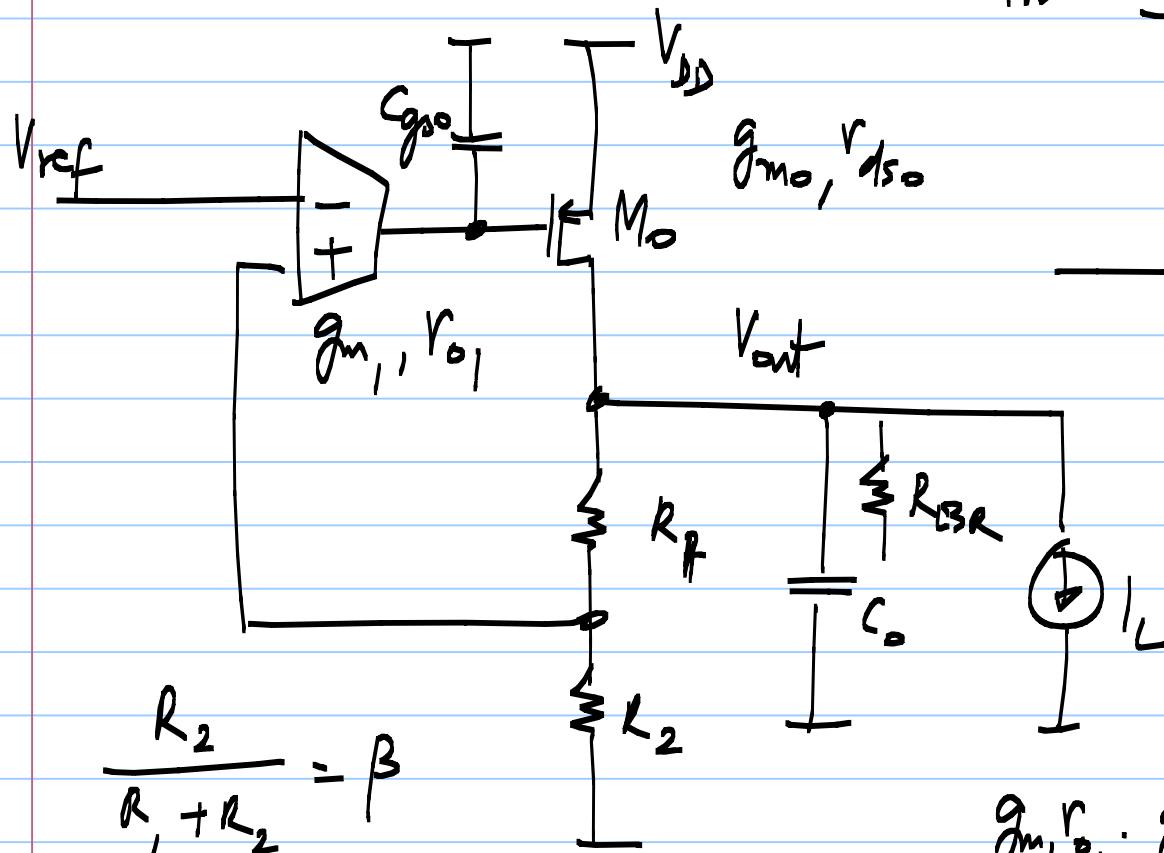

$$\frac{R_2}{R_1 + R_2} = \beta$$

$$\omega_n, \text{loop} = \frac{1}{g_{m1} r_{o1} \cdot g_{m0} r_{ds0} + \beta} = \frac{1}{r_{ds0} C_0}$$

For good phase margin

$$\rho_2 > \omega_{v, \text{loop}}$$

$$\frac{|}{C_{GS} r_o} > g_m r_o \cdot \frac{g_m}{C_o} \cdot \beta$$

Worst case
is $\approx |_{L, \max}$

$$r_o < \sqrt{\frac{C_o}{C_{GS}} \cdot \frac{|}{g_m \cdot g_m \cdot \beta}}$$

$$A_v = g_m \cdot r_o \cdot g_m \cdot r_{ds} \cdot \beta =$$

g_m, r_{ds} vary widely because of variations in

$$|_L \quad g_m = \sqrt{\frac{2|_L}{MCox W/L}}$$

$$r_{ds} = \frac{|}{\lambda |_L}$$

limited because of the constraint on r_o

$$A_v = g_{m_1} r_{o_1} \cdot g_{m_0} \cdot r_{ds_0} \cdot \beta$$


$$= g_{m_1} \sqrt{\frac{C_o}{C_{gs_0}}} \frac{1}{g_{m_1} g_{m_0} \beta} \cdot g_{m_0} \cdot r_{ds_0} \cdot \beta$$


$$= \sqrt{\frac{C_o}{C_{gs_0}}} \cdot \sqrt{g_{m_1} g_{m_0} \beta} \cdot r_{ds_0}$$


* Upper limit on A_v due to upper limit on r_{o_1}

(stability constraint)

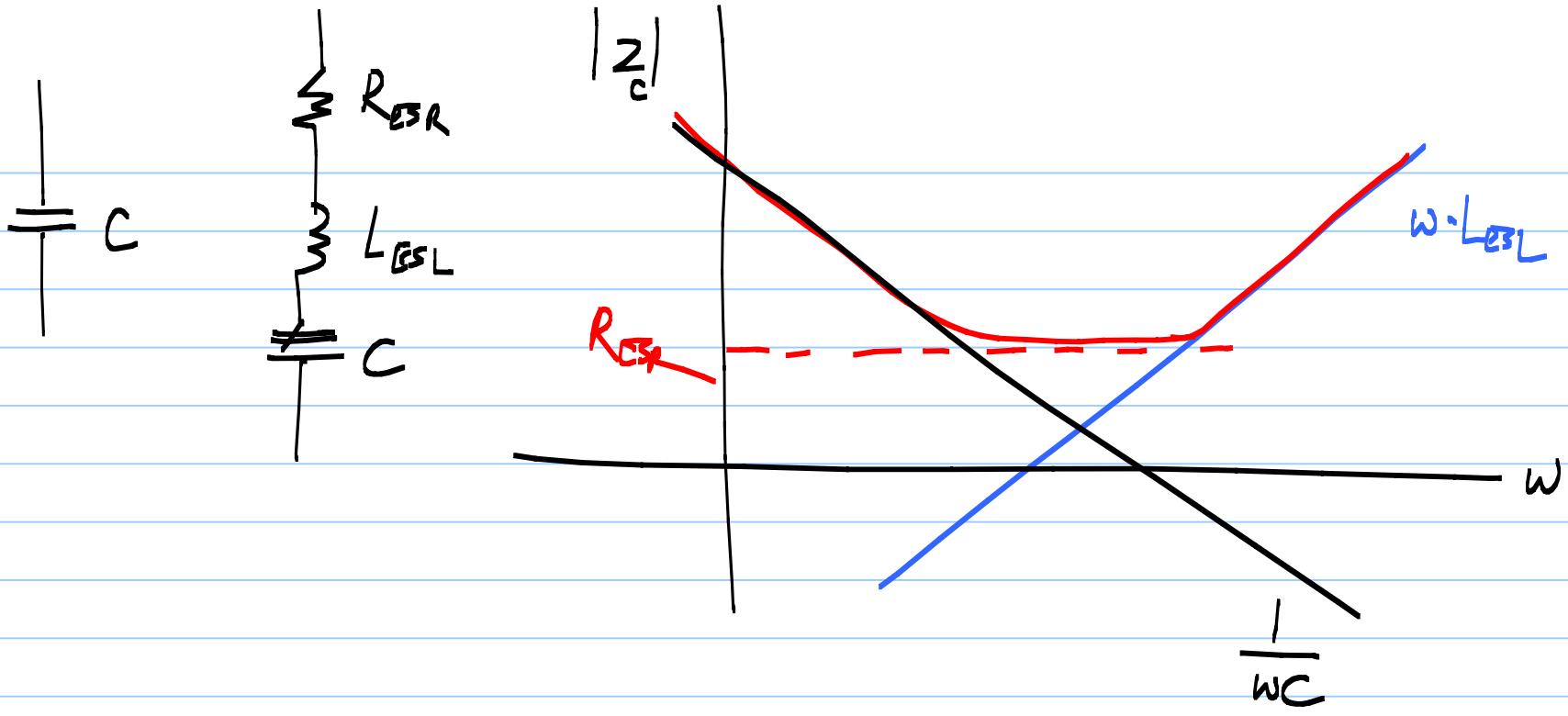
$$\Rightarrow R_{out} = \frac{r_{ds_0}}{1 + A_v} \quad \text{cannot be reduced indefinitely.}$$



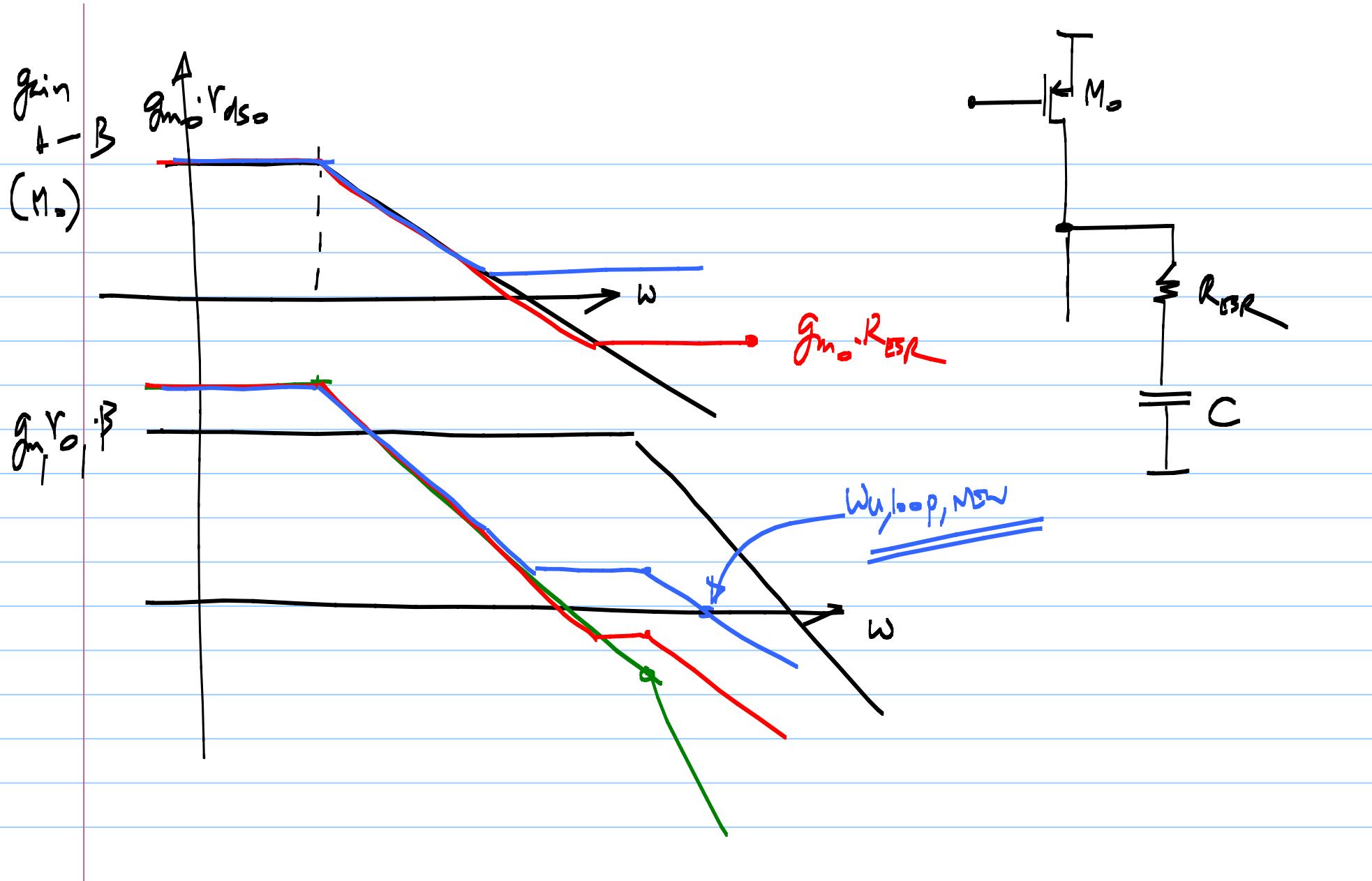

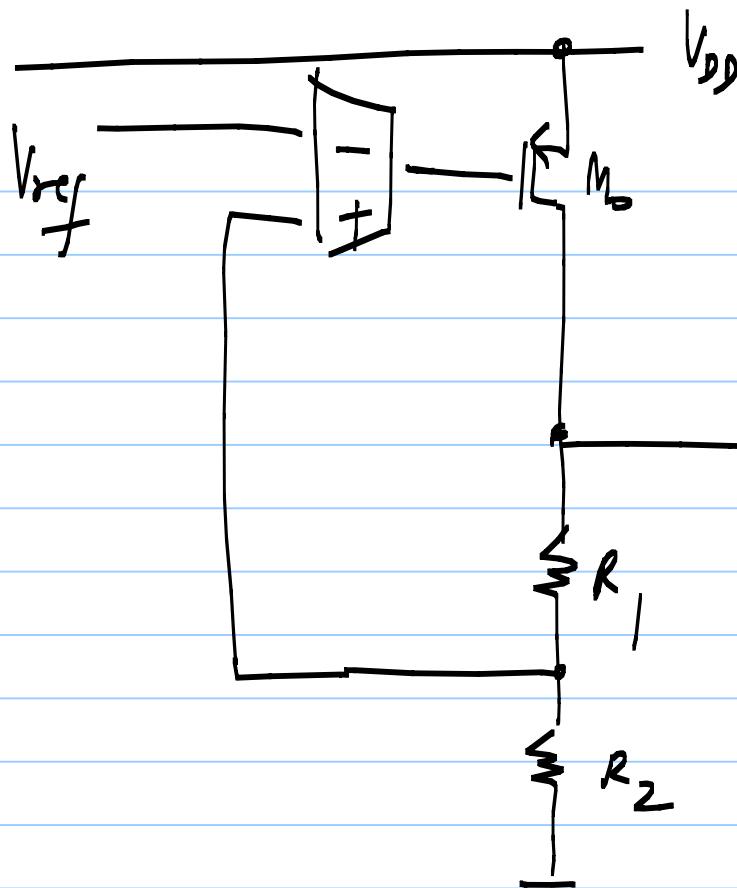


Gain
of M_2
($\rightarrow \Delta$)

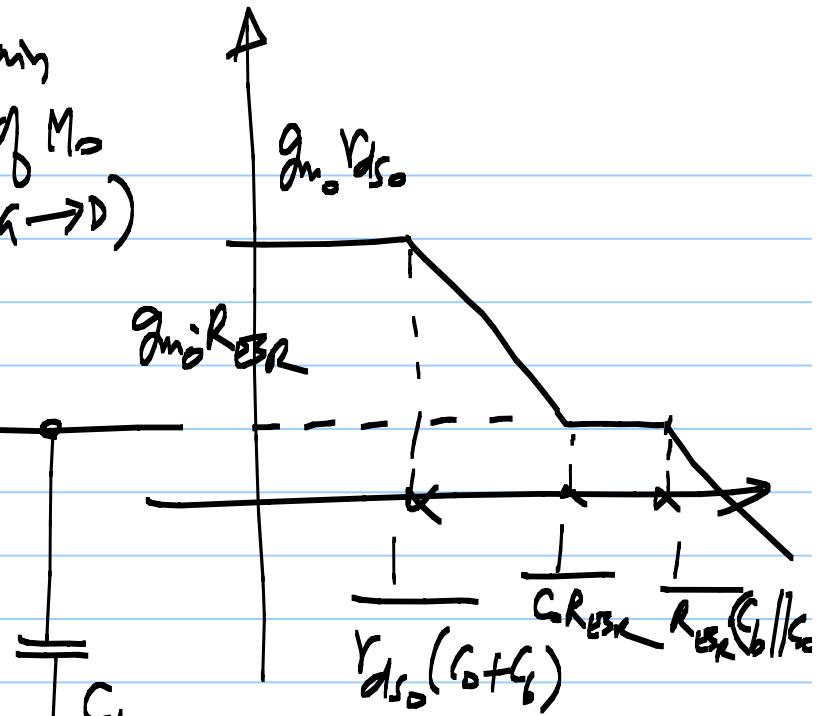



$$\frac{1}{r_{ds0}(C_0 + C_b)}$$

$$\frac{1}{C_R R_{BSR}} \parallel \frac{1}{R_{BSR} (C_b || C_L)}$$

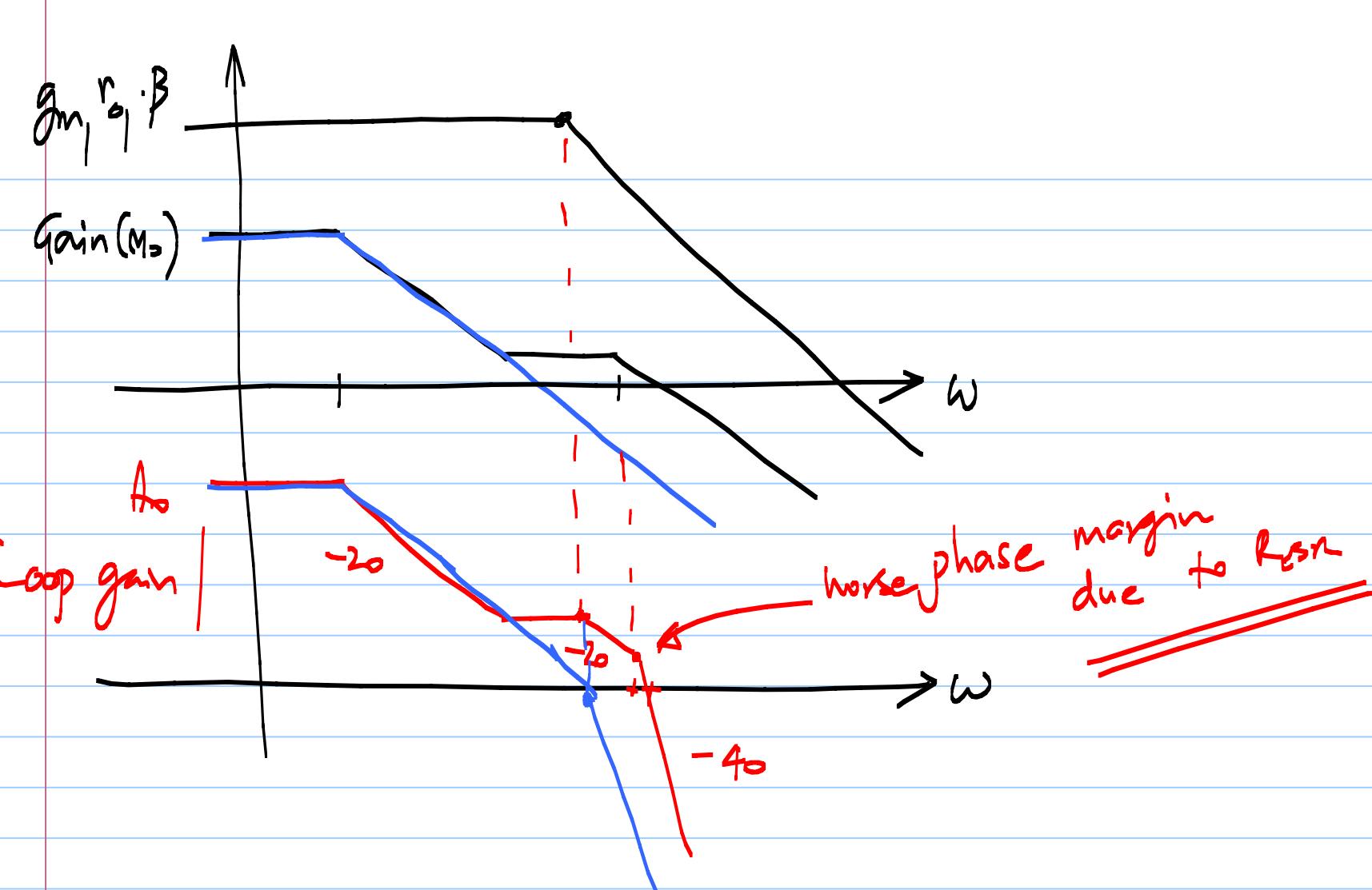C_b : smaller than C_0
physically smaller — smaller ESR



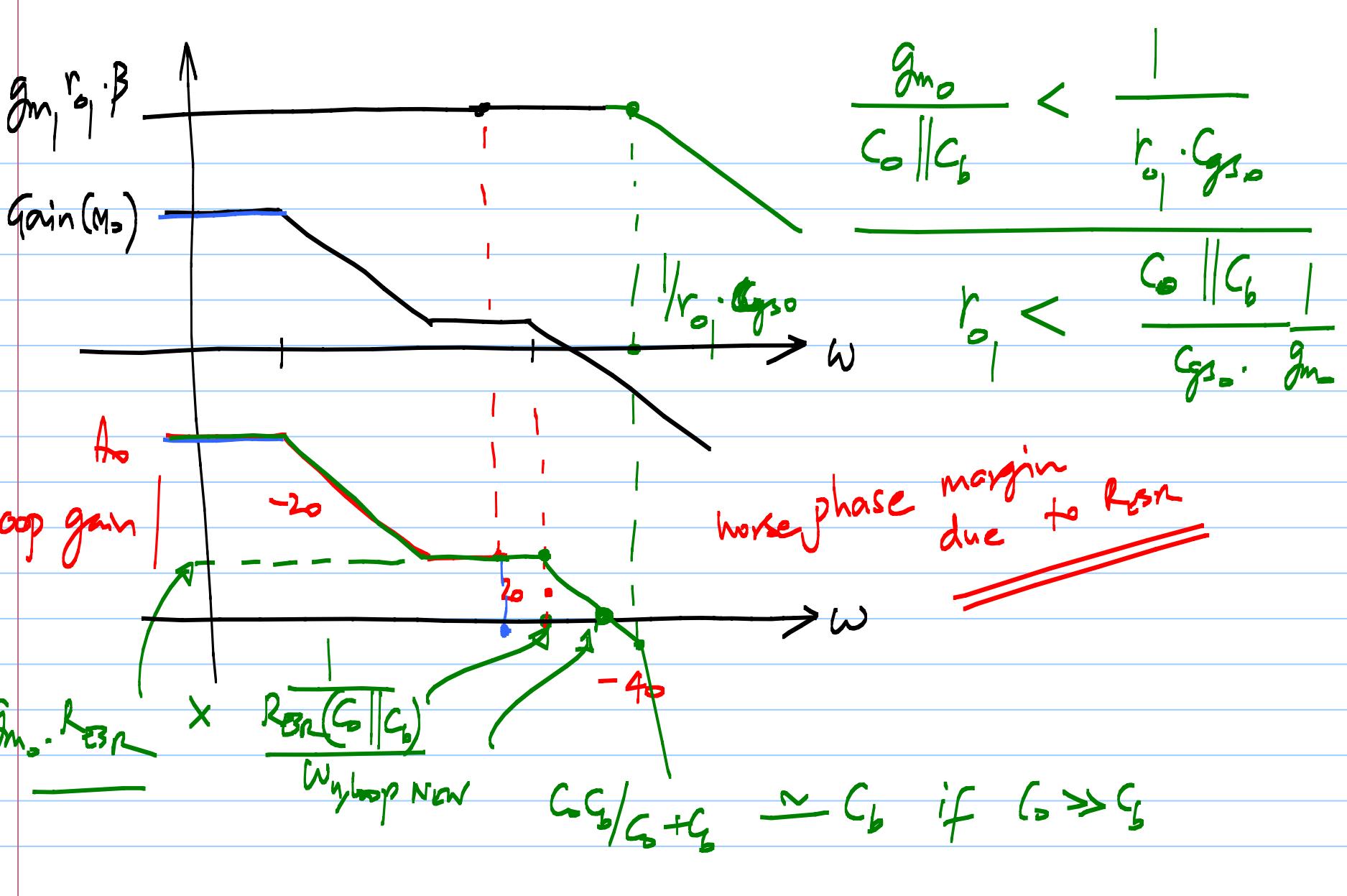

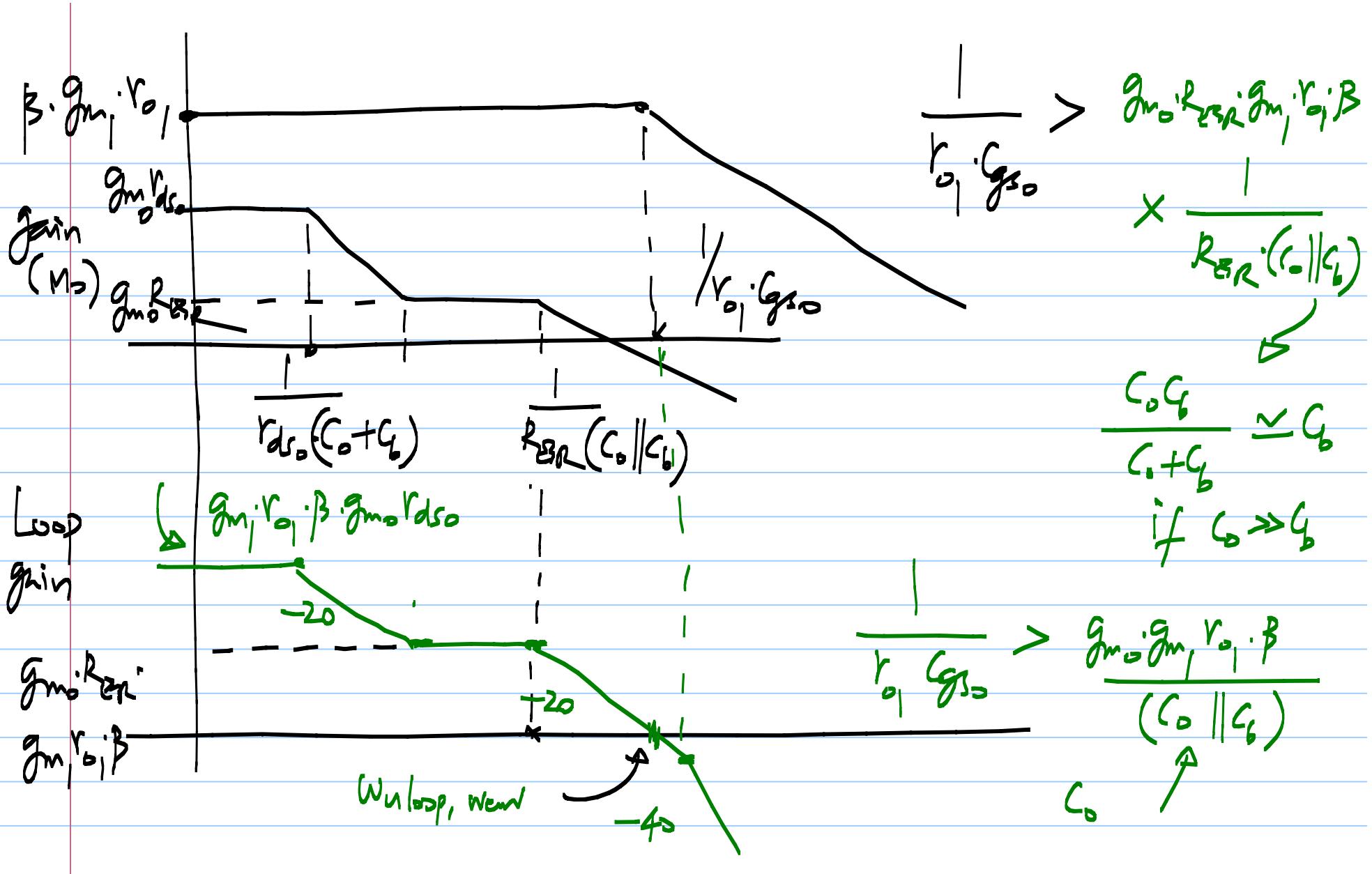

$$r_{o_1} < \sqrt{\frac{C_o || C_b}{C_{gs_0}} \cdot g_m, g_{m_0} \cdot \beta}$$

new limit


$$r_{o_1} < \sqrt{\frac{C_o}{C_{gs_0}} \cdot g_m, g_{m_0} \cdot \beta}$$


old limit

* Constraint on r_{o_1} due to stability


* \Rightarrow Constraint on dc loop gain

& R_{out} (load regulation)

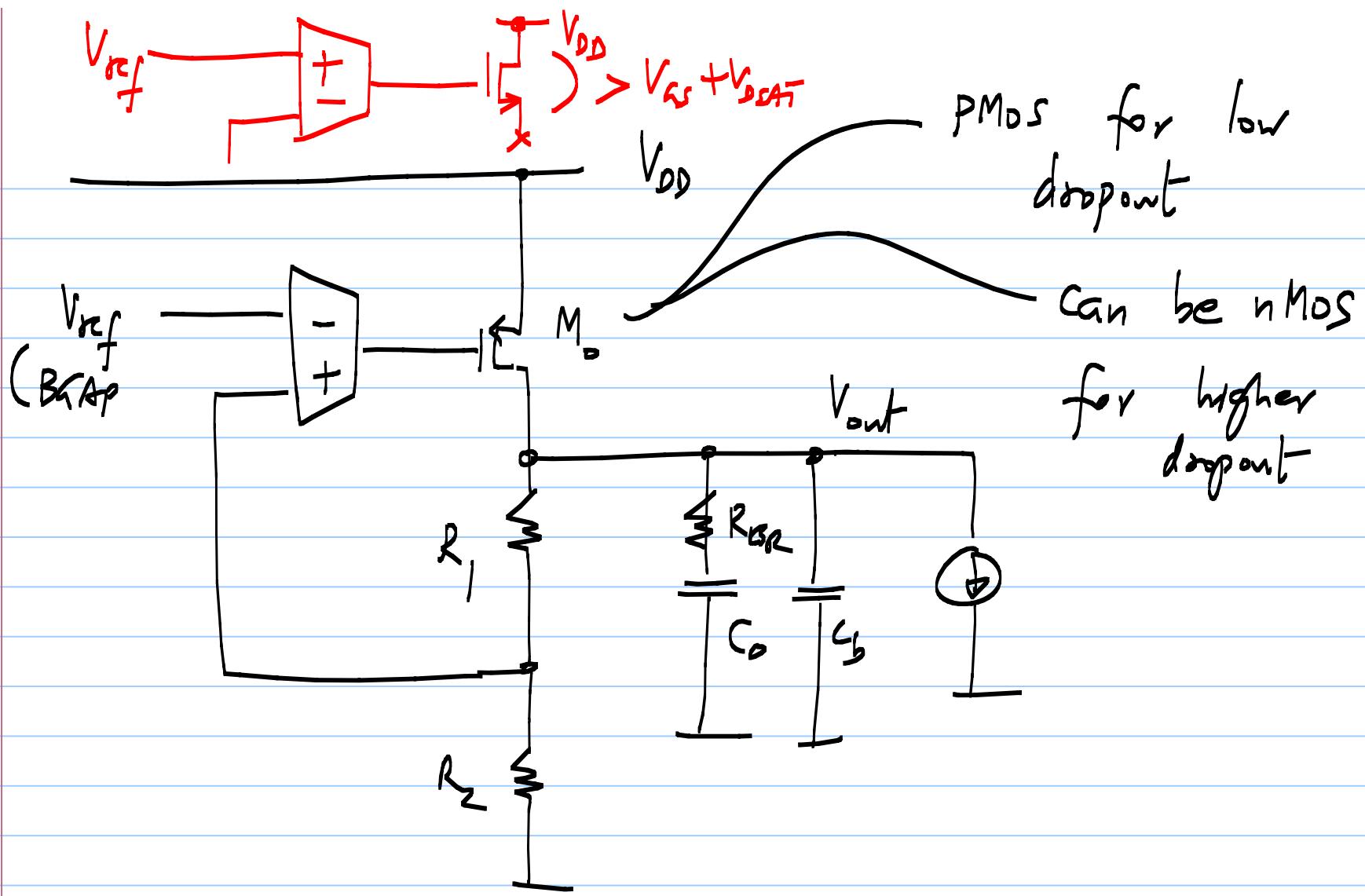

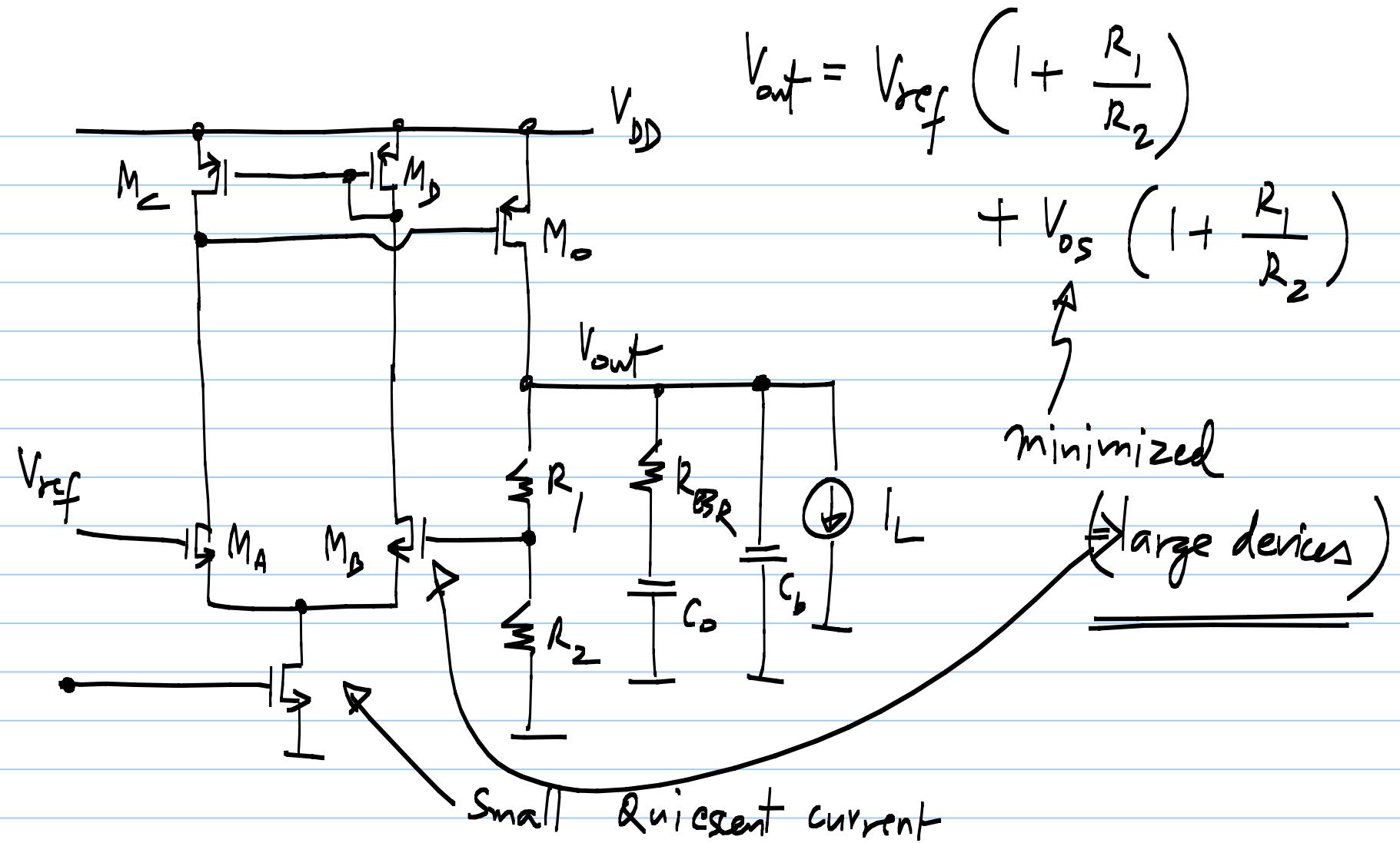


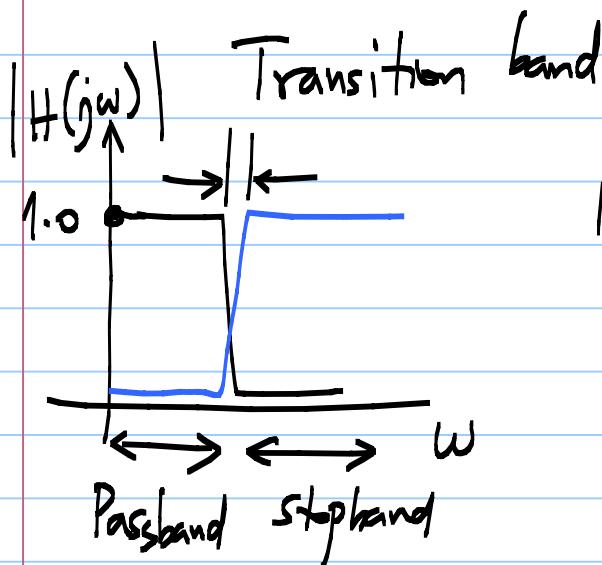Continuous time filters – selecting certain frequencies
rejecting other frequencies



Low pass filter

High pass filter

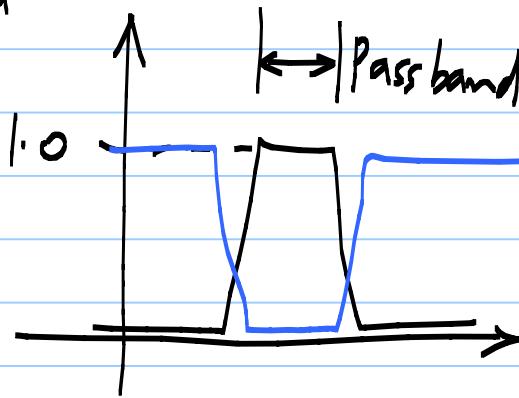

Bandpass filter

Bandstop (Band reject)
filters.

Filter design:

Matlab
Filter
tables

Zverev

* choosing the type & order

from specifications

transfer function

$H(s)$

Passive


R, L, C

Active

active
 $+ L, C$



Given

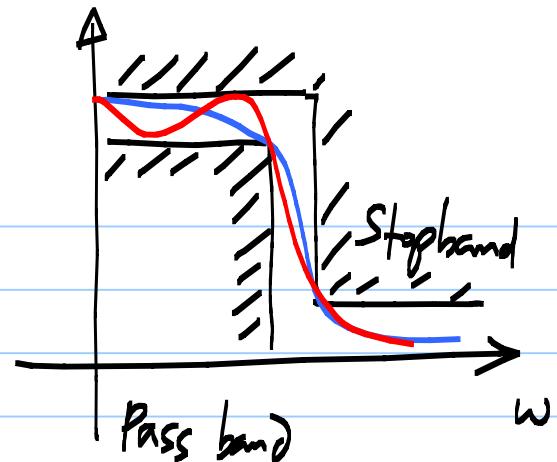



Butterworth
Chebyshev
Inv. Chebyshev
Elliptic
Bessel

Given a second order transfer function & prototype:

(Low pass)

$$\frac{V_{out}(s)}{V_i(s)} = \frac{1}{\frac{s^2}{\omega_p^2} + \frac{s}{\omega_p} + 1}$$

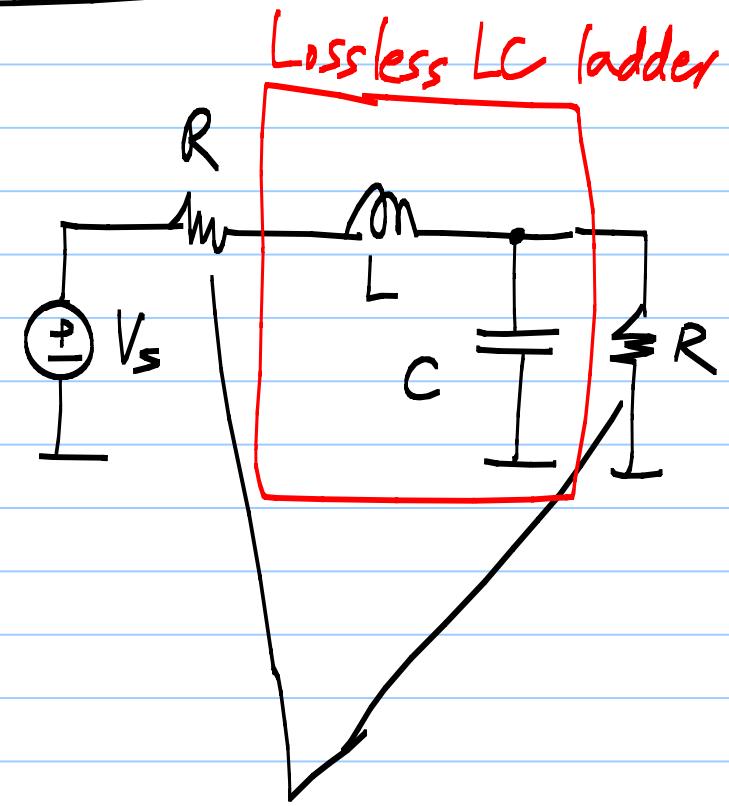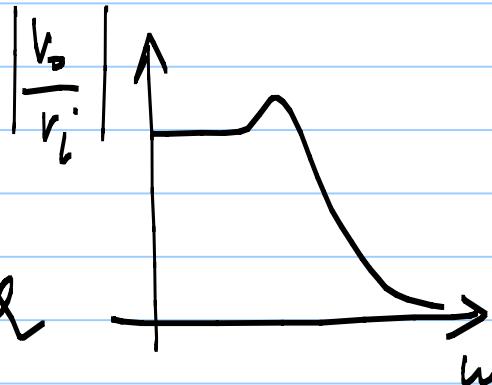dc gain : 1
 nat. freq: ω_p
 Quality factor: Q



Doubly terminated
Ladder Prototype