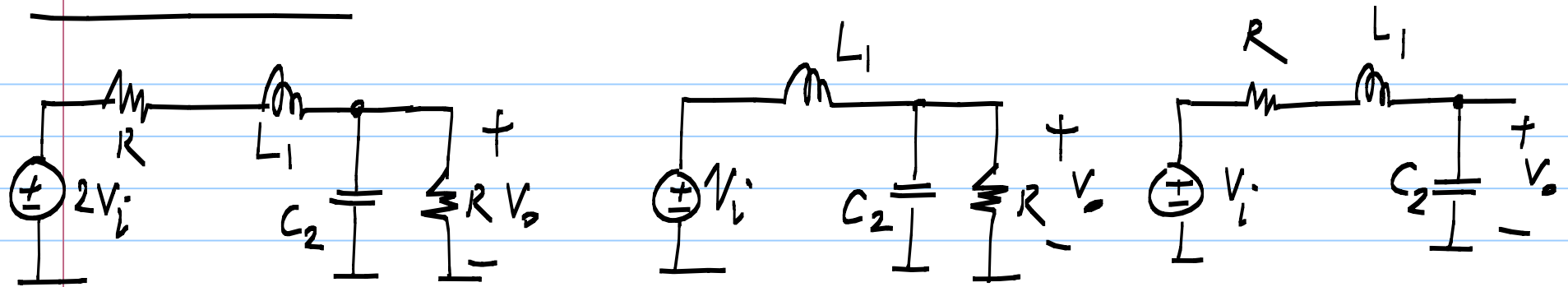


Lecture 57 : Continuous-time filters






$$\frac{V_o}{V_i} = \frac{1}{s^2 L_1 C_2 + s \left(C_2 R + \frac{L_1}{R} \right) + 1} \quad \frac{1}{s^2 L_1 C_2 + s \frac{L_1}{R} + 1} \quad \frac{1}{s^2 L_1 C_2 + s C_2 R + 1}$$

$$\omega_p = \frac{1}{\sqrt{L_1 C_2}} \quad \frac{1}{\sqrt{L_1 C_2}} \quad \frac{1}{\sqrt{L_1 C_2}}$$

$$Q_p = \frac{1}{R \sqrt{\frac{C_2}{L_1}} + \frac{1}{R} \sqrt{\frac{L_1}{C_2}}} \quad R \sqrt{\frac{C_2}{L_1}} \quad \frac{1}{R} \sqrt{\frac{L_1}{C_2}}$$

Lecture 57 : Continuous-time filters

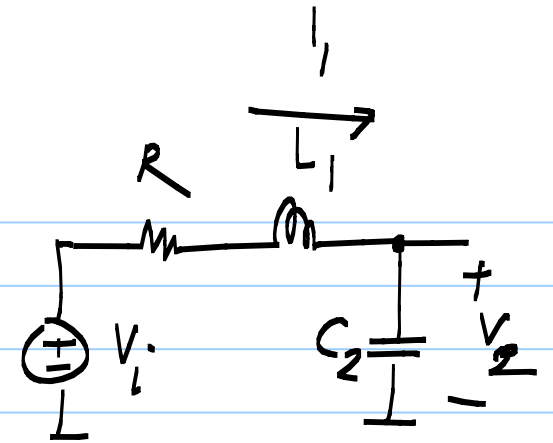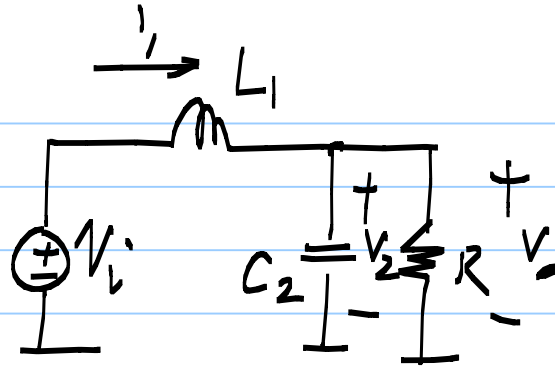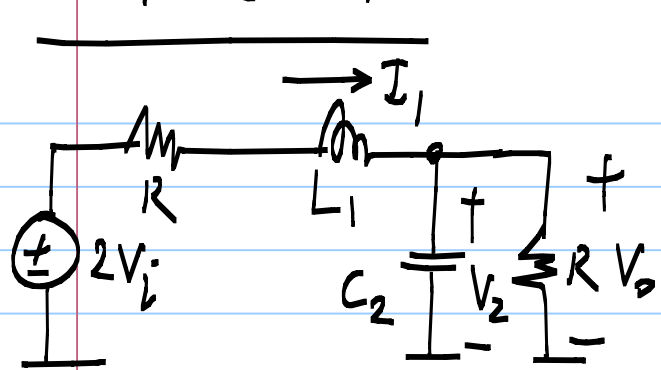

$$2V_i - I_1 R - V_2 = sL_1 I_1$$

$$V_i - V_2 = sL_1 I_1$$

$$V_i - I_1 R - V_2 = sL_1 I_1$$

$$I_1 - V_2/R = sC_2 V_2$$

$$I_1 - V_2/R = sC_2 V_2$$

$$I_1 = sC_2 V_2$$

$$2V_i - V_1 - V_2 = \frac{sL_1}{R} V_1$$

$$V_i - V_2 = \frac{sL_1}{R} V_1$$


$$V_i - V_1 - V_2 = \frac{sL_1}{R} V_1$$

$$V_1 - V_2 = sC_2 R V_2$$

$$V_1 - V_2 = sC_2 R V_2$$

$$V_1 = sC_2 R V_2$$

Lecture 57 : Continuous-time filters

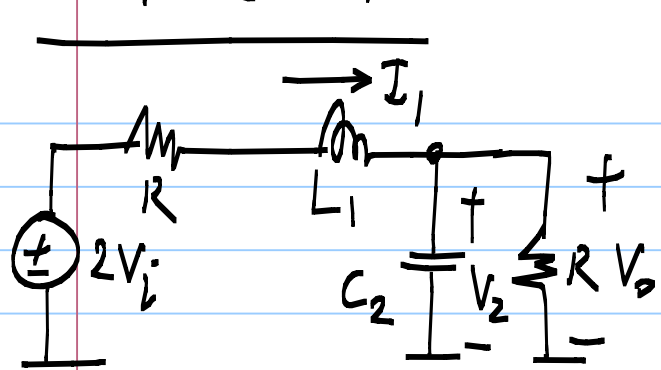


$$2V_i - V_1 - V_2 = \frac{sL_1}{R} \cdot V_1$$

$$V_1 - V_2 = sC_2 R \cdot V_2$$

$$\frac{2V_i - V_1 - V_2}{sL_1/R} = V_1$$

$$\frac{V_1 - V_2}{sC_2 R} = V_2$$

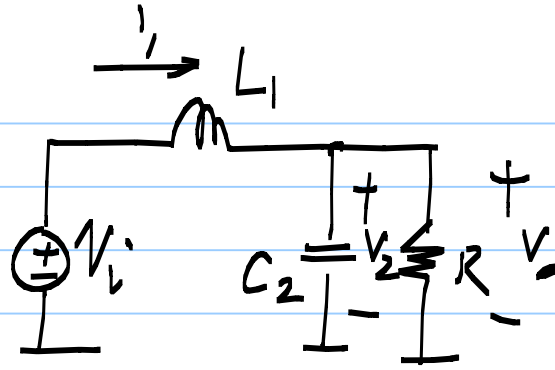


$$V_i - V_2 = \frac{sL_1}{R} \cdot V_1$$

$$V_1 - V_2 = sC_2 R \cdot V_2$$

$$\frac{V_i - V_2}{sL_1/R} = V_1$$

$$\frac{V_1 - V_2}{sC_2 R} = V_2$$

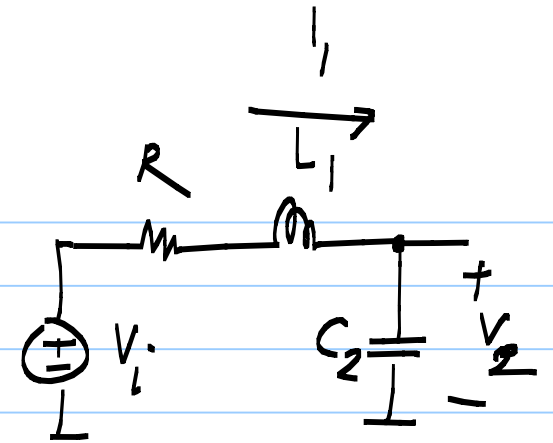

$$V_i - V_1 - V_2 = \frac{sL_1}{R} V_1$$


$$V_1 = sC_2 R \cdot V_2$$

$$\frac{V_i - V_1 - V_2}{sL_1/R} = V_1$$

$$\frac{V_1}{sC_2 R} = V_2$$

Equations describing the ladder filter implemented using integrators:


Transconductor-capacitor (g_m - C)

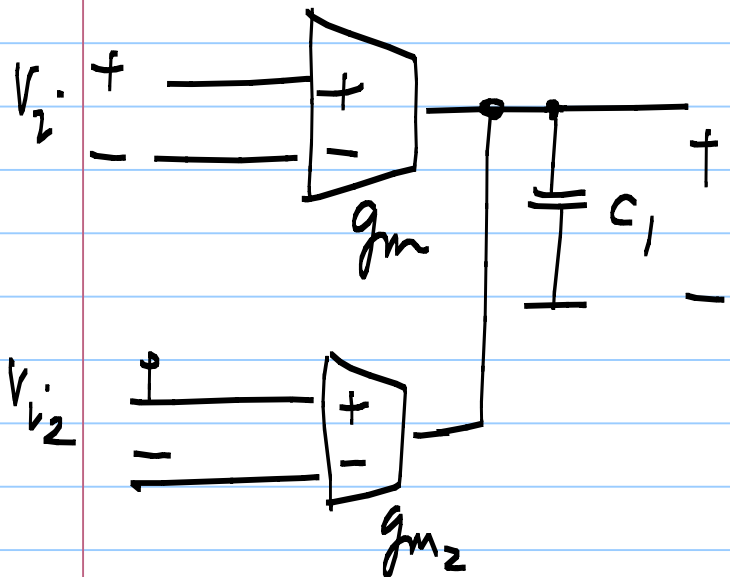



$$\frac{V_i g_{m1}}{sC_1} + \frac{V_{i2} g_{m2}}{sC_1}$$

g_m - C filters


Opamp-RC (Active RC integrator)

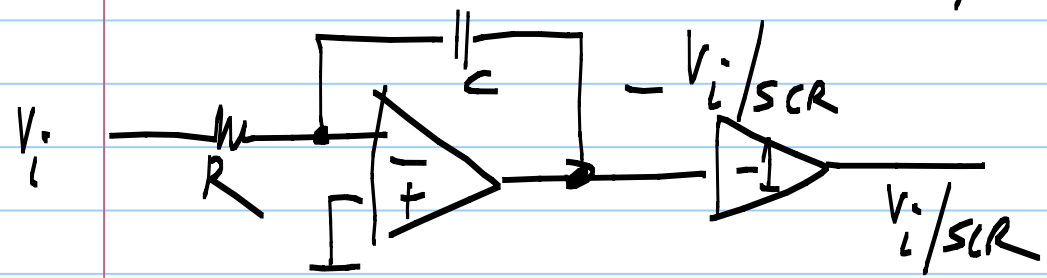

active RC filters

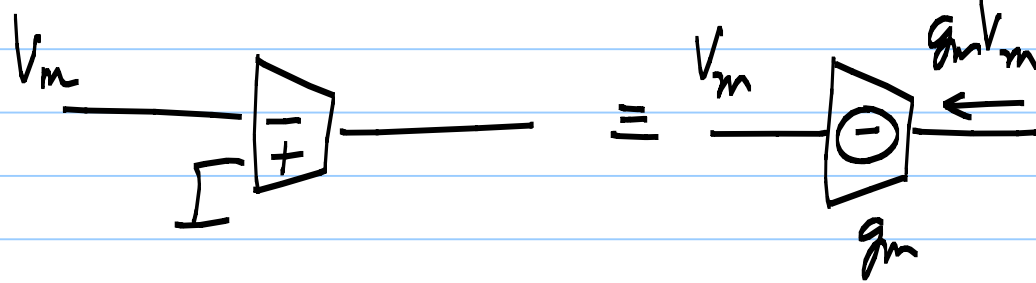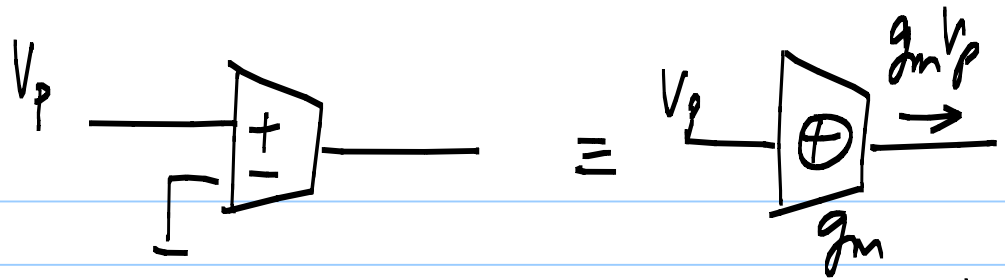


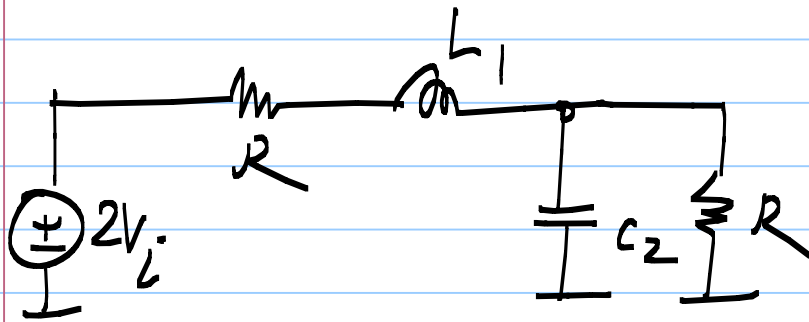
g_m - C implementation of lowpass filters :




$$\frac{2V_i - V_1 - V_2}{sL_1/R} = V_1$$

$$\frac{V_1 - V_2}{sC_2 R} = V_2$$
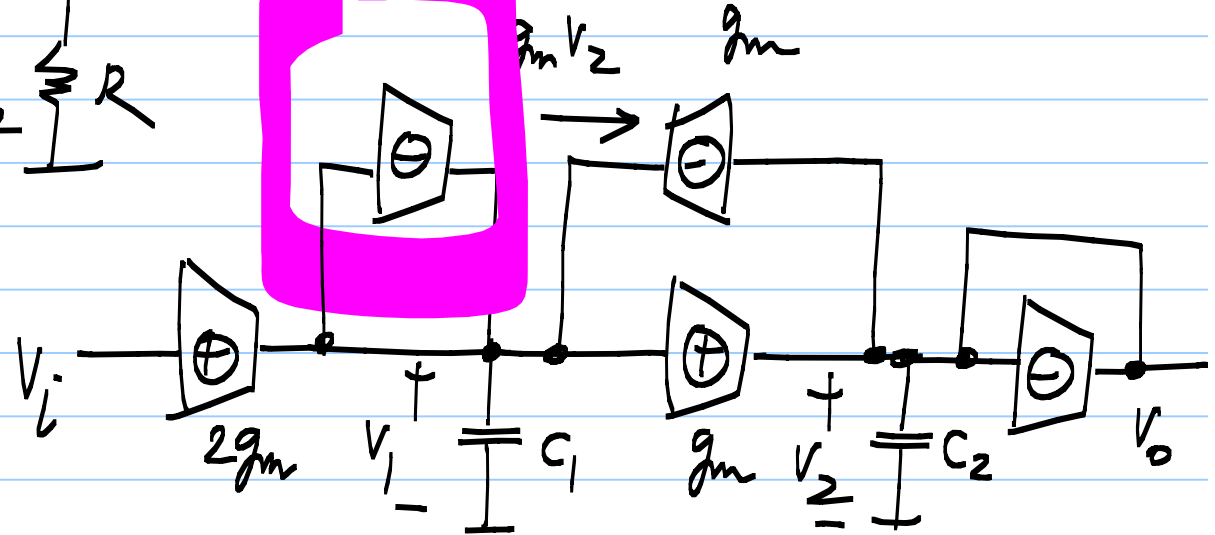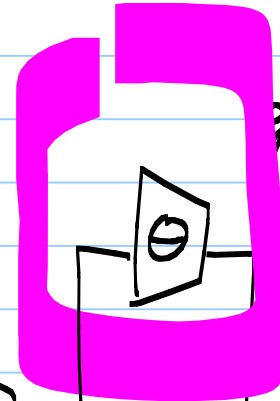
$$\frac{L_1}{sC_1} = \frac{2V_i - V_1 - V_2}{sL_1/R}$$


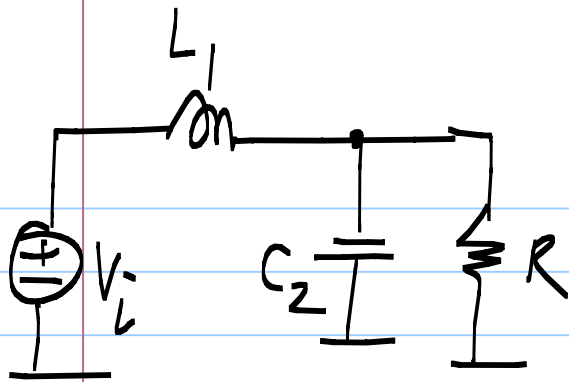
$$C_1 = \frac{C_1 R}{L_1} (2V_i - V_1 - V_2) \rightarrow g_m$$




$$\frac{V_i - V_2}{sL_1/R} = V_1$$

$$\frac{V_1 - V_2}{sC_2 R} = V_2$$


$$V_1 = \frac{I_{C_1}}{sC_1} = \frac{V_i - V_2}{sL_1/R}$$
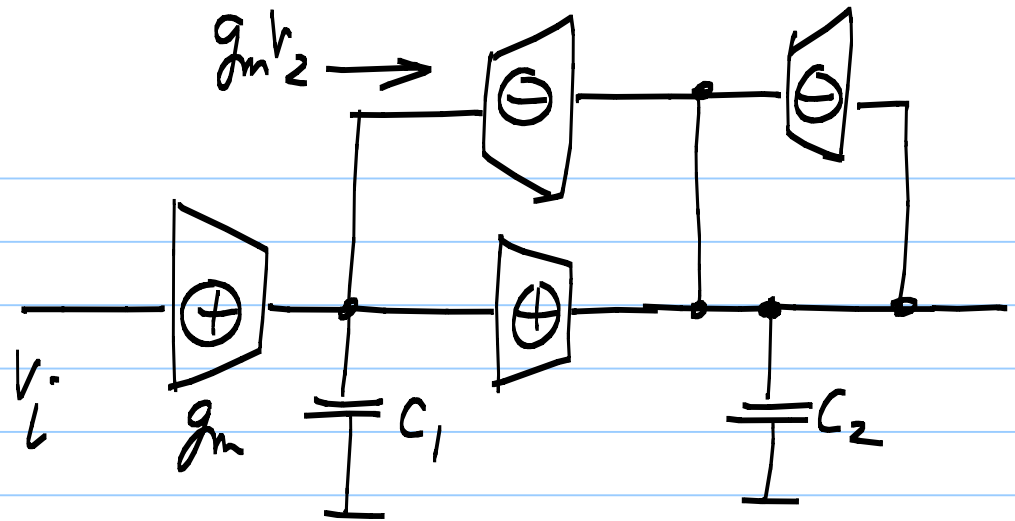
$$V_2 = \frac{I_{C_2}}{sC_2} = \frac{(V_1 - V_2)/R}{sC_2}$$




$$I_{C_1} = \underbrace{\frac{C_1 R}{L_1}}_{g_m} (V_i - V_2)$$


Doubly terminated filter

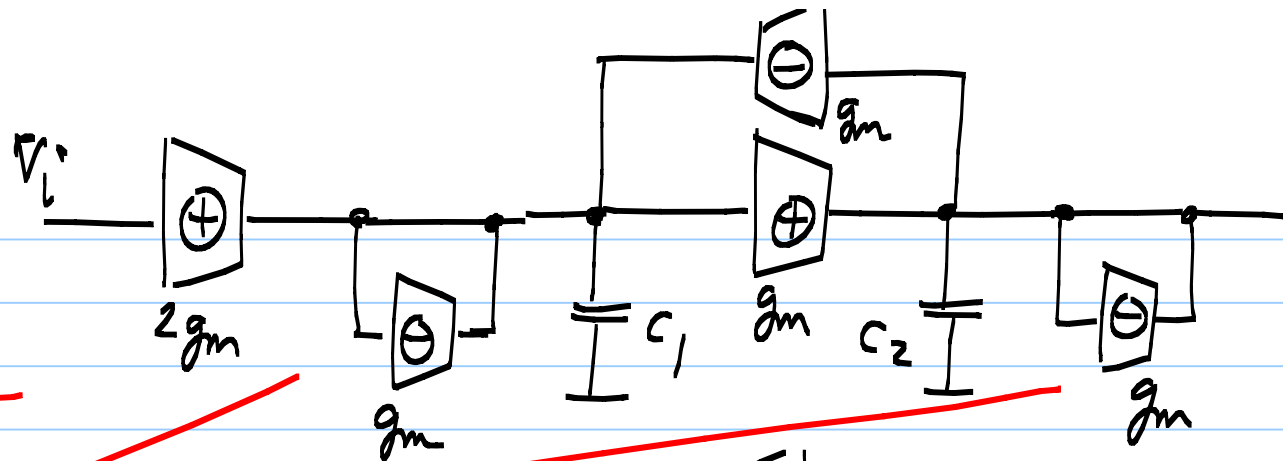


Singly terminated filter (output)

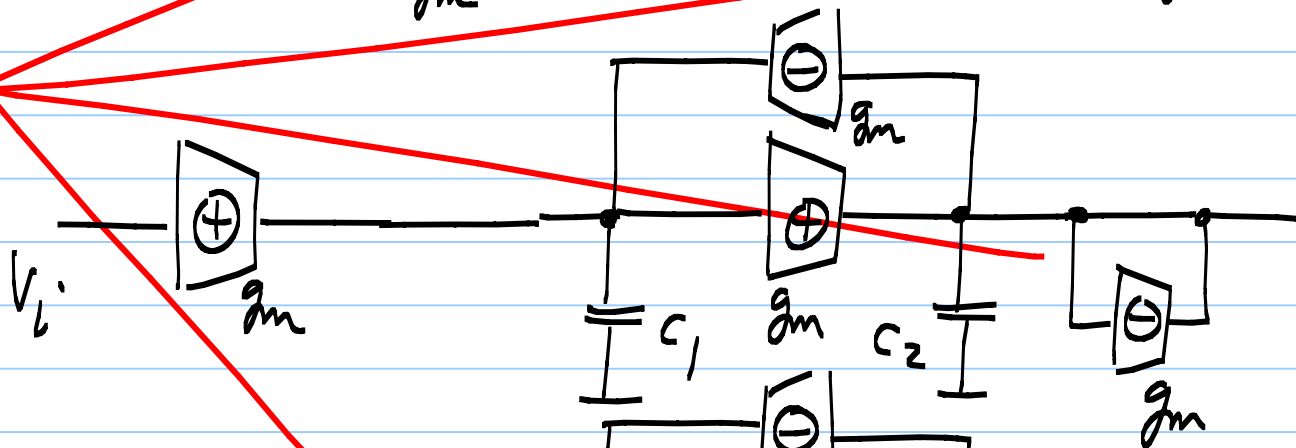


Singly terminated filter (input)

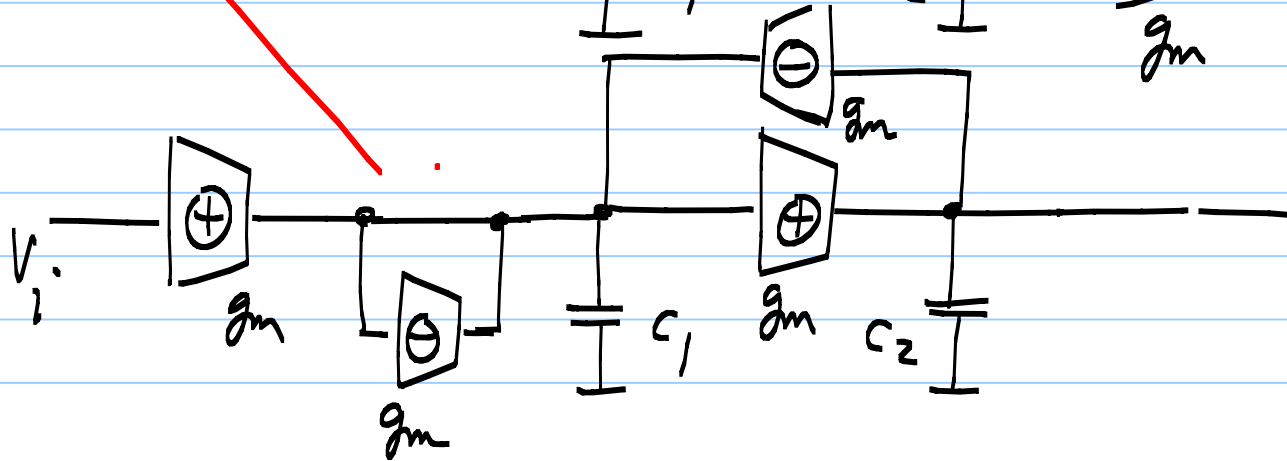

Conductance
 g_m
 (termination
 R)

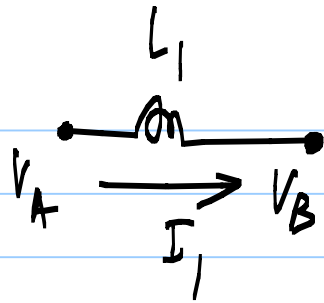



$$I_1 = \frac{V_A - V_B}{sL_1}$$

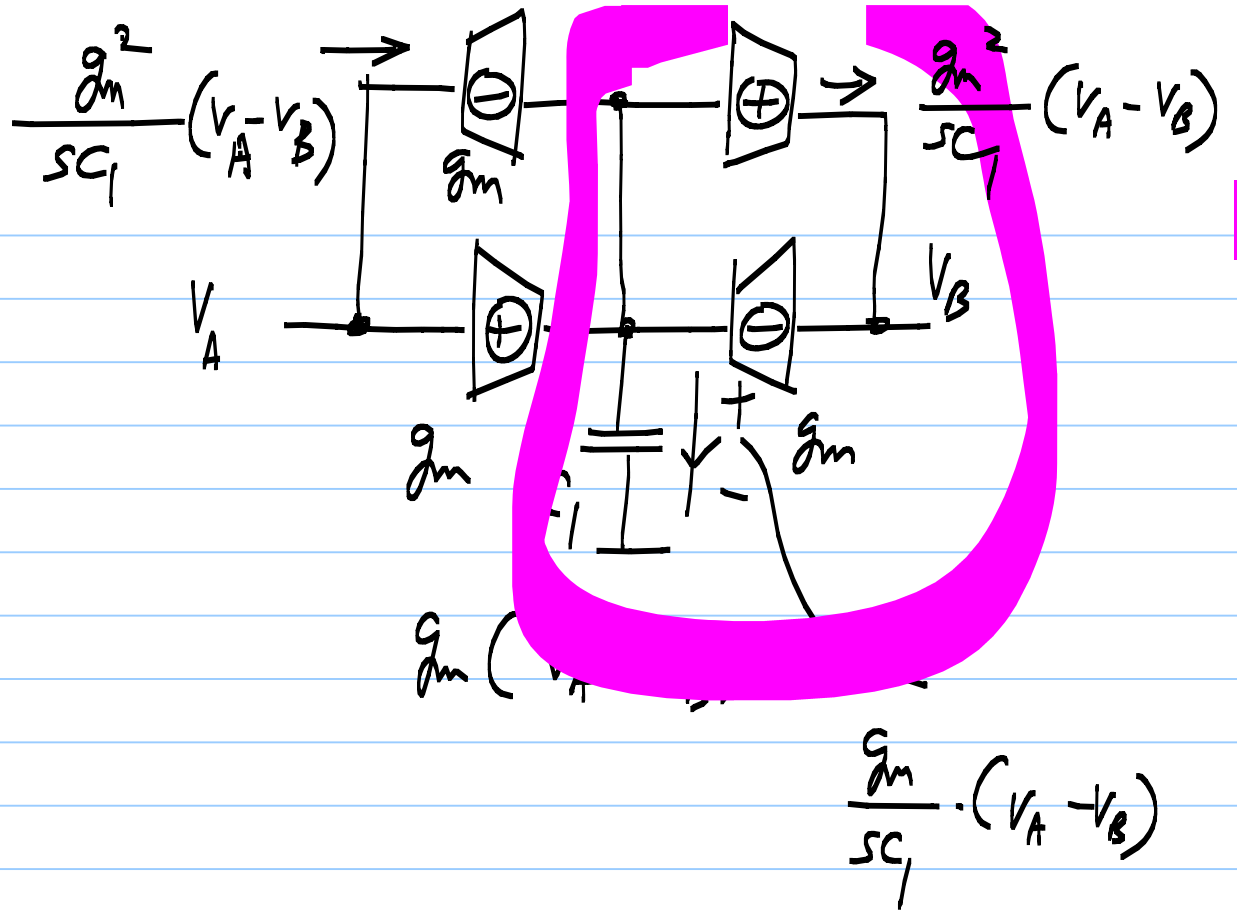

$$\frac{g_m}{sC_1} \cdot (V_A - V_B)$$

Active RC filters:

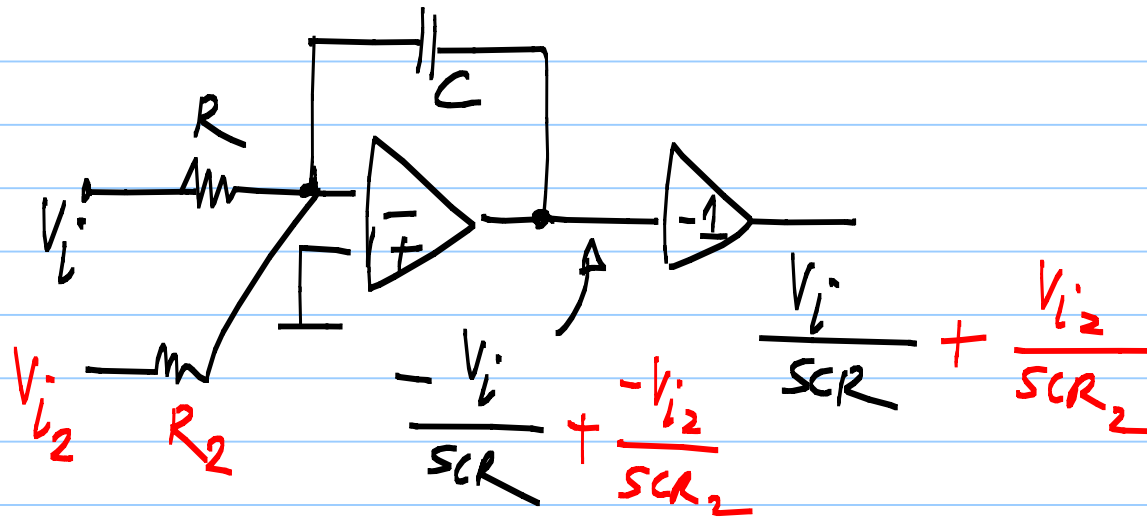


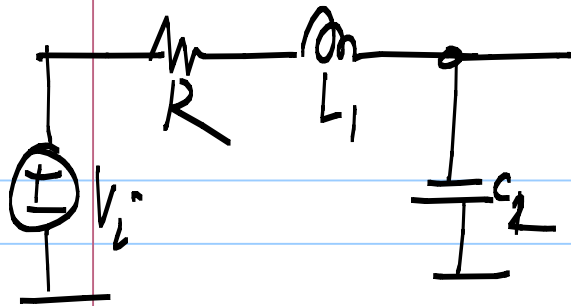



$$\frac{V_i - I_1 R - V_2}{sL_1} = I_1$$

$$\frac{V_i - V_1 - V_2}{sL_1 / R} = V_1$$

$$\frac{V_1}{sC_2 R} = V_2$$

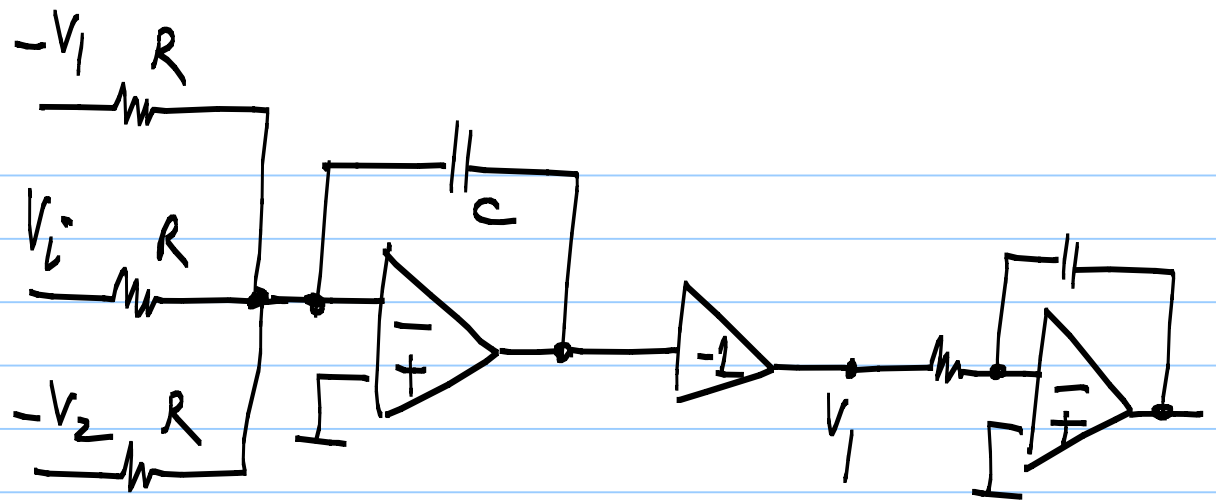


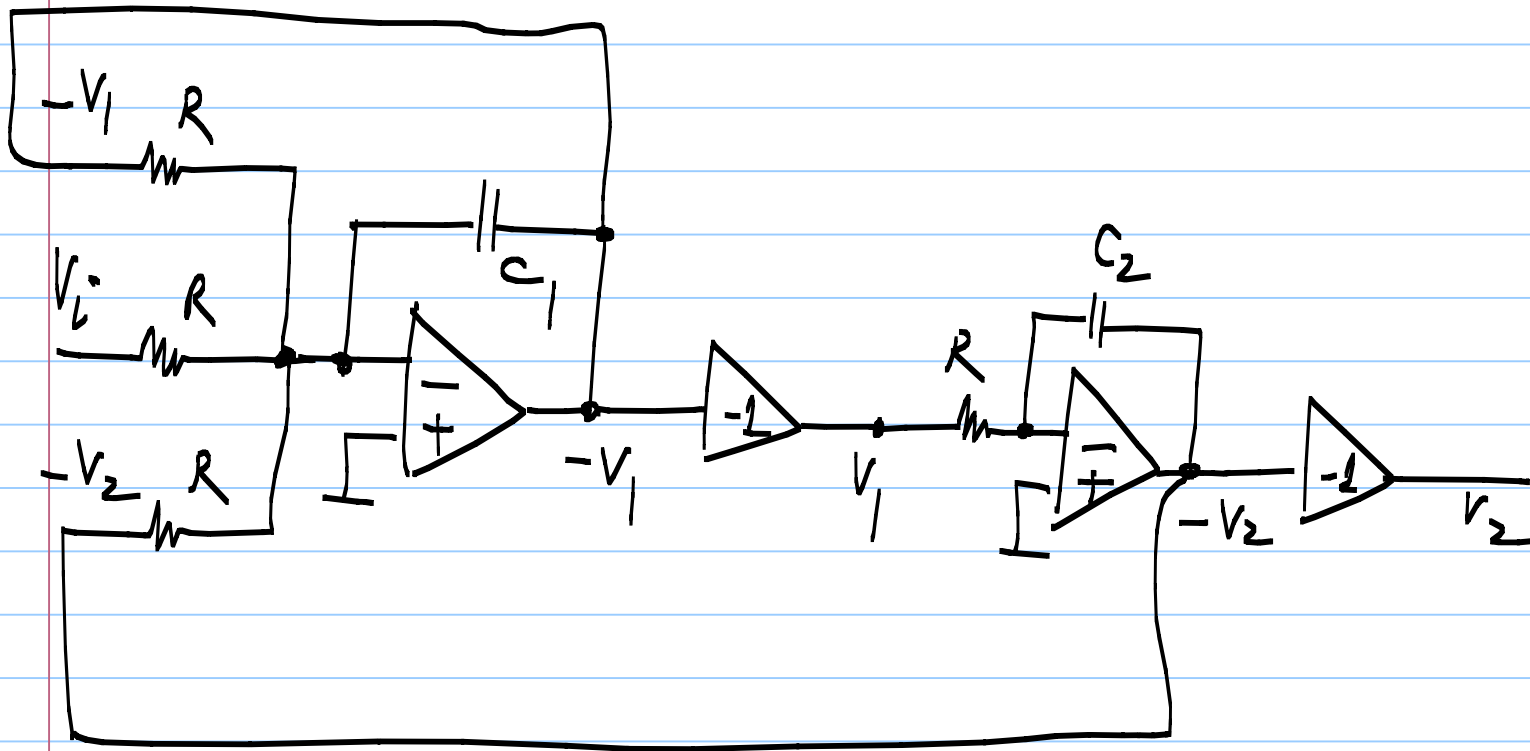


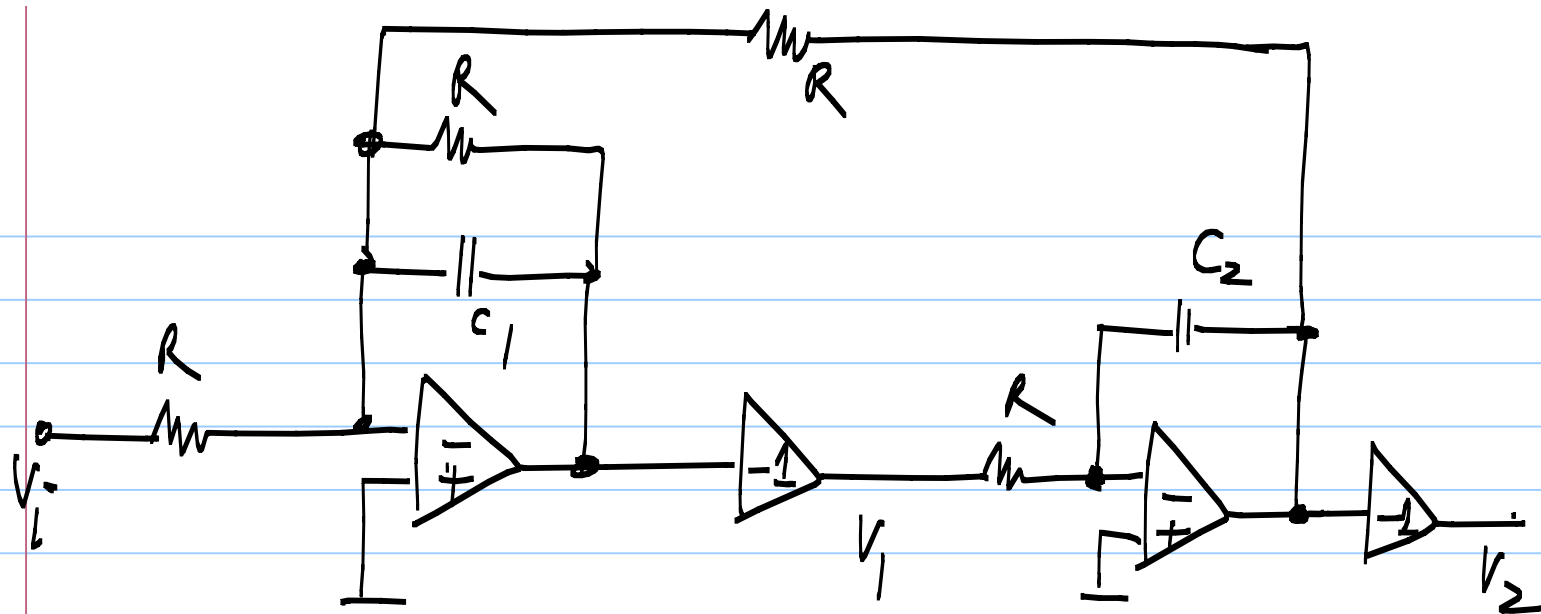



2nd order active-RC filter

Fully differential implementation:

$g_m - C$

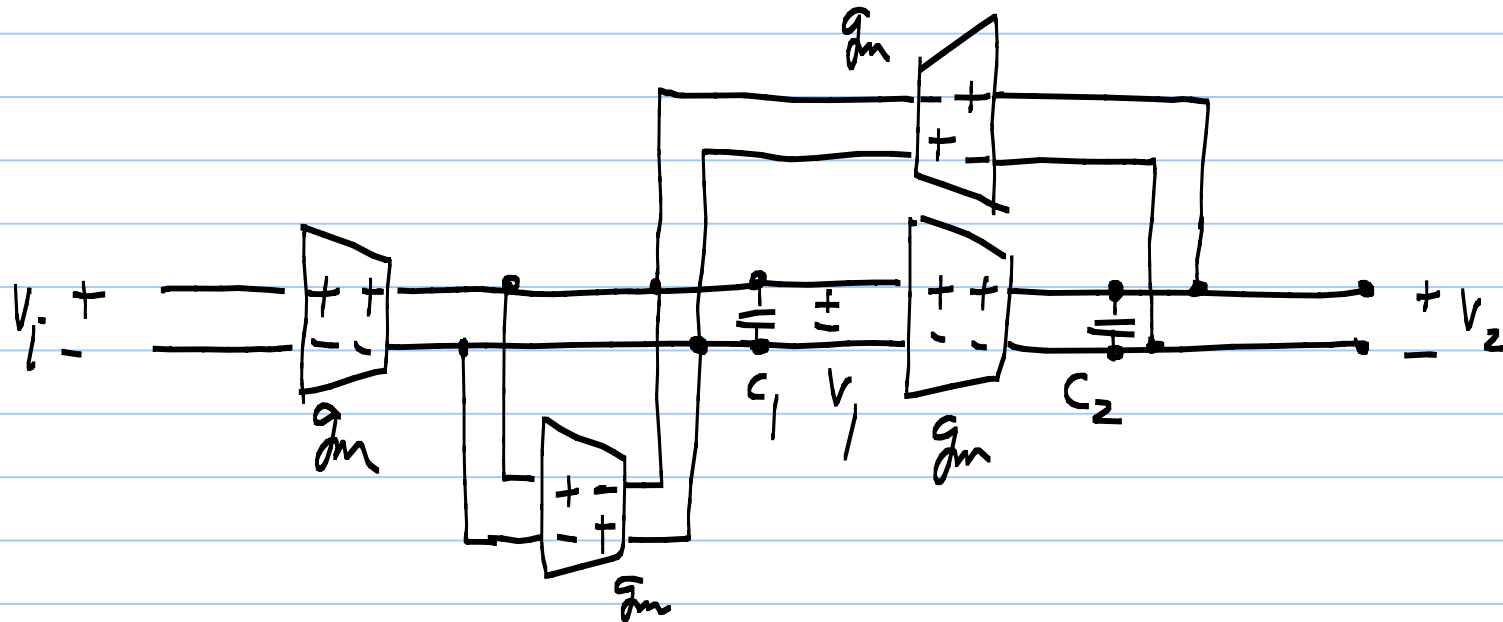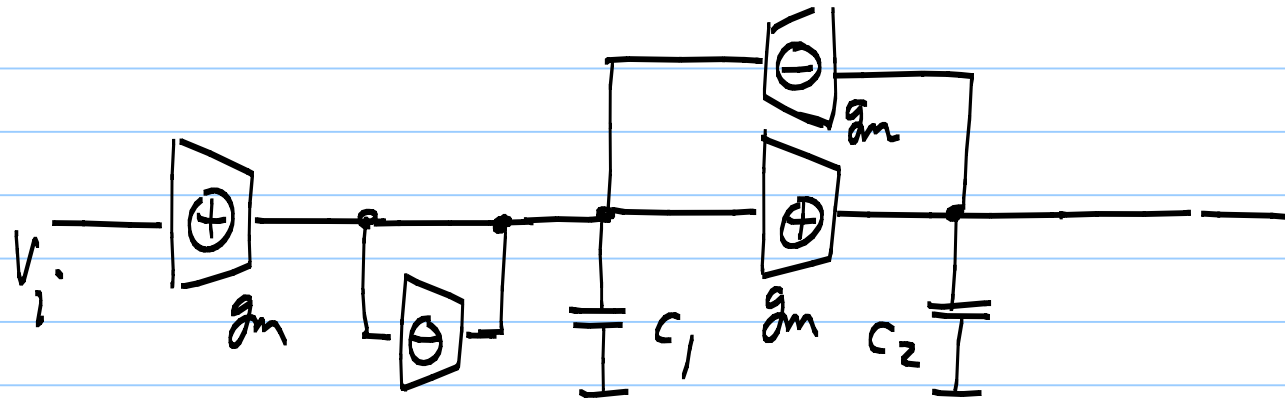

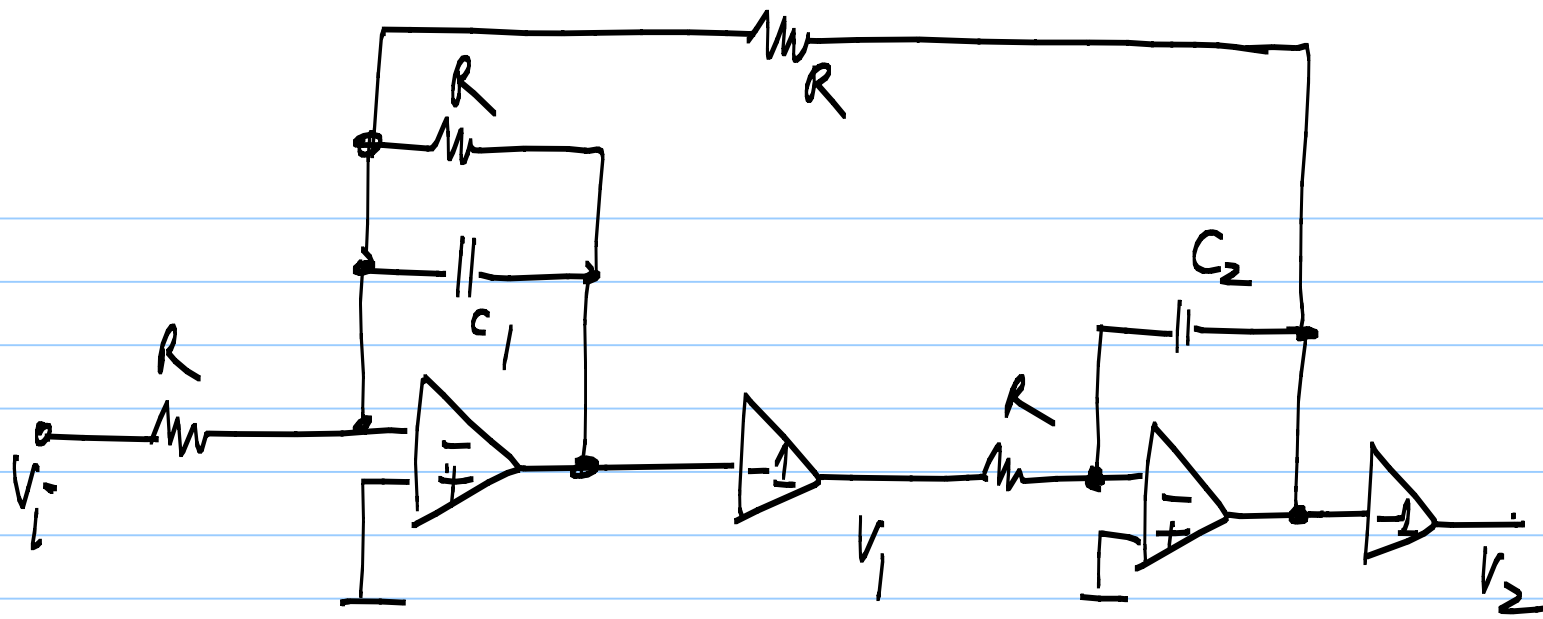

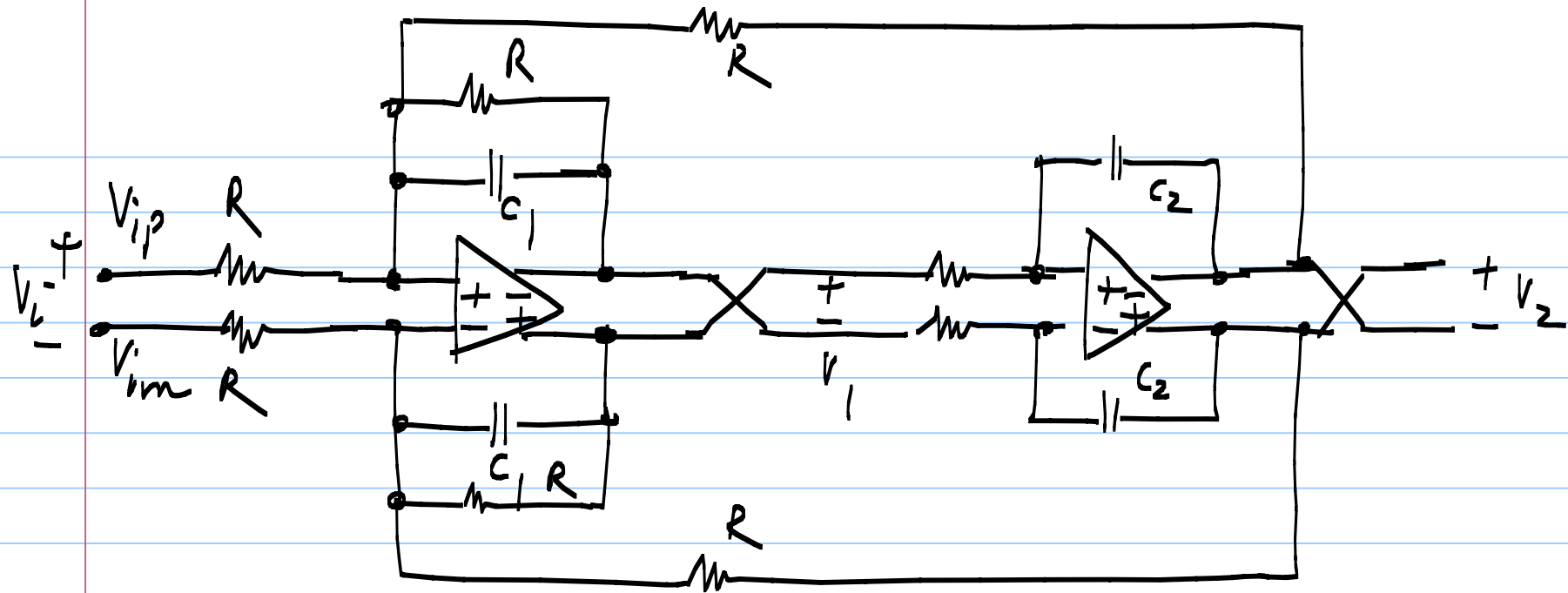

Fully differential active RC filter (2nd order)