

Phase locked loop frequency synthesizers

Analog Integrated Circuit Design

A video course under the NPTEL

Nagendra Krishnapura

Department of Electrical Engineering
Indian Institute of Technology, Madras
Chennai, 600036, India


National Programme on Technology Enhanced Learning

- Phase locked loop (PLL) requirements
- PLL frequency multiplier
 - Derivation
 - Phase model
- Type I PLL
 - Practical phase detectors
 - Type I PLL limitations
- Type II PLL
 - Feedback systems and stability
 - Type II PLL
- LC oscillator
- Programmable frequency divider

Phase locked loops



- Frequency synthesizers in radios for local oscillators
- Frequency multiplication for reference clock generation
- Phase alignment

Local oscillator requirements

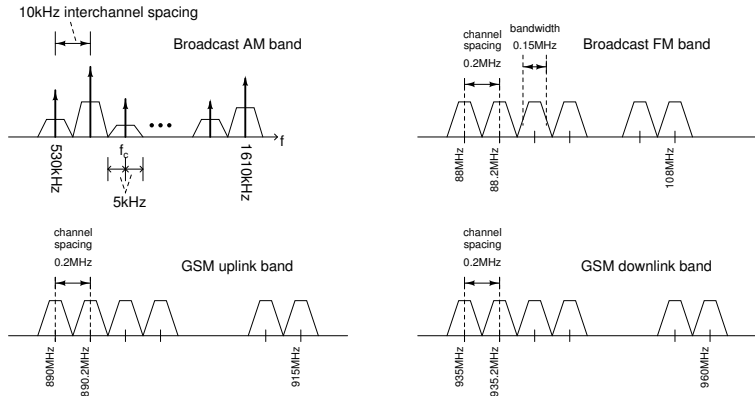

- Tuned to the desired channel frequency plus an intermediate frequency (IF)
- Generate equally spaced frequencies from a reference frequency
- Waveform shape not very important
- Spurious output and noise must be sufficiently low


Frequency divider

  

- Digital frequency divider can generate multiple frequencies
- Frequencies not equally spaced
- Reference frequency higher than output frequencies

Voltage multiplier


voltage difference
zero, at steady state

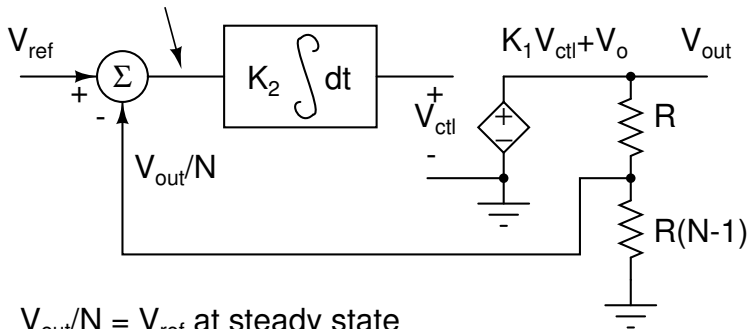

$$V_{out}/N = V_{ref} \text{ at steady state}$$

- A controlled source to generate the output voltage
- Divided output voltage subtracted from the reference to generate error
- Output source controlled by the integral of the error

Frequency multiplier

 


- A controlled source to generate the output frequency
 - A voltage controlled oscillator
- Divided output frequency subtracted from the reference frequency to generate error
- Output source controlled by the integral of the frequency error


Phase and frequency

- Sinusoid: $\cos(\theta(t))$
- Phase: $\theta(t)$
- Instantaneous frequency: $f_i = \frac{1}{2\pi} \frac{d\theta(t)}{dt}$
- Typically expressed as $f_i = f_o + f_e(t)$
 - f_o : average frequency
 - f_e : instantaneous frequency error
- Phase $\theta(t) = 2\pi f_o t + \Phi_o + 2\pi \int f_e(t) dt$
- Phase $\theta(t) = 2\pi f_o t + \Phi_o + \phi(t)$
 - Φ_o : phase offset-ideal ramp versus time
 - $\phi(t)$: instantaneous phase

Phase error

 


Frequency multiplier

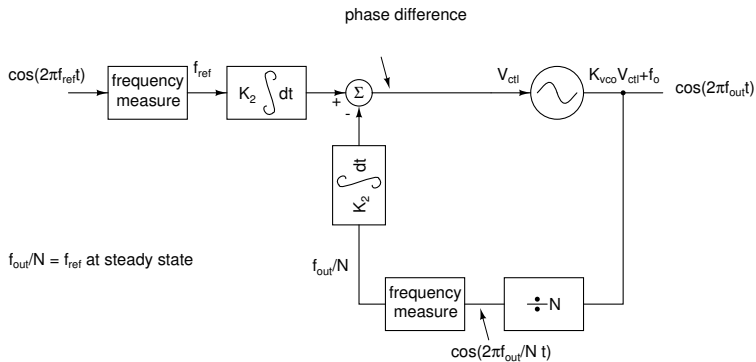

- Integration before subtraction
- Integral of the frequency is phase
- Integrator+subtractor measures phase difference between the reference input and the divided output (feedback)




Frequency multiplier—Phase locked loop

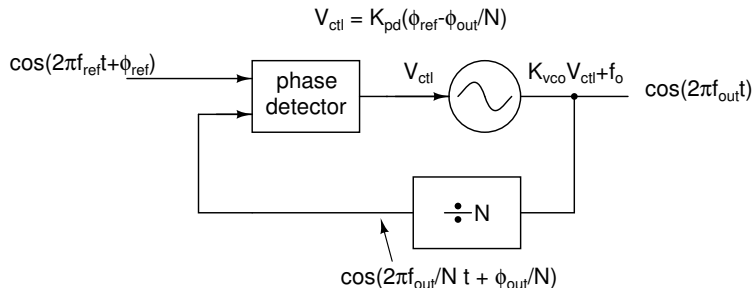

$f_{\text{out}}/N = f_{\text{ref}}$ at steady state


- Use a phase detector to generate the control voltage

Voltage controlled oscillator

   

- $f_{vco} = f_o + K_{vco} V_{ctl}$
 - f_o : Free running frequency
- $\theta_{vco} = 2\pi f_o t + 2\pi K_{vco} \int V_{ctl} dt$
- K_{vco} : VCO gain in Hz/V


Phase detector

 

K_{pd} : phase detector gain

- K_{pd} : Phase detector gain in V/radian
- Ideal phase detector: assumed to have an output $V_{pd} = K_{pd}(\phi_1 - \phi_2)$

Phase locked loop model

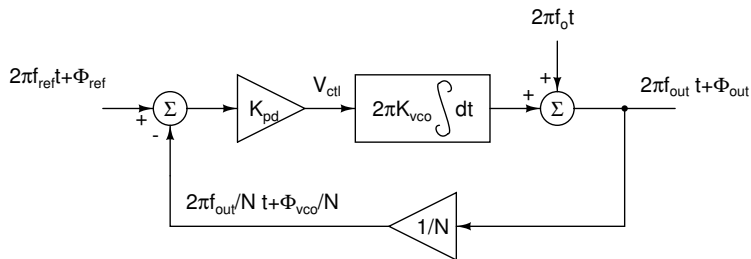

$$V_{ctl} = 2\pi(f_{ref} - f_{out}/N)t + \Phi_{ref} - \Phi_{out}/N$$


$$\text{At steady state, } f_{ref} = f_{out}/N; \quad V_{ctl} = \Phi_{ref} - \Phi_{out}/N$$

- Modelled in terms of phases of signals
- At steady state (lock), V_{ctl} is a constant $\Rightarrow f_{ref} = f_{out}/N$

- The loop locks with


$V_{ctl} = K_{pd}(\Phi_{ref} - \Phi_{out}/N) = (Nf_{ref} - f_o)/K_{vco}$ —This is the “operating point” of the circuit

Phase locked loop model

 


- An increment ϕ_{ref} in the input phase causes increments ϕ_{out} , V_{ctl}

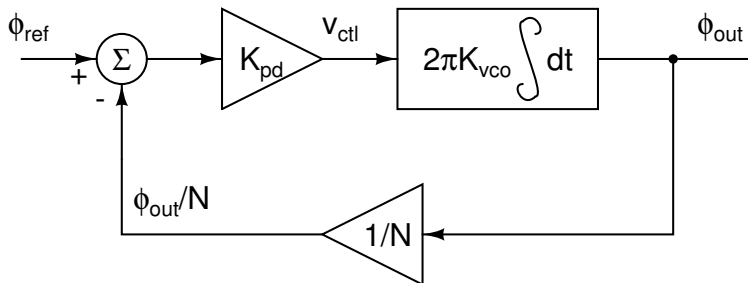Phase locked loop model—incremental picture



- An increment ϕ_{ref} in the input phase causes increments ϕ_{out} , v_{ctl}
- Type-I loop—One integrator in the loop
- “Phase model” of the PLL

Phase locked loop model—frequency domain

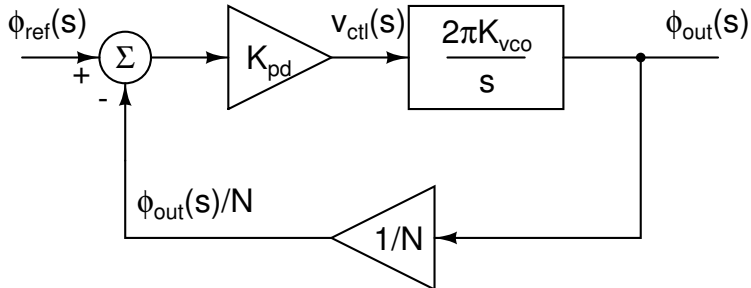

- Loop gain $L(s) = 2\pi K_{pd}K_{vco}/Ns$
- Transfer function
$$\phi_{out}(s)/\phi_{ref}(s) = N/(1 + Ns/(2\pi K_{pd}K_{vco}))$$
- Type-I loop—One integrator in the loop
- Closed loop bandwidth (= unity loop gain frequency)
$$= 2\pi K_{pd}K_{vco}/N \text{ rad/s}$$



Type-I PLL—limitations

- Phase error when locked ($f_{out} = Nf_{ref}$):
 - $\Phi_{ref} - \Phi_{out}/N = (Nf_{ref} - f_o)/K_{vco}K_{pd}$
 - dc value of K_{pd} matters; We have a constant K_{pd}
- $|\Phi_{ref} - \Phi_{out}/N| < 2\pi \Rightarrow |f_{out} - f_o| < 2\pi K_{pd}K_{vco}$
- Lock range limited by periodicity of phase detector
 - Period of all phase detectors not necessarily $\pm 2\pi$
 - Commonly used three state phase detector periodic with $\pm 2\pi$
- $K_{pd}K_{vco}$ large for wide lock range

Phase detector

- Frequency divider output has a varying duty cycle
- Phase detector should be sensitive to duty cycle
 - XOR gate etc. are not preferable
- Phase detector should be sensitive *only* to rising edges (or *only* to falling edges) of inputs


Tri state phase detector

  


- Output +1, -1, 0

- +1 if reference leads divider output
- -1 if reference lags divider output
- 0 if reference coincides with divider output

Tri state phase detector-waveforms

 



A leading B

 

A lagging B

- Flip flops assumed to be reset instantaneously

  
Tri state phase detector-frequency difference between inputs



- $f_A > f_B$: Eventually get two consecutive edges of A
- Circulates between 0 and +1 states: Average output > 0
- Similarly, average output > 0 for $f_A < f_B$

This detector is a phase/frequency detector (PFD)

Tri state phase detector output

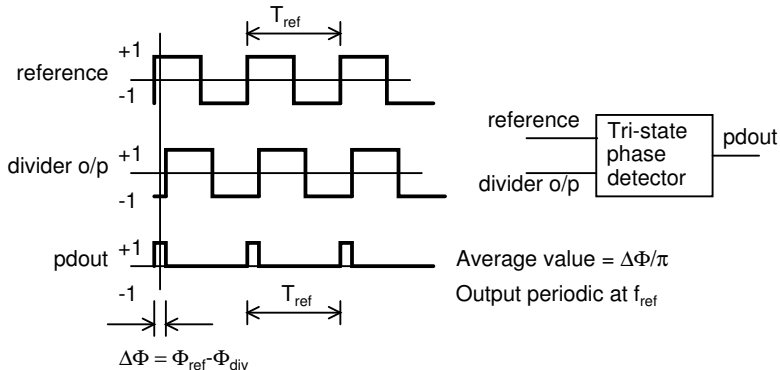

$$V_{out}(f) = \frac{\Delta\Phi}{2\pi} \sum_{n=-\infty}^{\infty} \text{sinc}\left(\frac{n\Delta\Phi}{2\pi}\right) \delta(f - nf_{ref})$$



$$V_{out}(t) = \frac{\Delta\Phi}{2\pi} + \frac{\Delta\Phi}{\pi} \sum_{n=1}^{\infty} \text{sinc}\left(\frac{n\Delta\Phi}{2\pi}\right) \cos(2\pi nf_{ref}t)$$

Tri state phase detector


- Output average value = $\Delta\Phi/2\pi$
 - $K_{pd} = 1/2\pi$
 - Phase detector offset = 0
 - Loop locks with $\Delta\Phi = \Phi_{ref} - \Phi_{out}/N = 0$ for $Nf_{ref} = f_o$
 - Input range = $\pm 2\pi$
 - PLL lock range = $f_o - 2\pi K_{pd}K_{vco} < f_{out} < f_o + 2\pi K_{pd}K_{vco}$
- Output contains f_{ref} and its harmonics
- Output = $1/2\pi (\Delta\Phi + \sum_n a_n \cos(2\pi n f_{ref} t))$
- Periodic signal in addition to $K_{pd}\Delta\Phi$

All real phase detectors have a periodic “error” in addition to the “dc” term proportional to phase error

Phase detector-Output spectrum

  


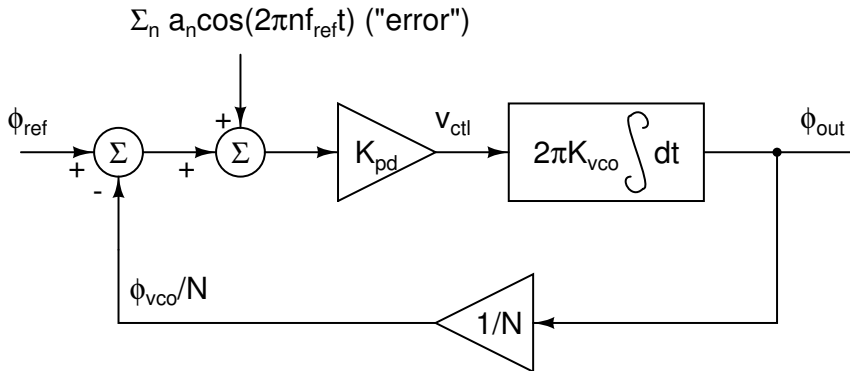PLL with tri state phase detector—periodic error




- Error $e(t)$ added to the input of the phase detector
- Disturbances in the VCO output phase $\phi_{out}(t)$ even with a perfect reference ($\phi_{ref}(t) = 0$)
- VCO output: $\cos(2\pi N f_{ref} t + N\Phi_{ref} + \phi_{out}(t))$
- VCO output not periodic at Nf_{ref}

Phase error

 

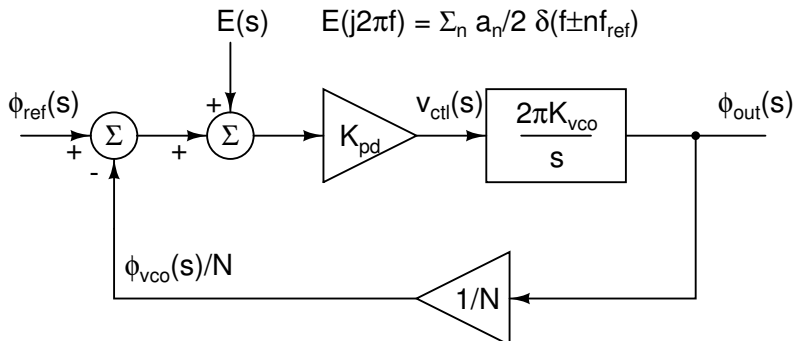PLL with tri-state phase detector—frequency domain



$\phi_{ref}(s) = 0$ for a perfectly periodic reference

- Transfer function from the error to the output
$$\phi_{out}(s)/E(s) = \phi_{out}(s)/\phi_{ref}(s) = N/(1 + Ns/(2\pi K_{pd}K_{vco}))$$
- $E(j2\pi f) = \sum_n (a_n/2)\delta(f \pm n f_{ref})$

$$\begin{aligned}\frac{\phi_{out}(s)}{E(s)} &= \frac{\phi_{out}(s)}{\phi_{ref}(s)} \\ &= N \frac{2\pi K_{pd} K_{vco} / Ns}{1 + 2\pi K_{pd} K_{vco} / Ns} \\ &= N \frac{1}{1 + sN / 2\pi K_{pd} K_{vco}}\end{aligned}$$


Loop gain

$$L(s) = \frac{2\pi K_{pd} K_{vco}}{Ns}$$

Closed loop bandwidth (Hz)

$$f_{-3dB} = \frac{K_{pd} K_{vco}}{N}$$

Type I PLL

 

Feedback system

In our system,

$$\frac{\phi_{out}(s)}{E(s)} = N \frac{2\pi K_{pd} K_{vco} / Ns}{1 + 2\pi K_{pd} K_{vco} / Ns}$$

In general, in a feedback system with a loop gain $L(s)$

$$H_{closedloop}(s) = H_{ideal}(s) \frac{L(s)}{1 + L(s)}$$

Where $H_{ideal}(s)$ is the ideal closed loop gain (with $L = \infty$). This can be approximated as

$$\begin{aligned} H_{closedloop}(s) &= H_{ideal}(s)L(s) && |L| \ll 1 \\ &= H_{ideal}(s) && |L| \gg 1 \end{aligned}$$

PLL with tri state phase detector—Output signal

Considering only the term at f_{ref} , and $b_1 \ll 1$

$$\begin{aligned}V_{out}(t) &= \cos(2\pi Nf_{ref}t + b_1 \sin(2\pi f_{ref}t)) \\&= \cos(2\pi Nf_{ref}t) \cos(b_1 \sin(2\pi f_{ref}t)) \\&\quad - \sin(2\pi Nf_{ref}t) \sin(b_1 \sin(2\pi f_{ref}t)) \\&\approx \cos(2\pi Nf_{ref}t) - b_1 \sin(2\pi f_{ref}t) \sin(2\pi Nf_{ref}t) \\&= \cos(2\pi Nf_{ref}t) \\&\quad - b_1/2 \cos(2\pi(N-1)f_{ref}t) \\&\quad - b_1/2 \cos(2\pi(N+1)f_{ref}t)\end{aligned}$$

- Spurious tones in the output at a spacing of $\pm f_{ref}$ from the desired frequency—“Reference feedthrough”
- In general, spurious tones will be present at $\pm nf_{ref}$ from the desired PLL output

Reference feedthrough


$$\begin{aligned} b_1 &= a_1 |H(j2\pi f_{ref})| \\ &= a_1 N \left| \frac{K_{pd}K_{vco}/jNf_{ref}}{1 + K_{pd}K_{vco}/jNf_{ref}} \right| \\ &\approx a_1 N \left| \frac{K_{pd}K_{vco}}{jNf_{ref}} \right| \\ &= 2\Delta\Phi \frac{Nf_{-3dB}}{f_{ref}} \operatorname{sinc} \frac{\Delta\Phi}{2\pi} \end{aligned}$$

- Maximum value of $b_1 = 4K_{pd}K_{vco}$ when $\Delta\Phi = \pi$

Reference feedthrough—example


- To generate 1 GHz from 1 MHz reference
 - $b_1/2 = 10^{-2}$ (spurious tones at $(N \pm 1)f_{ref}$ 40 dB below the fundamental output at Nf_{ref})
 - $N = 10^3$
 - $\Delta\phi = \pi$ (locked with a phase shift of π)
- $f_{-3dB}/f_{ref} = 5 \times 10^{-6} \Rightarrow f_{-3dB} = 5 \text{ Hz}$
- Lock range = $2\pi Nf_{-3dB} \approx 10\pi \text{ kHz}$
- Lock range is too small; Can't switch to the next channel which is 1 MHz away!
- May not be able to lock for any value of N , unless the free running frequency happens to be Nf_{ref} for some N

Type I phase locked loop

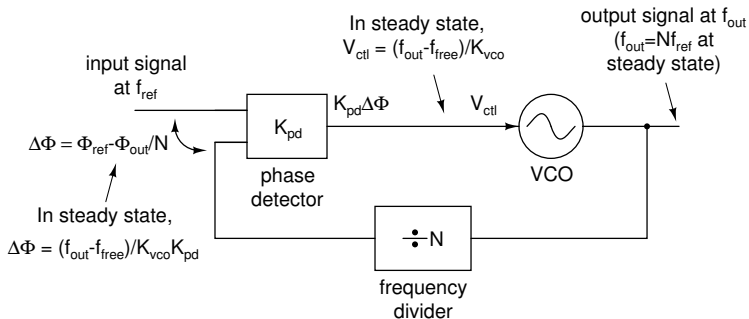


$\Delta\Phi = 0$ if f_{out} happens to be equal to f_{ref} . Zero spurs!

 Changing the free running frequency of a VCO




- Add a bias to the input to change the free running frequency

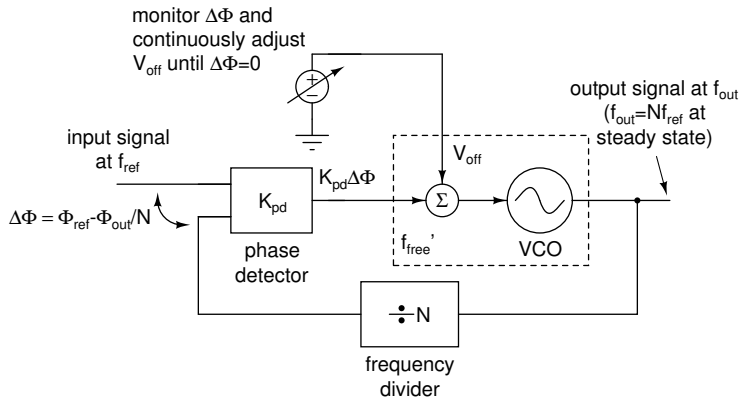Slowly change the bias until $\Delta\phi = 0$




- Slowly change the bias V_{off} until $\Delta\phi = 0$

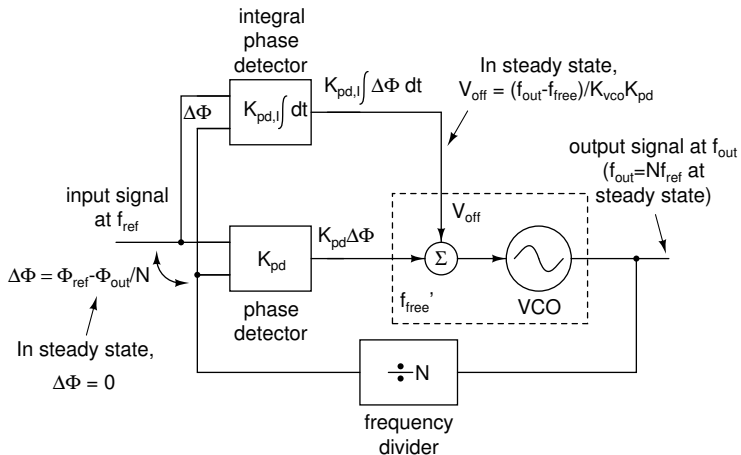Slowly change the bias until $\Delta\phi = 0$



- Measure $\Delta\phi$ and integrate it to control V_{off}

Type II Phase locked loop

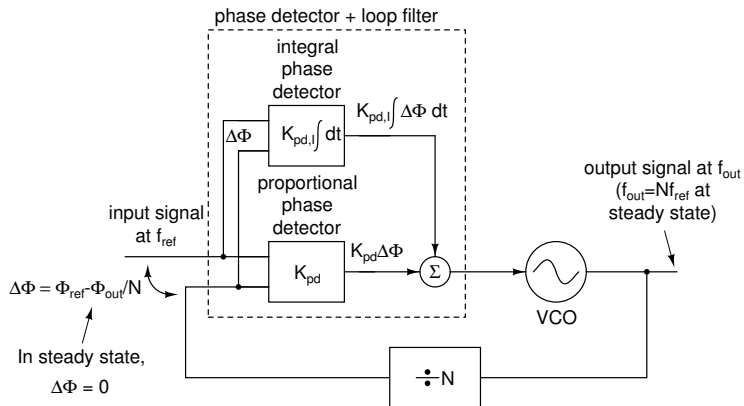


- Proportional + integral loop filter

Type II PLL with a tri state phase detector

- Lock range is not limited by the phase detector
- Loop locks with zero phase difference between reference and feedback signals
- Tri state phase detector output is zero for zero input phase difference \Rightarrow No reference feedthrough!
- Reference feedthrough does exist in reality due to mismatches

Type II PLL—phase model

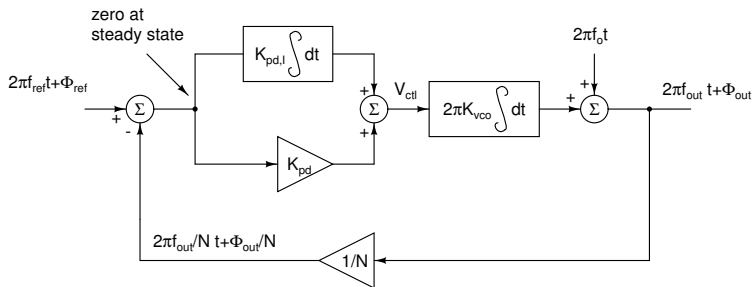


$$dV_{ctl}/dt \propto 2\pi(f_{ref} - f_{out}/N)t + \Phi_{ref} - \Phi_{out}/N$$

At steady state, $f_{ref} = f_{out}/N$; $\Phi_{ref} - \Phi_{out}/N = 0$;

- Proportional + integral loop filter

Type II PLL—incremental model

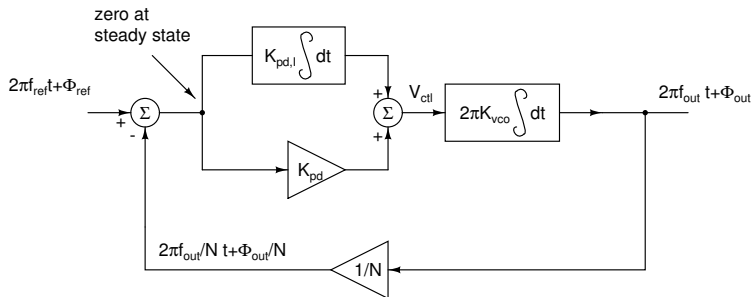


$$dV_{\text{ctl}}/dt \propto 2\pi(f_{\text{ref}} - f_{\text{out}}/N)t + \Phi_{\text{ref}} - \Phi_{\text{out}}/N$$

At steady state, $f_{\text{ref}} = f_{\text{out}}/N$; $\Phi_{\text{ref}} - \Phi_{\text{out}}/N = 0$;


- Proportional + integral loop filter

Type II PLL—incremental model

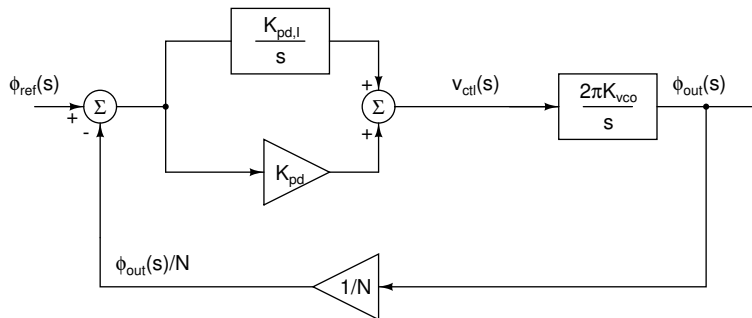


- Proportional + integral loop filter

Type II PLL—Frequency domain

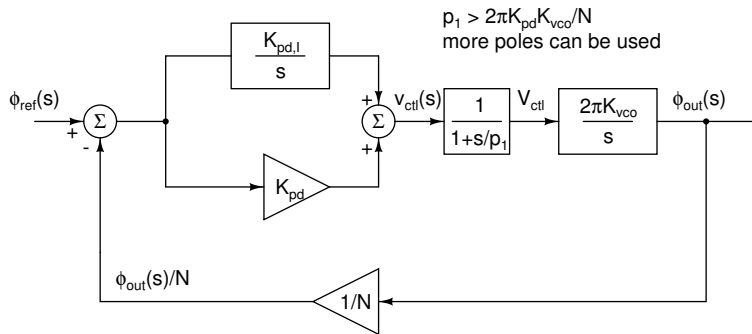


Type II PLL—Implementation

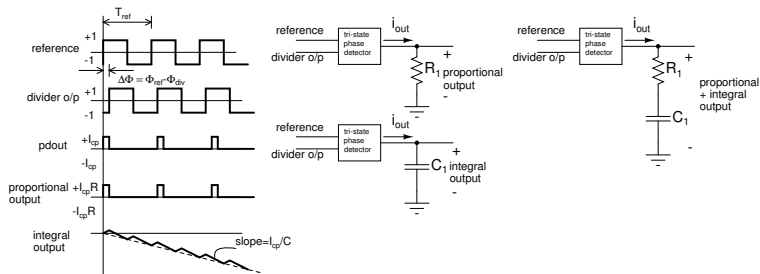




- Phase detector with a current output ($\pm I_{cp}$)
- Integral term $K_{pd,I}/s$: Current flowing into a capacitor C_1
- Proportional term K_{pd} : Current flowing into a resistor R_1
- Series RC to obtain the sum
- $K_{pd} = I_{cp}R_1/2\pi$; $K_{pd,I} = I_{cp}C_1/2\pi$

 Tri state phase detector with charge pump




- Q_A and Q_B drive a charge pump
- Charge driven into the loop filter $I_{cp} T_{ref} \Delta\Phi / 2\pi$

   Tri state phase detector implementation example




- D flip flops with reset implemented using SR latches

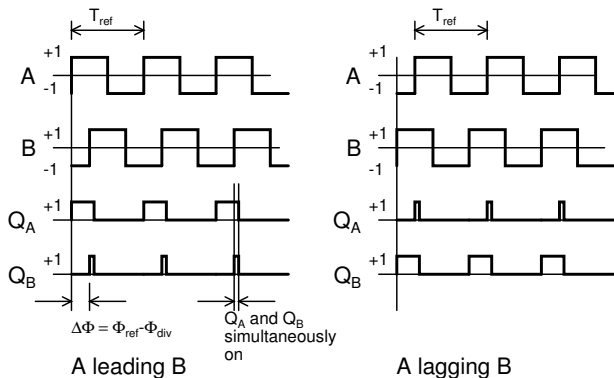Tri state phase detector-reset path delay




- Q_A and Q_B simultaneously high for a short duration
- Q_A - Q_B proportional to $\Delta\Phi$

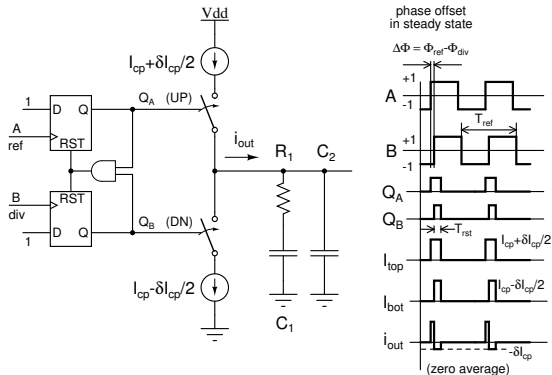Tri state phase detector-current source mismatch



- Ideally $\Delta\Phi = 0$ in a type-II loop \Rightarrow no ref. feedthrough
- Mismatch between top and bottom current sources and switching transients causes a non zero $\Delta\Phi$ and reference feedthrough
- Current pulse area $\propto \delta I_{cp} T_{rst}$ much smaller than in a Type I PLL (area $\sim I_{cp} T_{ref}$)

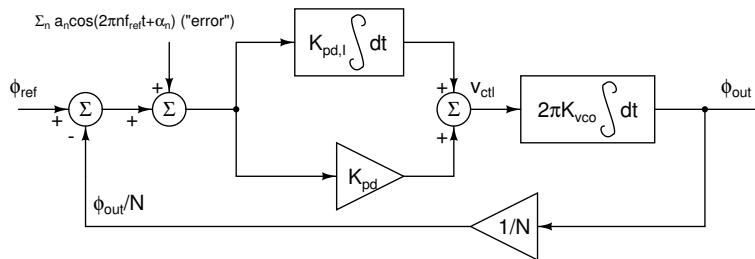
Type II PLL with a tri state phase detector




- Loop locks with a small phase offset (due to mismatch) between ϕ_{ref} and ϕ_{vco}/N for all frequencies
- Error $E(t)$ is periodic at f_{ref} :
$$E(t) = \sum_{n=1}^{\infty} a_n \cos(2\pi n f_{ref} t + \alpha_n)$$
- Amplitude of $E(t)$ related to mismatch; much smaller than in a type-I PLL

Type II PLL with a tri state phase detector-Frequency domain
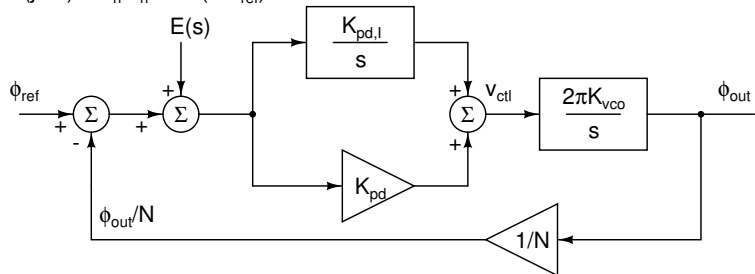
$$E(j2\pi f) = \sum_n a_n e^{j\alpha_n} \delta(f - nf_{ref})$$



Type II PLL—Additional attenuation poles

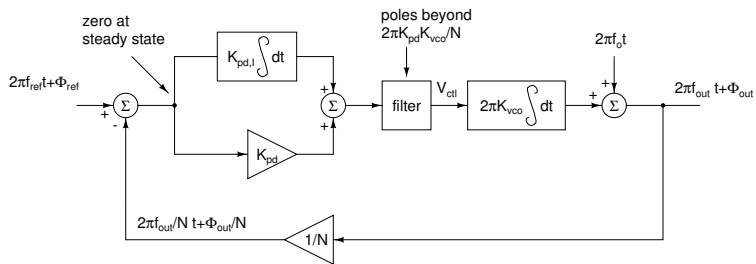


$$dV_{ctl}/dt \propto 2\pi(f_{ref} - f_{out}/N)t + \Phi_{ref} - \Phi_{out}/N$$

At steady state, $f_{ref} = f_{out}/N$; $\Phi_{ref} - \Phi_{out}/N = 0$;


- Additional poles beyond the unity loop gain frequency to reduce reference feedthrough

Type II PLL—Additional attenuation poles

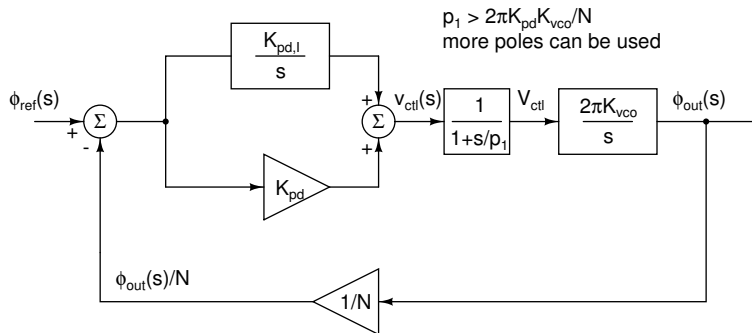


- Additional poles beyond the unity loop gain frequency to reduce reference feedthrough

Type II PLL—Additional attenuation poles

 

- Extra RC sections for additional poles
- Must be sufficiently beyond the unity loop gain frequency to ensure sufficient phase margin

Noise sources in a PLL

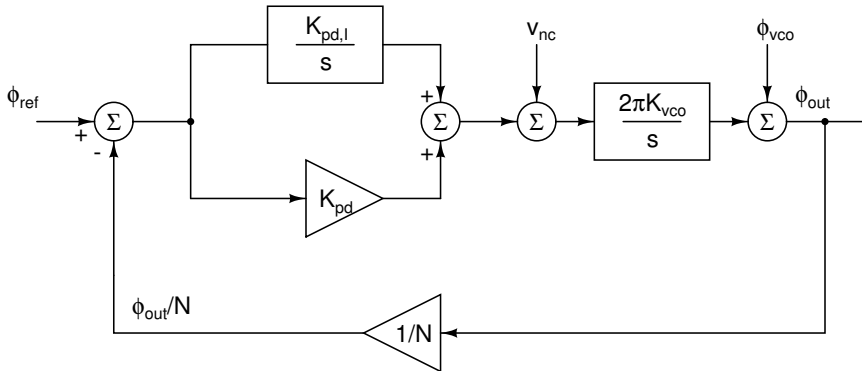

- Noise can be added as ϕ_{ref} (reference phase noise, charge-pump noise, divider output phase noise) or v_{nc} (loop filter noise) or ϕ_{vco} (VCO phase noise)
- Need to compute transfer functions from each of these noise sources to ϕ_{out}

Type-II PLL: transfer functions

$$L(s) = \frac{\omega_{u,loop}}{s} \frac{z_1}{s} \left(1 + \frac{s}{z_1} \right)$$

$$\omega_{u,loop} = \frac{2\pi K_{pd} K_{vco}}{N} = \frac{I_{cp} R K_{vco}}{N}$$

$$z_1 = \frac{K_{pd,l}}{K_{pd}} = \frac{1}{RC}$$

$$\frac{\phi_{out}(s)}{\phi_{ref}(s)} = N \frac{1 + s/z_1}{1 + s/z_1 + s^2/z_1\omega_{u,loop}}$$

$$\frac{\phi_{out}(s)}{V_{nc}(s)} = \frac{N}{K_{pd}} \frac{s/z_1}{1 + s/z_1 + s^2/z_1\omega_{u,loop}}$$


$$\frac{\phi_{out}(s)}{\phi_{vco}(s)} = \frac{s^2/z_1\omega_{u,loop}}{1 + s/z_1 + s^2/z_1\omega_{u,loop}}$$

Type-II PLL: transfer functions

$$\frac{L(s)}{1 + L(s)} = \frac{1 + s/z_1}{1 + s/z_1 + s^2/z_1\omega_{u,loop}}$$

- Two poles and a zero
- Zero $z_1 = K_{pd,I}/K_{pd}$
- Natural frequency $\omega_n = \sqrt{2\pi K_{pd,I}K_{vco}/N}$
- Quality factor $Q = \sqrt{z_1/\omega_{u,loop}} = \sqrt{NK_{pd,I}/2\pi K_{vco}}/K_{pd}$
- Damping factor $\zeta = 1/2Q = 1/2\sqrt{\omega_{u,loop}/z_1}$
- For well separated (real) poles ($z_1 \ll \omega_{u,loop}$),
 $p_1 \approx z_1 + z_1^2/\omega_{u,loop} \approx z_1$, $p_2 \approx \omega_{u,loop} - z_1$,
- Pole zero doublet $\{p_1, z_1\}$; p_1 at a slightly higher frequency than z_1


Type-II PLL: transfer functions

 

$$\frac{\phi_{out}(s)}{\phi_{ref}(s)} = N \frac{1 + s/z_1}{1 + s/z_1 + s^2/z_1\omega_{u,loop}}$$

- Peaking in $|\phi_{out}/\phi_{ref}|$ because of the zero
- Damping factor $\zeta \gg 1$ to avoid peaking \Rightarrow slow settling

Type-II PLL: transfer functions

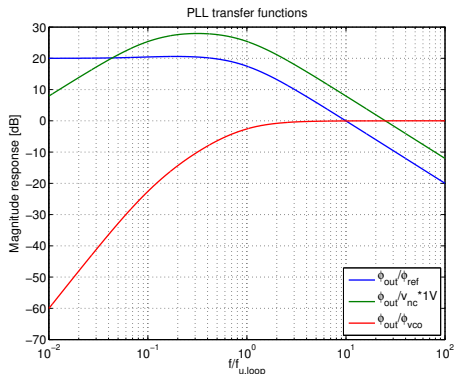


(Example parameters:

$$N = 10, z_1 = 0.1\omega_{u,loop}, N/K_{pd} = 2\pi K_{vco}/\omega_{u,loop} = 25 V^{-1})$$

- $|\phi_{out}/\phi_{ref}|$: Lowpass with a dc gain N
- $|\phi_{out}/v_{nc}|$: Bandpass with peak gain $N/K_{pd} = 25 V^{-1}$
- $|\phi_{out}/\phi_{vco}|$: Highpass with a high frequency gain of 1

Type-II PLL phase noise example

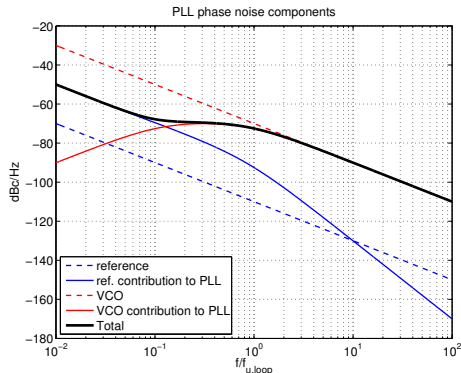


(Example parameters:

$$N = 10, z_1 = 0.1\omega_{u,loop}, N/K_{pd} = 2\pi K_{vco}/\omega_{u,loop} = 25 \text{ V}^{-1})$$

- Reference contribution dominant below $0.1\omega_{u,loop}$
- VCO contribution dominant above $0.1\omega_{u,loop}$
- VCO contribution reduced by the loop upto $\omega_{u,loop}$
- Charge pump and loop filter noise ignored in the above


Type-II PLL: Reference input

 

$$\frac{\phi_{out}(s)}{\phi_{ref}(s)} = N \frac{1 + sK_{pd,I}/K_{pd}}{s^2 \frac{N}{2\pi K_{pd,I}K_{vco}} + s \frac{K_{pd}}{K_{pd,I}} + 1}$$

- Low pass response; Reference noise attenuated at high frequencies
- Low frequency gain of N , -3 dB bandwidth of $2\pi K_{pd}K_{vco}/N$
- Pole zero doublet $p_1 \approx z_1 = K_{pd,I}/K_{pd}$; p_1 at a slightly higher frequency than z_1


Type-II PLL: Noise added to control node

 

$$\frac{\phi_{out}(s)}{V_{ctl}(s)} = \frac{N}{K_{pd}} \frac{sK_{pd}/K_{pd,I}}{s^2 \frac{N}{2\pi K_{pd,I}K_{vco}} + s \frac{K_{pd}}{K_{pd,I}} + 1}$$

- radians/Volt
- Bandpass response
- Mid band gain of N/K_{pd}
- Lower cutoff at $K_{pd,I}/K_{pd}$, Upper cutoff at $2\pi K_{pd}K_{vco}/N$



Type-II PLL: VCO noise

 

$$\frac{\phi_{out}(s)}{\phi_{vco}(s)} = \frac{s^2 \frac{N}{2\pi K_{pd,l} K_{vco}}}{s^2 \frac{N}{2\pi K_{pd,l} K_{vco}} + s \frac{K_{pd}}{K_{pd,l}} + 1}$$


- Second order highpass response
- Feedback loop effectively inactive beyond $2\pi K_{pd,l} K_{vco}/N$

Type-II PLL phase noise example

  

LC oscillator

LC oscillator


 


$$G_N \geq G_p$$



for sustained
oscillation

- Lossless LC resonator sustains a sinusoidal voltage indefinitely
- LC resonator loss modeled using a parallel resistance R_p
- Compensate the loss of a lossy LC resonator using a parallel negative resistance
- Oscillation frequency $f_o = 1/2\pi\sqrt{LC}$


LC resonator losses

  
  
$$R_{P,L} = (\omega L)^2 / R_{s,L} \cong Q_L^2 R_{s,L}$$



 
$$R_{P,C} = 1/(\omega C)^2 R_{s,C} \cong Q_C^2 R_{s,C}$$



$$R_P = R_{P,L} || R_{P,C}$$


- Capacitor and Inductor series resistances represented by equivalent parallel resistances
- Effective R_p is a parallel combination of losses from all components

Negative resistance-implementation

 


- Transconductor G_N connected in positive feedback

Negative resistance-implementation

 


- Cross coupled differential pair
- Negative conductance = $g_m/2$ where g_m is the transconductance of each MOS device

LC oscillator

 


- Parallel LC tank with cross coupled differential pair
- This and its variants are the most commonly used topologies of CMOS integrated oscillators

LC oscillator-amplitude

 

- Complete switching of MOS devices assumed
- Equivalent to a square wave current of amplitude $I/2$ driving the parallel LC tank




LC oscillator-amplitude

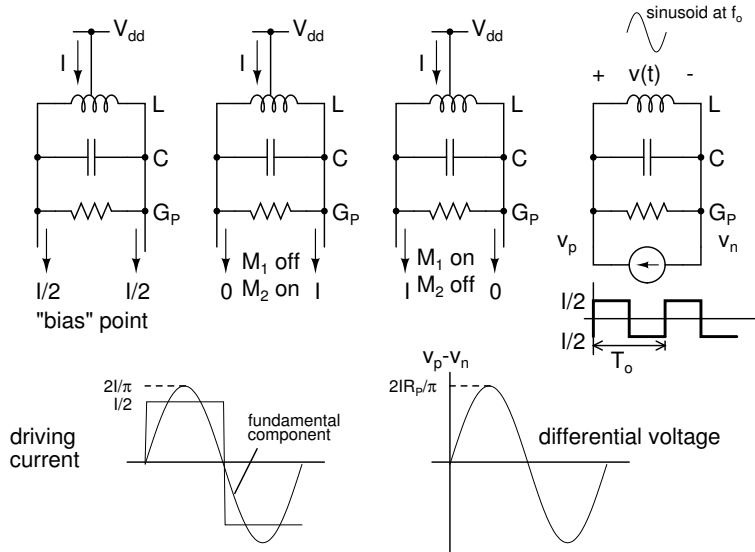

LC oscillator-amplitude





- Equivalent to a square wave current of amplitude $I/2$ driving the parallel LC tank
- All components except the fundamental filtered out
- Amplitude of the differential sinusoidal voltage = $2IR_P/\pi$

LC oscillator-tunability

   


- Tunable using a varactor
- Reverse biased p-n junction
- MOS device in accumulation—larger tuning range; more popular in CMOS ICs

Accumulation MOS varactor

    


- nMOS in n-well
- Multi fingered structure to reduce gate, channel resistance
- $W \sim$ few microns; $L > L_{\text{min}}$ to reduce parasitics
- Gate contacts at both ends to further reduce resistance
- Quality factor: 20+

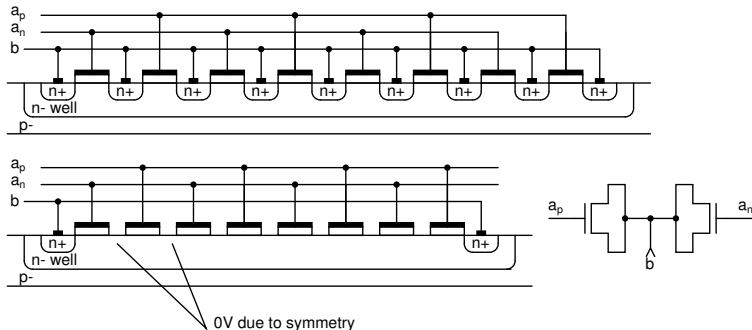MOS varactor with differential excitation




- Interdigitated fingers—alternate ones connected to a_p and a_n
- Region between gates connected to a_p and a_n at 0 V due to symmetry
- All n+ contacts except the ones at the end can be removed [7]
- Smaller structure, lower series resistance, and smaller parasitic capacitances

On chip inductors

 


- Planar inductor on one of the metal layers
- Top level metal preferred
 - Farther from the substrate
 - Smaller parasitic capacitance
 - Lesser coupling to substrate, and hence, loss
- Thicker top level metal ($\sim 2 \mu\text{m}$) available in mixed signal processes

Inductor loss mechanisms

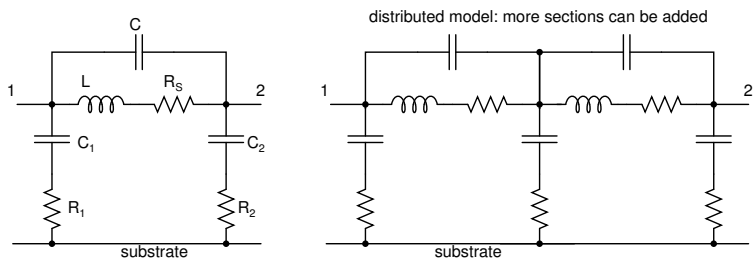

- Winding resistance
 - $R_{\square} L/W$
 - Effective R_{\square} larger due to skin effect
 - Copper: $2 \mu\text{m}$ skin depth ($\propto 1/\sqrt{f}$) at 1 GHz
- Capacitive coupling to substrate and its resistance
- Inductive coupling to (resistive) substrate
- Quality factors upto 15 possible, typically 8-10
- Use adequate thickness and number of vias during layout

Differential inductor

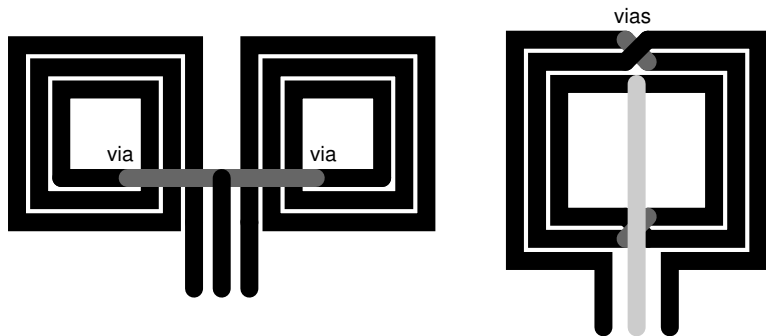

- Symmetrical differential inductor
 - More compact for a given differential inductance
 - Larger potential difference between turns \Rightarrow larger effect of interwinding parasitic capacitance
- Symmetrically laid out single ended inductors
 - Greater area
 - Interwinding parasitic capacitance not very significant


Inductor simulation

- Some processes have scalable inductor library and models
- Typically needs to be simulated from process parameters—metal thickness, resistivity, intermetal spacing etc.
- Inductance value
 - FastHenry, Asitic etc.
 - Accurate estimation possible
- Quality factor
 - FastHenry, Asitic etc.
 - Harder to accurately estimate losses due to substrate coupling
- Parasitic capacitance
 - First order parallel plate estimation—OK for single ended inductors
 - FastCap etc.
 - Use distributed models for accuracy—2 to 3 sections are sufficient

VCO design: bias current and transistor sizing


- Bias current is a function of tank losses and desired amplitude
 - Maximize the inductance for a large amplitude from a small current
- Transistors typically minimum length at high frequencies—longer to lower $1/f$ corner
- Bias source: longer than minimum length to lower $1/f$ noise
- Minimize all parasitics to maximize tuning range from the varactor
- Transistor W/L to get the desired g_m for startup in the worst case
 - Large $g_m \Rightarrow$ increased phase noise; So don't go crazy!
 - Minimize g_m variations over process and temperature; Less overdesign

5 GHz VCO in 0.18 μm CMOS

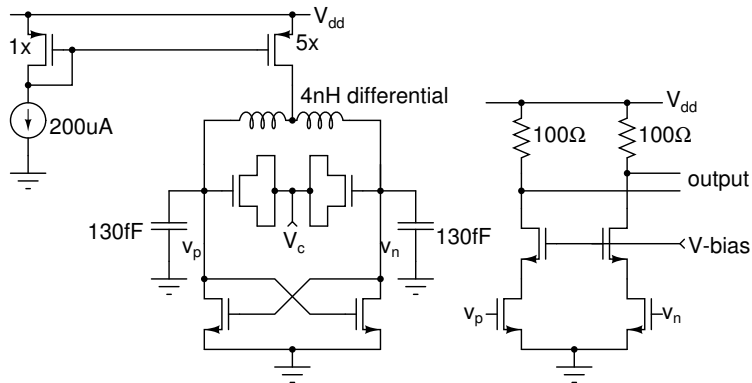


- $L = 4 \text{ nH}$ and $C = 0.25 \text{ pF}$ (differential) chosen
- 6 turn inductor on top metal layer, $\approx 140 \mu\text{m}$ square
- From inductor simulations, $Q \approx 6$
- Minimum length transistors
- Cascode buffer for measurement


5GHz VCO-inductor

 


5GHz VCO layout

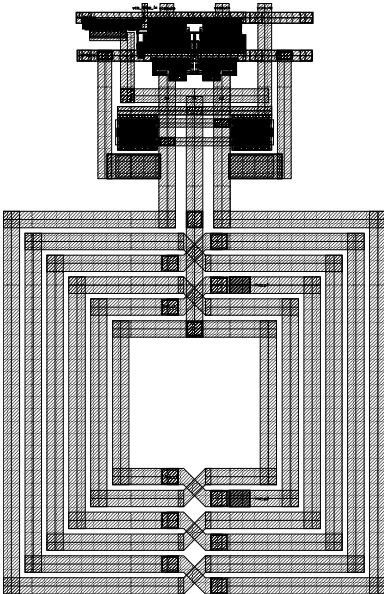


5GHz VCO layout

 

 VCO (higher freq. version)-measured f vs. V




VCO-simulated phase noise

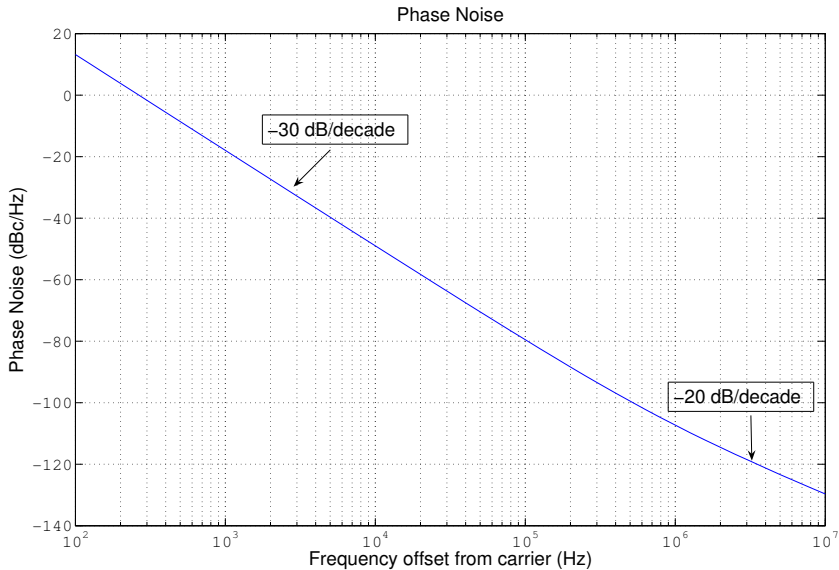


Programmable frequency divider

Programmable divider-Synchronous counter

 


- All of the circuitry running at full speed
- Very high power dissipation
- Asynchronous operation preferred

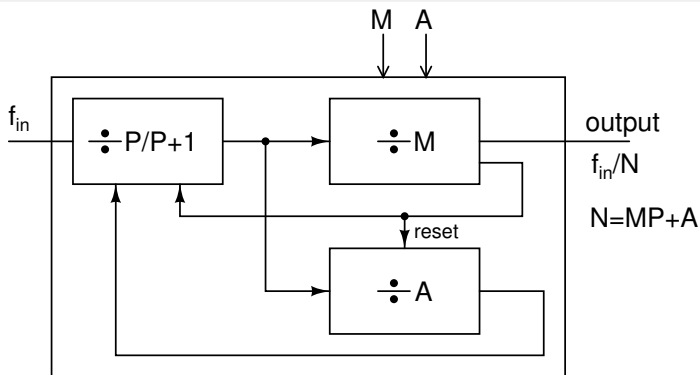Programmable divider-Pulse swallow architecture





- Dual modulus prescaler $\div P/P + 1$
- Divide by $P + 1$ for A cycles
- Divide by P for $M - A$ cycles
- Full cycle = $(P + 1)A + P(M - A) = MP + A$
- Only the dual modulus prescaler running at full speed
- Programmability using M and A

 Programmable divider using divide-by-2/3 cells




- Each stage divides by 2 (if $p_k = 0$)
- Each stage divides by 3 (if $p_k = 1$) once in each output cycle
- With L stages, the division factor range from 2^L to $2^{L+1} - 1$
- Modular approach

  Programmable divider using divide-by-2/3 cells



- Each stage divides by 2 (if $p_k = 0$)
- Each stage divides by 3 (if $p_k = 1$) once in each cycle
- With L stages, the division factor range from 2^L to $2^{L+1} - 1$
- Modular approach

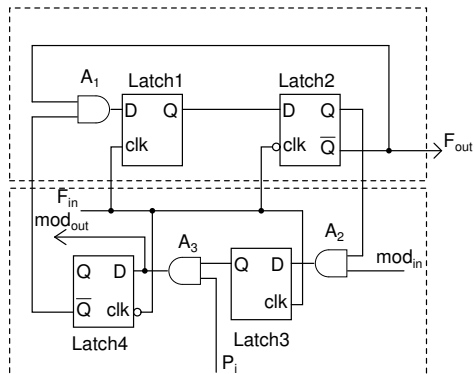Divide-by-2/3 cell for the programmable divider



References



Behzad Razavi, *RF Microelectronics*, Prentice Hall, 1998.



Behzad Razavi (editor), *Monolithic Phase Locked Loops and Clock Recovery Circuits-Theory and Design*, IEEE Press, 1996.



Behzad Razavi (editor), *Phase Locking in High Performance Systems-From Devices to Architectures*, IEEE Press, 2003.



Nagendra Krishnapura, "Introducing Negative Feedback with an Integrator as the Central Element," *2012 International Symposium on Circuits and Systems (ISCAS)*, Seoul, South Korea, 20-23 May 2012.



Nagendra Krishnapura, "Synthesis Based Introduction to Opamps and Phase Locked Loops," *2012 International Symposium on Circuits and Systems (ISCAS)*, Seoul, South Korea, 20-23 May 2012.



Marc Tiebout, *Low Power VCO Design in CMOS (Springer Series in Advanced Microelectronics)*, Springer 2005.



A. S. Porret et al., "Design of high-Q varactors for low-power wireless applications using a standard CMOS process", *IEEE Journal of Solid-State Circuits*, pp. 337-345, Volume 35, Issue 3, March 2000.



C. Vaucher et al., "A family of low-power truly modular programmable dividers in standard 0.35- μm CMOS technology," *IEEE Journal of Solid-State Circuits*, vol. 35, no. 7, pp. 1039-1045, July 2000.