



EE5311


MODULE-5

SEQUENTIAL CIRCUITS

SEQUENTIAL CIRCUITS



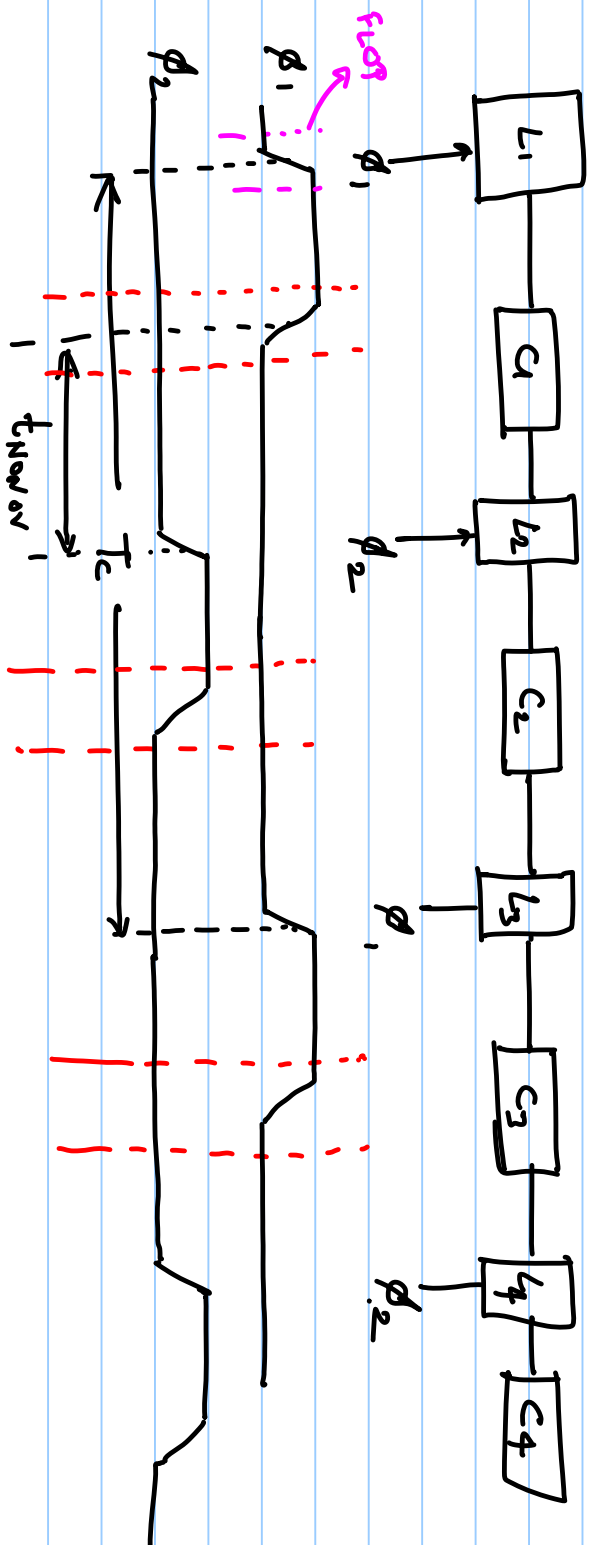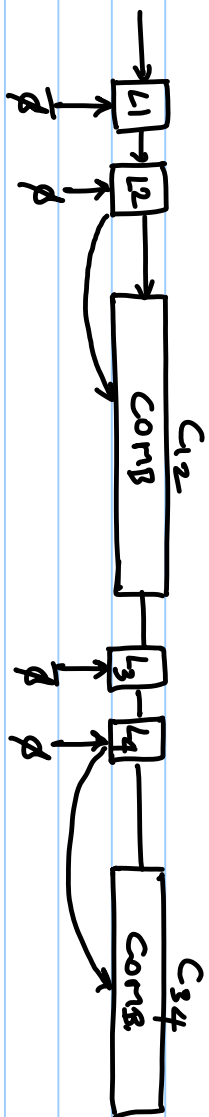

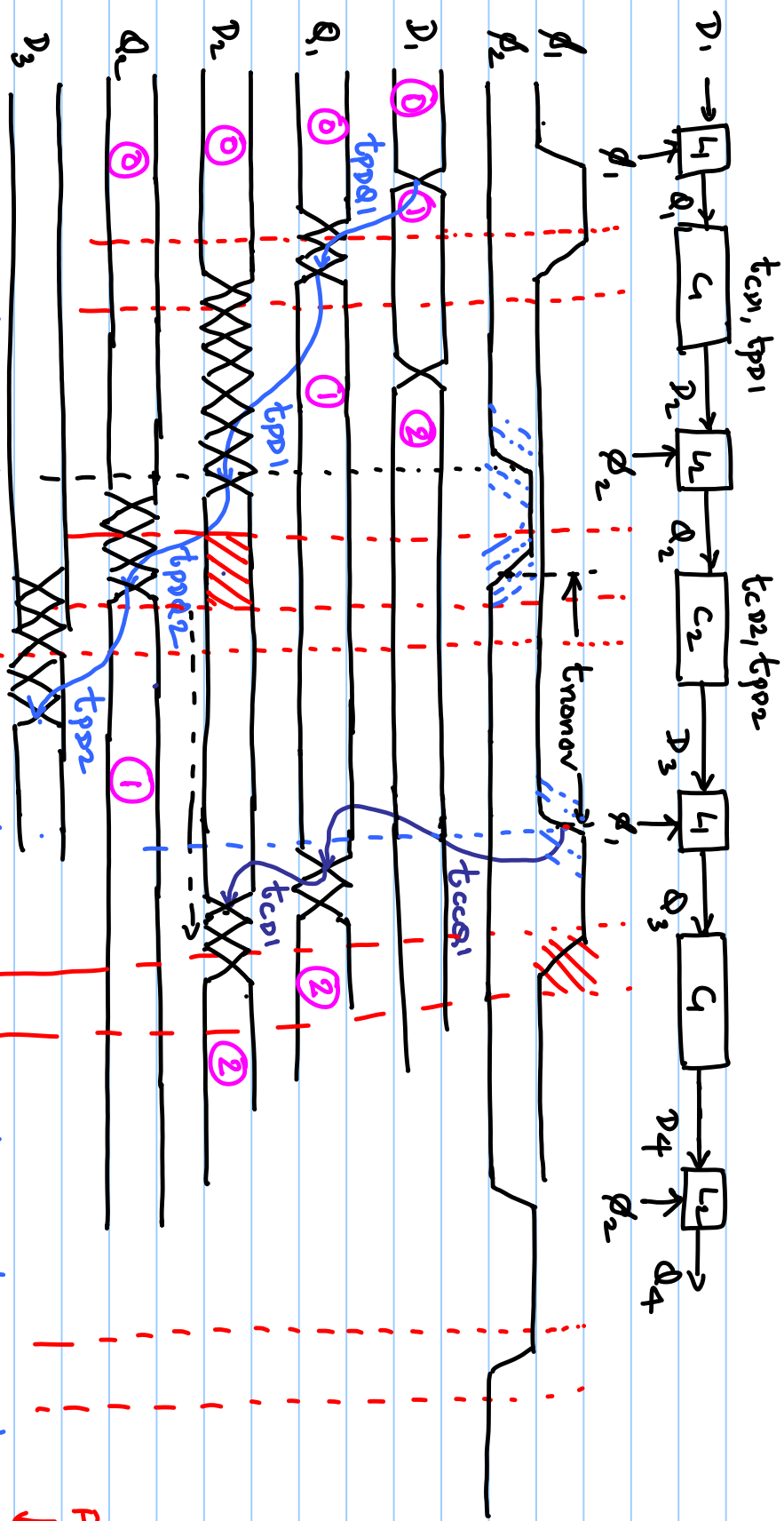

SKETCH
TOLERANT

MAX $T_c \geq t_{pdq1} + t_{pd1} + t_{pdq2} + t_{pd2}$

$t_{skew} + t_{nomov} \leq t_{nomov} + t_{ccq1} + t_{cd1}$

For Every
LATCH

