
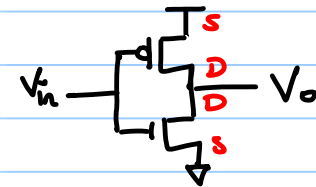


28/08/2019

EE5311 MODULE-3: THE INVERTER

VOLTAGE TRANSFER CHARACTER (VTC)

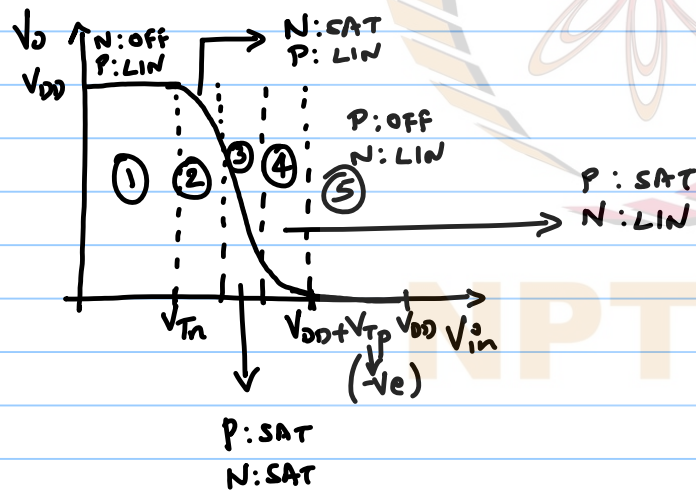

$$I_{Dsn} = -I_{Dsp}$$



$$V_{gsn} = V_{in}$$

$$V_{dsn} = V_O$$

$$V_{gsp} = V_{in} - V_{DD}$$

$$V_{dsp} = V_O - V_{DD}$$

LOAD LINE ANALYSIS

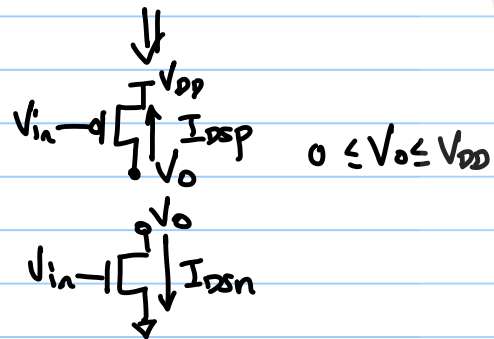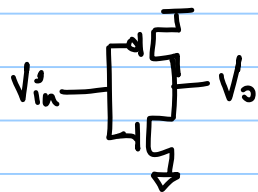

$$I_{DSN} = -I_{DSP}$$

$$V_{GSN} = V_{in}$$

$$V_{DSN} = V_o$$

$$V_{GSP} = V_{in} - V_{DD}$$

$$V_{DSP} = V_o - V_{DD}$$

SWEEP ' V_o ' WITH V_{in} as a param.


$$V_n = V_1, V_2, V_3, V_4, V_5.$$

$$\downarrow < V_{Tn}$$


Both
in
SAT

$$\downarrow > V_{DD} + V_{Tp}.$$

NPTTEL

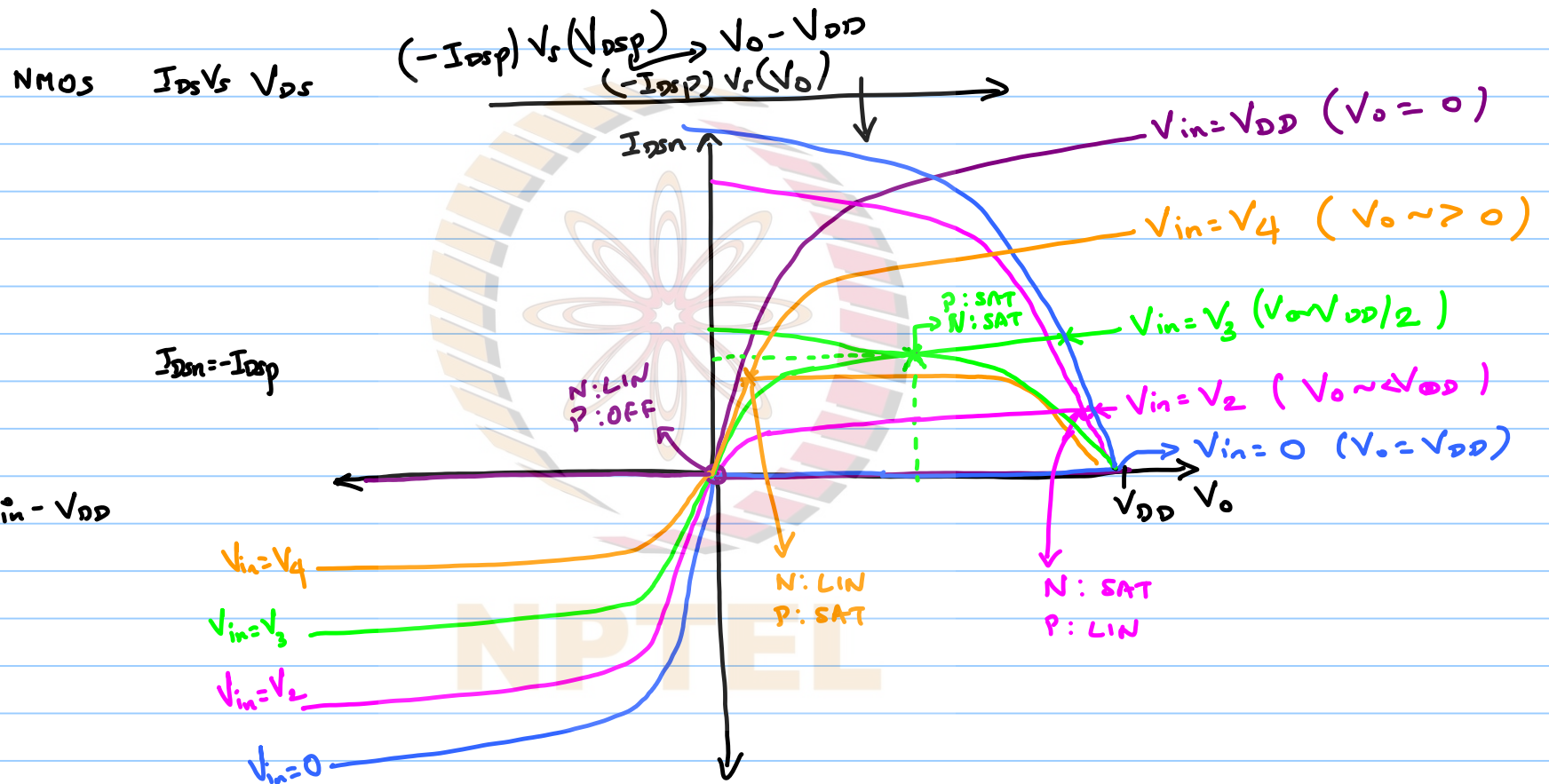

TRIP POINT

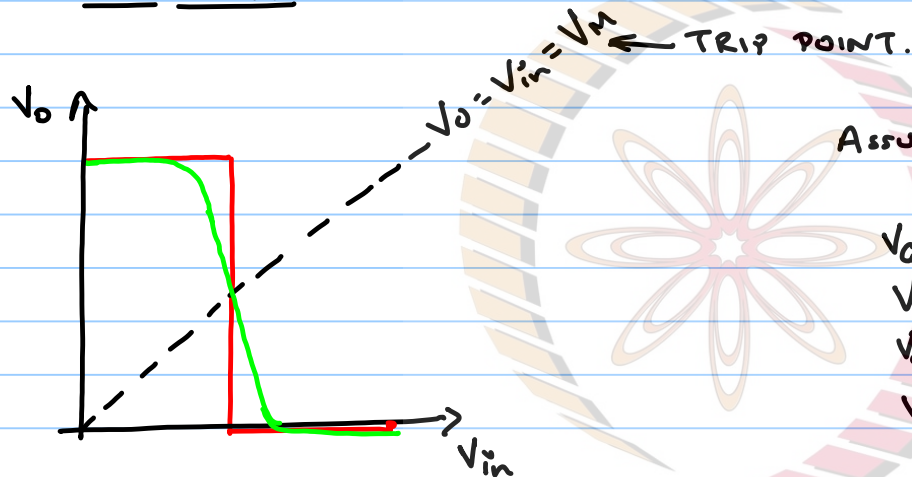


Assume : 1 N & P are in vel sat regim
 $\lambda_n = \lambda_p = 0$

$$V_{asn} = V_{in} = V_M$$

$$V_{dsn} = V_o = V_M$$

$$V_{asp} = V_{in} - V_{DD} = V_M - V_{DD}$$
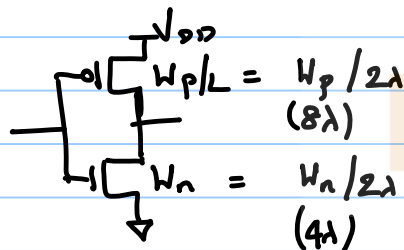
$$V_{dsp} = V_o - V_{DD} = V_M - V_{DD}$$



$$I_{dsn} = K_n \frac{W_n}{L} V_{dsatn} (V_M - V_{tn} - \frac{V_{dsatn}}{2})$$

$$I_{dsp} = K_p \frac{W_p}{L} V_{dsatp} (V_M - V_{DD} - V_{tp} - \frac{V_{dsatp}}{2})$$

$$(I_{dsn} = -I_{dsp})$$

IN 180nm: $2\lambda = 180\text{nm}$.

$\lambda \rightarrow$ NOT SAME AS CLM (λ_n, λ_p)

$$\Rightarrow \frac{k_n' W_n V_{DSATn}}{K} (V_M - V_{Tn} - \frac{V_{DSATn}}{2}) = - \frac{k_p' W_p V_{DSATp}}{K} (V_M - V_{DD} - V_{Tp} - \frac{V_{DSATp}}{2})$$

$$r = \frac{k_p' W_p V_{DSATp}}{k_n' W_n V_{DSATn}} \quad (\text{+ve no.})$$


$$\therefore V_M = \frac{\left(V_{Tn} + \frac{V_{DSATn}}{2} \right) + r \left(V_{DD} + V_{Tp} + \frac{V_{DSATp}}{2} \right)}{1+r}$$

$$V_{DSATn} = -V_{DSATp}, \quad V_{Tn} = -V_{Tp}$$

$$(W_p/W_n) = |k_n'/k_p'| \sim 2$$

$$\Rightarrow r = 1$$

$$\Rightarrow V_M = \frac{V_{DD}}{2}$$

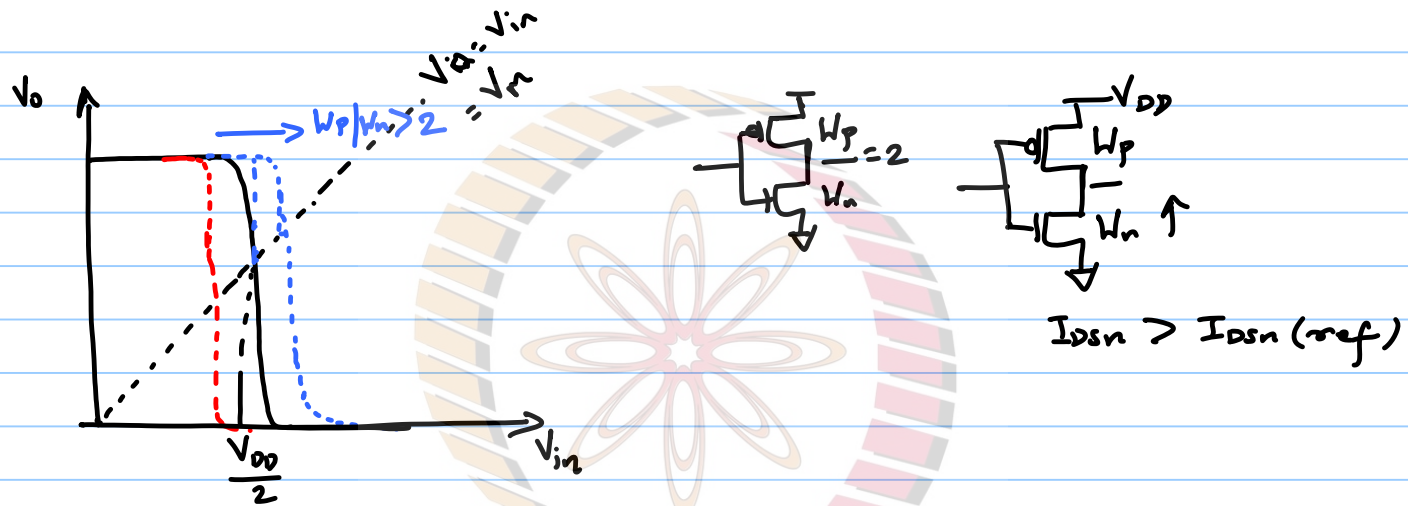

LONG CHANNEL DEVICES

$$V_{in} = V_o = V_M$$

$$I_{Dsn} = -I_{Dsp}$$

$$I_{Dsn} = \frac{1}{2} K_n' \frac{W_N}{L} (V_M - V_{Tn})^2$$

$$I_{Dsp} = \frac{1}{2} K_p' \frac{W_P}{L} (V_M - V_{DD} - V_{Tp})^2$$

$$I_{Dsn} = -I_{Dsp}$$

$$\Rightarrow k_n' W_n (V_M - V_{Tn})^2 = -k_p' W_p (V_M - V_{DD} - V_{Tp})^2$$

$$\Rightarrow \gamma = \sqrt{\frac{-k_p' W_p}{k_n' W_n}}$$

$$\Rightarrow (V_M - V_{Tn}) = \pm \gamma (V_M - V_{DD} - V_{Tp})$$

$$\Rightarrow V_M (1 + \gamma) = V_{Tn} + \gamma (V_{DD} + V_{Tp})$$

$$\therefore V_M = \frac{V_{Tn} + \gamma (V_{DD} + V_{Tp})}{1 + \gamma}$$